

ECE 311 - Fundamentals of Electronics Lab

Department of Electrical and Computer Engineering
University of Idaho

Title: Rectifiers

Goal: To design and verify the operation of a “half-wave” and “full-wave bridge” rectifier.

Preliminary: (Follow preliminary requirements. Due at the beginning of the laboratory period)

1. Select a value for R_L for a half-wave rectifier (depicted in Figure 1) so $i_{L,peak} \approx 1\text{mA}$ when $v_s = 10V_{peak}$. Choose a standard 5% resistor value. Check the circuit solution using LTSpice. Let the frequency of v_s be 60Hz. Show plots of v_s , v_o , and i_{D1} .
2. Using the same values for R_L , v_s , and the frequency of v_s from 1), determine the expected value of $i_{L,peak}$ for a full-wave rectifier depicted in Figure 2. Simulate the circuit in LTSpice. Show plots of v_s , v_o , and i_{D1} .

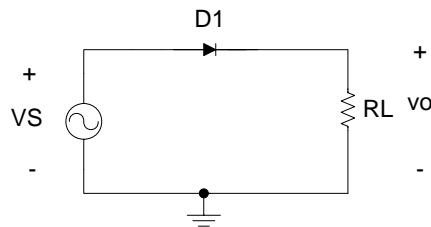


Figure 1 Schematic for a half-wave rectifier

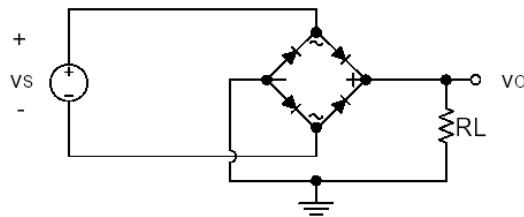


Figure 2 Schematic for a full-wave rectifier

Laboratory Procedure:

- 1) Select, measure, and record the value of a resistor based on your calculation in the preliminary.
- 2) Build the half-wave rectifier depicted in Figure 1. Sketch the waveform at v_s and v_o . Calculate $i_{d,peak}$.
- 3) Repeat 2) using the resistor from 1) with the full-wave rectifier depicted in Figure 2.