

Specification: Unsigned Averager

Design a circuit to compute the sample mean of a string of eight 8-bit, unsigned integers. The output is also 8 bits.

The equation for the sample mean is:

$$\bar{x} = \frac{1}{N} \sum_{i=1}^N x_i$$

Where $\{x_i\}$ are the input samples and N is the sample size. In our case $N=8$, so:

$$\bar{x} = \frac{1}{8} \sum_{i=1}^8 x_i \text{ or equivalently } \bar{x} = \frac{1}{8} \sum_{i=0}^7 x_i$$

Specifications:


inputs

- data* 8-bit data input vector, non-negative integer
- start* control signal to start computation
- init* control signal to initialize module

outputs

- mean* 8-bit data output vector, non-negative integer
- ready* status signal: module is ready to start a new computation

Before use, the module must be initialized by asserting the *init* signal for one clock period (rising edge to rising edge). When the module is ready to start a computing sequence, it asserts *ready* and waits for the *start* signal to be asserted. The start signal should last at least one clock cycle. On receiving a *start* signal, the module de-asserts *ready*. On the first falling clock edge after the clock period containing the *start* signal, the module expects the first data sample to be stable at the *data* input. On this, and each subsequent falling edge, the averager latches a data sample. When eight samples have been read, the module completes the computation, and latches an 8-bit output.

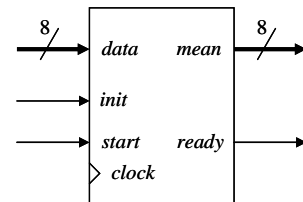

The module then reasserts *ready*, and waits for the *start* signal to begin the next computational sequence. The last mean value is retained at the output until a new one is ready.