
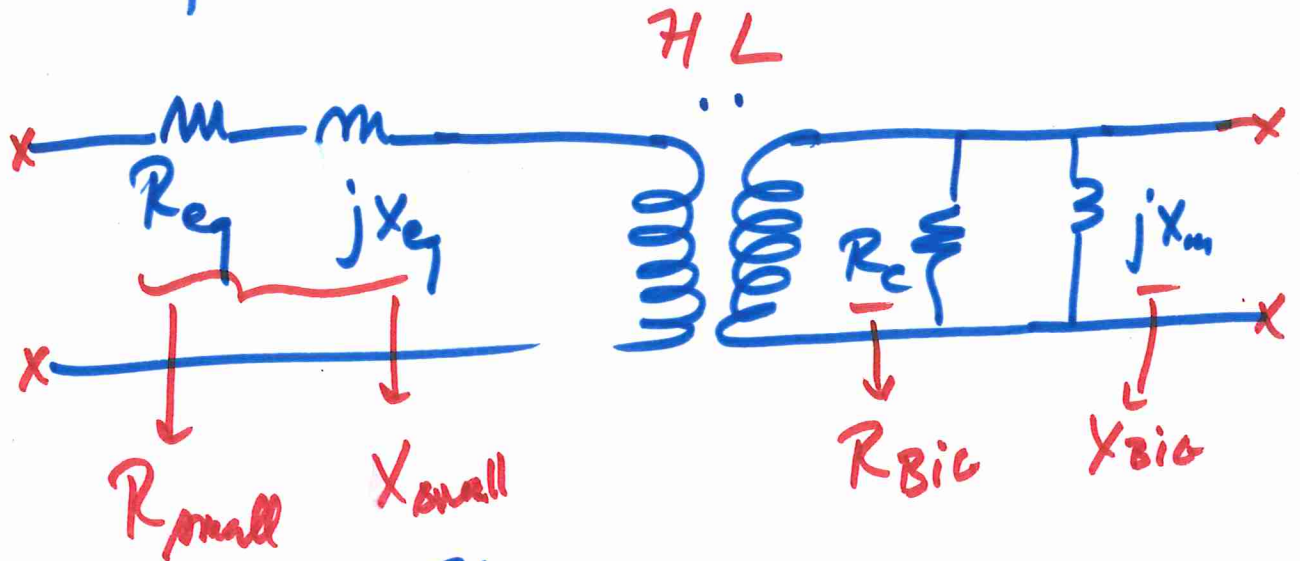


Transformers:

(1)

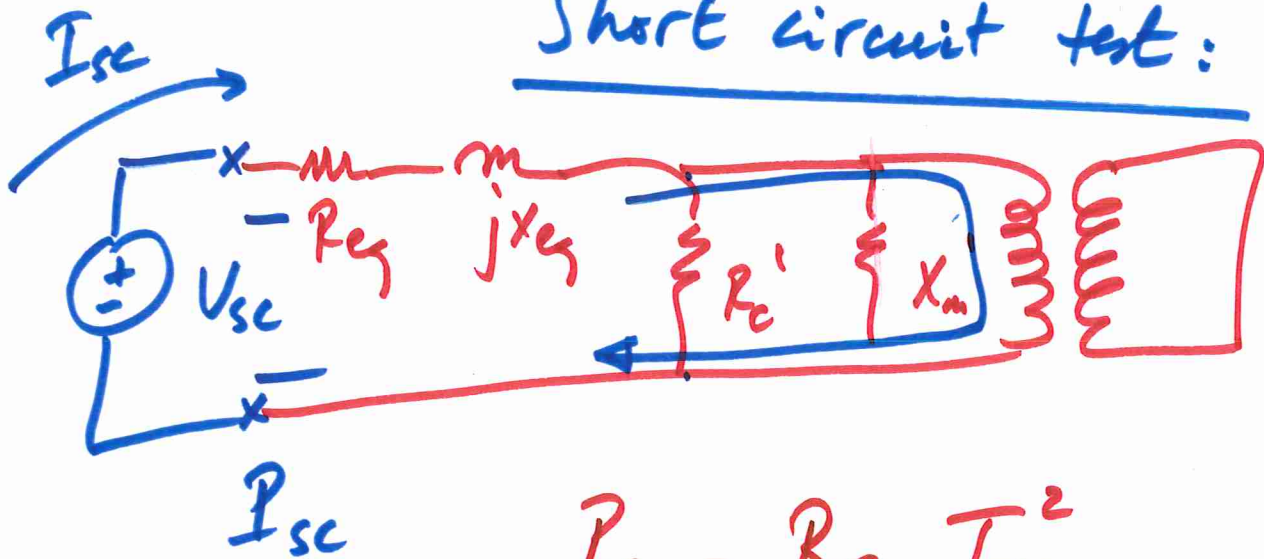

Short circuit test:



$$I_{sc} = R_{e1} I_{sc}^2$$


$$R_{e1} = \frac{P_{sc}}{I_{sc}^2}$$

$$Z_{e1} = R_{e1} + jX_{e1} = \frac{V_{sc}}{I_{sc}}$$

(2).

METHOD 1


$$X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$$

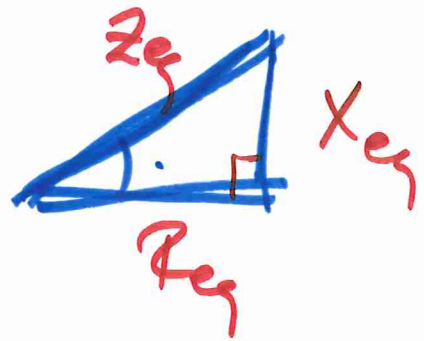

METHOD 2


$$\cos \theta = \frac{P_{sc}}{S_{sc}} = \frac{I_{sc}}{V_{sc} I_{sc}}$$
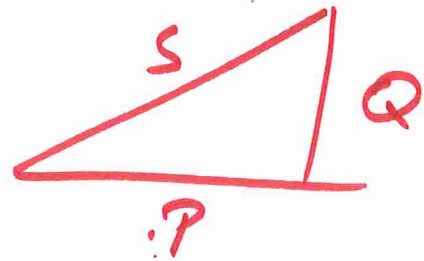
$$\theta = \cos^{-1} \left(\frac{P_{sc}}{V_{sc} I_{sc}} \right)$$



$$X_{eq} = R_{eq} \tan(\theta) = R_{eq} \tan \left(\cos^{-1} \left(\frac{P_{sc}}{V_{sc} I_{sc}} \right) \right)$$

Open circuit test:

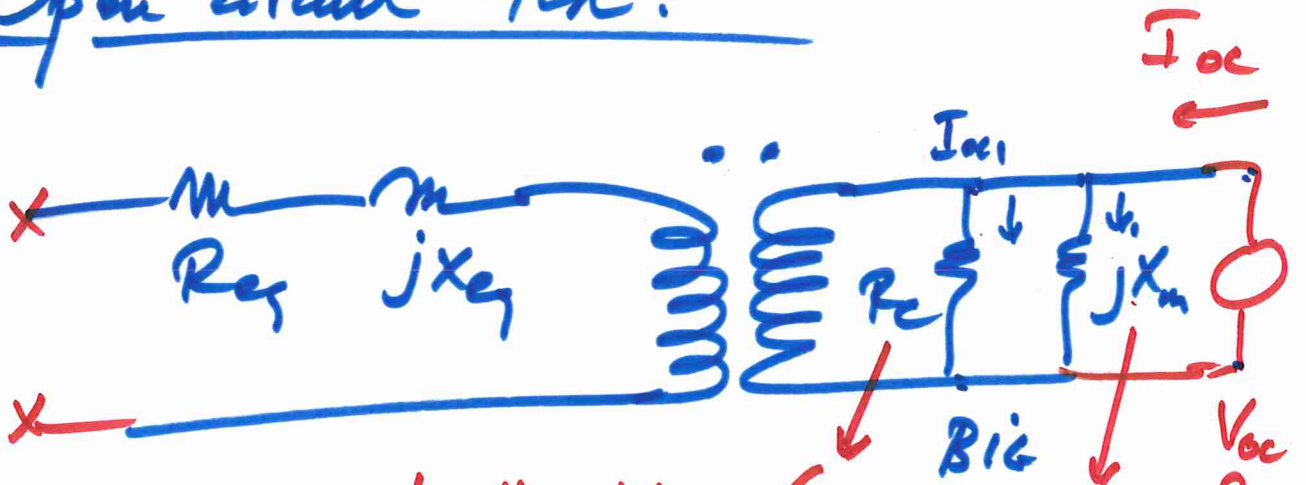

admittance $Y = G_c - jB_m$
 G_c → Conductance
 $-jB_m$ → susceptance.

$$Y = \frac{I_{oc}}{V_{oc}}$$

$$Y = G_c - jB_m$$

(3)

$$G_c = \frac{I_{oc}}{V_{oc}^2}$$

$$P_{oc} = R_c \cdot I_{oc}^2$$


$$P_{oc} = R_c \cdot \left(\frac{V_{oc}}{R_c}\right)^2$$

$$P_{oc} = \frac{V_{oc}^2}{R_c} = V_{oc}^2 \cdot G_c$$


$$Y = G_c - jB_m$$

Unit
Siemens
 Ω^{-1}

$$B_m = \sqrt{Y^2 - G_c^2}$$

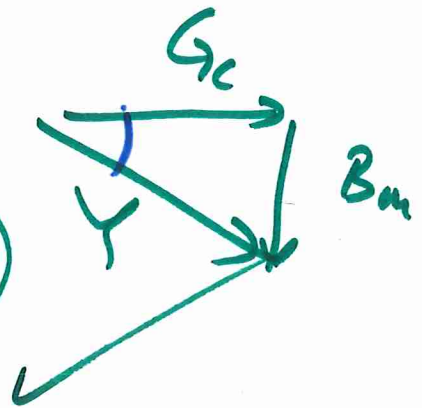

Example:

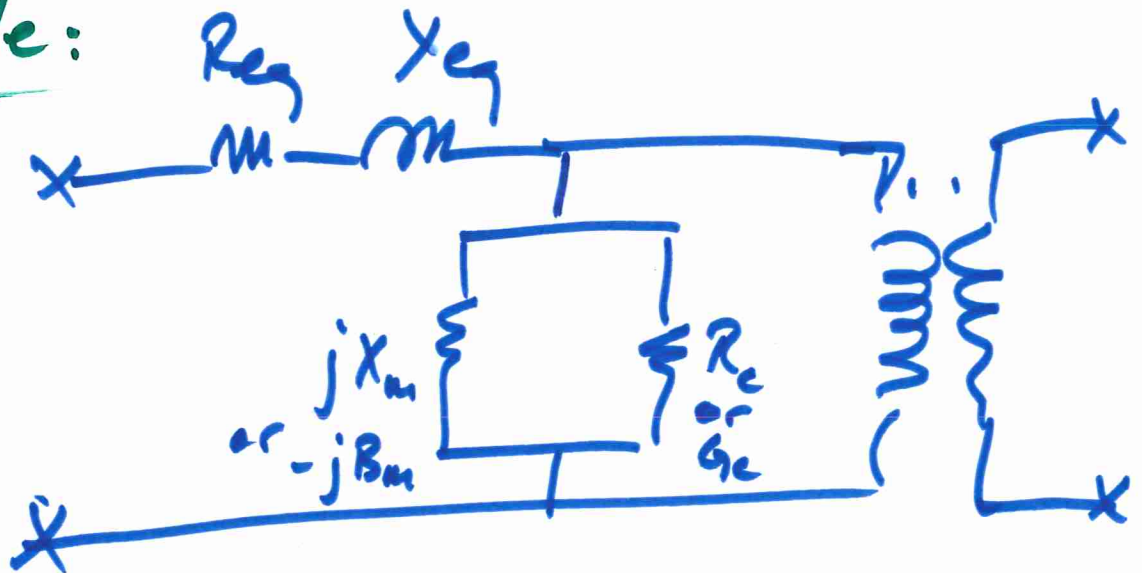

- SC, $I_{sc} = 9A$, $P_{sc} = 71.2 \text{ kW}$, $V_{sc} = 9.86 \text{ kV}$
- OC, $I_{oc} = 5.46A$, $P_{oc} = 52.3 \text{ kW}$, $V_{oc} = 22 \text{ kV}$

Find R_{eq} , X_{eq} , R_c , X_m .