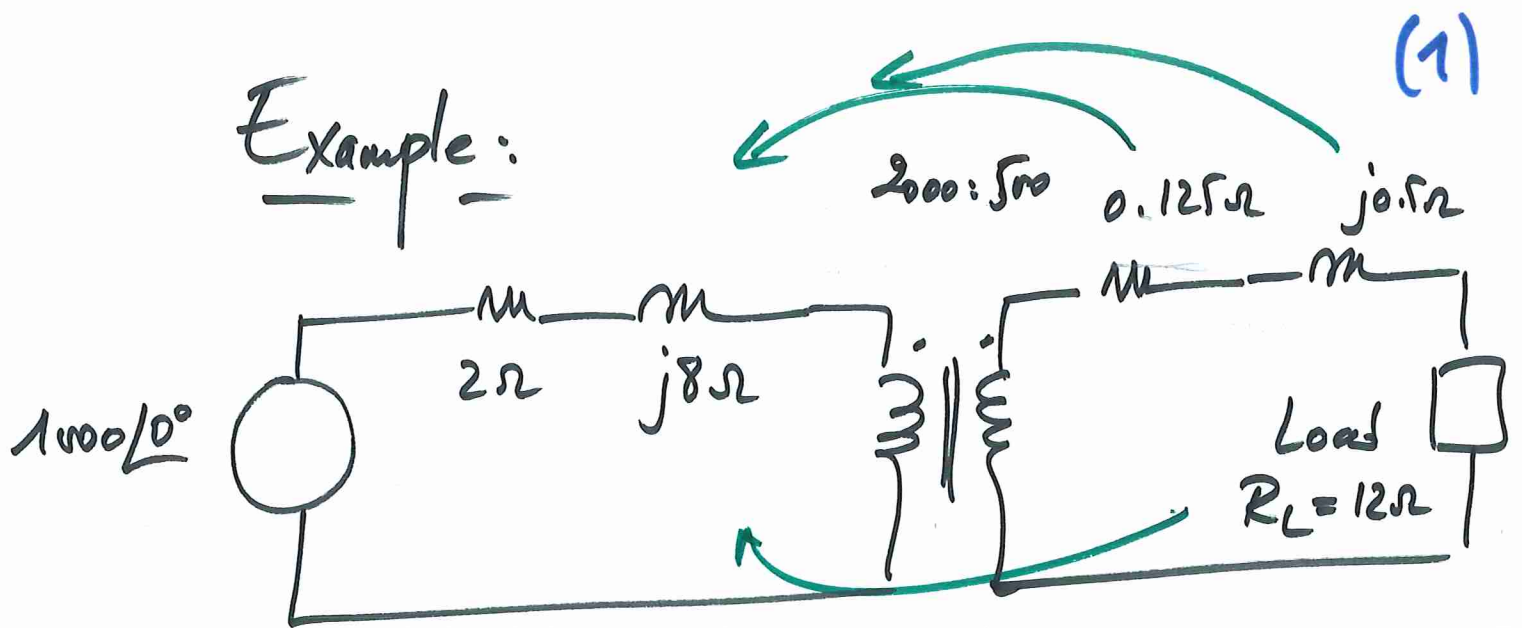




Example:



1) Find V_{Load} .

2) Find the voltage regulation

Solution:

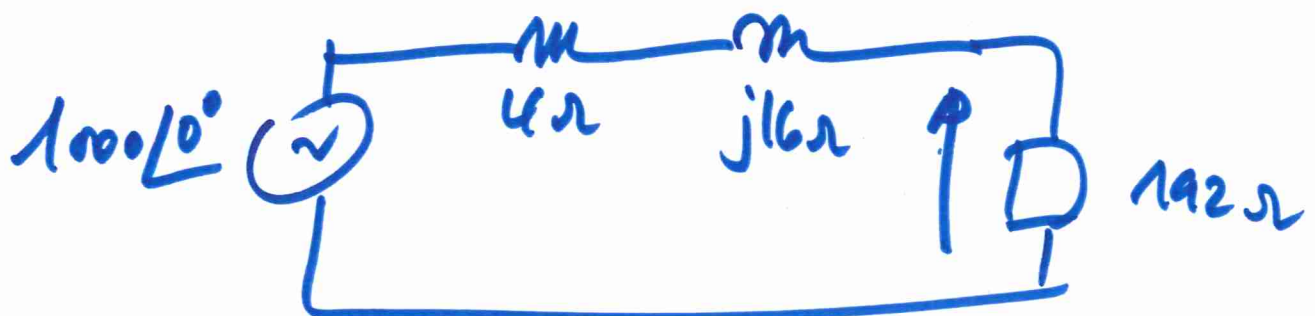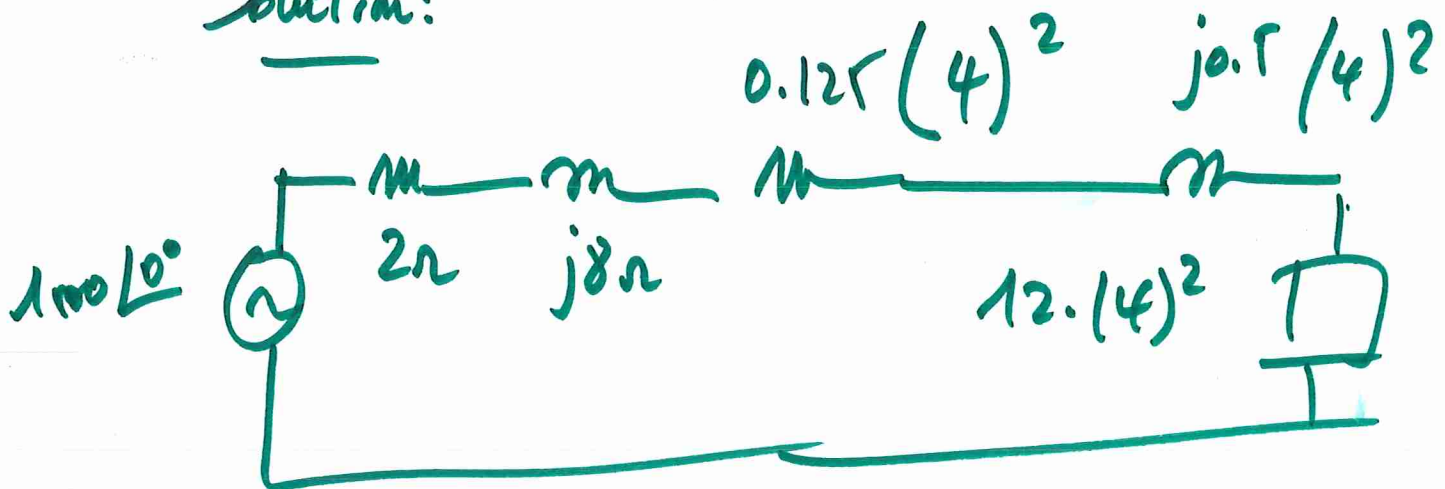

$$\bar{I} = \frac{1000\angle 0^\circ}{(4 + j16) + 192} = 5.08 \angle -4.67^\circ \text{ A}$$

(2).

$$\bar{V}_{\text{load}} = (192\Omega) \bar{I} = \underline{975.36} \angle \underline{-4.67^\circ} \text{ V}$$

$$\bar{V}_{\text{load}} \text{ (LV)} = \frac{975.36 \text{ V}}{4} = \underline{243.8} \angle \underline{-4.67^\circ}$$

$$V_R = \frac{|V_{NL}| - |V_{FL}|}{|V_{FL}|} \cdot 100$$

243.8
243.8

V_{NL} ? $|V_{NL}| = 250.$


$$V_R = 100 \left(\frac{250 - 243.8}{243.8} \right) = \underline{2.54\%}$$

(3)

$$\eta = \frac{P_{out}}{P_{in}} \rightarrow \text{Real power.}$$

$$= \frac{P_{in} - P_{loss}}{P_{in}} \rightarrow \text{related to } R|I|^2.$$

Autotransformer:

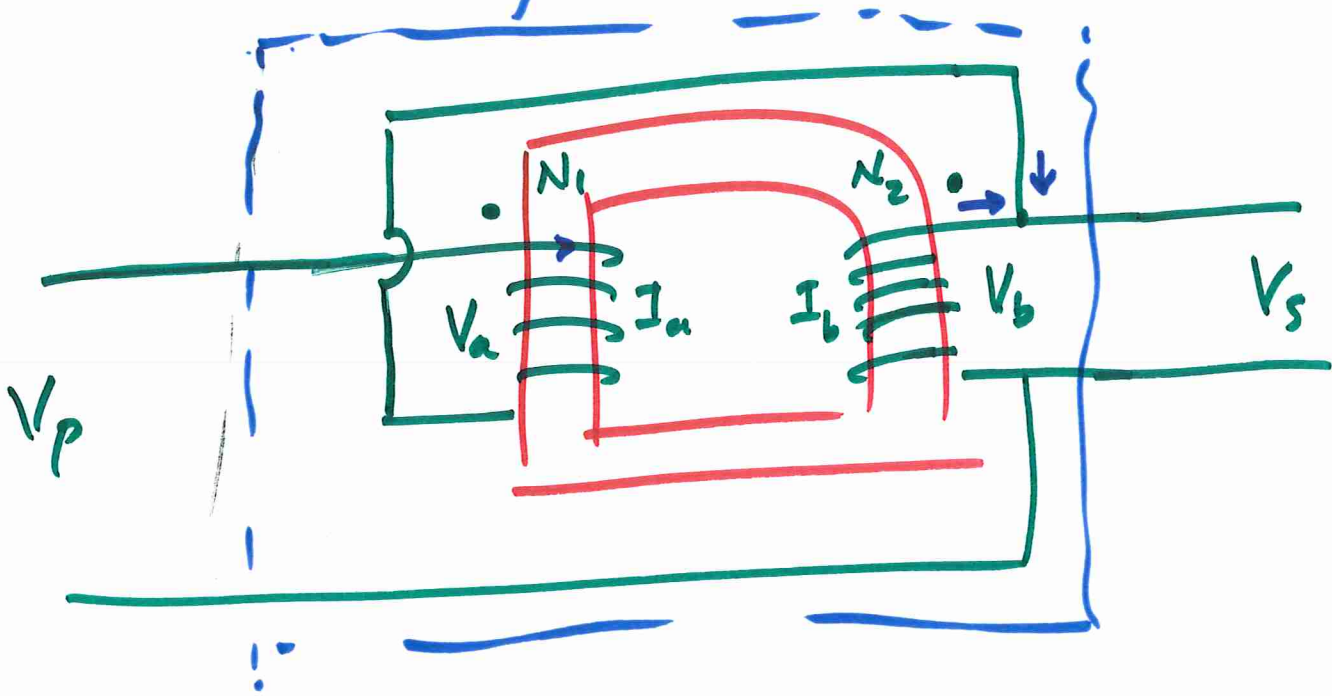

$$\frac{V_a}{V_b} = \frac{N_1}{N_2}, \quad \frac{I_a}{I_b} = \frac{N_2}{N_1}$$

$$\bar{V}_p = \bar{V}_a + \bar{V}_b, \quad I_p = I_a$$

$$V_s = V_b, \quad I_s = I_a + I_b$$


$$\frac{V_p}{V_s} = \frac{V_a + V_b}{V_b} = \frac{V_b \left(\frac{N_1}{N_2}\right) + V_b}{V_b} = \frac{N_1 + N_2}{N_2}$$

$$\frac{I_p}{I_s} = \frac{I_a}{I_a + I_b} = \frac{I_a}{I_a + \left(\frac{N_1}{N_2}\right) I_a} = \frac{1}{\frac{N_2 + N_1}{N_2}}$$

$$\frac{I_p}{I_s} = \frac{N_2}{N_1 + N_2}$$

$$S_p = S_s$$
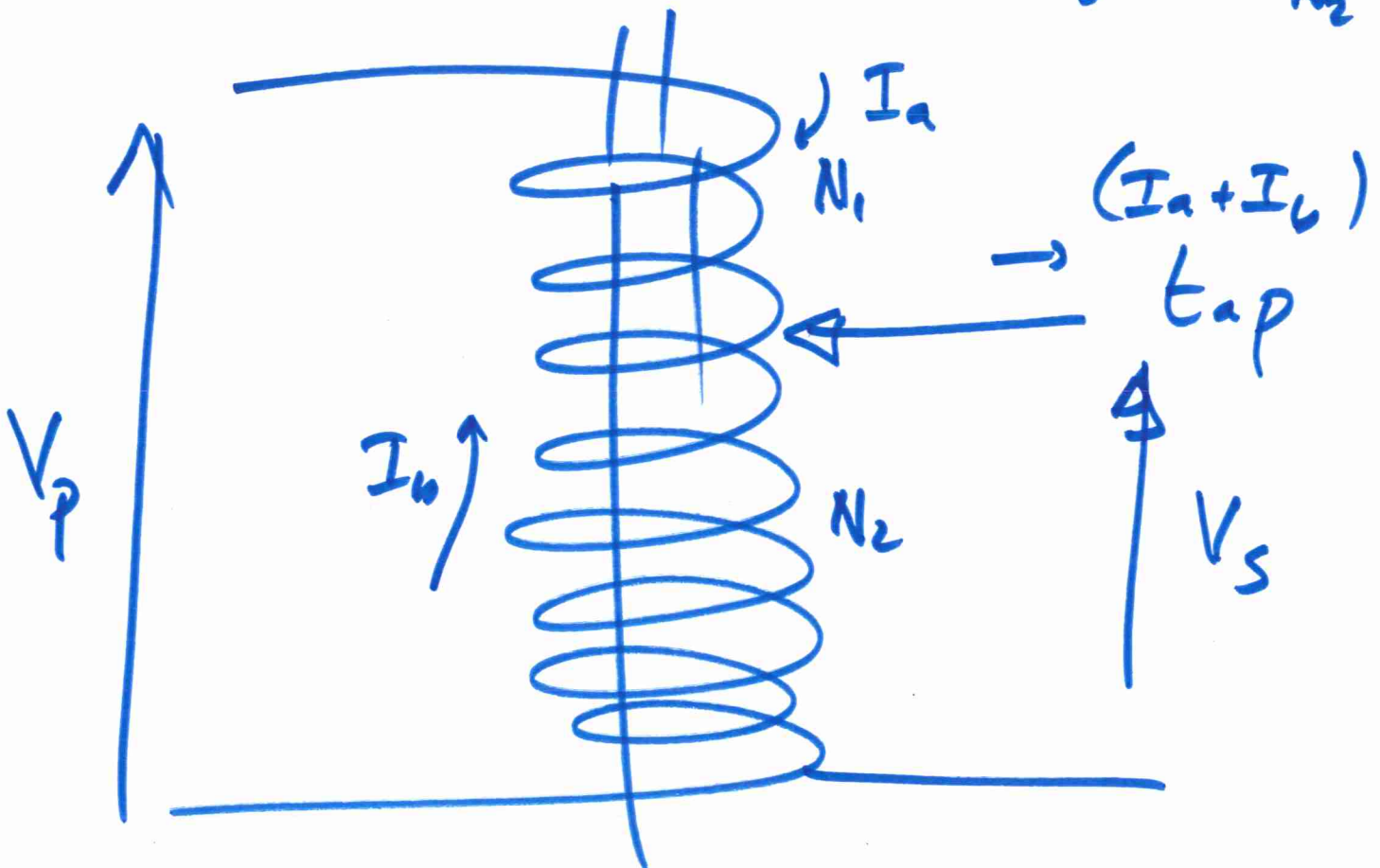
$$\frac{V_p}{V_s} = \frac{N_1 + N_2}{N_2}$$




Example:

A regular transformer 15 kVA.

600V : 120V , 60 Hz.

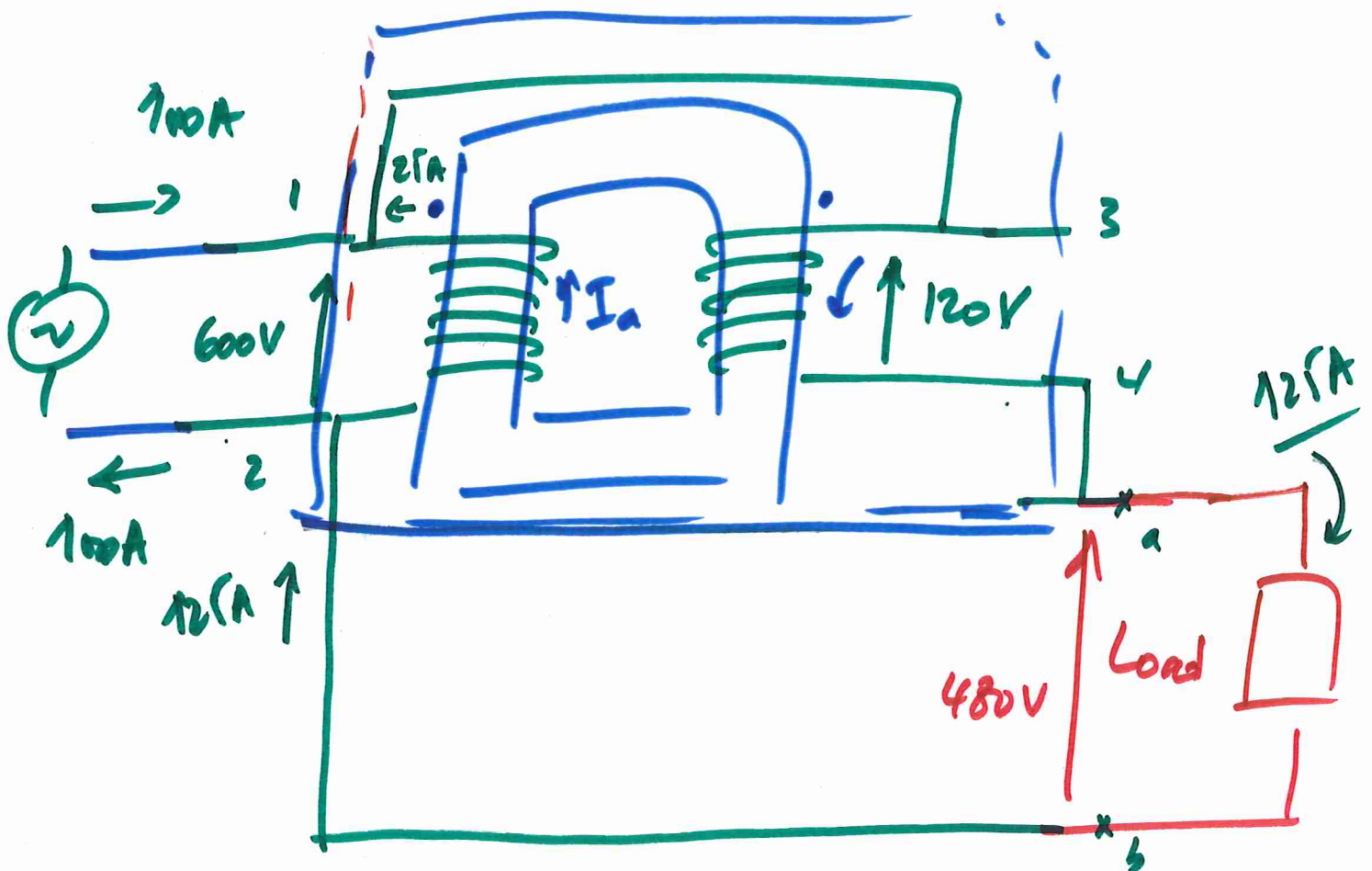- ① Connect as 600V : 480V autotransformer
- ② Find V, I, S at each side.



$$I_a = \frac{15 \text{ kVA}}{600 \text{ V}} = \underline{25 \text{ A}}$$

$$I_b = \frac{15 \text{ kVA}}{120 \text{ V}} = \underline{125 \text{ A}}$$

$$S_p = 600 \text{ V} \cdot 100 \text{ A} = \underline{60 \text{ kVA}}$$

$$S_r = (480 \text{ V}) (125 \text{ A}) = \underline{60 \text{ kVA}}$$