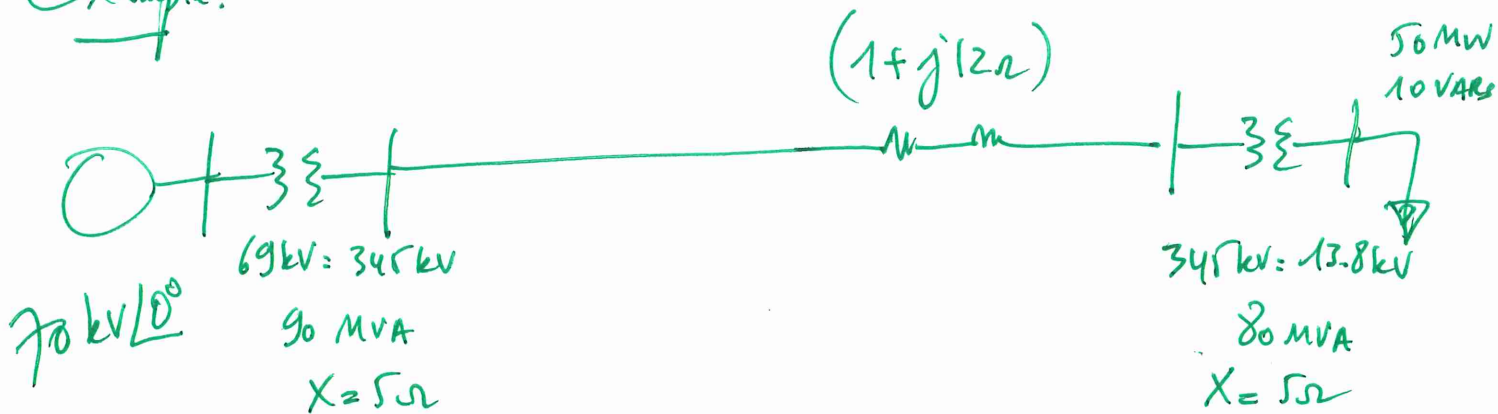


Per Unit analysis:

Advantages:

- Visual analysis of a large power system simplifies.
- Remove transformers to simplify circuit analysis.
- Historically reduced rounding errors on computers.

Example:




Per unit:

1/ Decide power S_{base} .

2/ Pick one voltage & calculate the voltages in the remaining base. zones.

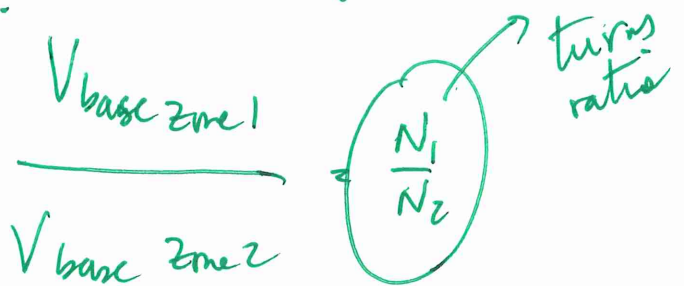3/ Each time you cross a transformer create a new zone.




4/ Calculate Z_{base} in different zones.

5/ Change items in pu.

6/ Do circuit analysis.

7/ Change back if needed

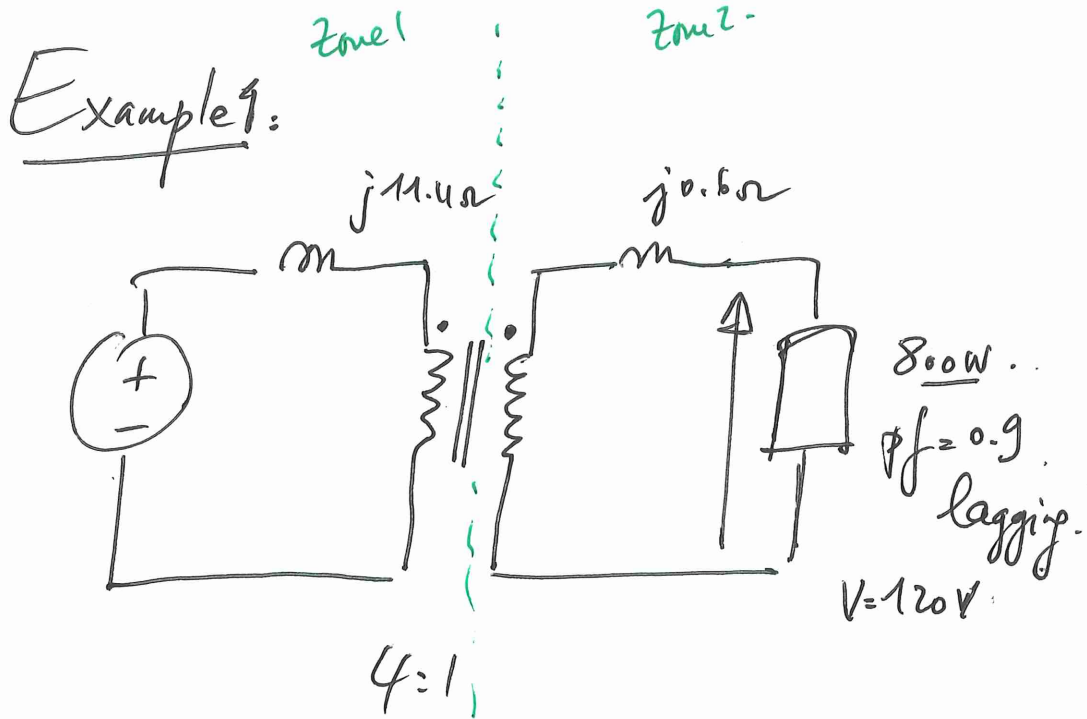

Set up the pu equivalent circuit.

Solution:


$$\begin{cases} S_{\text{BASE}} = 800 \text{ VA} \\ V_{\text{base}_2} = 120 \text{ V} \end{cases}$$

$$V_{\text{base}_1} = \underline{480 \text{ V}}$$

$$\left. \begin{aligned} Z_{\text{base}_1} &= \frac{(480 \text{ V})^2}{800 \text{ MVA}} = \underline{288 \Omega} \\ Z_{\text{base}_2} &= \frac{(120 \text{ V})^2}{800 \text{ MVA}} = 18 \Omega \end{aligned} \right\}$$

$$jX_{1\text{pu}} = \frac{j11.4 \Omega}{288 \Omega} = j0.04 \text{ pu}$$

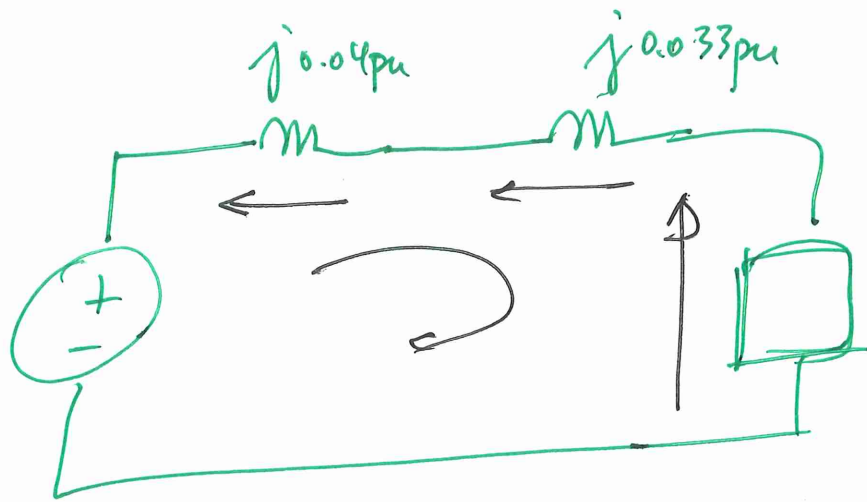
$$jX_{2\text{pu}} = \frac{j0.6 \Omega}{18 \Omega} = j0.033 \text{ pu}$$



$P = 1 \text{ pu}$
 $\text{pf} = 0.9 \text{ lagging}$
 $V = 1 \text{ pu}$

$$\bar{I} = \frac{1}{0.9} \angle -\cos^{-1}(0.9)$$

$$\bar{I} = 1.11 \angle -25^\circ$$

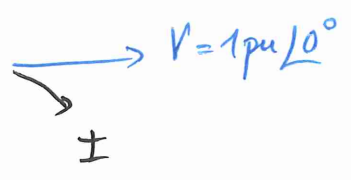

$$\bar{V}_s = (1 \angle 0^\circ) + j(0.073) \cdot 1.11 \angle -25^\circ$$

$$\bar{V}_s = 1.037 \angle 4.1^\circ$$