

Challenges: (Opportunities)

1/ Safety ←


2/ Efficiency, reliability

3/ automation → [Cyber-security]

Cost privacy.

4/ Storage

↳ EVs.

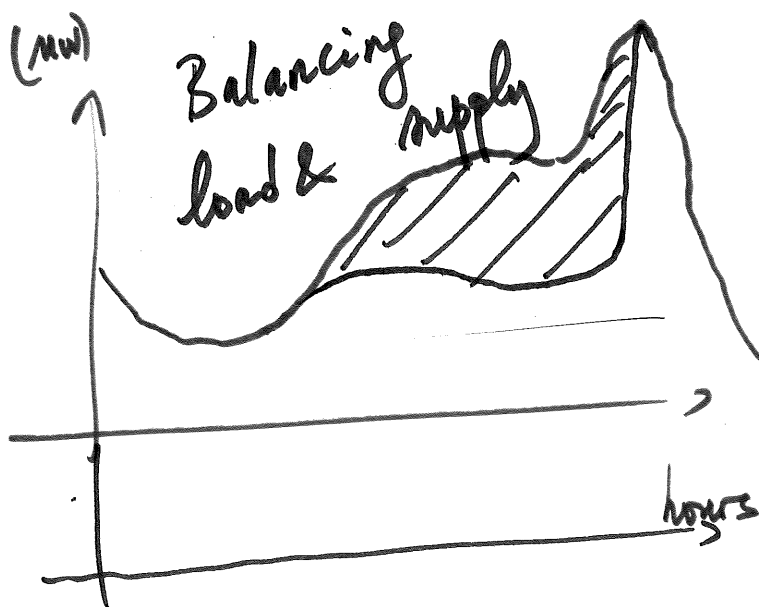

3/ Pollution

4/ Cost

5/ More renewable. (Inverter based generation).

Challenges: (Opportunities)

1/ Safety ←


2/ Efficiency, reliability

3/ automation → [Cyber-security]

Cost privacy.

4/ Storage

↳ EVs.

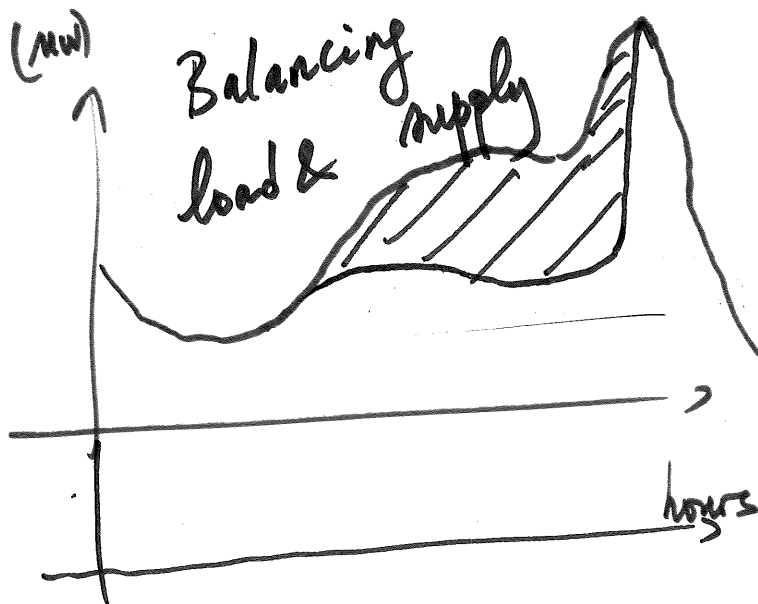

3/ Pollution

4/ Cost

5/ More renewable. (Inverter based generation).

(2)


AC systems:

$$v(t) = V_{max} \cos(\omega t + \delta)$$

V_{max} → Magnitude
 Amplitude
 ω → angular frequency
 δ → phase angle.

60 Hz
 50 Hz

Japan 50 Hz / 60 Hz

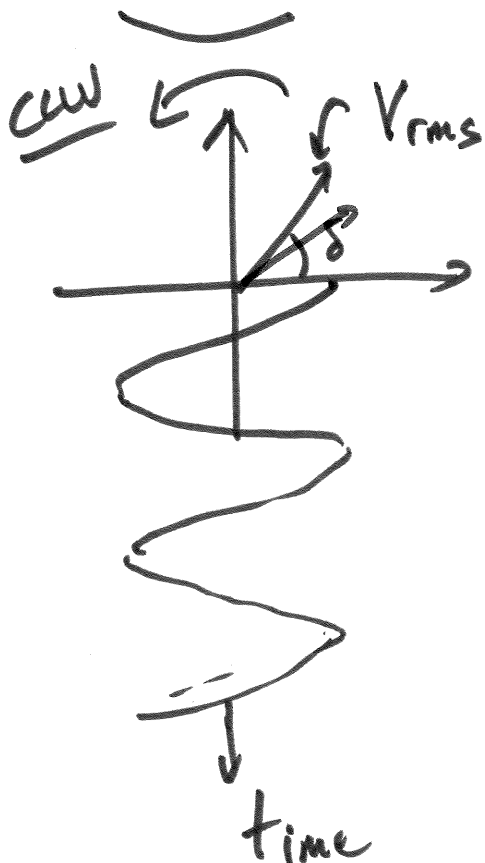

Steinmetz

Phasors.

exponential.

$$\bar{V} = V_{rms} e^{j\delta}$$

$$= V_{rms} \angle \delta \quad \text{Polar form}$$

$$= \underbrace{V_{rms} \cos \delta + j V_{rms} \sin \delta}_{\text{rectangular}}$$

(3).

Example: $i(t) = 100 \cos(\omega t + 60^\circ) \text{ [A]}$

Polar form: $\frac{100}{\sqrt{2}} \angle 60^\circ \checkmark_{OK} \text{ [A]}$

Exponential form: $\frac{100}{\sqrt{2}} e^{j60^\circ} \text{ [A]}$

Rectangular: $\frac{100}{\sqrt{2}} (\cos(60^\circ) + j \sin(60^\circ))$
 $\frac{100}{\sqrt{2}} \left(\frac{1}{2} + j \frac{\sqrt{3}}{2} \right)$

Example: $\bar{V} = 100 \angle 45^\circ \text{ [V]}$

Instantaneous value $v(t) = 100\sqrt{2} \cos(\omega t + 45^\circ) \text{ [V]}$

(4)


Real & reactive power & instantaneous power

$$p(t) = v(t) \cdot i(t)$$

$$v(t) = V_{\max} \cos(\omega t) \quad \rightarrow \quad \frac{V_{\max}}{\sqrt{2}} \angle 0^\circ$$

$$i(t) = I_{\max} \cos(\omega t - \phi) \quad \rightarrow \quad \frac{I_{\max}}{\sqrt{2}} \angle -\phi$$

\bar{I} is lagging

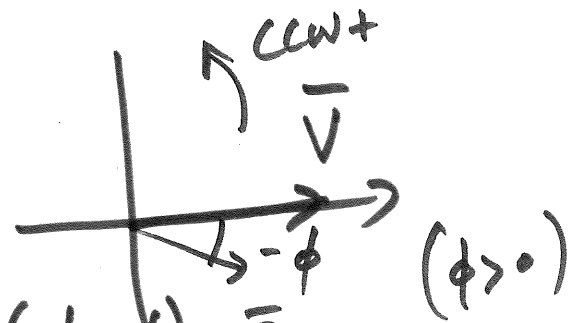

$$p(t) = V_{\max} \cos(\omega t) I_{\max} \cos(\omega t - \phi) \quad \bar{I}$$

$$= V_{\max} I_{\max} \underbrace{\cos^A(\omega t) \cos^B(\omega t - \phi)}$$

$$\cos A \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

$$p(t) = \frac{V_{\max} I_{\max}}{2} [\cos(2\omega t - \phi) + \cos(\phi)]$$

(2) (sqrt(2) * sqrt(2))


$$p(t) = V_{rms} I_{rms} [\cos(2\omega t - \phi) + \cos(\phi)] \quad (5)$$

$$P_{AVE} = V_{rms} I_{rms} \cos(\phi)$$

↳ Real power.

$$F_{AVE} = \frac{1}{T} \int_0^T f(t) dt$$

Example:

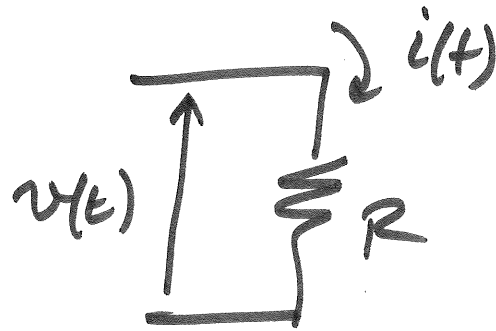

$$v(t) = V_{max} \cos(\omega t)$$

$$i(t) = I_{max} \cos(\omega t - \phi)$$

$$p(t) = V_{max} I_{max} \cos^2(\omega t)$$

$$= \frac{V_{max} I_{max}}{2} [\cos(2\omega t) + \cos(\phi)]$$

$$p(t) = V_{rms} I_{rms} [\cos(2\omega t) + 1]$$