


(1)

01/17/24

53

 $p(t)$? Example: resistor.

$$v(t) = R i(t)$$

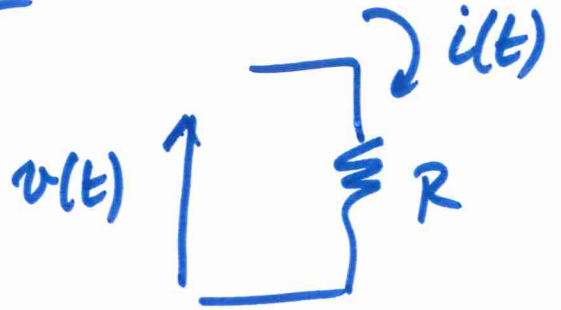

$$i(t) = I_{\max} \cos(\omega t)$$

$$v(t) = V_{\max} \cos(\omega t)$$

$$p(t) = v(t) i(t) = V_{\max} I_{\max} \cos(\omega t) \cos(\omega t)$$

MATH:


$$\cos(A) \cos(B) = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

$$\cos(A) \cos(A) = \frac{1}{2} [\cos(2A) + \underbrace{\cos(0)}_1]$$

$$p(t) = \frac{V_{\max} I_{\max}}{2} [\cos(2\omega t) + 1]$$

$$= \frac{V_{\max}}{\sqrt{2}} \frac{I_{\max}}{\sqrt{2}} [1 + \cos(2\omega t)]$$
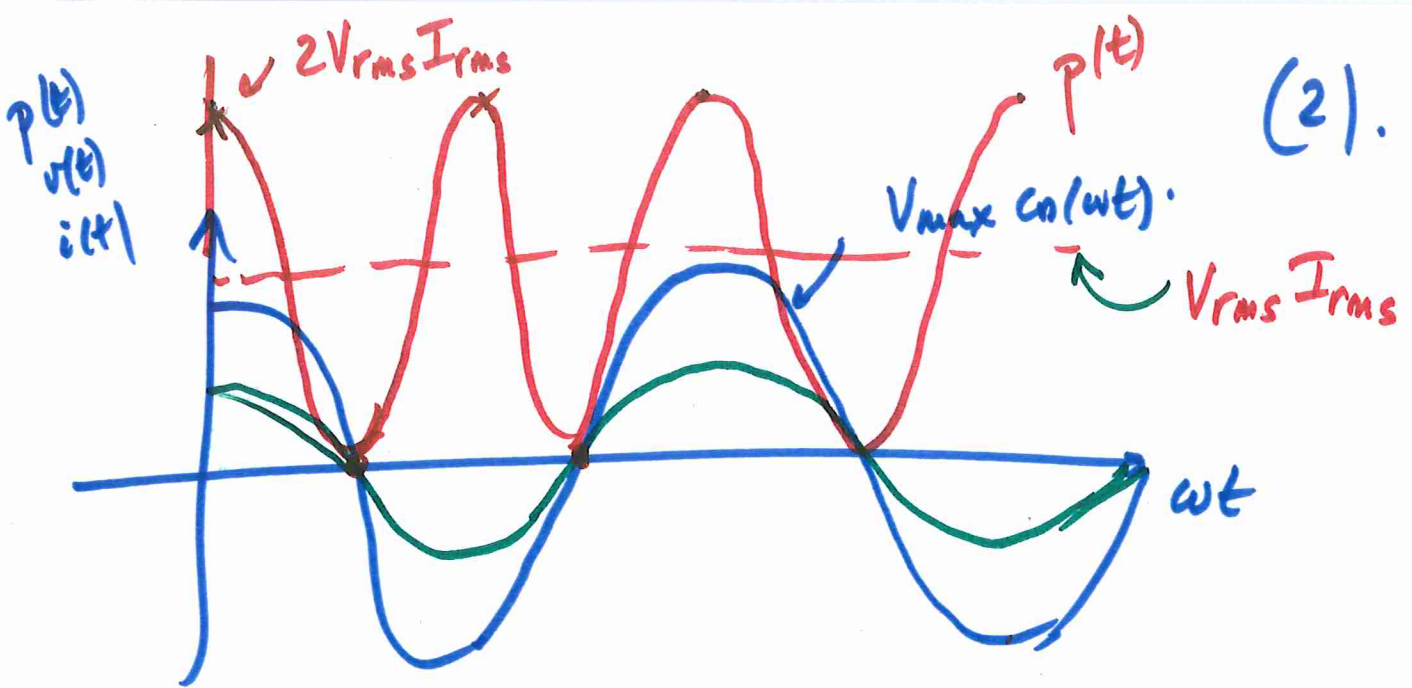
$$p(t) = V_{\text{rms}} I_{\text{rms}} (1 + \cos(2\omega t))$$




power is oscillating at twice the frequency (ω)

if $v(t)$ is at 60 Hz, $p(t)$ oscillates at 120 Hz.

$$P_{AVE} = V_{rms} I_{rms}$$

Inductor:

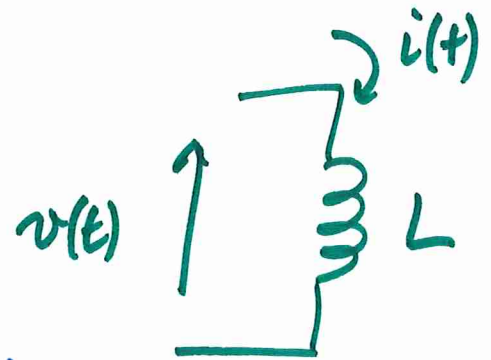
$$\begin{cases} v(t) = V_{max} \cos(\omega t) \\ i(t) = I_{max} \cos(\omega t - 90^\circ) \end{cases}$$



$$v(t) = L \frac{di(t)}{dt}$$

$$I e^{j(\omega t - 90^\circ)}$$

Current lags voltage by 90° .

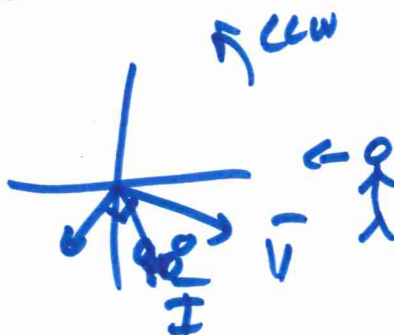


$$p(t) = V_{\max} \cos(\omega t) I_{\max} \cos(\omega t - 90^\circ) \quad (3).$$

$$p(t) = \frac{V_{\max} I_{\max}}{2} \cos(2\omega t - 90^\circ).$$

$$p(t) = \frac{V_{\max} I_{\max}}{2} \sin(2\omega t)$$
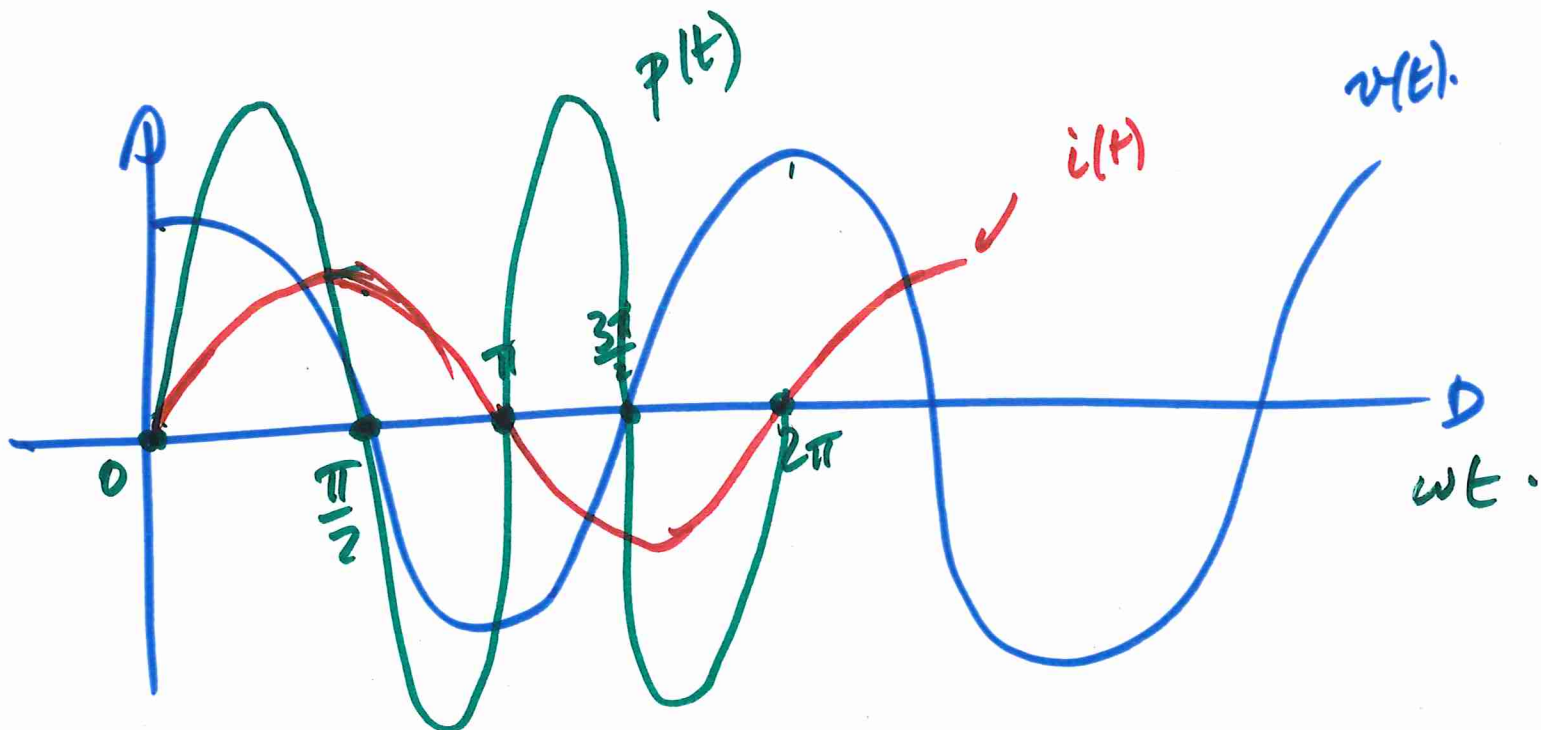
$$p(t) = V_{\text{rms}} I_{\text{rms}} \sin(2\omega t) \checkmark$$



$$P_{\text{AVE}} = 0 \text{ W}$$


Capacitor:

$$v(t) = V_{\max} \cos(\omega t)$$


$$i(t) = I_{\max} \cos(\omega t + 90^\circ)$$

$$i(t) = C \frac{dv}{dt}$$


Current leads the voltage by 90°.

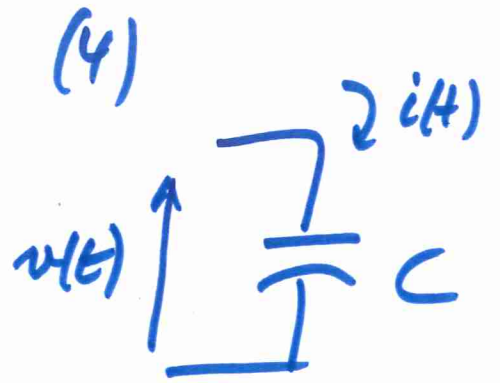
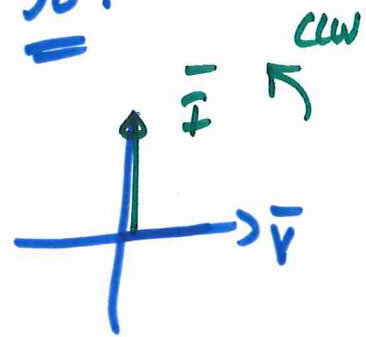
$$p(t) = \frac{V_{\max} I_{\max}}{2} \left[\cos(2\omega t + 90^\circ) + \cos(-90^\circ) \right]$$


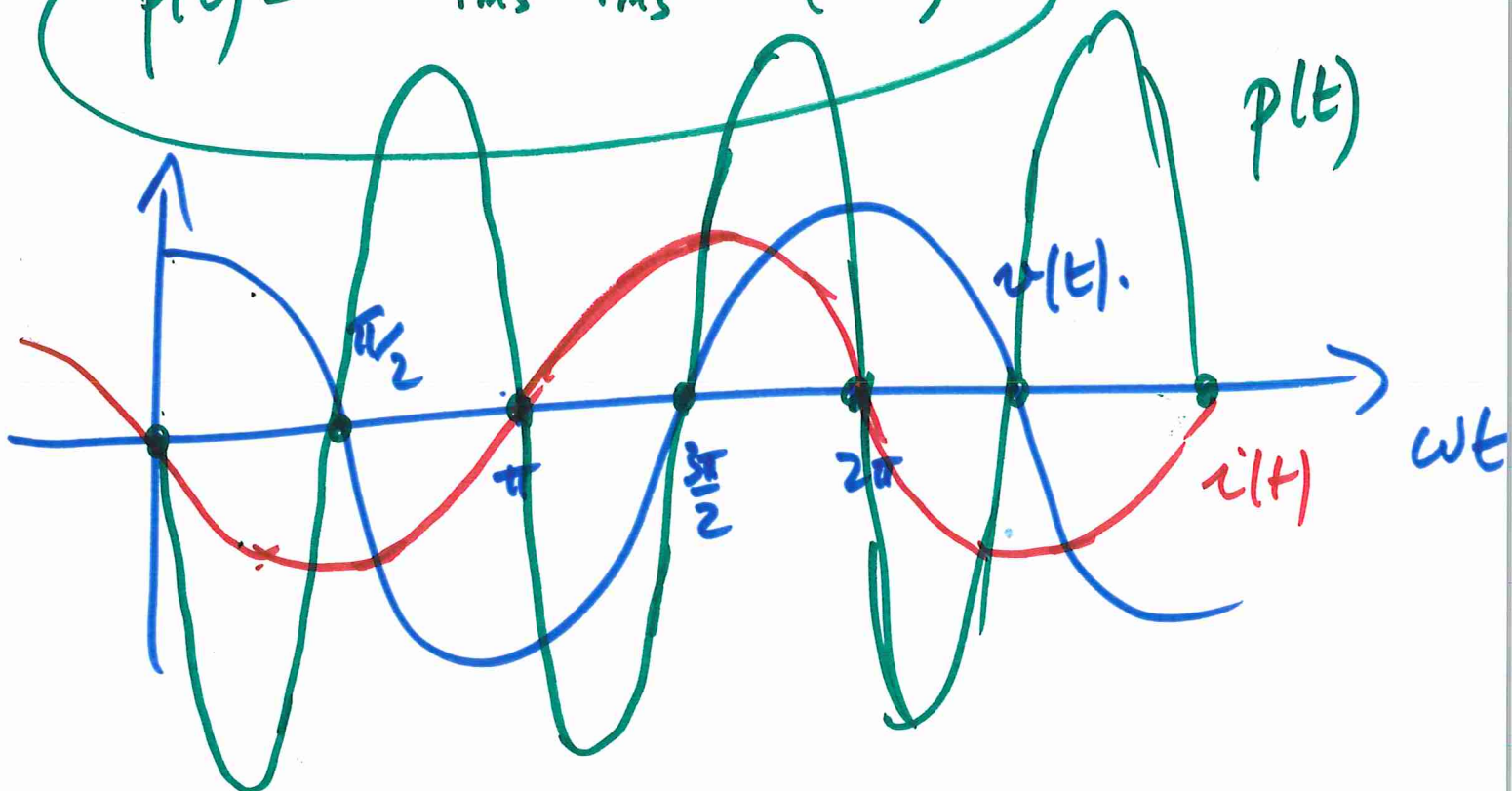
$$p(t) = -V_{\text{rms}} I_{\text{rms}} \sin(2\omega t)$$



In general:

Real power: $P_{\text{real}} = P_{\text{AVE}} = VI \cos(\theta_V - \theta_I)$

Reactive power: $Q = VI \sin(\theta_V - \theta_I)$.

$$\begin{cases} v(t) = V_{\text{max}} \cos(\omega t) \\ i(t) = I_{\text{max}} \cos(\omega t - \theta) \end{cases}$$

$$p(t) = \underbrace{VI \cos \theta}_{P_{\text{real}}} \underbrace{[1 + \cos(2\omega t)]}_{\text{}} + \underbrace{\left(\frac{VI \sin \theta}{Q} \right)}_{\text{}} \underbrace{\sin(2\omega t)}_{\text{}}$$

Resistor: $P = V_{\text{rms}} I_{\text{rms}}, Q = 0$ VARs.
[W].

Inductor: $P = 0, Q = V_{\text{rms}} I_{\text{rms}}$ VARs.

Capacitor: $P = 0, Q = -V_{\text{rms}} I_{\text{rms}}$ VARs.