

# transformers:


Losses  $RI^2$  ( $I \downarrow$ ), losses  $\downarrow$


$P \rightarrow$  far away  $P = VI \cos(\theta_1 - \theta_2)$   
 $P = \text{Re}(\bar{V} \bar{I}^*)$

Step up the voltage  $V \uparrow$ ,  $I \downarrow$  for  
 the same power  
transmitted!

Gen, Motors, transformers ✓ ok.

Ideal transformer:

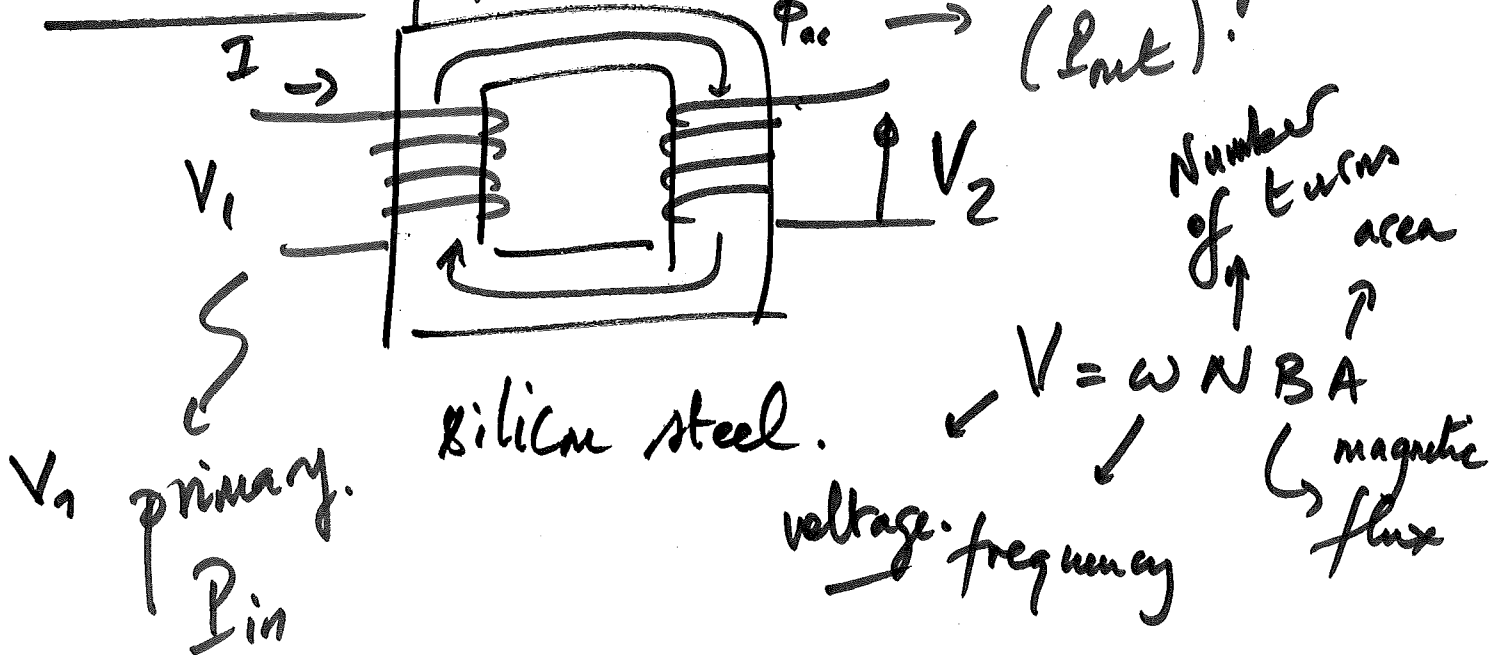

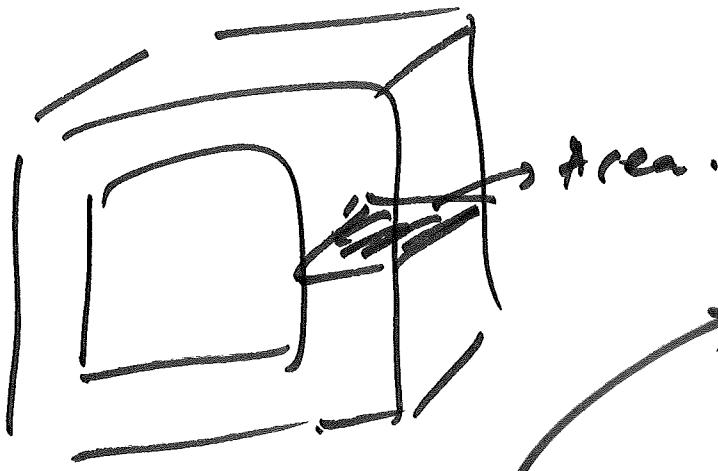


$$N_1 I_1 = N_2 I_2$$


$$\left( \frac{V_1}{V_2} = \frac{N_2}{N_1} \right)$$

$$\left( \frac{V_1}{N_1} \right) = \left( \frac{V_2}{N_2} \right)$$

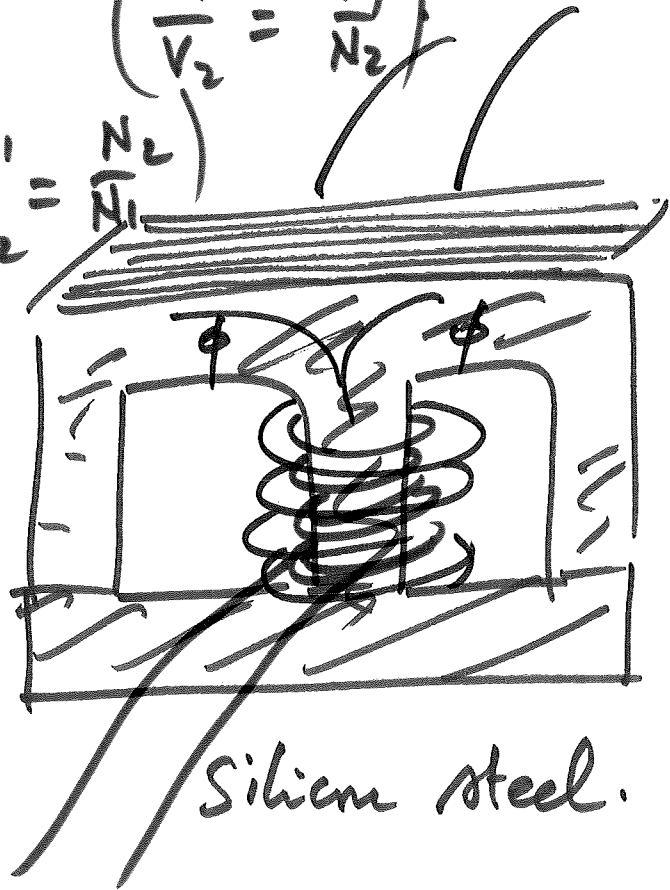
$$\left( \frac{I_1}{I_2} = \frac{N_2}{N_1} \right)$$




Silicon steel.

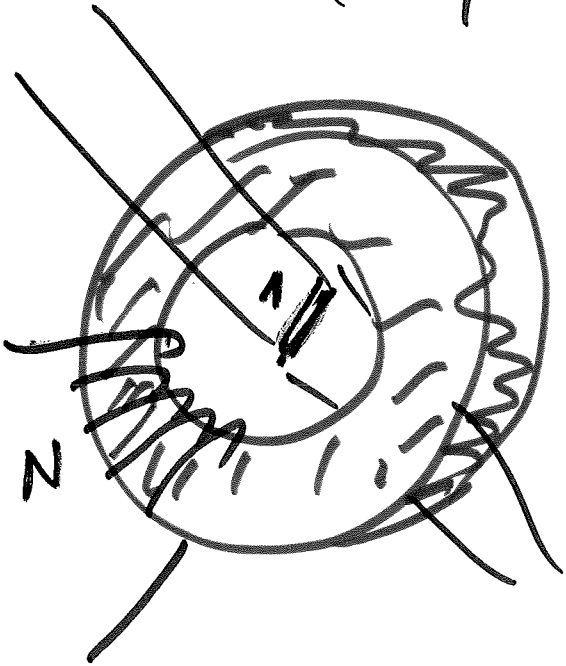
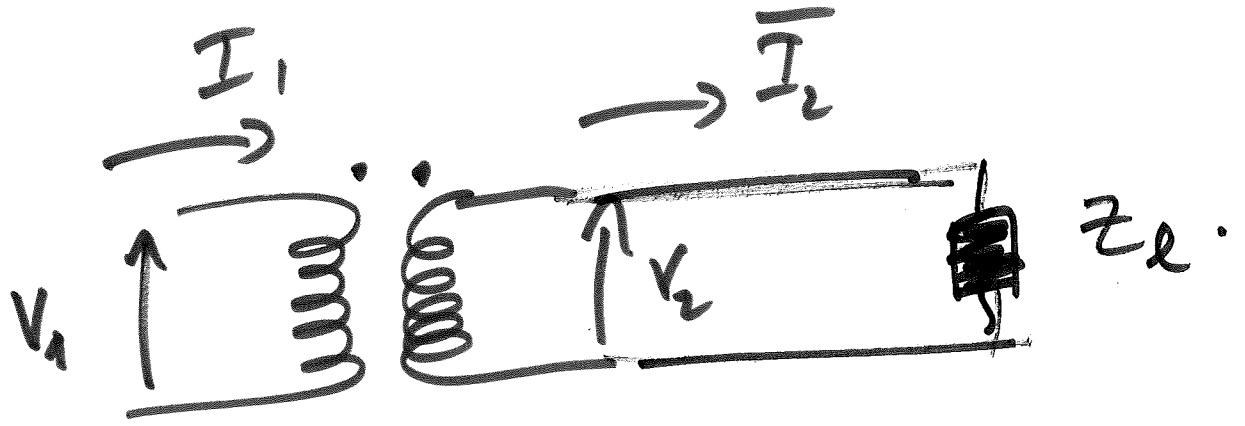
$$S_{in} = V_1 \cdot I_1^* = \left( \frac{N_1}{N_2} \right) V_2 \left( \frac{N_2}{N_1} \right) I_2^* = S_{out}$$



$N_1 : N_2$

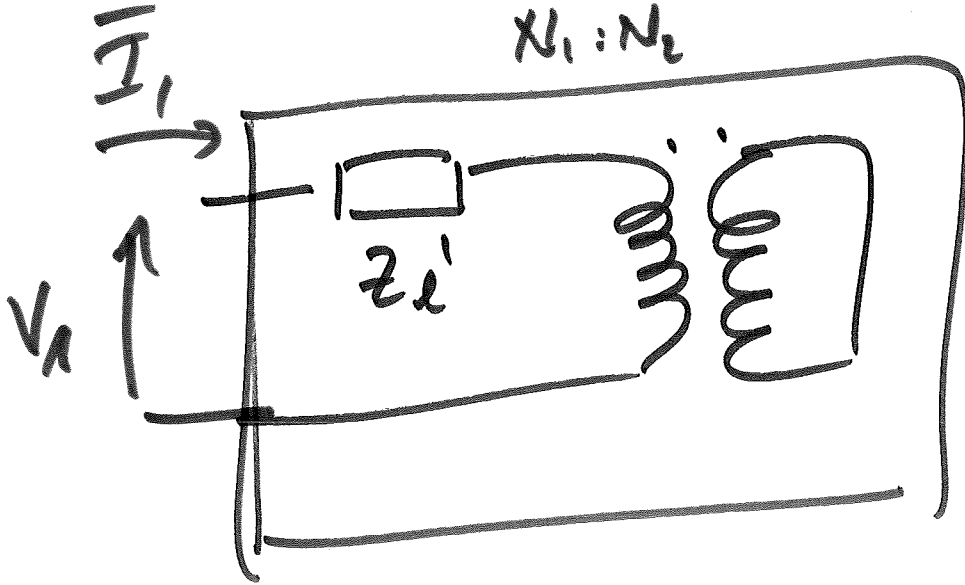

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\frac{V_1}{I_1} = \frac{\left(\frac{N_1}{N_2}\right) V_2}{\left(\frac{N_2}{N_1}\right) I_2} = \left(\frac{N_1}{N_2}\right)^2 \frac{V_2}{I_2}$$

$$\frac{V_1}{I_1} = \left(\frac{N_1}{N_2}\right)^2 Z_L = Z'_L \quad (\text{Impedance reflection})$$