


(1)

02/02/24.

Example:

14.4kV.

$(1.5 + j10) \Omega$
Line.

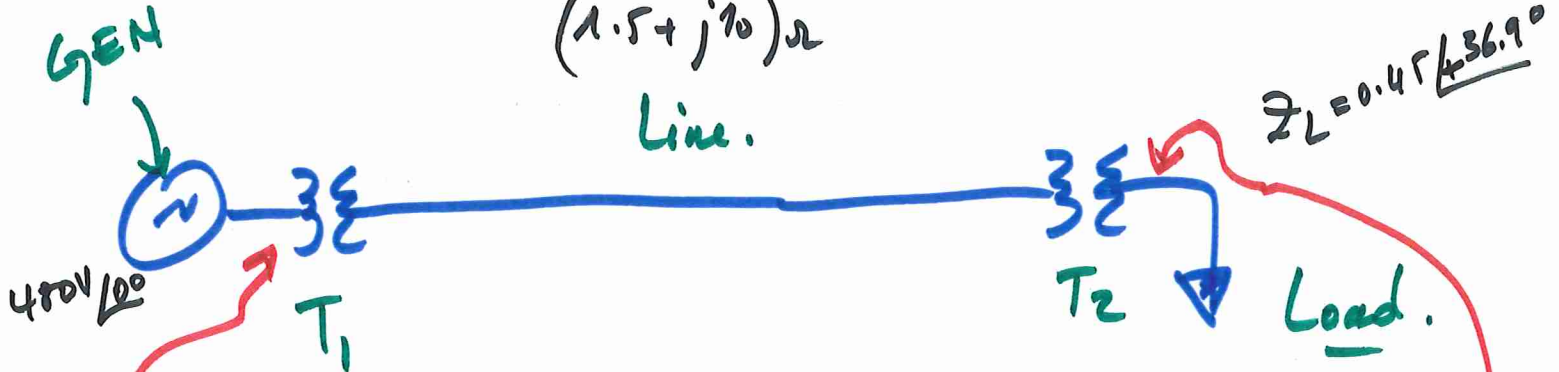

T₁: 480V: 14.4kV


$Z_1 = (0.00238 + j0.00952) \Omega$

T₂: 14.4kV: 480V

$Z_2 = (0.00476 + j0.0203) \Omega$

480V side.

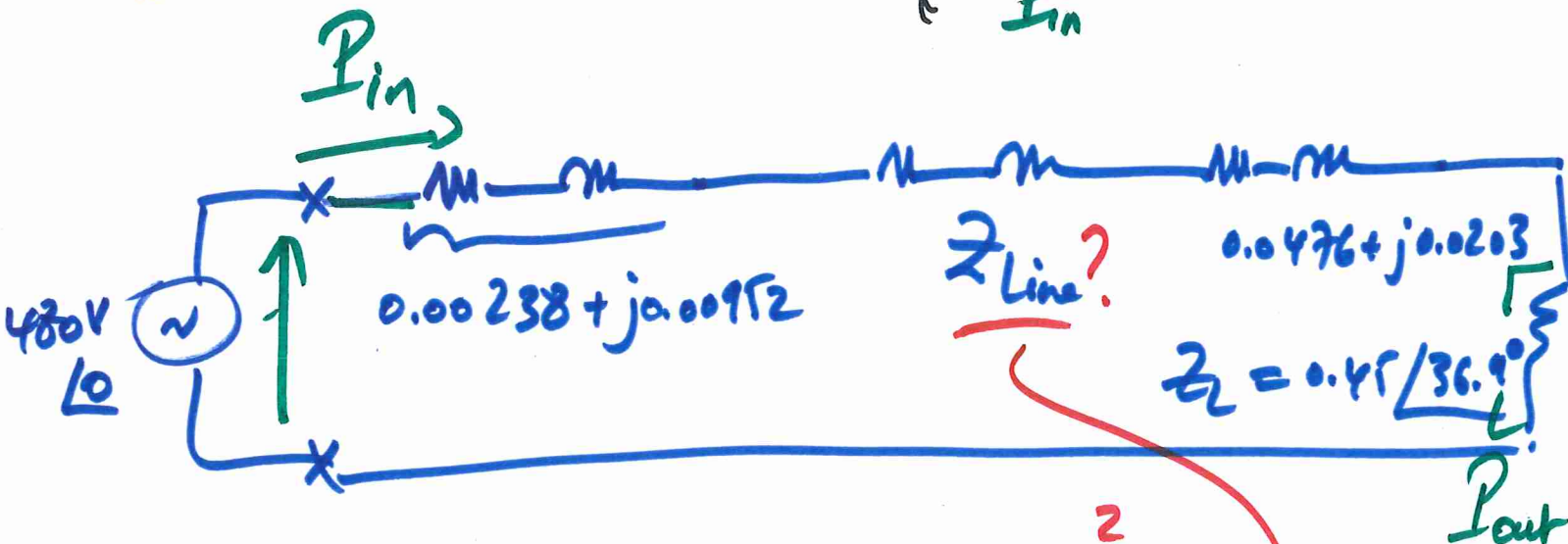Find efficiency, $\eta = \frac{P_{out}}{P_{in}}$ (1)



$Z_{Line} = (1.5 + j10) \cdot \left(\frac{480}{14400}\right)^2 = (1.67 \cdot 10^{-3} + j0.011) \Omega$

②

$$V_L = (480 \angle 0^\circ) \left(\frac{0.45 \angle 36.9^\circ}{z_1 + z_{\text{line}} + z_2 + z_{\text{load}}} \right)$$

$$V_L = (447.1 - j25.4) \text{ [V]}.$$

$$P_{\text{out}} = \text{Re} \left(\frac{|V_L|^2}{z_{\text{load}}} \right)$$

$$P_{\text{out}} = 356.4 \text{ W}.$$


$$P_{\text{in}} = \text{Re} \{ \bar{V}_{\text{source}} \bar{I}^* \}.$$

$$\bar{I} = \frac{480 \angle 0^\circ}{z_1 + z_{\text{line}} + z_2 + z_{\text{load}}} = \left(760.6 - j641.7 \right) \text{ [A]}$$

$$P_{\text{in}} = 365.1 \text{ W}$$

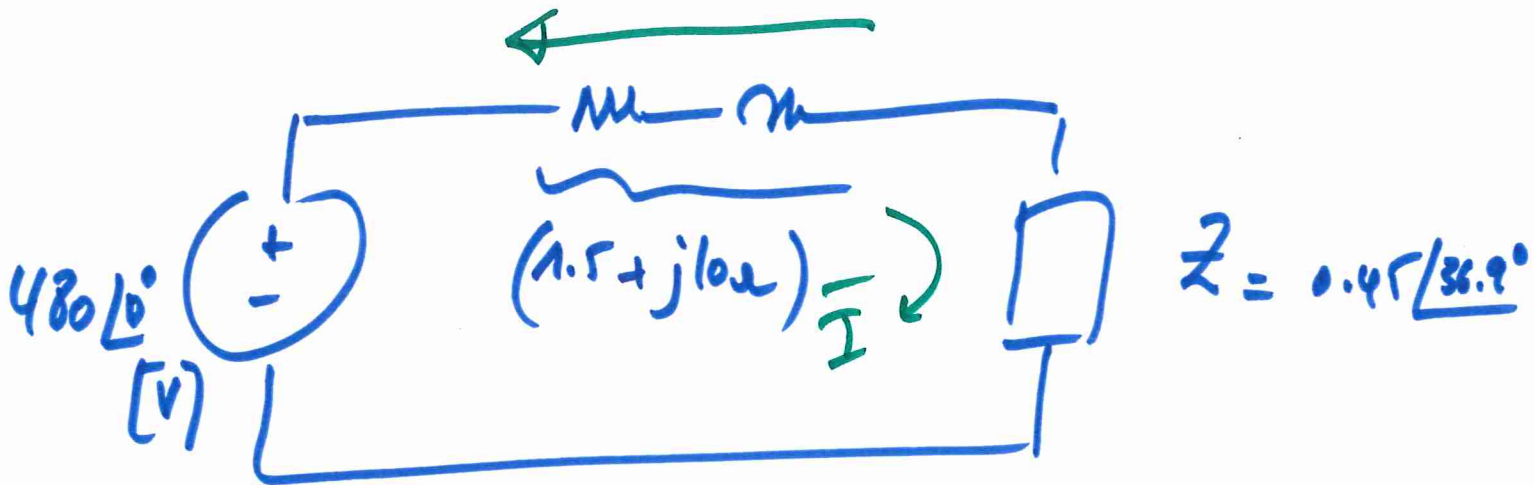(3)

$$\eta = \frac{P_{out}}{P_{in}} = \underline{0.976}$$



$$V_{out} = V_s \cdot \frac{Z_{Load}}{Z_{Load} + Z_{Line}} = \underline{(15.2 - j14.1)V}$$

$$P_{out} = \text{Re} \left(\frac{|V_o|^2}{Z_{Load}^*} \right) = \underline{761.1W} \rightarrow \text{Check!}$$

$$P_{in} = \text{Re} (\bar{V}_s \bar{I}^*) = \text{Re} \left(\bar{V}_s \left(\frac{\bar{V}_{Load}}{Z_{Load}} \right)^* \right)$$

$$P_{in} = 3.93 \text{ kW}$$

$$\eta = \frac{P_{out}}{P_{in}} = \underline{0.193}$$


$$\hookrightarrow (7.2 - j45.3)$$

Example: Operating at its rated S
Transformer 500 kVA.

2400 : 480 V
60 Hz.

- $R_1 = 0.058 \Omega, R_2 = 0.002 \Omega.$
- $X_1 = 0.29 \Omega, X_2 = 0.012 \Omega.$ "one"
- $R_c = 2000 \Omega, X_m = 400 \Omega.$

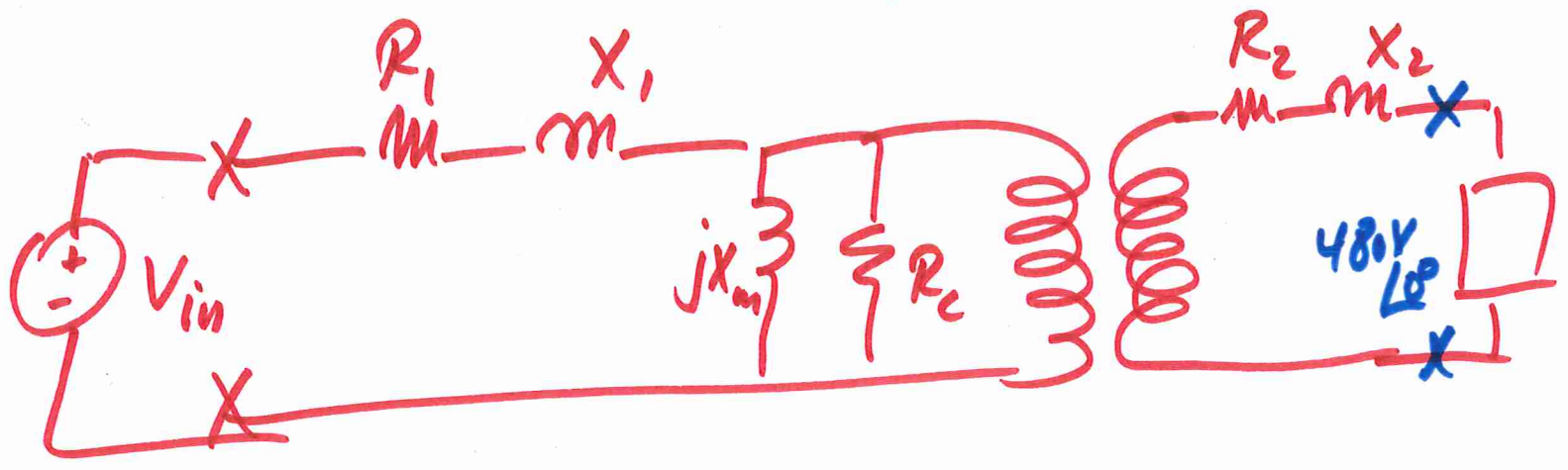$V_{out} = 480V, P_{out} = 0.866$ Lagging.



Find $V_{in}, P_{in}, \eta \rightarrow$ Efficiency.