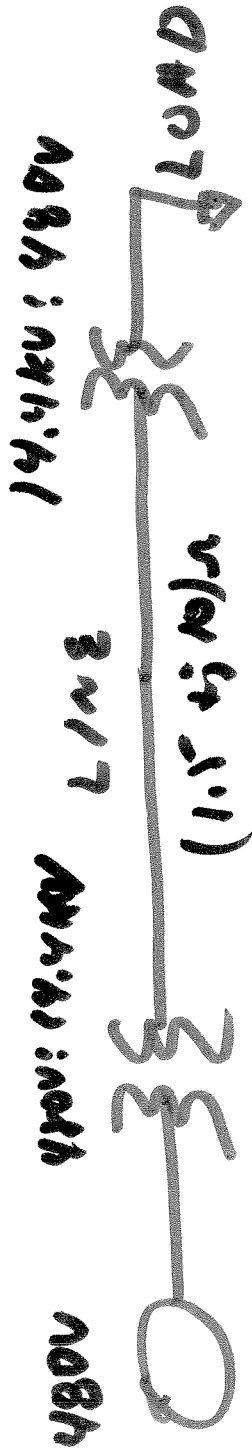


ECE 320 & ECE 329

ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 10




Generator Transformer Transmission Transformer

$$Z_1 = 0.00238 + j0.00952 \Omega$$

$$Z_2 = 0.00476 + j0.00204 \Omega$$

FIND EFFICIENCY.

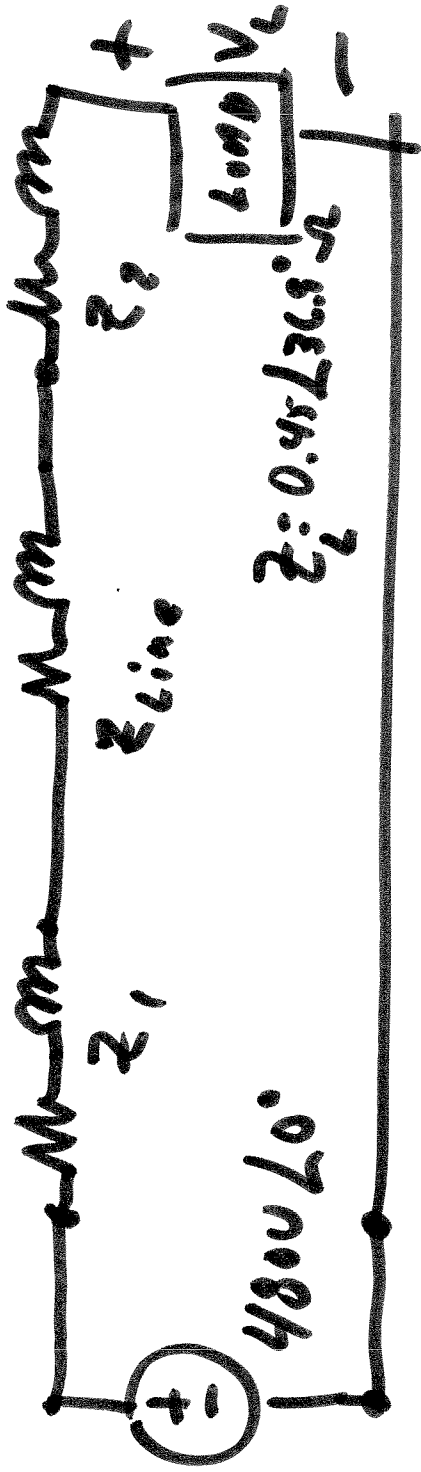

$$Z_{\text{Lin}} = \frac{(1.5 + j10)\Omega}{\left(\frac{14400\text{V}}{480\text{V}}\right)^2}$$

$$Z_{\text{Lin}} = (1.67 + j0.3) \Omega$$

$$V_L = 480\text{V} \angle 0^\circ \left[\frac{0.45 \angle 36.9^\circ \Omega}{Z_1 + Z_{\text{Lin}} + Z_2 + Z_L} \right]$$

$$V_L = (447.1 - j25.4)\text{V}$$

$$P_{\text{out}} = R_L \left[\frac{|V_L|^2}{(0.45 \angle 36.9^\circ \Omega)^2} \right] = \underline{\underline{356.4\text{ W}}}$$

$$P_{in} = \operatorname{Re} [V_s I^*]$$

$$V_s = 480 \angle 0^\circ \text{ V}$$


$$I = \frac{480 \angle 0^\circ}{z_1 + z_{in} + z_2 + z_c} = (760.6 - j641.7) \text{ A}$$

$$P_{in} = \operatorname{Re} [(480 \angle 0^\circ)(760.6 + j641.7)]$$

$$P_{in} = 365.1 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{356.4 \text{ W}}{365.1 \text{ W}} = 0.976$$

w/o TRANSFORMERS

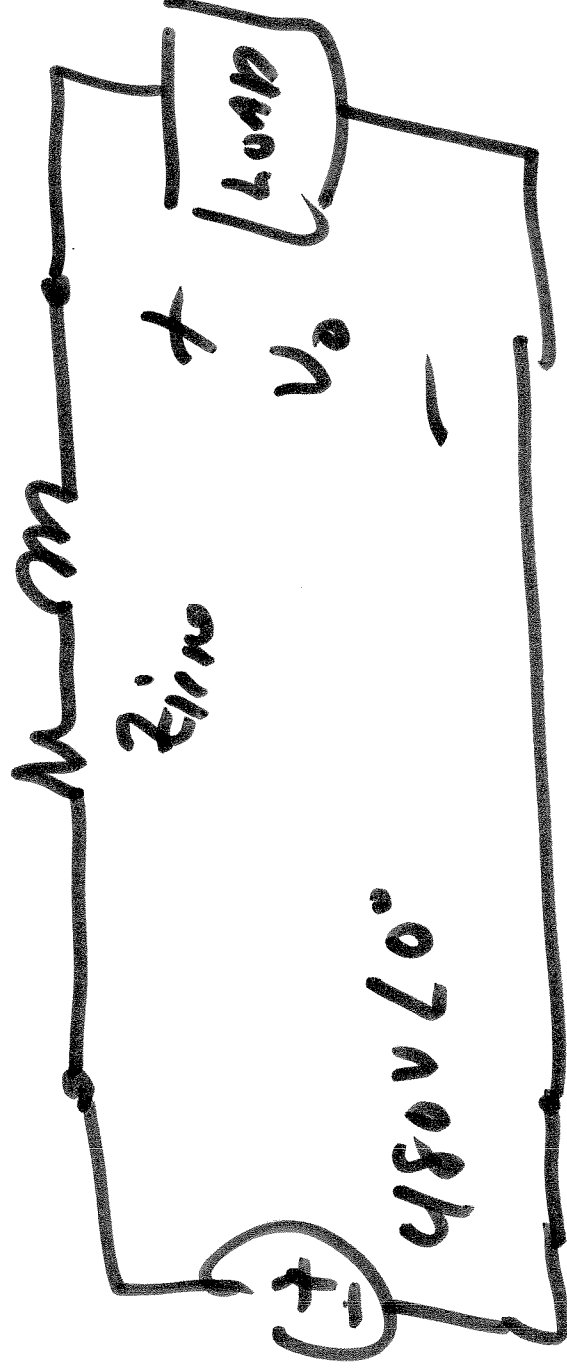

$$V_o = V_s \cdot \frac{Z_L}{Z_L + Z_{line}} = (18.2 - j14.1) \text{ V}$$

$$P_o = R_o \left(\frac{V_o}{Z_L} \right)^2 = 761.1 \text{ W}$$


$$P_{in} = R_0 [V_s I^*]$$


$$I^* = \frac{V_d}{Z_L} = (8.2 - j45.3) A$$

$$P_{in} = R_0 (190.20 W) (8.2 + j45.3) A$$

$$P_{in} = 3.73 \text{ kW}$$
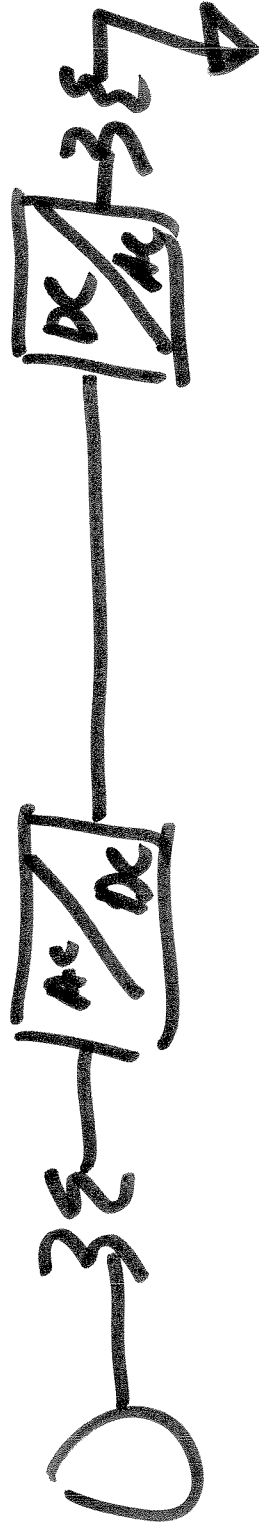
$$\eta = \frac{P_o}{P_{in}} = \frac{261.1 W}{3930 W} = \underline{\underline{0.123}}$$



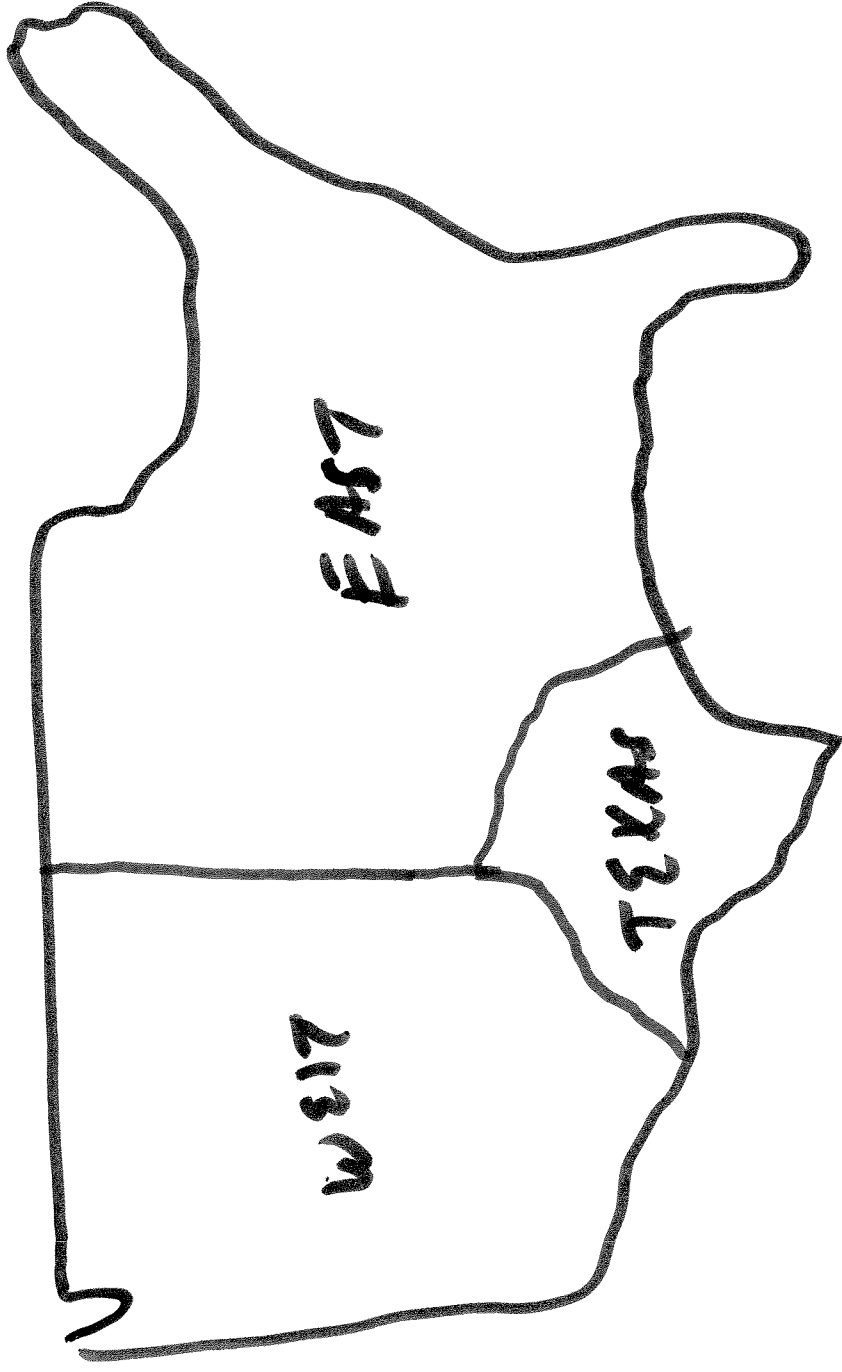




ADMITTANCE $Y_{oc} = \frac{I_{oc}}{V_{oc}}$

CONDUCTANCE $G_{oc} = \frac{P_{oc}}{V_{oc}^2}$

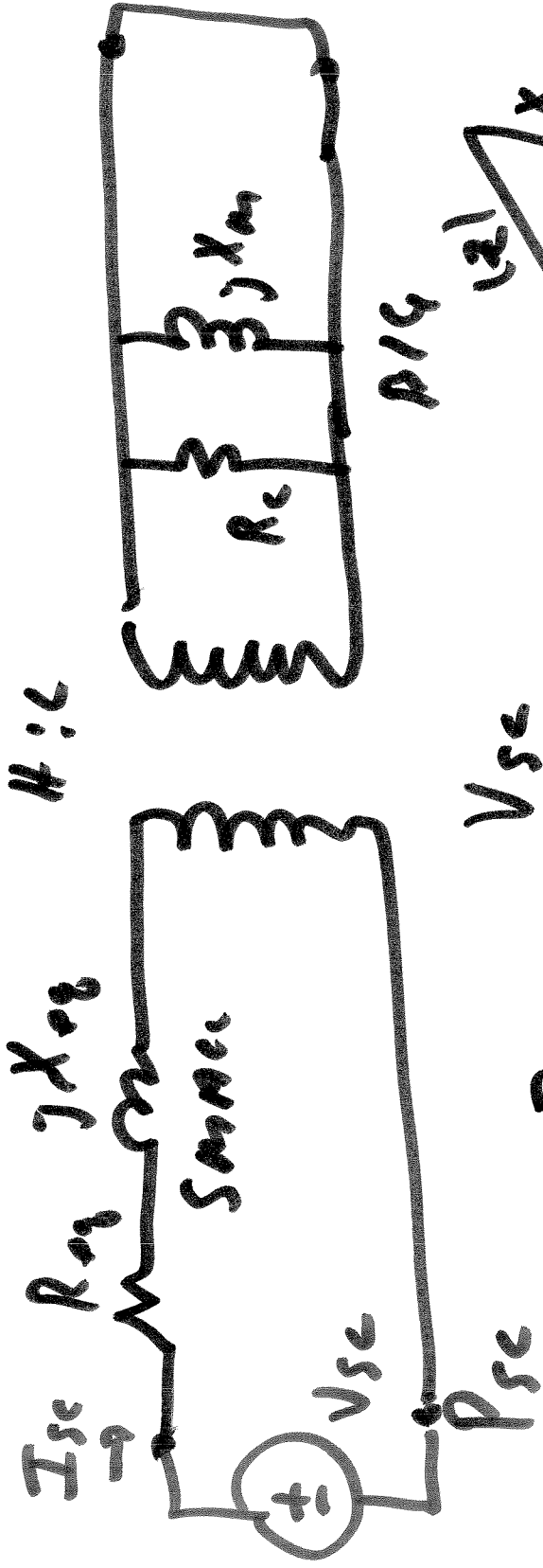SUSCEPTANCE $B_{oc} = \sqrt{Y_{oc}^2 - G_{oc}^2}$






$$Z_{sc} = \frac{V_{sc}}{I_{sc}} = R$$

$$R_{sc} = \frac{P_{sc}}{I_{sc}^2} = R_{sc}$$


$$X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2} = X_{sc}$$

AUTO TRANSFORMER

(VARIAC) $+V(\frac{N_2}{N_1})-$

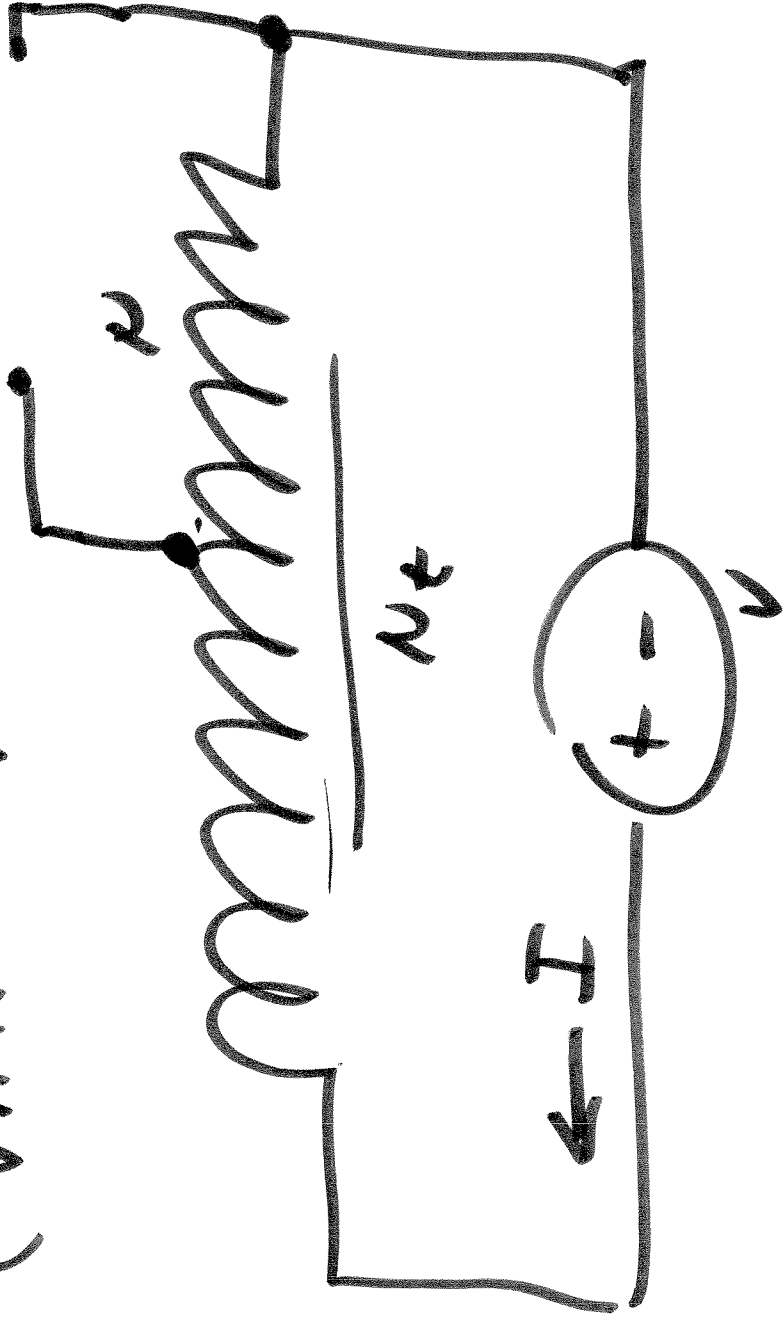

$\Sigma P_{in} = P_{out}$

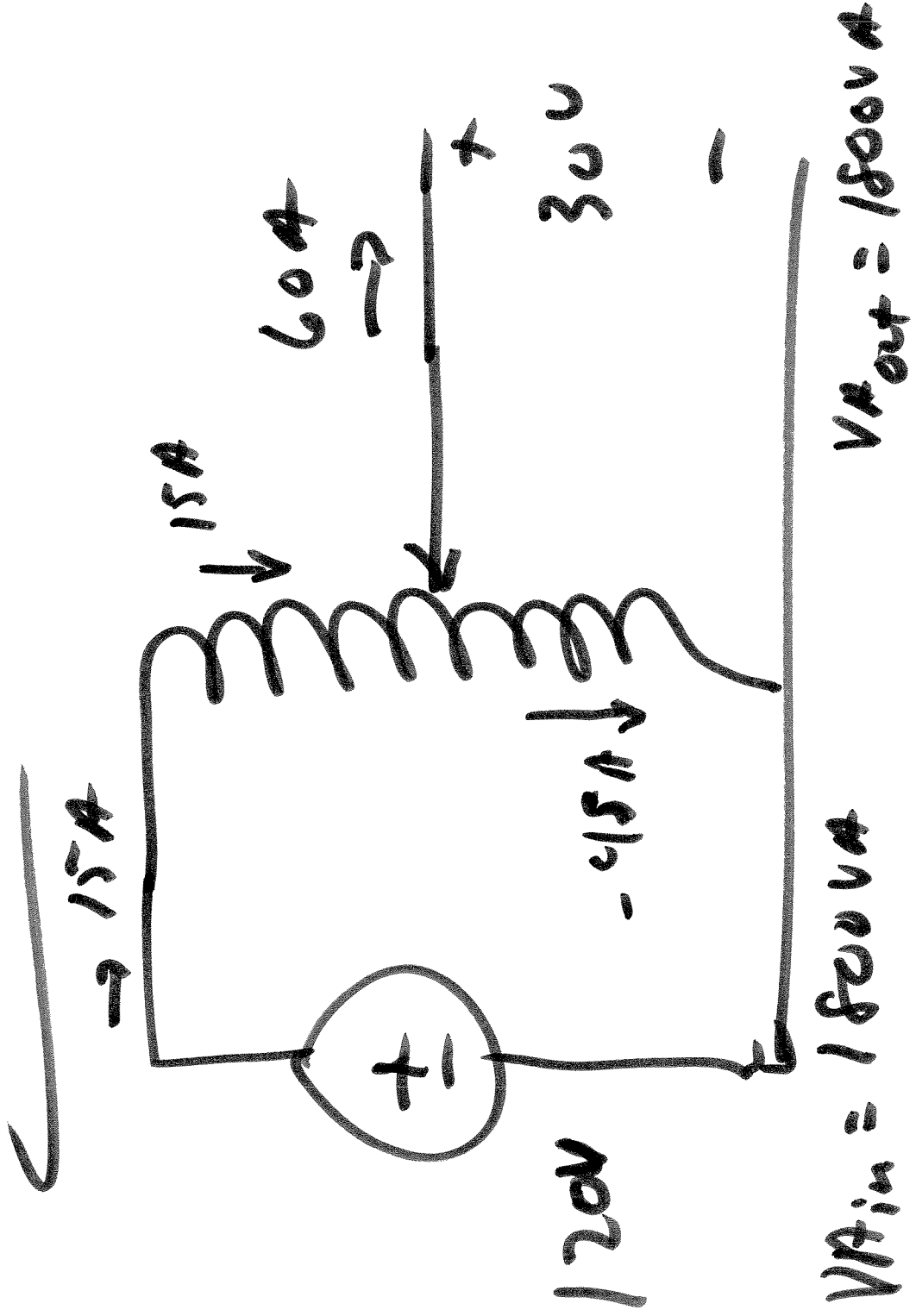

15 A

$$\frac{15}{4} = 3.75 \text{ A}$$

-45 A

ECE 320

Energy Systems I

Lesson 10

Transformers

☺ Variable transformer

☺ Works like a voltage divider

☺ Wind only one coil

☹ Mechanical size scale

☹ No isolation