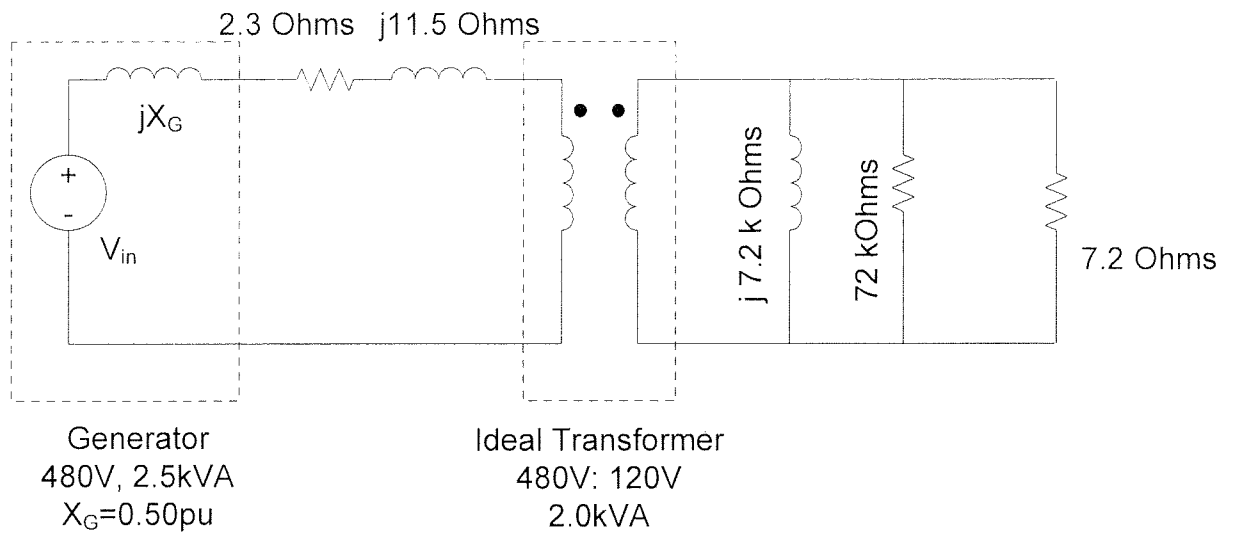


ECE 320 & ECE 329


ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 17


1. (6 points) For the transformer circuit shown below:
 - a. Specify the base for each region of the circuit.
 - b. Convert all the impedances to per unit on the base that you specify.
 - c. Draw the per unit circuit that your analysis creates.



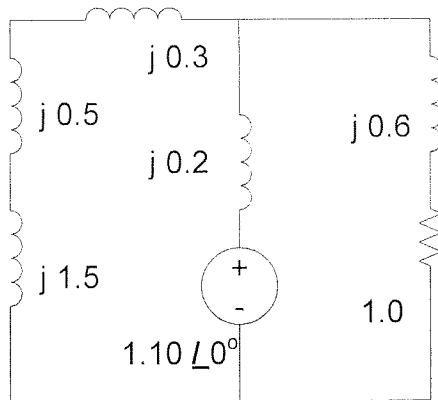2. (4 points) For the per unit circuit shown below, find the real power dissipated in the resistor.



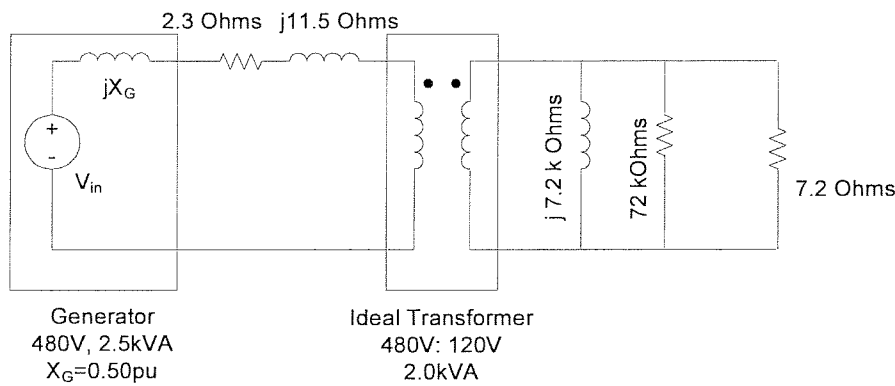1. (6 points) For the transformer circuit shown below:
 - a. Specify the base for each region of the circuit.
 - b. Convert all the impedances to per unit on the base that you specify.
 - c. Draw the per unit circuit that your analysis creates.



Select a base of 480V : 120V, 2.0kVA

$$Z_{\text{baseR}} := \frac{(120 \cdot \text{V})^2}{2000 \cdot \text{V} \cdot \text{A}} = 7.2 \Omega$$

$$Z_{\text{baseL}} := \frac{(480 \cdot \text{V})^2}{2000 \cdot \text{V} \cdot \text{A}} = 115.2 \Omega$$

$$R_{\text{Lpu}} := \frac{7.2 \cdot \Omega}{Z_{\text{baseR}}} = 1$$

$$X_{\text{p}} := \frac{11.5 \cdot \Omega}{Z_{\text{baseL}}} = 0.1$$

$$R_{\text{Cpu}} := \frac{72 \cdot \text{k}\Omega}{Z_{\text{baseR}}} = 1 \times 10^4$$


$$R_{\text{p}} := \frac{2.3 \cdot \Omega}{Z_{\text{baseL}}} = 0.02$$

$$X_{\text{Mpu}} := \frac{7.2 \cdot \text{k}\Omega}{Z_{\text{baseR}}} = 1 \times 10^3$$

Convert the generator to per unit on the system base.

$$Z_{\text{baseG}} := \frac{(480 \cdot \text{V})^2}{2500 \cdot \text{V} \cdot \text{A}} = 92.16 \Omega$$
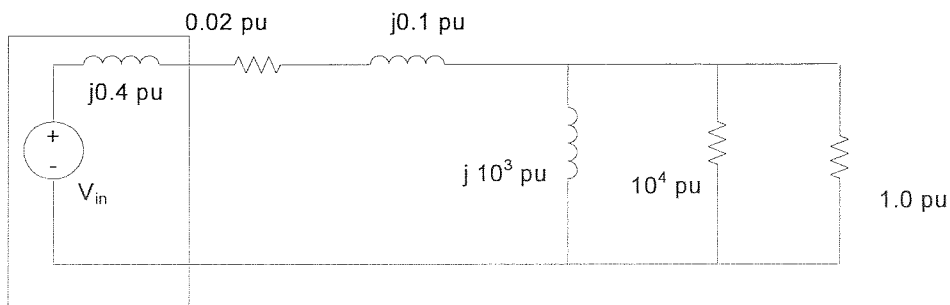
$$X_{\text{G}} := \frac{0.50 \cdot Z_{\text{baseG}}}{Z_{\text{baseL}}} = 0.4$$




2. (4 points) For the per unit circuit shown below, find the real power dissipated in the resistor.

$$j := \sqrt{-1}$$

A node method

$$\frac{V_x - 1.1}{j \cdot 0.2} + \frac{V_x}{j \cdot 2.3} + \frac{V_x}{1.0 + j \cdot 0.6} = 0$$
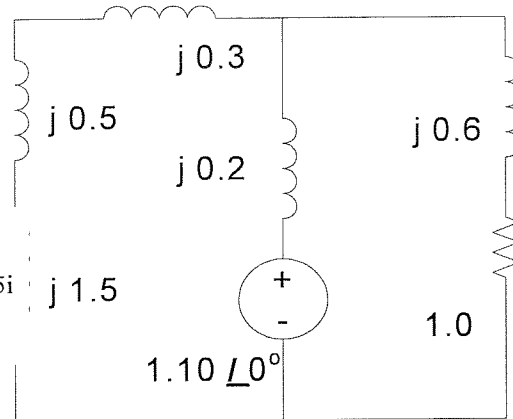
$$V_x := \frac{\frac{1.1}{j \cdot 0.2}}{\frac{1}{j \cdot 0.2} + \frac{1}{j \cdot 2.3} + \frac{1}{(1.0 + j \cdot 0.6)}} = 0.922 - 0.115i$$



Find the resistor current.

$$I_r := \frac{V_x}{1.0 + j \cdot 0.6} = 0.627 - 0.491i$$

Find the resistor power.


$$P_r := \frac{(|I_r|)^2}{1.0} = 0.634$$

Alternative method: use loop equations.

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} := \begin{pmatrix} j \cdot 2.5 & -j \cdot 0.2 \\ -j \cdot 0.2 & 1.0 + j \cdot 0.8 \end{pmatrix}^{-1} \begin{pmatrix} 1.1 \\ -1.1 \end{pmatrix} = \begin{pmatrix} -0.05 - 0.401i \\ -0.627 + 0.491i \end{pmatrix}$$

$$P_r := \frac{(|I_r|)^2}{1.0} = 0.634$$

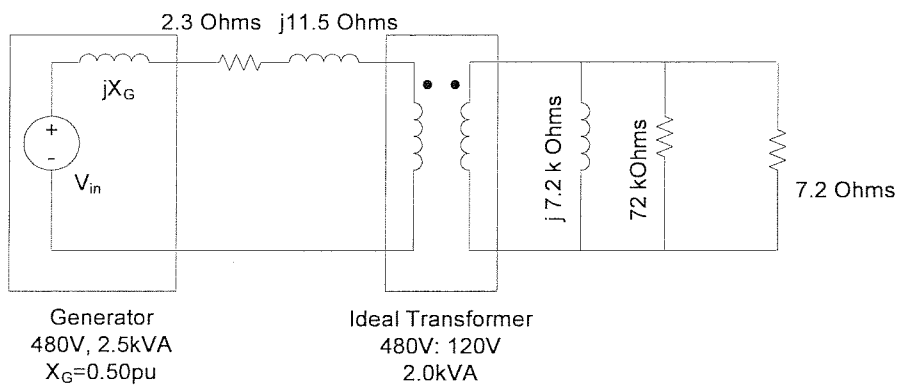1. (6 points) For the transformer circuit shown below:
 - a. Specify the base for each region of the circuit.
 - b. Convert all the impedances to per unit on the base that you specify.
 - c. Draw the per unit circuit that your analysis creates.



Select a base of 480V : 120V, 2.0kVA

$$Z_{\text{baseR}} := \frac{(120 \cdot \text{V})^2}{2000 \cdot \text{V} \cdot \text{A}} = 7.2 \Omega$$

$$Z_{\text{baseL}} := \frac{(480 \cdot \text{V})^2}{2000 \cdot \text{V} \cdot \text{A}} = 115.2 \Omega$$

$$R_{\text{Lpu}} := \frac{7.2 \cdot \Omega}{Z_{\text{baseR}}} = 1$$

$$X_{\text{p}} := \frac{11.5 \cdot \Omega}{Z_{\text{baseL}}} = 0.1$$

$$R_{\text{Cpu}} := \frac{72 \cdot \text{k}\Omega}{Z_{\text{baseR}}} = 1 \times 10^4$$


$$R_{\text{p}} := \frac{2.3 \cdot \Omega}{Z_{\text{baseL}}} = 0.02$$

$$X_{\text{Mpu}} := \frac{7.2 \cdot \text{k}\Omega}{Z_{\text{baseR}}} = 1 \times 10^3$$

Convert the generator to per unit on the system base.

$$Z_{\text{baseG}} := \frac{(480 \cdot \text{V})^2}{2500 \cdot \text{V} \cdot \text{A}} = 92.16 \Omega$$
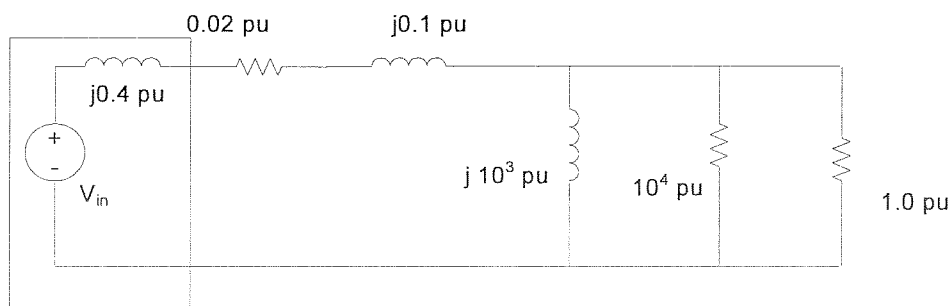
$$X_{\text{G}} := \frac{0.50 \cdot Z_{\text{baseG}}}{Z_{\text{baseL}}} = 0.4$$



ECE 320 / 329 Syllabus

Lsn	Date	Topic	Assignment
Single Phase AC Power			
1	11-Jan-12	Single Phase AC; Power Calculations	Circuits Text
2	13-Jan-12	Recitation: Single Phase AC; Power Calculations	Lesson 1
	16-Jan-12	Holiday	
3	18-Jan-12	Power in Single Phase AC Circuits	Circuits Text
4	20-Jan-12	Reactive and Complex Power	Circuits Text
5	23-Jan-12	Reactive and Complex Power Examples	Circuits Text
6	25-Jan-12	Recitation: Power in Single Phase AC Circuits	Lessons 1-5
Transformers			
7	27-Jan-12	AC Power; Ideal Transformers	C:65-76, 109-115
8	30-Jan-12	Non-ideal transformers	C: 76-90
9	1-Feb-12	Non-ideal transformers	C: 90-94, 100-109
10	3-Feb-12	Non-ideal transformers	C: 76-94, 100-109
11	6-Feb-12	Recitation: Transformers	Lessons 7-10
12	8-Feb-12	Per Unit	C: 94-99
13	10-Feb-12	Transformers Review	C: 76-94, 100-115
Per Unit			
14	13-Feb-12	Per Unit	C: 94-99
15	15-Feb-12	Per Unit	C: 94-99
16	17-Feb-12	Recitation: Per Unit	Lessons 11-12
	20-Feb-12	Holiday	
DC Motors			
17	22-Feb-12	Introduction to DC Motors: Linear DC Motors	C: 32-46, 473-485
18	24-Feb-12	Exam #1: Power Fundamentals and Transformers	Lessons 1-13
19	27-Feb-12	Introduction to DC Motors: Linear DC Motors	C: 32-46, 473-485
20	29-Feb-12	DC Motors	C:514-527
21	2-Mar-12	Recitation: Linear DC Motors	Lessons 21-23
22	5-Mar-12	DC Motors	C: 514-527,533-562
23	7-Mar-12	DC Motors	C: 514-527,533-562
24	9-Mar-12	DC Motors	C: 514-527,533-562
Spring Break			
25	19-Mar-12	DC Motors Example	C: 573-578, 592-594
26	21-Mar-12	Recitation: DC Motors	Lessons 24-28
Circuit Analogs and Lumped Parameter Magnetics			
27	23-Mar-12	Electromechanical Analogs	Handout
28	26-Mar-12	Electromechanical Analogs	Handout
29	28-Mar-12	Exam #2: DC Motors	Lessons 17, 19-26
30	30-Mar-12	Electromechanical Analogs	Handout
31	2-Apr-12	Recitation: Electromechanical Analogs	Lessons 27, 28, 30
32	4-Apr-12	Electromechanical Analogs; Magnetic Circuits	C:1-8
33	6-Apr-12	Magnetic Circuits	C:1-8,28-32

ECE 320 / 329 Syllabus

Lsn	Topic	Assignment
Power Electronics		
34	9-Apr-12 Fundamentals of Power Electronics	H: 185-196
35	11-Apr-12 Ideal Converters: Buck	H: 185-196
36	13-Apr-12 Ideal Converters: DC to DC	H: 196-214
37	16-Apr-12 Ideal Converters: DC to DC	H: 196-214
38	18-Apr-12 Recitation: Ideal DC to DC Converters	Lessons 34-37
39	20-Apr-12 Isolated switch mode power supplies	H: 236-255
40	23-Apr-12 Isolated switch mode power supplies	H: 236-255
41	25-Apr-12 Industrial & Commercial Distribution Systems	Demonstration
42	27-Apr-12 Exam #3: Analogs, Power Electronics	Lessons 27-28, 30-40
Wiring and Power Quality		
43	30-Apr-12 Industrial & Commercial Distribution Systems	Lab Handout
44	2-May-12 Industrial & Commercial Distribution Systems	Lab Handout
45	4-May-12 Power Quality	Demonstration, C:218-222
Final Examination		
46	7-May-12 Final Exam: Due 2:30pm Pacific Time	Lessons 1-45

Textbooks

- Circuits Text: Find and use your own text from your circuits course. If you lost yours, any calculus-based circuits textbook is fine. The major on-line book retailers have a good selection.
- C: Chapman, Electric Machinery Fundamentals, Fifth Ed, ISBN 978-0073529547
We use the Fifth Edition for this course. The Third and Fourth Editions are pretty similar but the homework problems have different numbers. This is the most popular text available for learning electric machines.
- H Daniel W. Hart, Introduction to Power Electronics, ISBN 978-0073380674 (2010 edition)
This is the best introductory power electronics textbook that I have found. No other explains the basics like Dr. Hart.


Outreach Students:

- ECE 320 requires completion of all four exams.
- ECE 329 requires completion of the Final Exam only.

1. Problem 1.9 on page 58 in the textbook.
2. Problem 1.10 on page 58 in the textbook.
3. Problem 1.21 on page 63 of the textbook.
4. Identify the following parts of a DC machine. Your choice of method to identify them.

Armature	Field	Stator	Rotor
Leads	Terminals	Brushes	Field Poles
Field windings	Field magnets	Frame	End caps
Commutator	Armature winding	Teeth	Slots
Bearings	Shaft		

5. For the two circuits below, find the energy efficiency. The inputs are the independent sources; the outputs are the dependent sources.

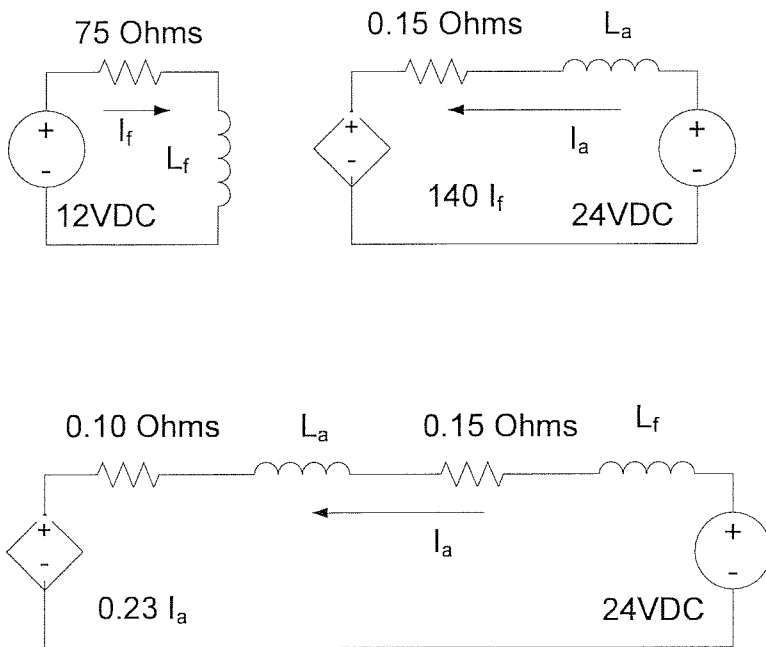

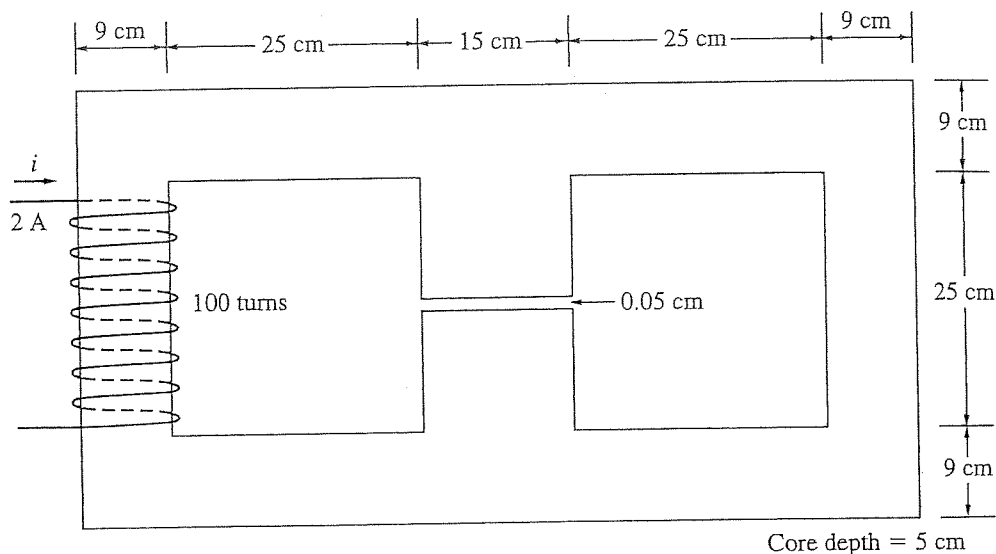


FIGURE P1-5
The core of Problem 1-8.

1-9. A wire is shown in Figure P1-6 that is carrying 2.0 A in the presence of a magnetic field. Calculate the magnitude and direction of the force induced on the wire.

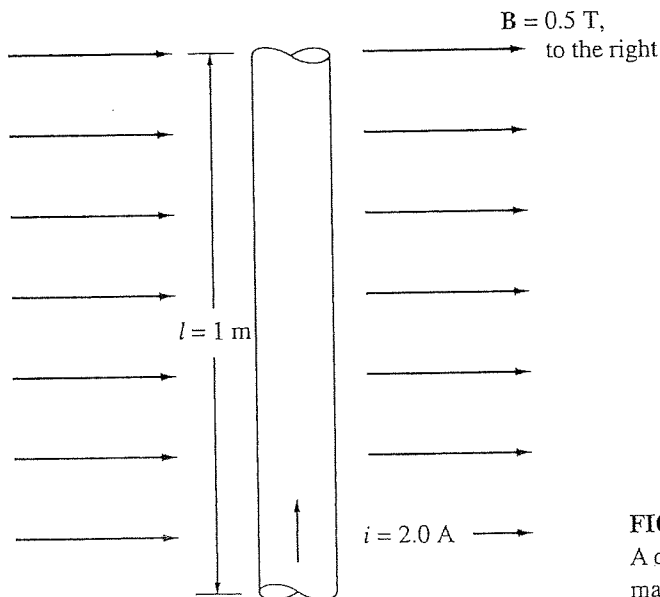
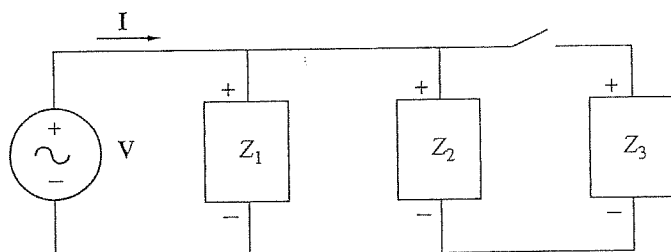


FIGURE P1-6
A current-carrying wire in a magnetic field (Problem 1-9).

- 1-10. A wire is shown in Figure P1-7 that is moving in the presence of a magnetic field. With the information given in the figure, determine the magnitude and direction of the induced voltage in the wire.
- 1-11. Repeat Problem 1-10 for the wire in Figure P1-8.
- 1-12. The core shown in Figure P1-4 is made of a steel whose magnetization curve is shown in Figure P1-9. Repeat Problem 1-7, but this time do *not* assume a constant value of μ_r . How much flux is produced in the core by the currents specified? What is the relative permeability of this core under these conditions? Was the assumption

- (c) Assume that the switch shown in the figure is now closed, and calculate the current I , the power factor, and the real, reactive, and apparent power being supplied by the source.
- (d) How much real, reactive, and apparent power is being consumed by each load with the switch closed?
- (e) What happened to the current flowing from the source when the switch closed? Why?


FIGURE P1-14

The circuit of Problem 1-19.

- 1-20. Demonstrate that Equation (1-59) can be derived from Equation (1-58) using simple trigonometric identities.

$$p(t) = v(t)i(t) = 2VI \cos \omega t \cos(\omega t - \theta) \quad (1-58)$$

$$p(t) = VI \cos \theta (1 + \cos 2\omega t) + VI \sin \theta \sin 2\omega t \quad (1-59)$$


Hint: The following identities will be useful:

$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$

$$\cos(\alpha - \beta) = \cos \alpha \cos \beta + \sin \alpha \sin \beta$$

- 1-21. A linear machine shown in Figure P1-15 has a magnetic flux density of 0.5 T directed into the page, a resistance of 0.25Ω , a bar length $l = 1.0$ m, and a battery voltage of 100 V.

- (a) What is the initial force on the bar at starting? What is the initial current flow?
- (b) What is the no-load steady-state speed of the bar?
- (c) If the bar is loaded with a force of 25 N opposite to the direction of motion, what is the new steady-state speed? What is the efficiency of the machine under these circumstances?

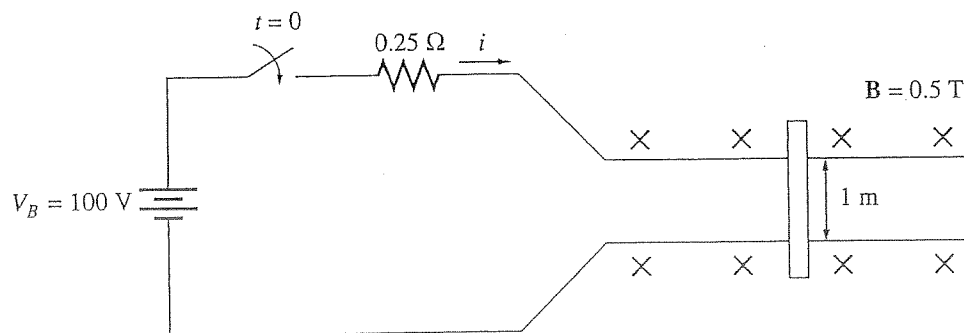
FIGURE P1-15

The linear machine in Problem 1-21.

;

$$\theta = \cancel{\theta} 0.524$$

$$\theta = 30 \cdot \text{deg}$$

ECE 320

Energy Systems I

Lesson 17

Elementary DC Machines

Commutator

Brush

Rotor

Stator

Armature -> rotor DC machine

Field -> Stator DC Machine

Leads

Terminals

Field poles

Field windings

Field magnets

Armature winding

Slots

Teeth

Fan

Shaft

Bearings