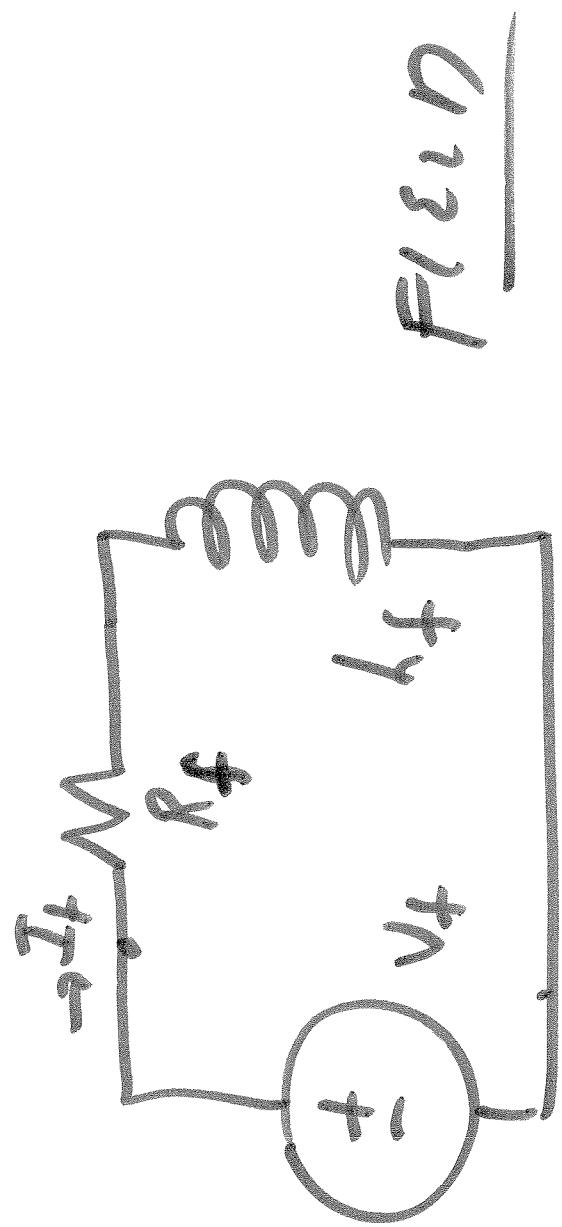



ECE 320 & ECE 329

ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 20



FEM

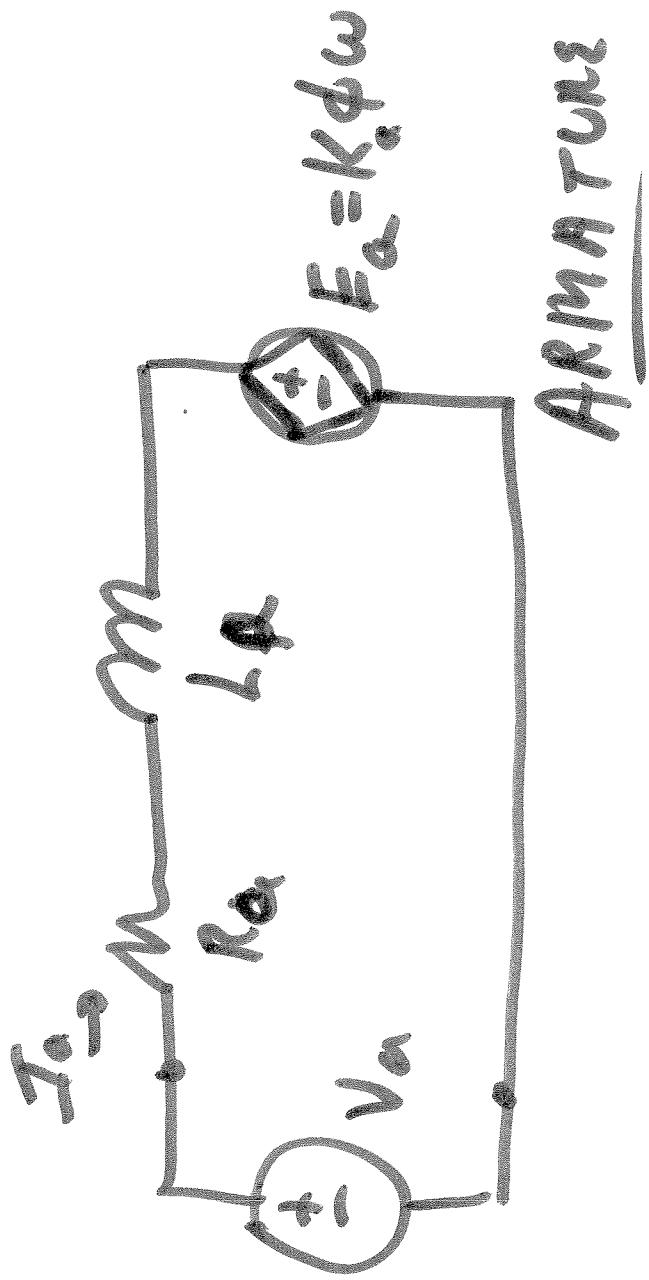

Armature

$$I_e = \frac{K_a \phi_d I_a}{V}$$


Annotations:

- Torque \propto Const Flux current I
- Angle ω
- Voltage V
- Ammeter
- Volts


$$V_a = E_a + R_a I_a + L_a \frac{dI}{dt}$$

$$P_m = T_e \omega = E_a I_a$$


DC Machine Field Connections

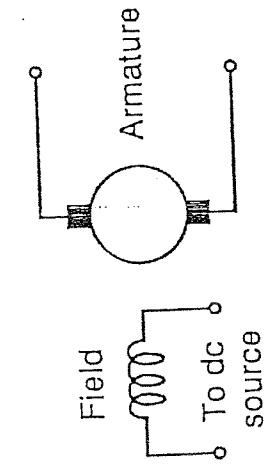


Separate Excitation

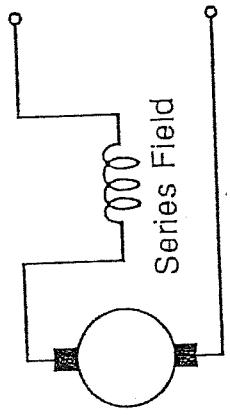

Series Field Connection

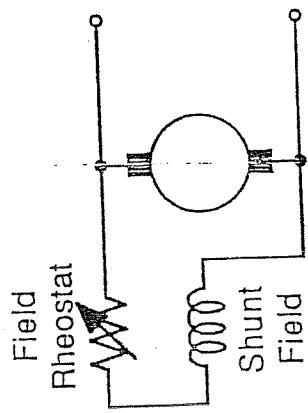


Shunt Field Connection

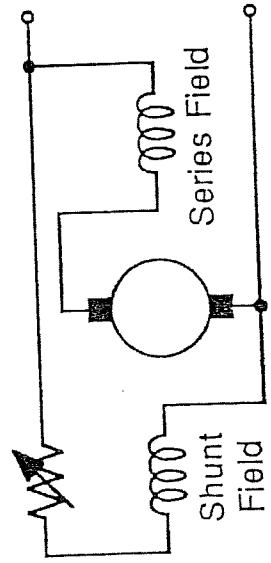

Compound Connection

DC Machine Fundamentals

● Wiring Diagram Symbols

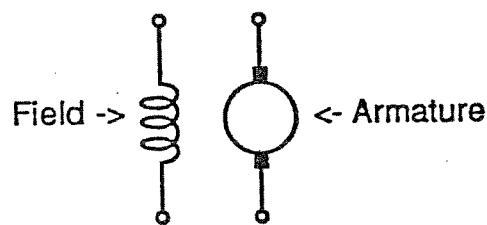

● Field Winding Connections


Separately excited

Shunt



Series

Compound

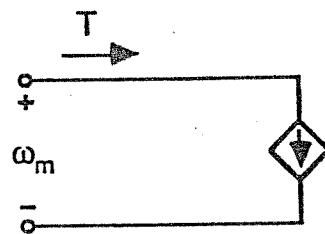● Equivalent Circuit Model (Generator Polarities)



$$\Phi_d = f(I_f)$$

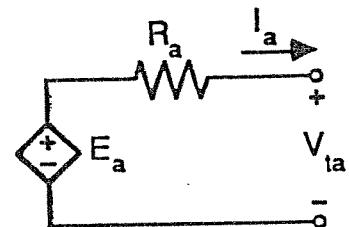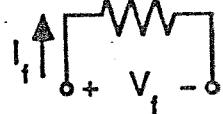

● Relationships

Torque Equation

$$T = K_a \Phi_d I_a$$

$$\omega_m = \frac{2\pi n}{60}$$

Field Equation

$$\Phi_d = f(I_f)$$

$$V_f = I_f R_f$$

$$K_a = \frac{P C_a}{2\pi m}$$

Voltage Equation

$$E_a = K_a \Phi_d \omega_m$$

$$V_{ta} = E_a - I_a R_a$$

ECE 320 / ECE 329

Energy Systems I

Lesson 20

DC Machines Guest Experts