

ECE 320 & ECE 329

ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS


SESSION no. 21

Geometry series
↓ turns

~~2kC~~ N

$$k_a = \frac{1}{2\pi a}$$

↑ parallel paths

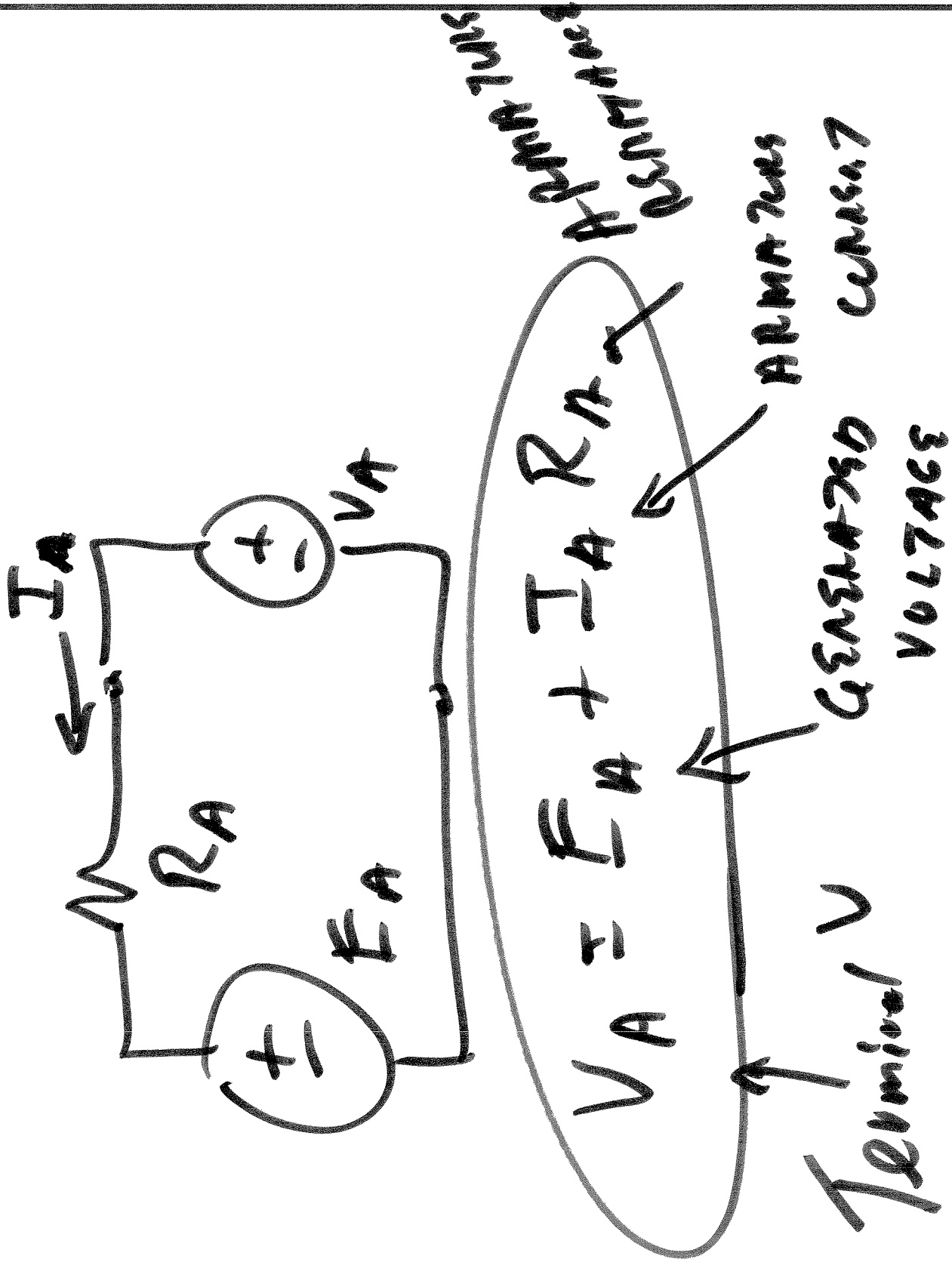


Power

$$P = T \omega = F_A v_A$$

DC Machine Fundamentals

Wiring Diagram Symbols

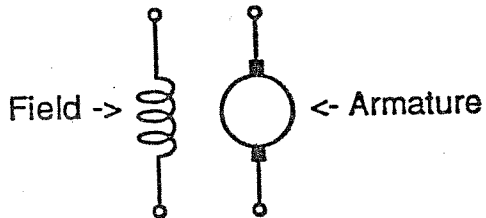

Field Winding Connections

Separately excited



Shunt

Series


Compound

Equivalent Circuit Model

(Generator Polarities)

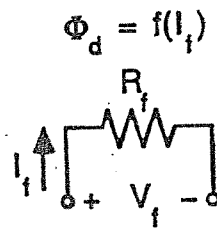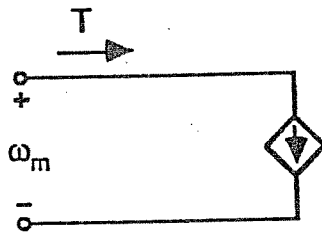

$$\Phi_d = f(I_f)$$

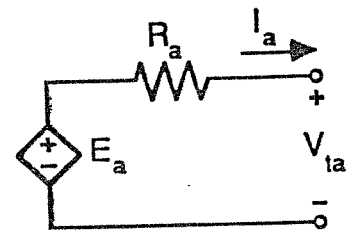

Relationships

Torque Equation

$$T = K_a \Phi_d I_a$$

$$\omega_m = \frac{2\pi n}{60}$$

Field Equation

$$\Phi_d = f(I_f)$$

$$V_f = I_f R_f$$


$$K_a = \frac{P C_a}{2\pi m}$$

Voltage Equation


$$E_a = K_a \Phi_d \omega_m$$

$$V_{ta} = E_a - I_a R_a$$


DC Machine Field Connections

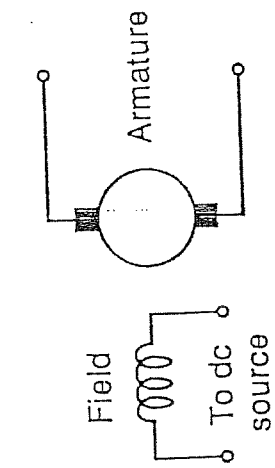


Separate Excitation

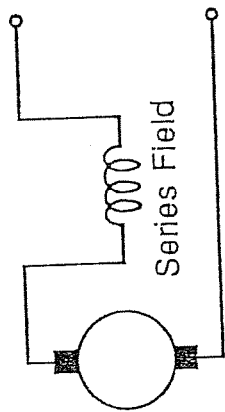

Series Field Connection

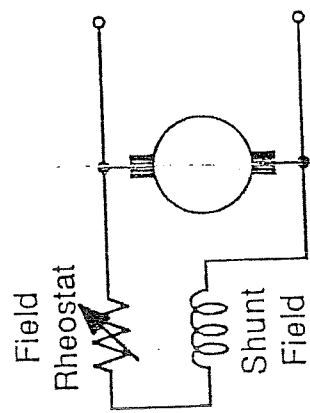

Shunt Field Connection

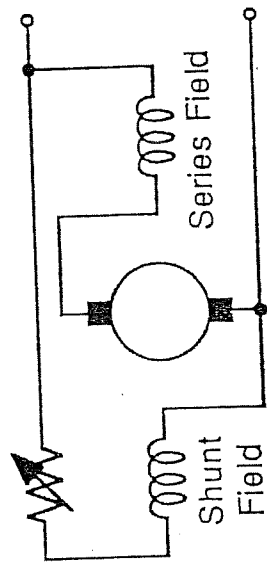

Compound Connection

ECE 320

Energy Systems I

Lesson 21

DC Motors

Next: examples; apply the basic equations! A model that predicts machine operation with a fairly few number of parameters.