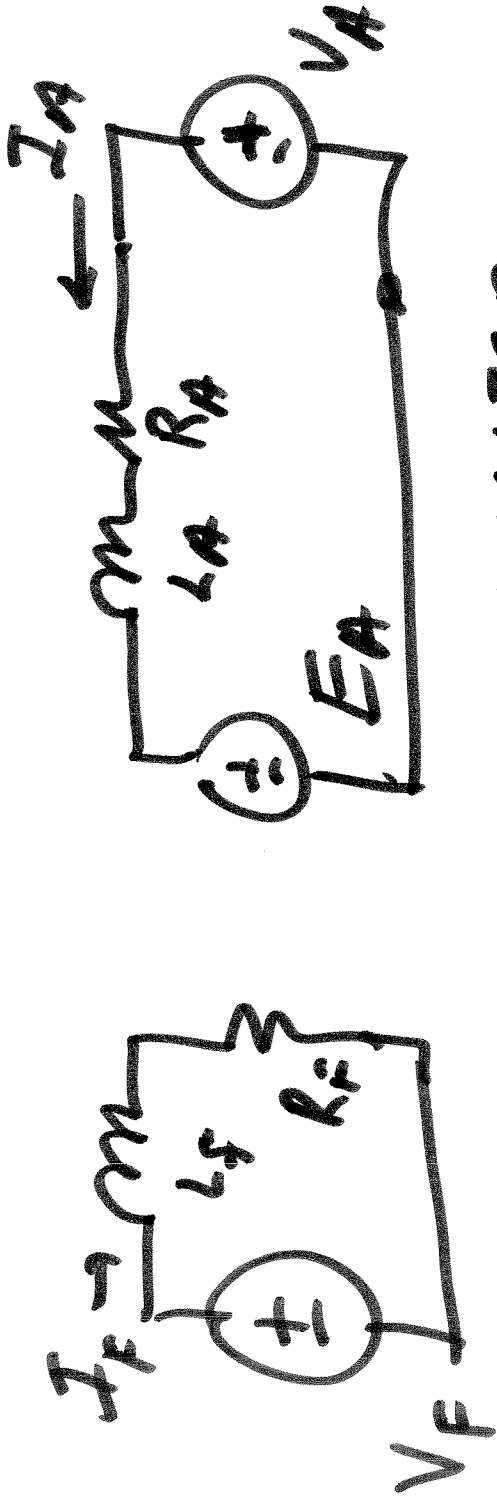


ECE 320 & ECE 329


ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 25


DC MACHINES (Motors)



SEPARATELY EXCITED

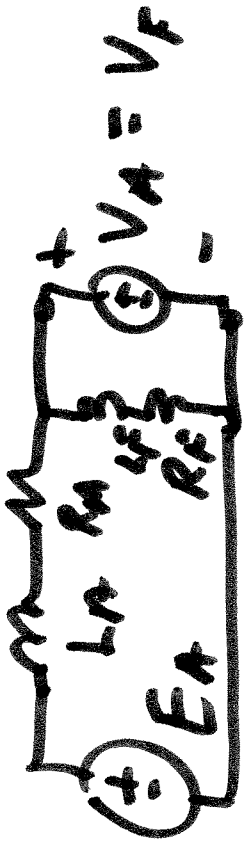

SHUNT

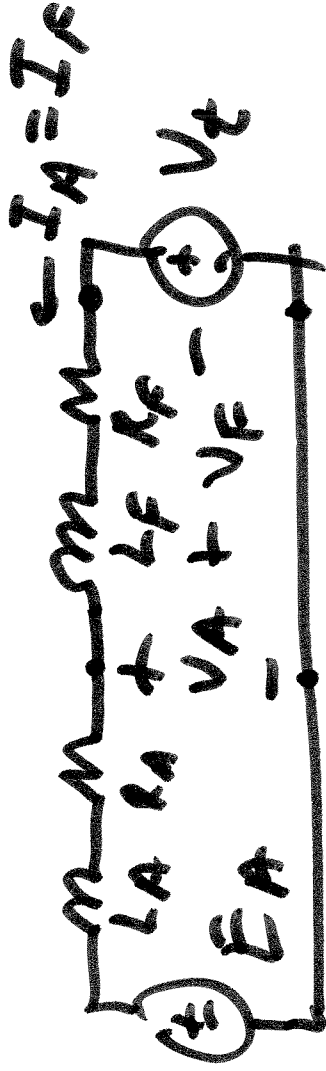

SERIES

$$\#1 \quad T_e = K \phi_a I_A$$

$$\#2 \quad E_A = K \phi_a \omega$$

$$\#3 \quad V_A = E_A + I_A R_A$$

$$\#4 \quad P_m = E_A I_A = T_e \omega$$

EXAMPLE

SEPARATELY EXCITED MOTOR

$$V_A = 125V \quad R_A = 0.02\Omega \quad P_{loss} = 0W$$

$$\omega = 3000 \text{ RPM} = 50 \frac{\text{rev}}{\text{sec}} \Rightarrow P_{out} = 0$$

$$\text{FIND } I_A, P_{in}, P_m = E_A I_A = T \omega$$

$$\text{WITH } V_A = 128V$$

NO LOAD $\rightarrow T_e = 0 ; T_c = k \phi_a I_A$

$$E_A = V_A - I_A R_A \quad \rightarrow I_A = 0$$

$$E_A = 125V - (0A)(0.02\Omega)$$

$$E_A = 125V$$

LOAD $V_A = 128V \quad E_A = 125V$

$$I_A = \frac{V_A - E_A}{R_A}$$

$$I_A = \frac{(128 - 125)V}{0.02\Omega} = 150A$$

$$P_{in} = V_A I_A = (128V)(150A)$$

$$\underline{\underline{P_{in} = 19.2 \text{ kW}}}$$


$$P_m = E_A I_A = (125V)(150A)$$

$$\underline{\underline{P_m = 18.75 \text{ kW}}}$$

$$P_{loss} = I_A^2 R_A = (150A)(0.62\Omega)$$

$$P_{loss} = 450 \text{ W}$$
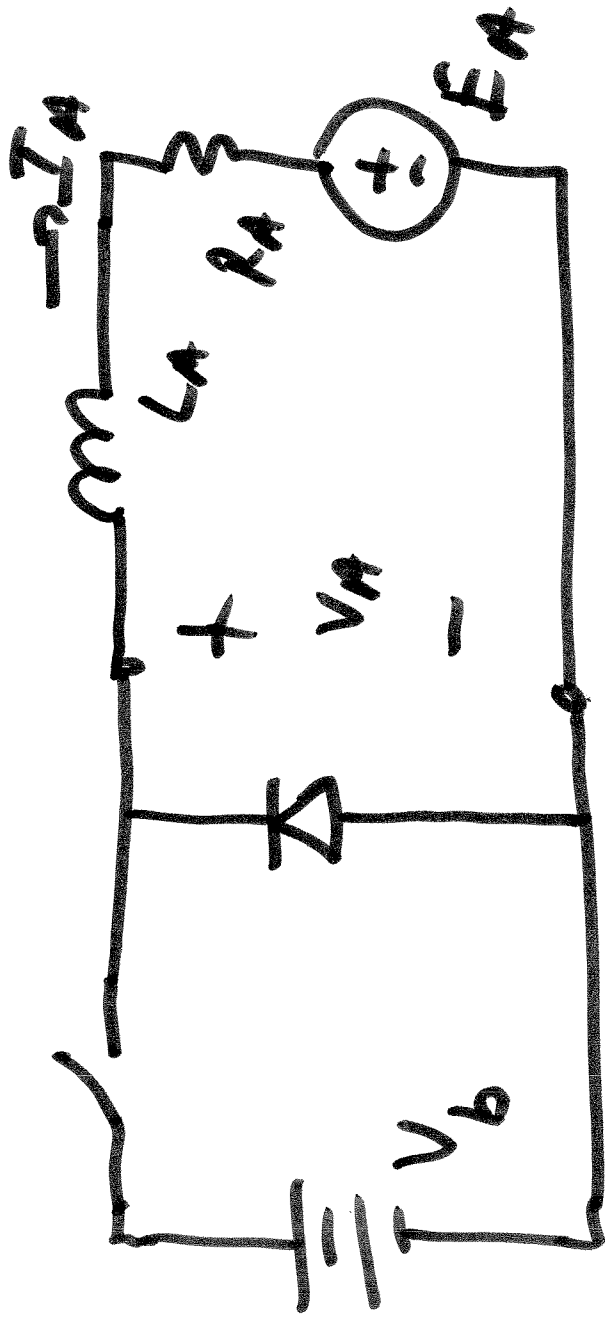
$$T_e = \frac{P_m}{\omega} = \frac{18.75 \text{ kW}}{2\pi(50 \frac{\text{rev}}{\text{sec}})} = 59.7 \text{ N}\cdot\text{m}$$



V_A
 I

**BUCK
DC
CONVERTER**

SEPARATELY EXCITED


DC MACHINE

$$V_A = I_A R_A + E_A$$

$$E_A = k \phi \omega \quad T_e = k \phi I_A$$

$$V_A = \frac{T_e}{k \phi} R_A + k \phi \omega$$
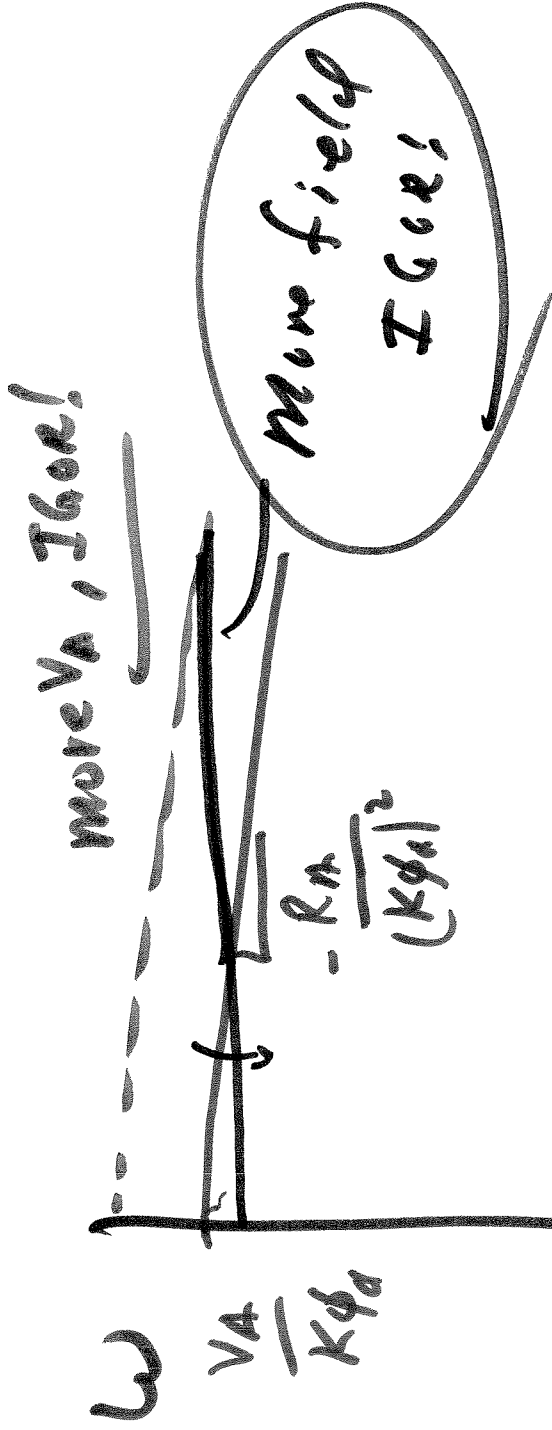
$$\omega = -\frac{k \phi T_e + V_A}{(k \phi)^2}$$



F(3)UP WEAKENING...
MORE SPEED!

$$E_A = K \phi_d \omega$$

$$V_A = E_A + I_A R_A$$


↑
Constant

↑
If E_A collapses

$I_A \uparrow \uparrow \uparrow$

$$T = K \phi_d I_a$$

MAGNETIZATION CURVE

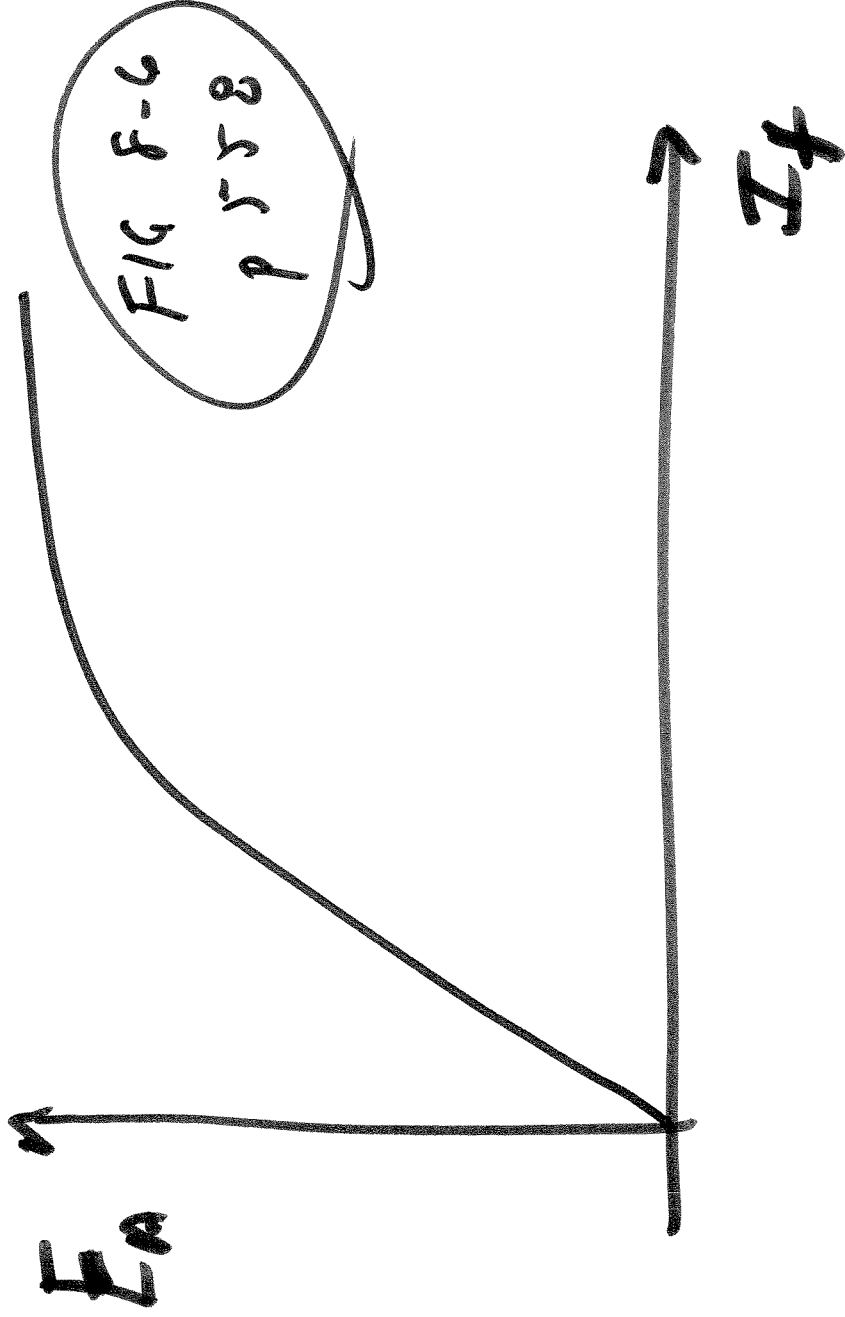

ECE 320

Energy Systems I

Lesson 25

DC Motors

Recitation Lesson 28

E_A =generated voltage, back emf

$E_A, E_G, E_{AF},$

How do I change the terminal voltage?

Transformer...it's DC...

Rheostat (shunt); voltage divider...