

ECE 320 & ECE 329

ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 27


531235

110702

→ SMALL MACHINES

→ UNIVERSAL: AC OR DC

→ HIGH TORQUE

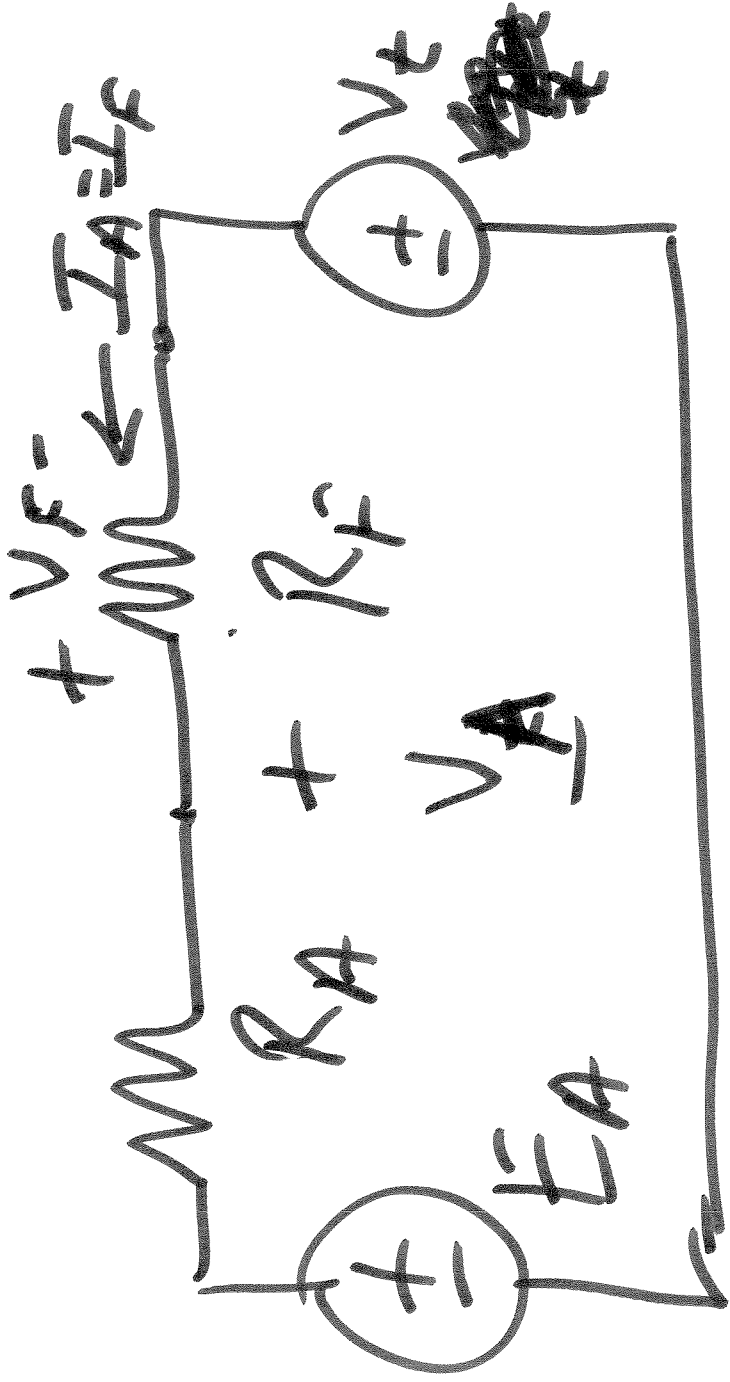

- SMALL NUMBER OF TURNS

- HEAVY WIRE


- HIGH START CURRENT

$$E_A = V_t - I_A (R_A + R_F)$$

$$E_A = K \phi \omega$$

$$T = K \phi I_A$$

NOT L) N E A R

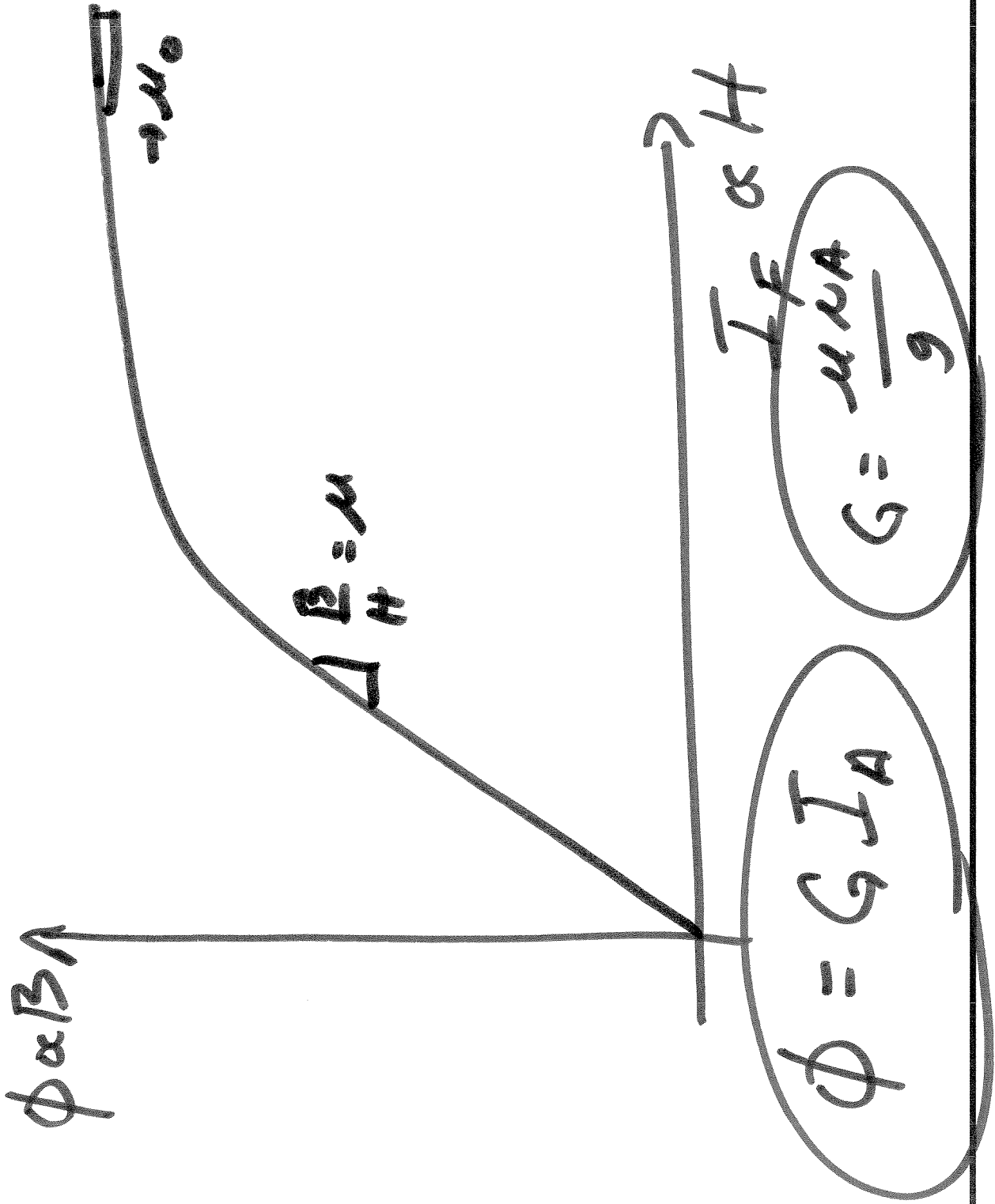

$$\tau = k_{\phi} I_A = K_G I_A^2$$


$$I_A = \sqrt{\frac{\tau}{K_G}}$$

$$F_A = k_{\phi} \omega = K_G I_A \omega$$

$$F_A = K_G \sqrt{\frac{\tau}{K_G}} \omega$$

$$K_G \sqrt{\frac{I}{K_G}} \omega = V_t - \sqrt{\frac{I}{K_G}} (R_A + R_F)$$
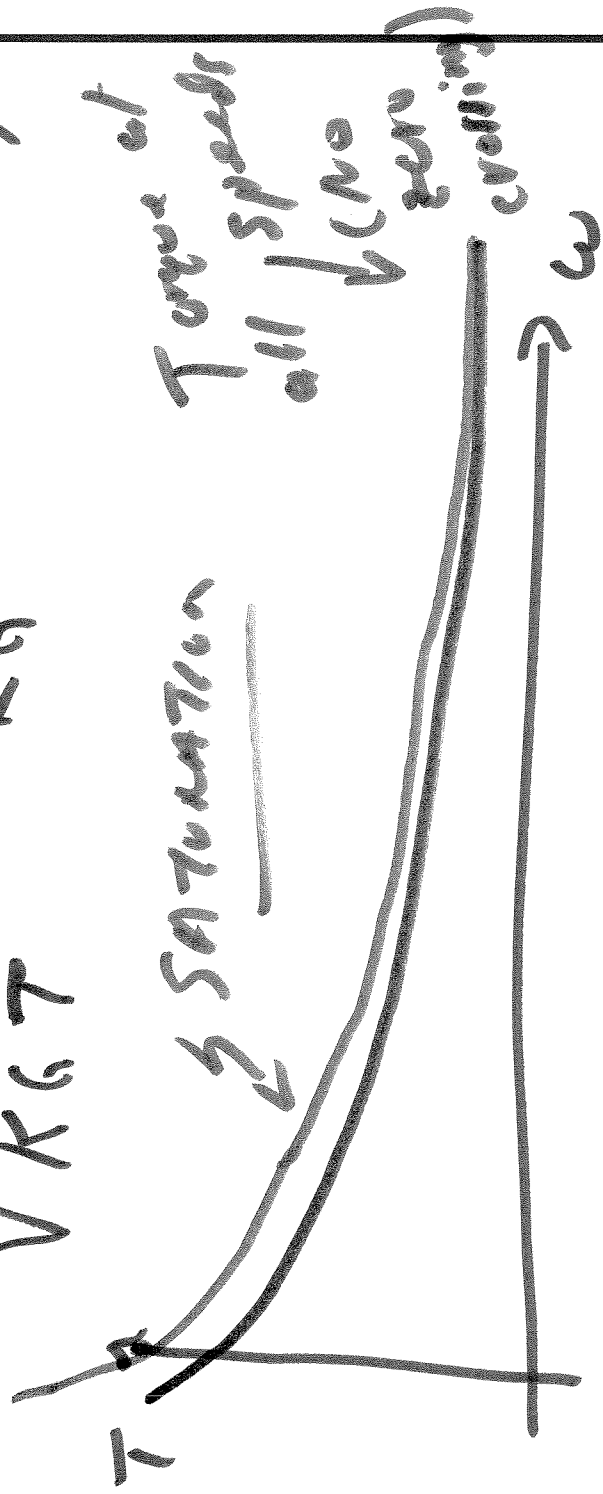
$$\omega = \frac{V_t}{\sqrt{K_G T}} - \frac{1}{K_G} (R_A + R_F)$$



Σ KAMRCS

SERIES DC MOTOR

750 RPM NOMINALLY RATED
AT 100A, 250V = VE

$$R_A = 0.15 \Omega \quad R_{FS} = 0.10 \Omega$$

FOR 25A, ~~$I_{fd} = 40\%$~~ OF RATED

FIND SPEED AT 25A.

$$E_A = V_t - I_A (R_A + R_E)$$

$$E_A = 250V - (100A)(0.15 + 0.10)\Omega$$

$$E_A = 225V$$

$$E_A = V_t - I_A (R_A + R_P)$$

$$E_A = 250V - (25A)(0.15 + 0.10)\Omega$$

$$E_A = 243.75V$$


$$\frac{\phi_{RMS}}{\phi_{LIGHT\ CORD}} = \frac{1}{0.4} = 2.5$$


$$\frac{E_A}{E_A} = \frac{K\phi \omega}{K\phi \omega} \leftarrow \text{RATED}$$
$$\frac{E_A}{E_A} = \frac{K\phi \omega}{K\phi \omega} \leftarrow \text{LIGHT LOAD}$$

$$\frac{225V}{243.75V} = 2.5 \frac{710 \text{ RPM}}{\omega_{\text{LIGHT}}}$$

$$\frac{\omega_{\text{LIGHT}}}{\omega_{\text{LIGHT}}} = 2031 \text{ RPM}$$

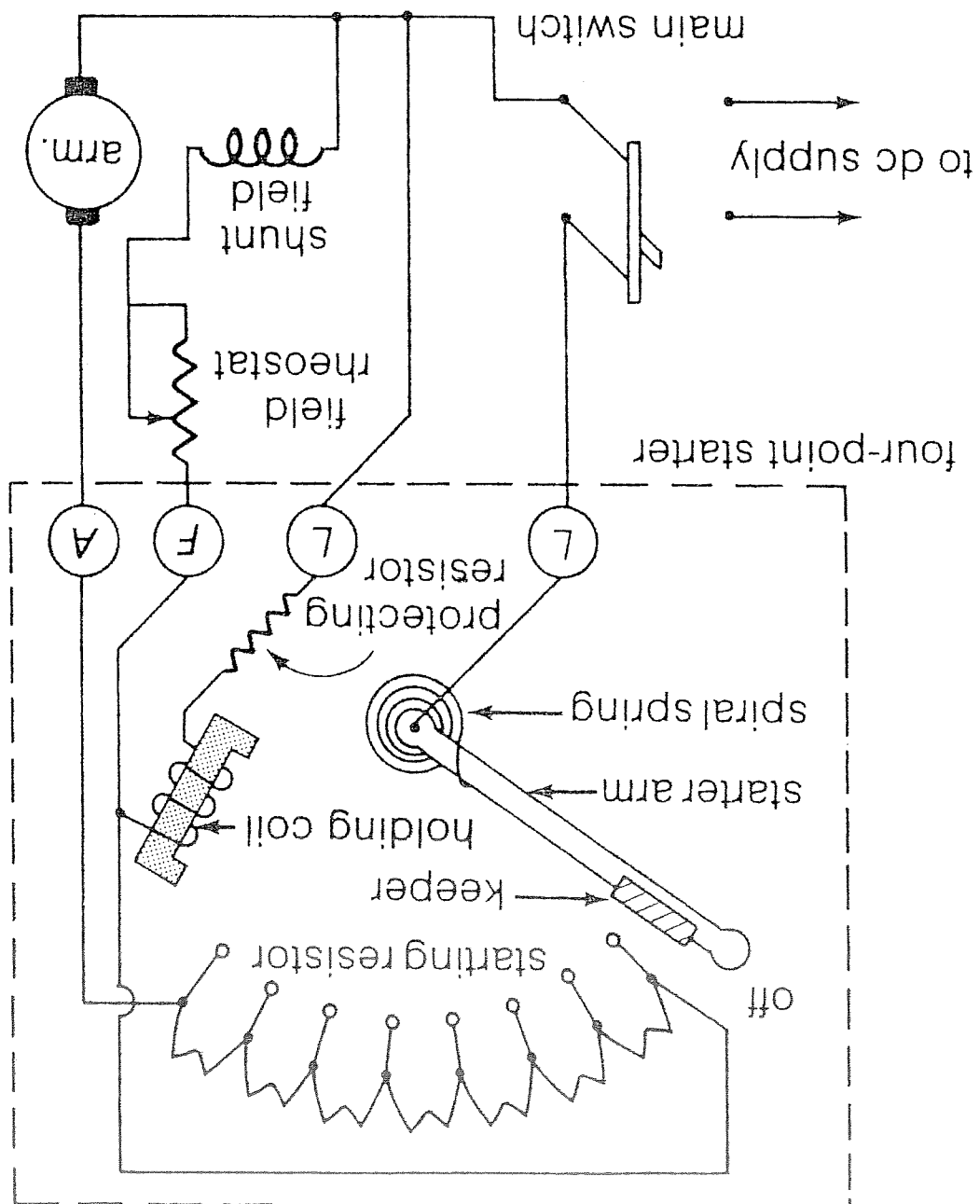FIELD WEAKENING DIMINISHES
THE INCREASED EA.



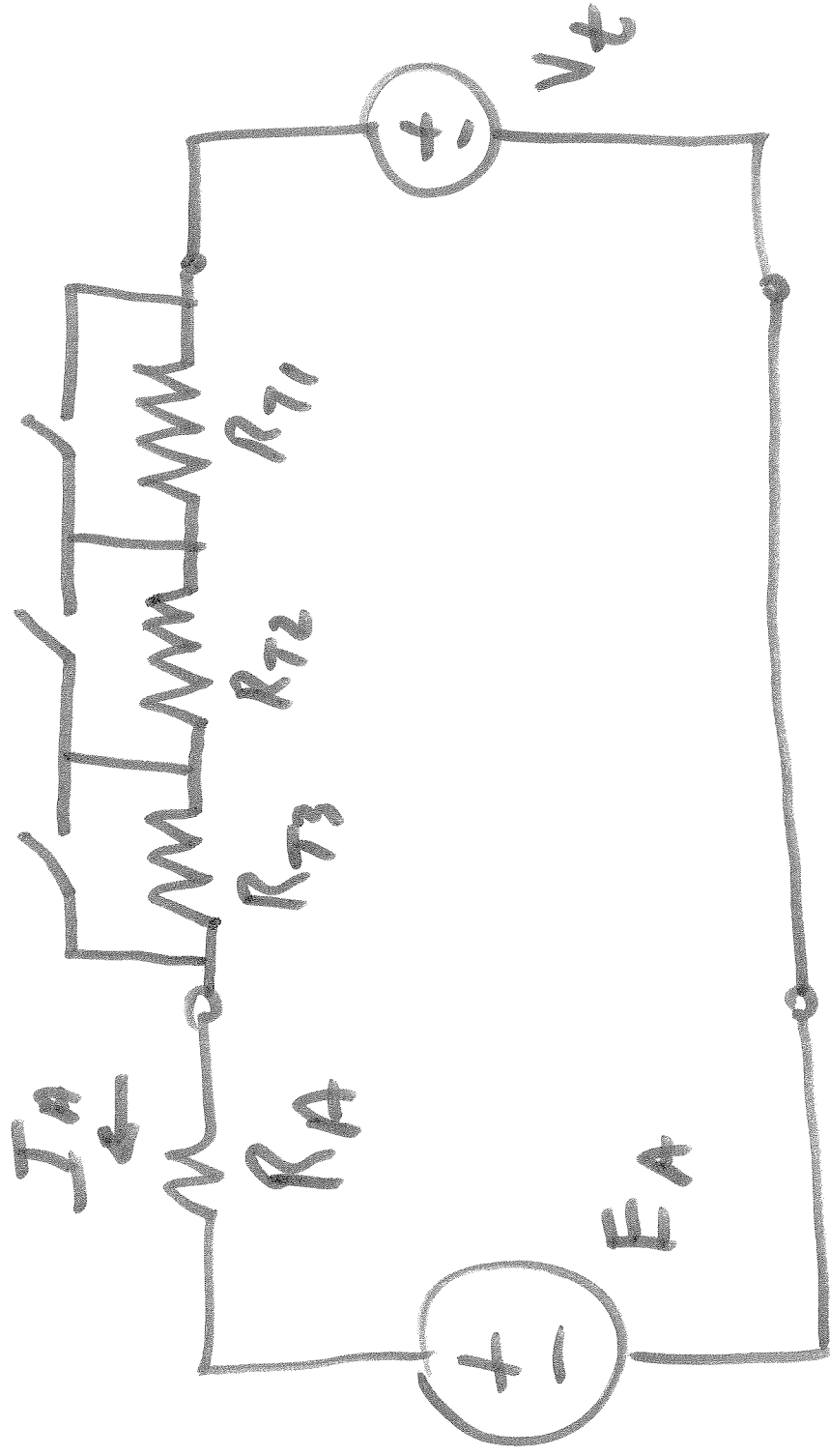

STARTING

DC Motor

START 17

$$230V = V_e$$

$$500 \text{ RPM} = \omega_{\text{RATIO}} \leftarrow$$

$$\frac{230V}{500 \text{ RPM}} = 0.46 \frac{V}{\text{RPM}}$$

$$37A = I_A \text{ RATIO}$$

$$0.39\Omega = R_A \quad 0.785$$

$$R_{T1} = 1.56\Omega \quad R_{T2} = 0.39\Omega$$

FIND STARTING BEHAVIOR
SWITCH WITH CURRENT FALLS

TO RATIO VALUE.

START $\omega = 0$

$$E_A = k \phi \omega = 0$$

$$I_{A0} = \frac{230\text{V}}{(1.56 + 0.78 + 0.39 + 0.39)\Omega}$$

$$I_{A0} = 73.7\text{ A} \quad \underbrace{\hspace{1.5cm}}_{3.12\Omega}$$

MACHINE STARTS ... GET TO $I_A = 37\text{ A}$

$$E_{A1} = 230\text{V} - (3.12\Omega)(37\text{A})$$


$$E_{A1} = \del{114.6}\text{V} \quad 114.6\text{V}$$

SWITCH → 540 x 7.667

1.56 Ω

$$I_A = \frac{(230 - 114.6)V}{(3.12 - 1.56)\Omega} = 74A$$

$$\sum (0.78 + 0.37 + 0.37) \Omega$$

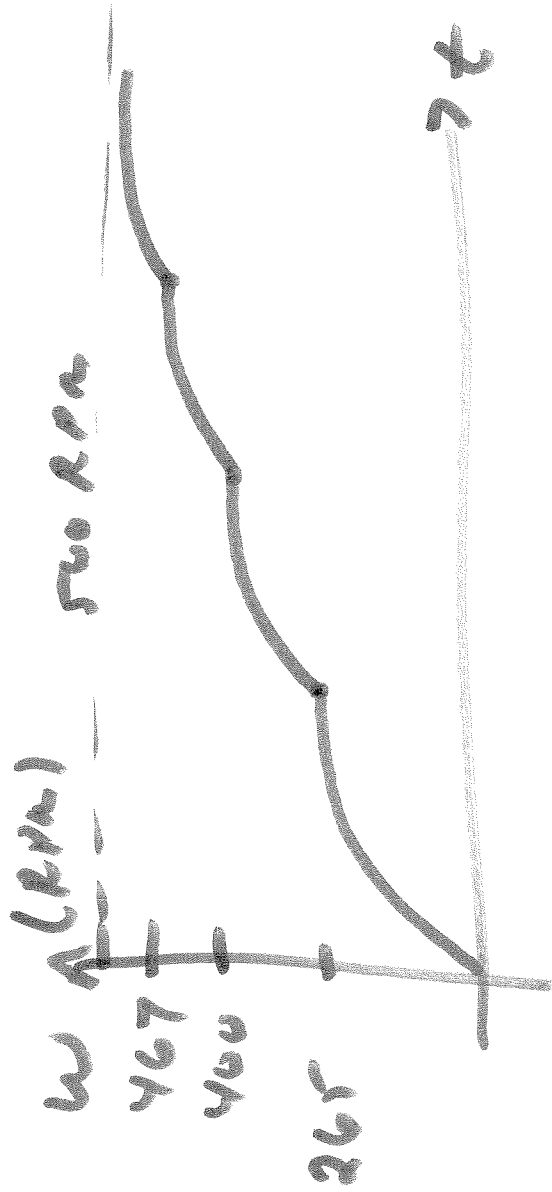

ECE 320

Energy Systems I

Lesson 27

DC Series Machines

DC Start Resistor Systems

If the series machine will start, it will come up to speed in most cases.

☹ Huge start current; it cannot run unloaded. (It will overspeed unloaded)