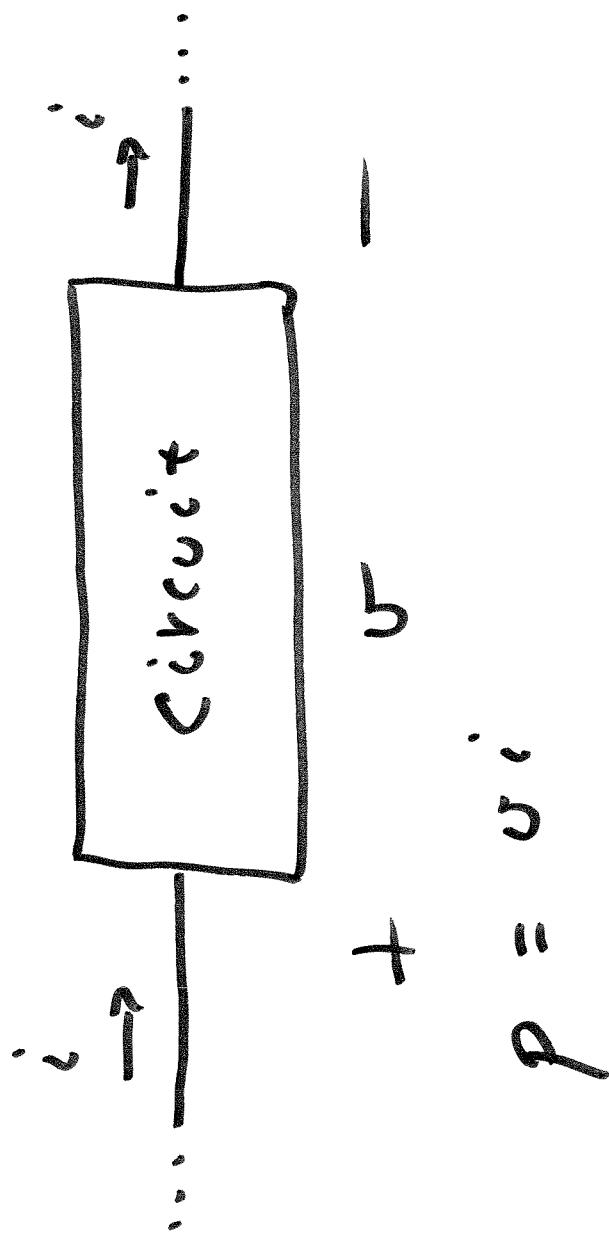


ECE 320 & ECE 329


ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 3



$P < 0$ GENERATE
ABSORB SOURCE
(LOAD)
(MOTOR)


$P > 0$ GENERATE
ABSORB
(LOAD)
(MOTOR)

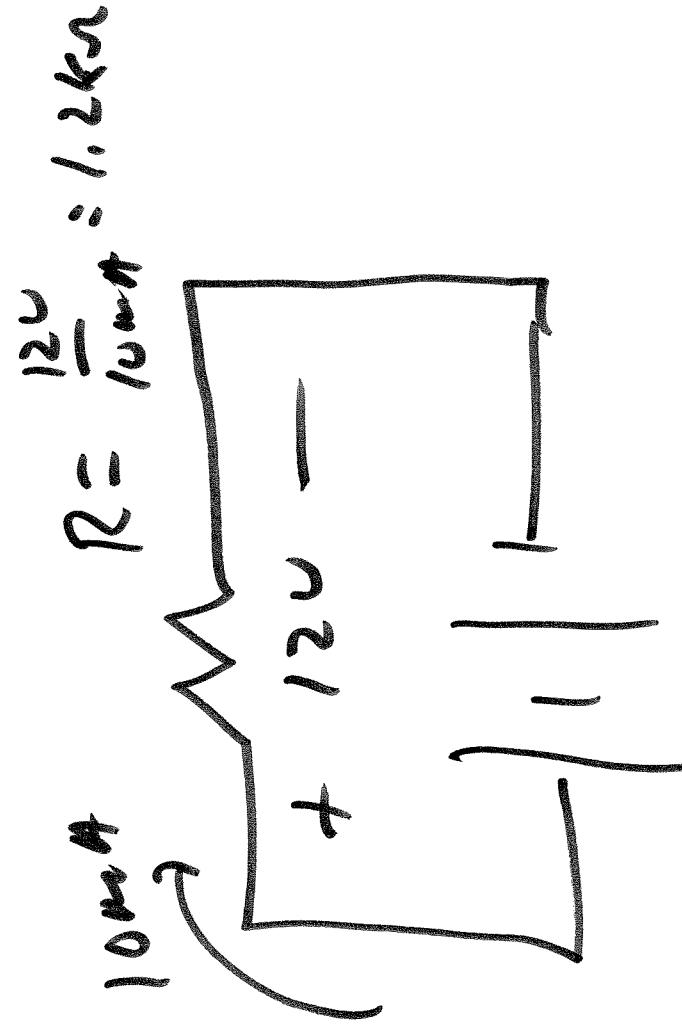

$$12V \text{ DC}$$

$$P = V_i i = (12V) (10\Omega) = \underline{\underline{120\text{ mW}}}$$
$$P = i^2 R = (10\Omega)^2 (12V) = \underline{\underline{120\text{ mW}}} =$$

$$\sum KIR = \sum E$$

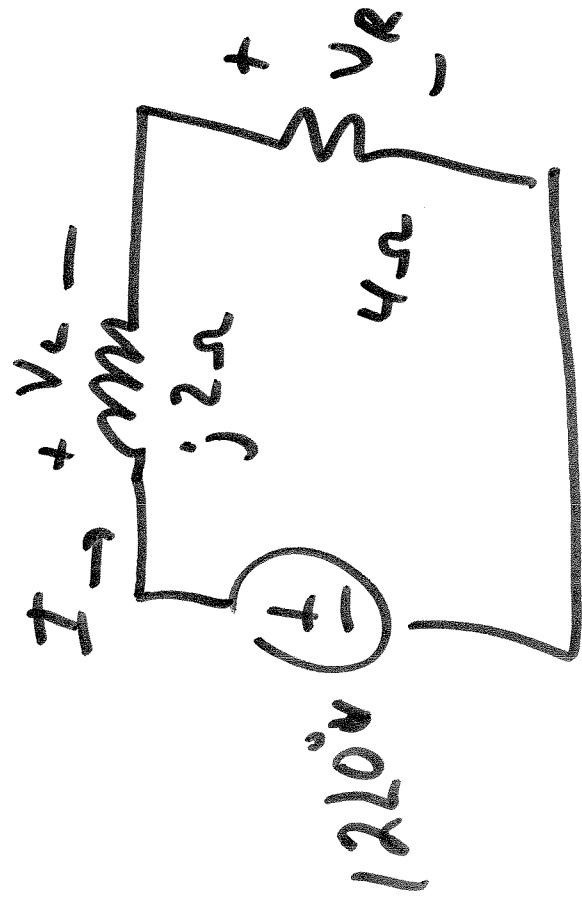

$$I = \frac{120}{(4 + j2)} = \frac{120}{4.47264}$$

$$I = 2.68 \angle -26.6^\circ A$$

$$P = I^2 R_4$$

$$P_4 = (2.68)^2 R_4$$

$$P_4 = 28.8 W$$

Find Real Avg Power in this circuit.

$$P_4 = \cancel{V_A} \cancel{I_A} R_e (V_4 I^*)$$

$$V_A = I R_4 = (2.48A)(4\Omega)$$

$$V_R = 10.7 \angle -26.6^\circ V$$

$$P = R_e ((10.7 \angle -26.6^\circ V) (2.68 \angle -26.6^\circ A))$$

$$P = 28.8 W$$

=====

$$P_4 = \cancel{V_A} / |I| \cos \theta$$
$$P_4 = (10.7V) (2.86A) (-26.6^\circ - -26.6^\circ)$$


$$P = 28.8 W$$

=====

$$Q_2 = I^2 / \rho X$$


$$Q_2 = 12.68 A / \rho^2 2 n$$

$$Q_2 = 14.4 \text{ Vars}$$

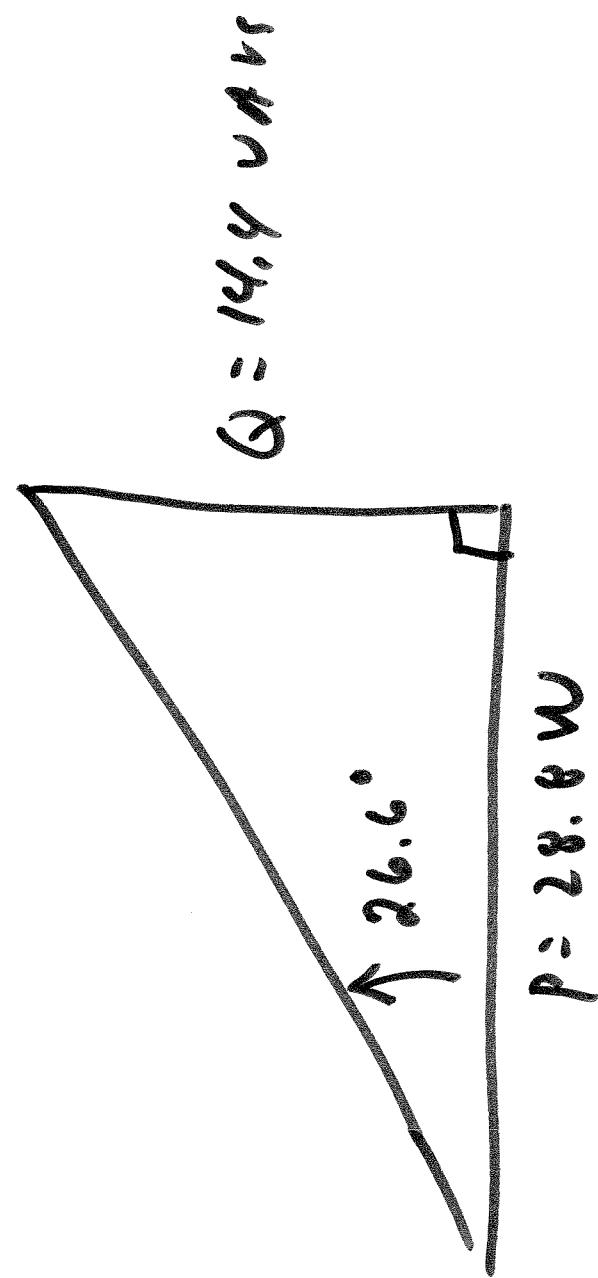

$$V(t) = V \cos(\omega t + \theta_V)$$
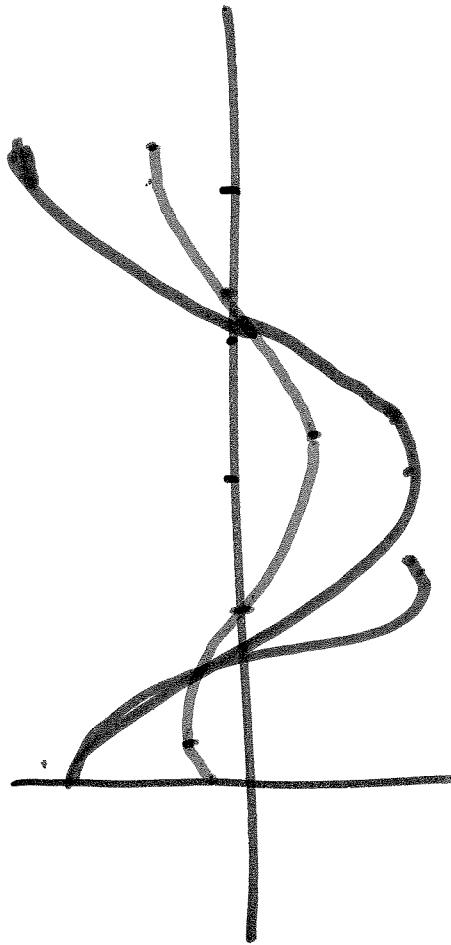
$$\dot{e}_i(t) = I \cos(\omega t + \theta_i)$$



$$\cos \theta + \cos \theta = \frac{1}{2} \cos(\alpha + \beta) + \frac{1}{2} \cos(\alpha - \beta)$$



$$p = \omega_{ci}$$

$$p(x) = \frac{\sqrt{I}}{\omega_i} (\omega_i (\omega_i + \theta_{ci}) (\cos(\omega_i t + \theta_{ci})) + \frac{\sqrt{I}}{\omega_i} \omega_i (2\omega_i + \theta_{ci} + \theta_{ci}) + \frac{\sqrt{I}}{2} \omega_i (\theta_{ci} - \theta_{ci}))$$

$$p(t) =$$

ECE320

Energy Systems I

Lesson 3

AC Power

Quiz on AC Power starts the lesson.

*Sign convention: load power is positive.

*We use rms values unless stated otherwise.