

ECE 320 & ECE 329

ENERGY SYSTEMS I

BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 31

DC / DC


Down (Back)

UP (Booster)

UP-Down (Buck-Booster)

UP-Down (Cuk)

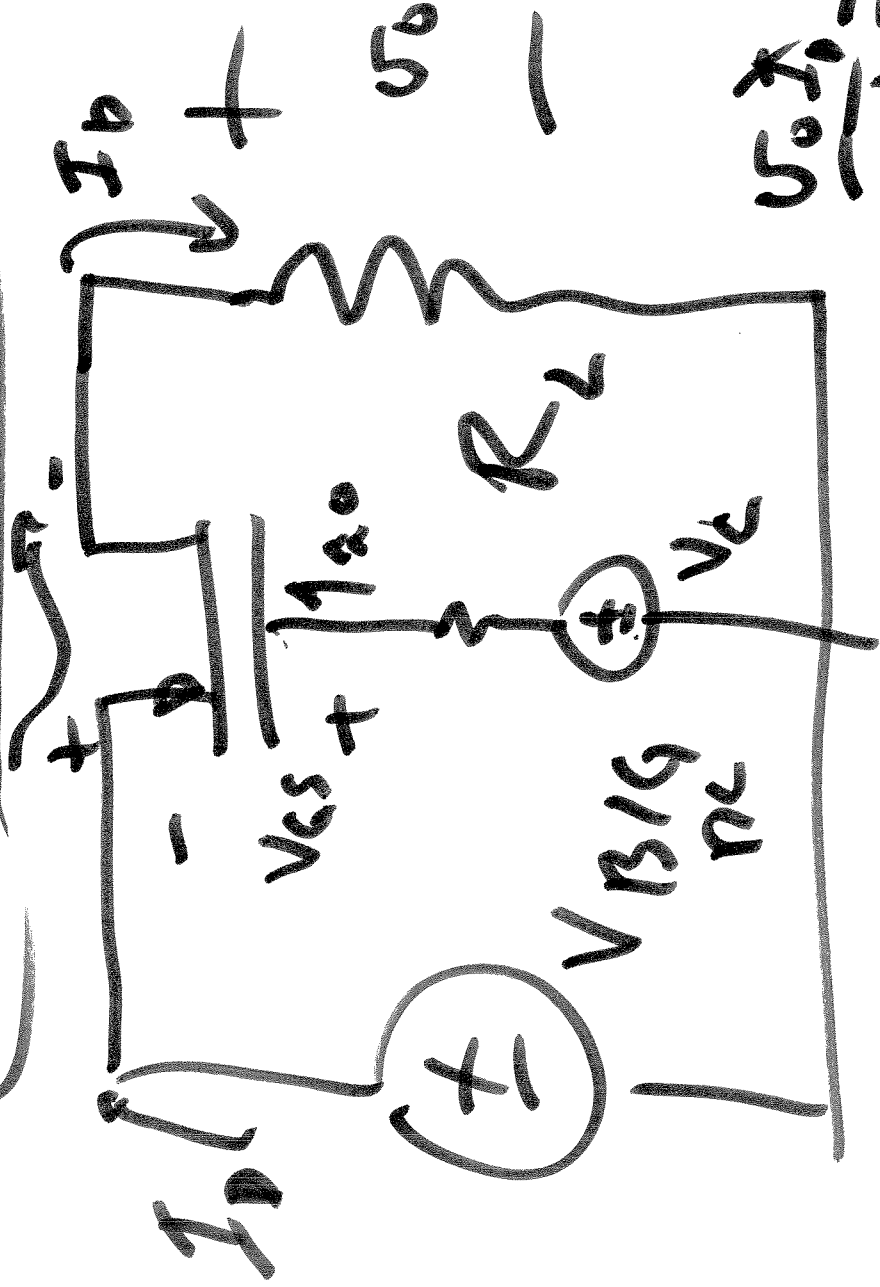
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$$




$$\frac{P_{out}}{P_{in}} = \frac{50 I_D}{50 I_{D0}}$$

$$P_s = \frac{v_s v_s + \frac{v_s}{m \cdot i}}{1}$$

Control

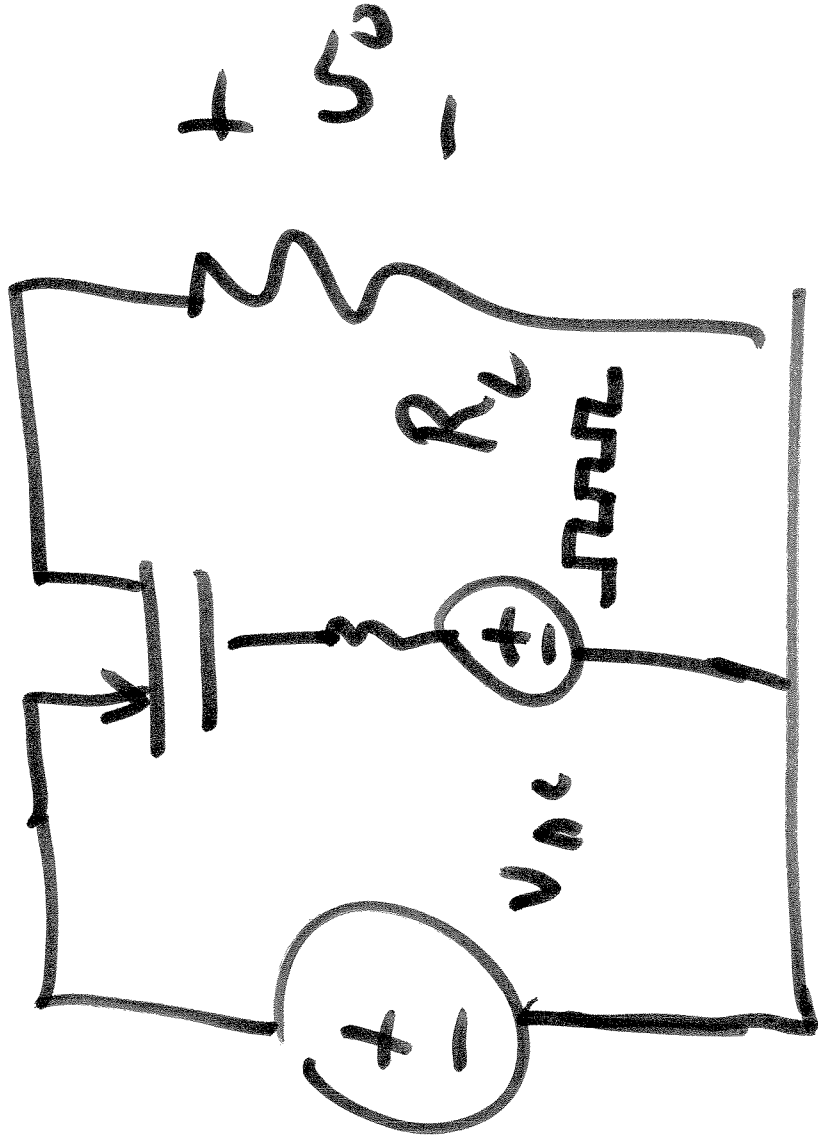

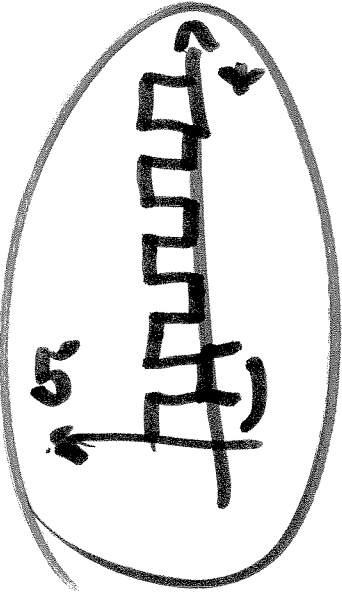


$u_o$



$u_{ih}$


on

off

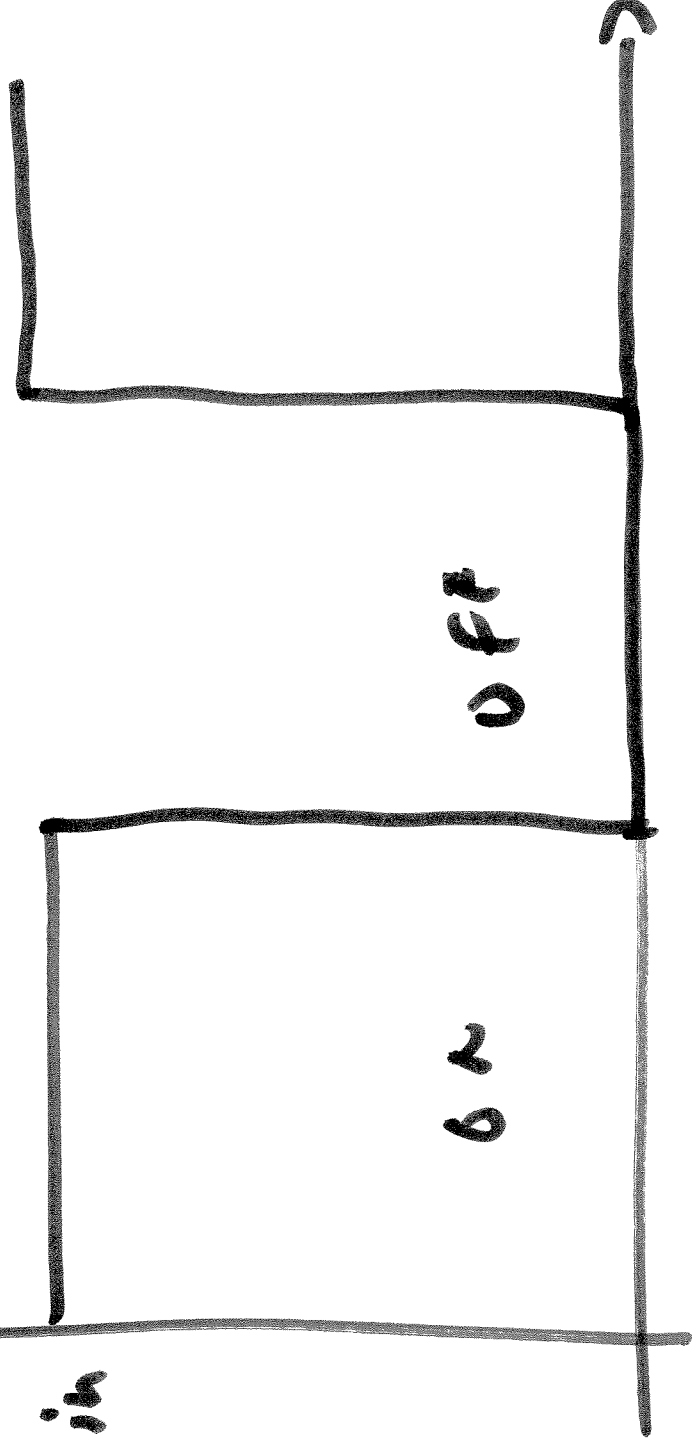

Buck

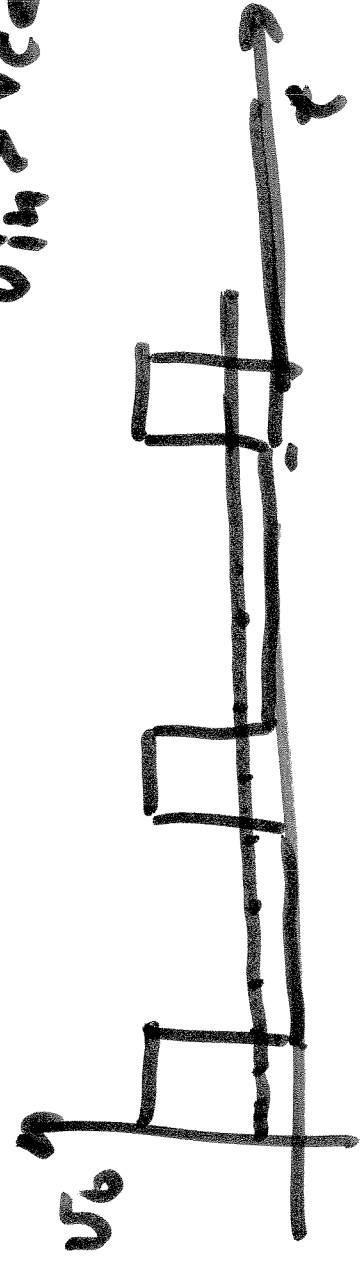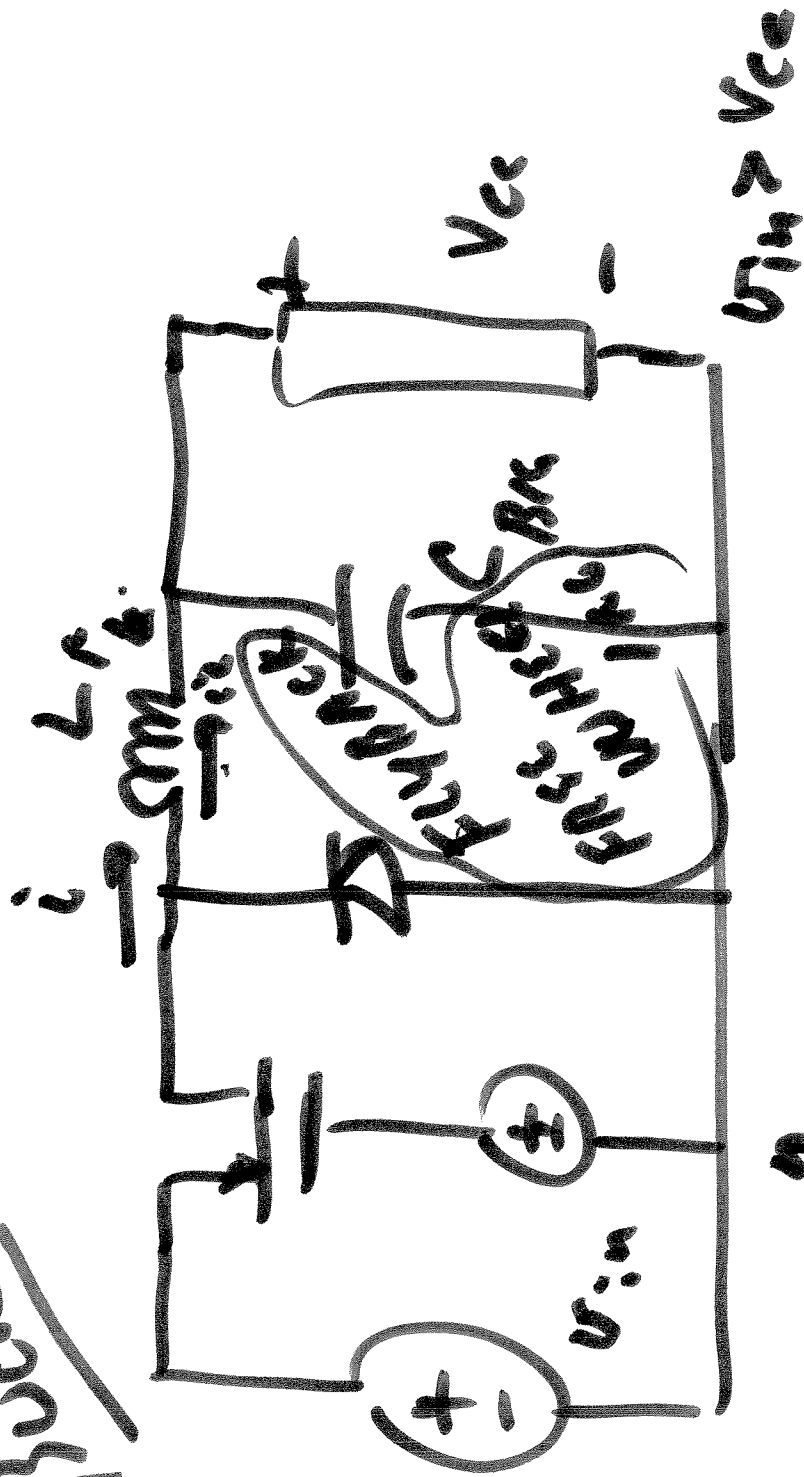

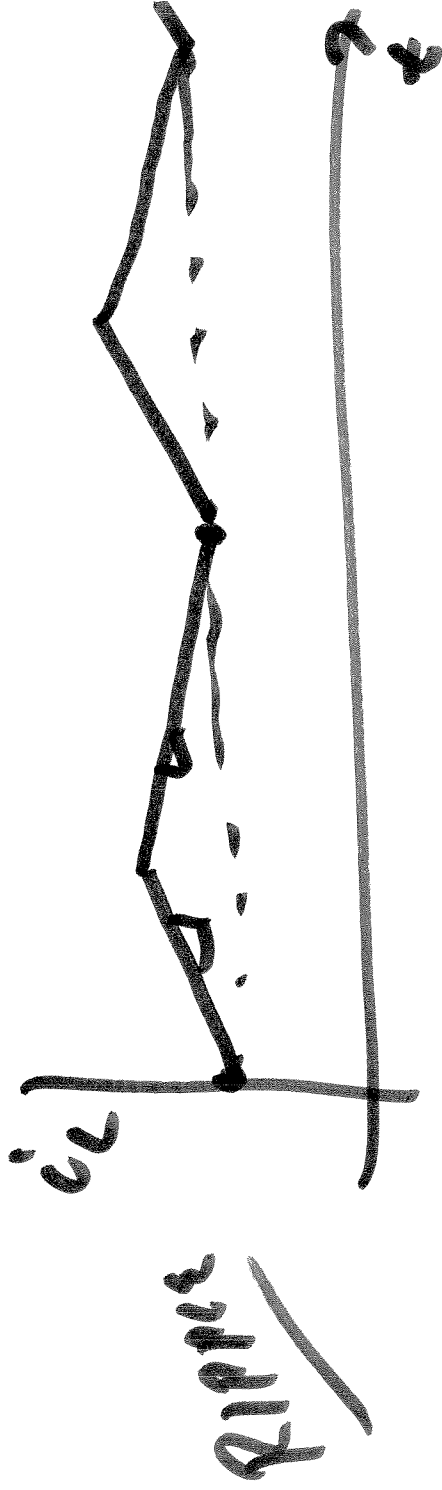

$$i_c = \int \frac{(V_{in} - V_{ce})}{L_F} dt$$


$$i_c = \int \frac{0 - V_{ce}}{L_F} dt$$



$$\frac{50}{1} = D$$

$v_{in}$

$$D = \frac{t_{on}}{T \text{ period}}$$

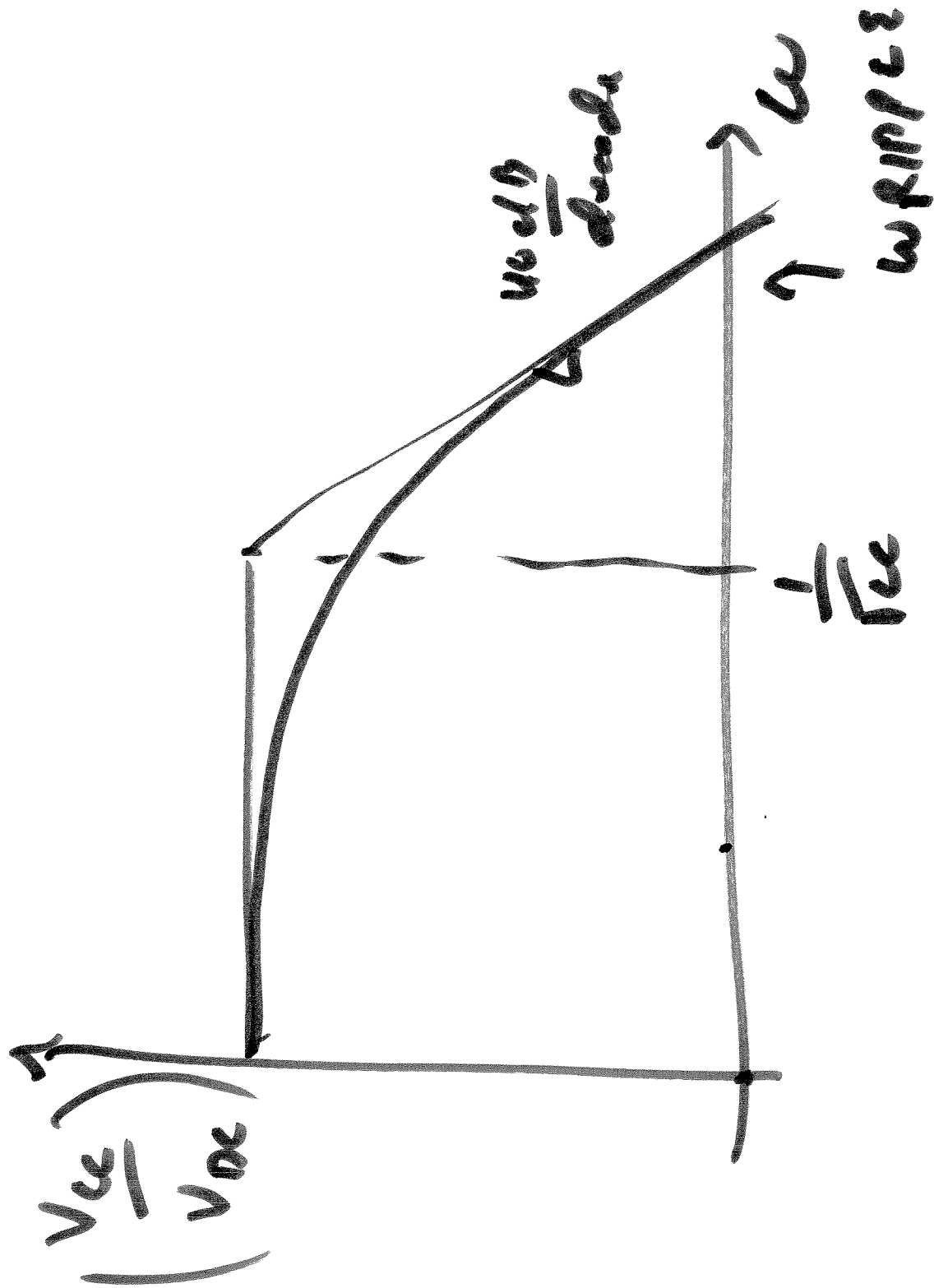

## Five Basic Laws of Power Electronic Circuits

1. Voltage across an inductor averages to zero for a complete cycle.
2. Current through a capacitor averages to zero for a complete cycle.
3. Inductor current is always continuous.
4. Capacitor voltage is always continuous.
5. Conservation of energy is always valid.

ECE 320 / ECE 329

Energy Systems I

Lesson 31

DC / DC Conversion

Voltage divider

☺ It works...

☺ It is simple...

☹ The efficiency is BAD...

Transistor...linear converter

☺ It works!

☺ Easily variable

☹ The efficiency is BAD...

Switched ...

If the switch is open, the switch consumes ZERO power ( $p=vi$ )

If the switch is closed, the switch consumes ZERO power ( $p=vi$ )

If I want to vary or control the output voltage, I switch at a different time interval.

Power electronics is the controlled, intelligent use of circuit transients to our advantage. We use switching circuits and filters.