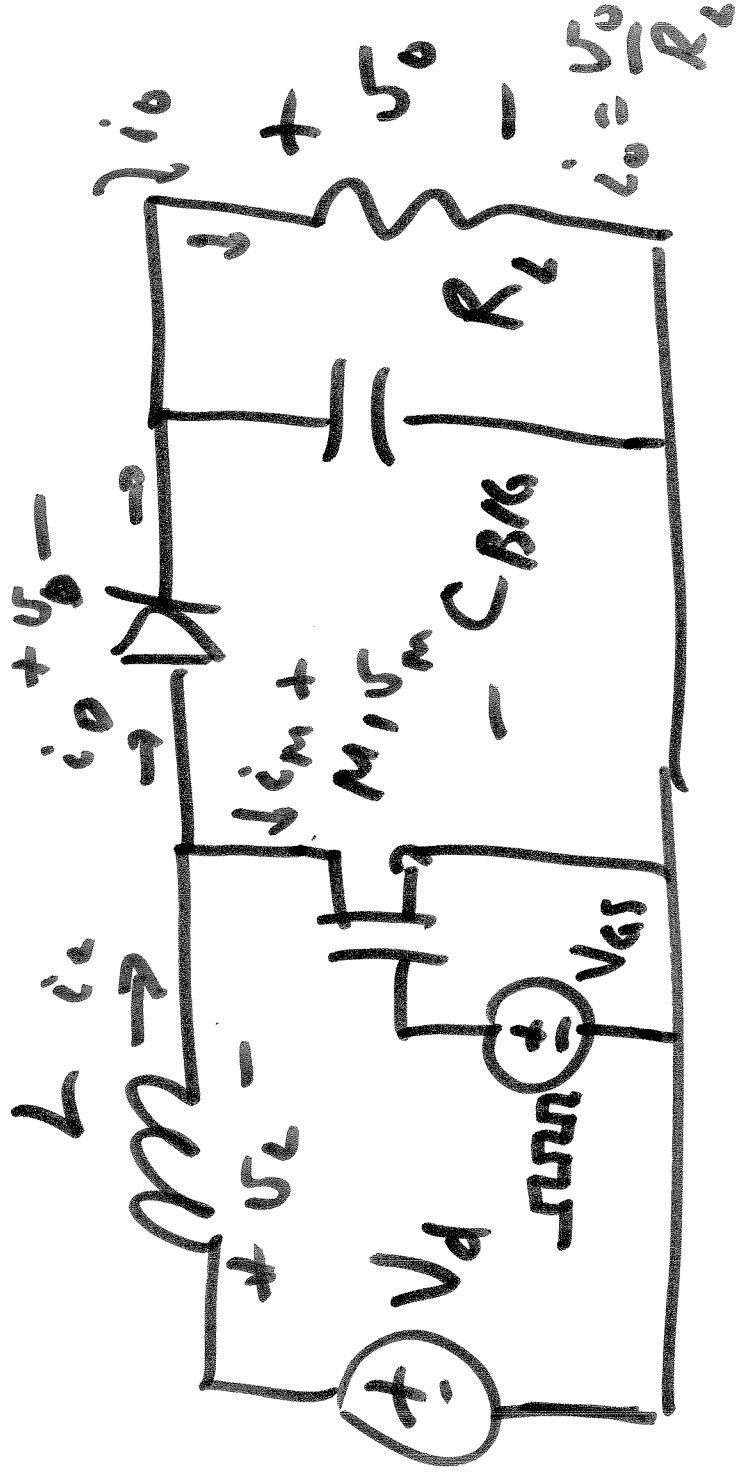


ECE 320 & ECE 329

ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 33


Boost Converter




$$\Delta \dot{e} = \int_0^T v_2 \, dt = 0$$

$$0 = \int_0^T v_1 \, dt + \int_{D_1}^T (v_1 - v_0) \, dt$$


$$v_0 = \frac{1}{1.5} = 1 - 0$$

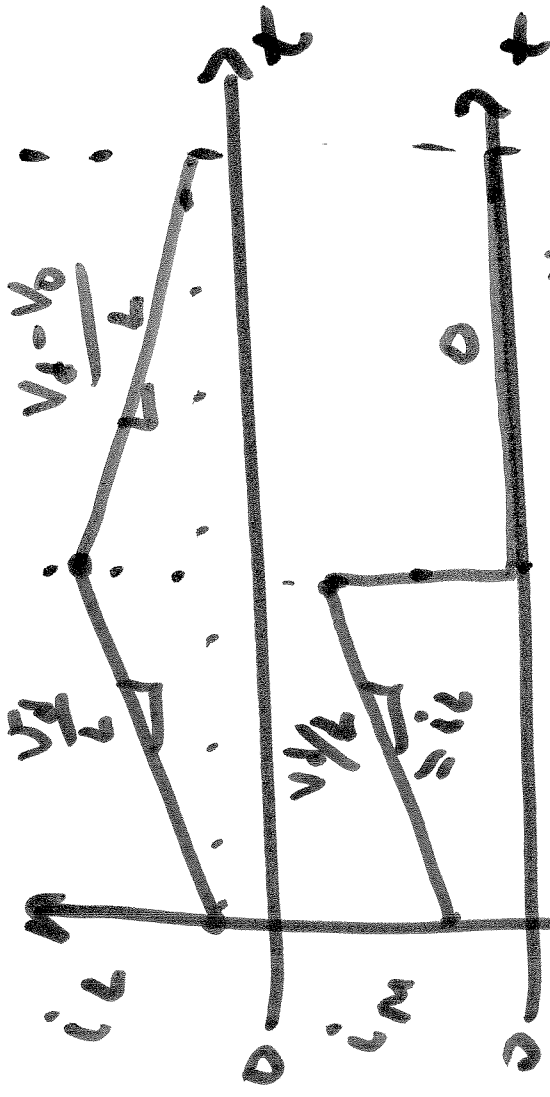

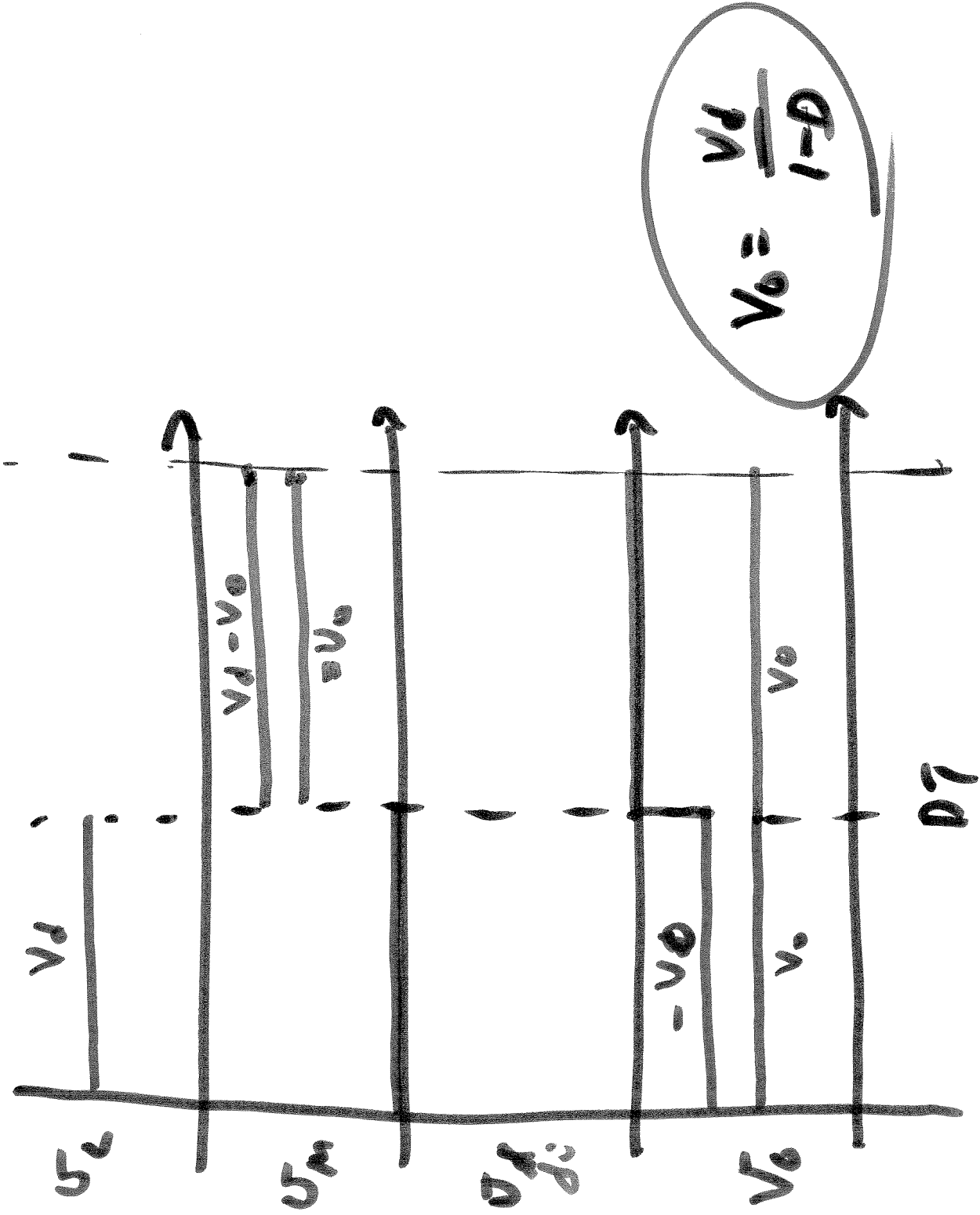

2X AMPLE

BOOST CONVERTER IDEAL DIODE & SWITCH

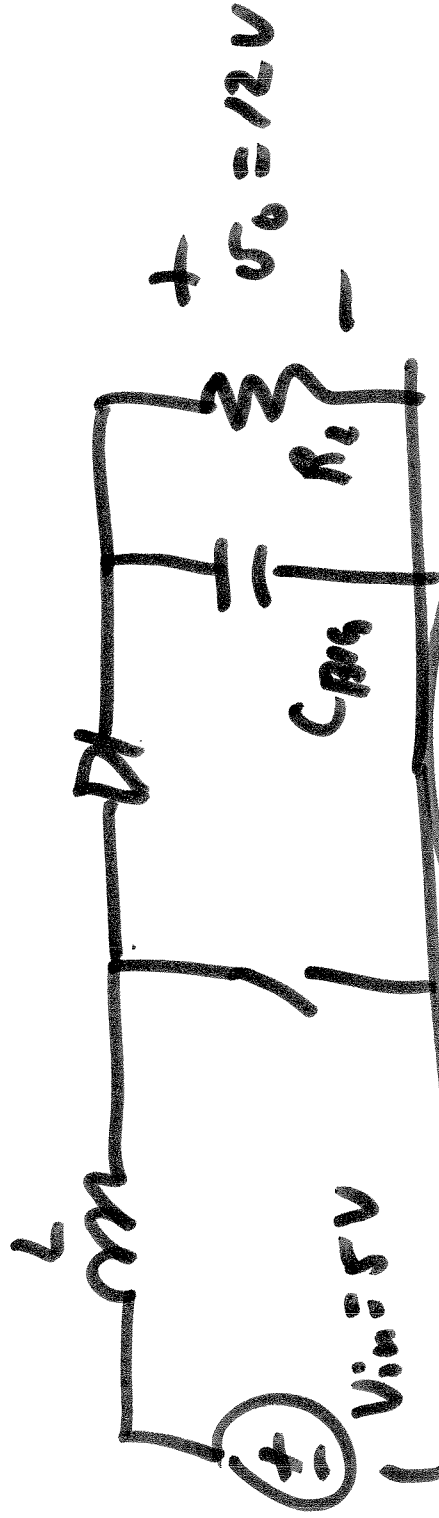

$P_{in} = 10W$ $P_{out} = 10W$
 $I_{di} = 2A$

$f_{sw} = 200kHz$ $F_{1 \mu s}$ i_L

Inductor

$$\frac{V_o}{V_{in}} = \frac{1}{1-D} = \frac{12V}{5V}$$

$$(1-D) \frac{12}{5} = 1$$

$$2.4 - 2.4D = 1$$

$$3.4 = 2.4D$$

$$D = \frac{3.4}{2.4} = 1.4167$$


$$D = \frac{1.4}{2.4} = 0.583$$


$$\Delta i_L = \frac{V_{in}}{L} D T$$

$$2A = \frac{5V}{L} (0.583) \frac{1}{200kHz}$$

$$L = \frac{5V}{2A} (0.583) (5\mu s)$$

$$L = 7.3 \mu H$$

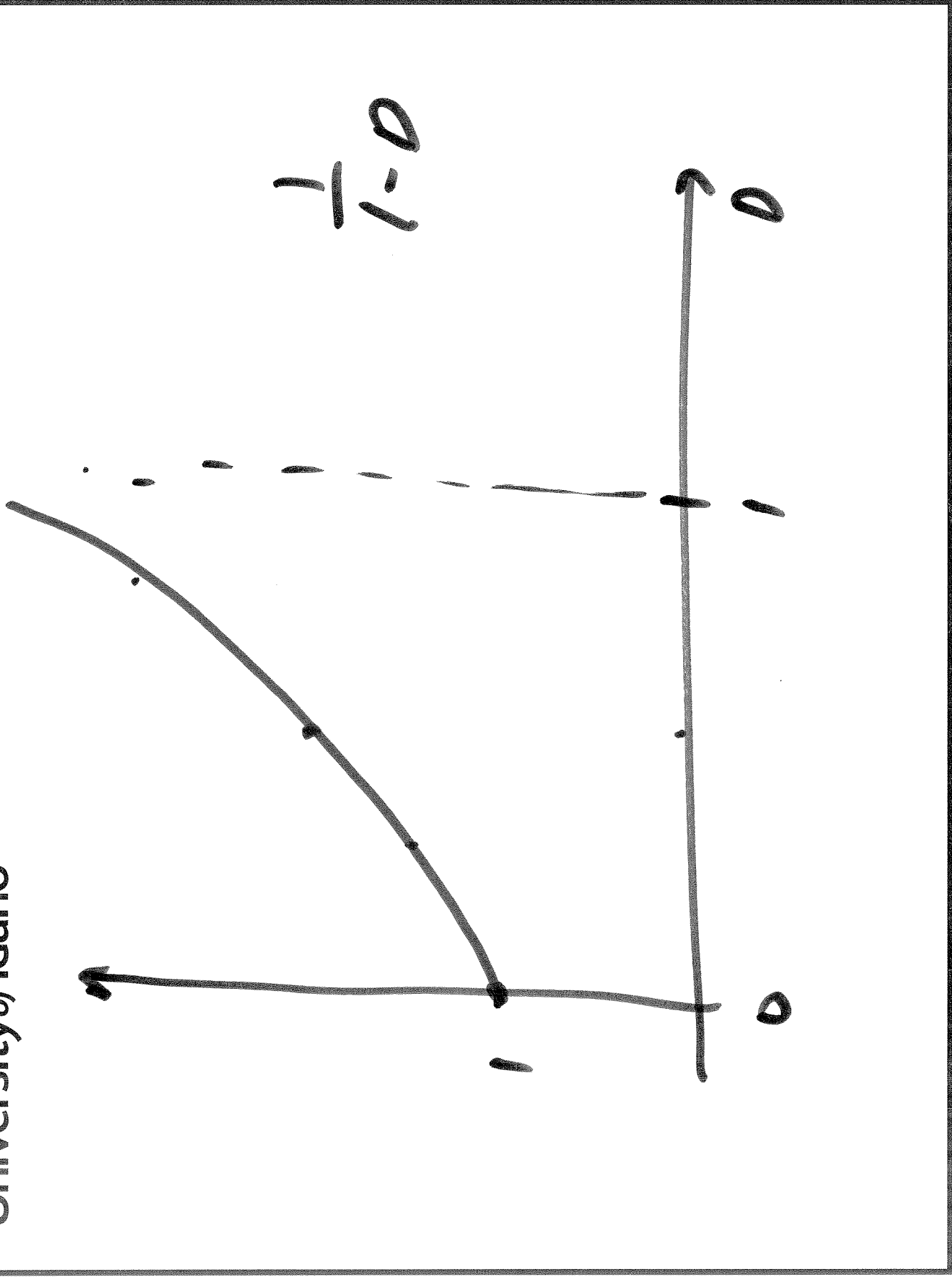

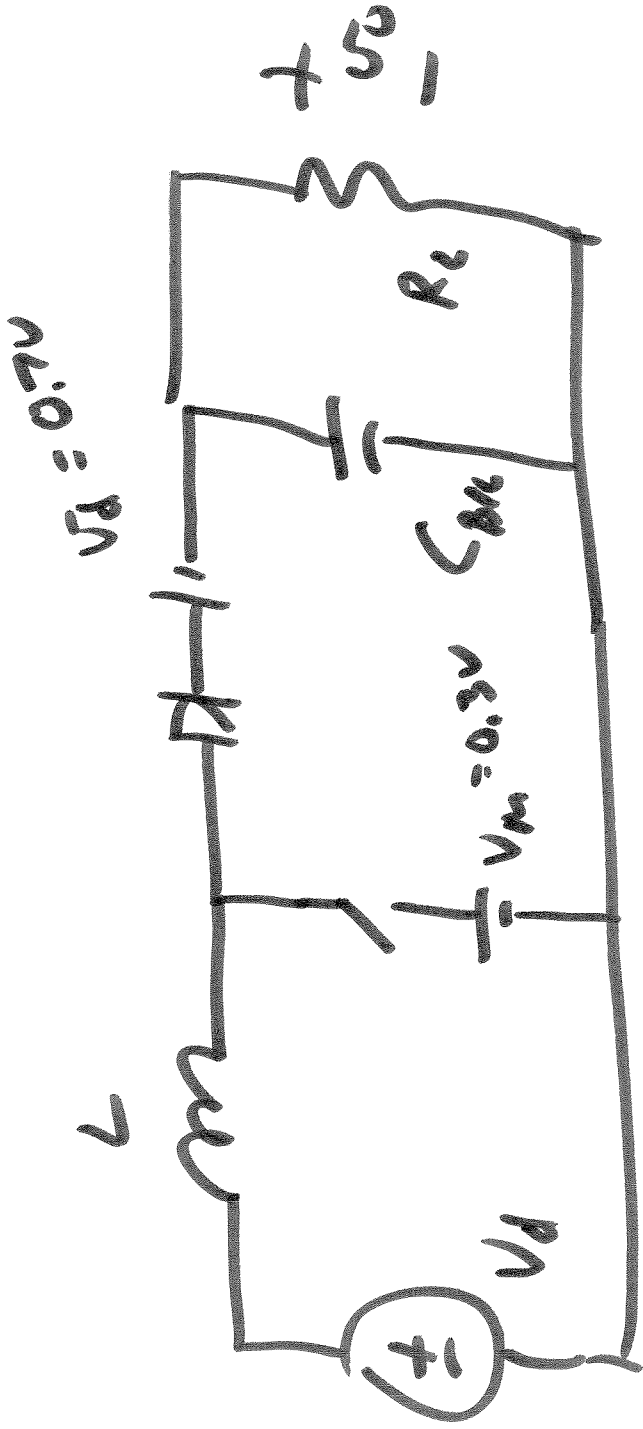

WHAT HAPPENS IF
WE CONSIDER V_d & V_m ?

Effect of inductor resistance

For boost converter, recall

$$V_o = \frac{V_s}{1 - D}$$

converters are not ideal. Some effects are possible to analyze. for example, inductors have resistance. It is a problem that we are trying to get rid of, but have not yet done so at a reasonable price. So we find,

$$P_{out} + P_{loss} = P_{source}$$

$$V_o \cdot I_o + I_{Lrms}^2 \cdot r_L = V_s \cdot I_{Lave}$$

We know from our work with the boost converter that

$$I_o = I_{Lave} \cdot (1 - D)$$

$$I_o = \frac{V_o}{R}$$

Combining these two equations,

$$\frac{V_o}{R} = I_{Lave} \cdot (1 - D)$$

$$I_{Lave} = \frac{V_o}{R \cdot (1 - D)}$$

Now go back to the power balance and substitute for the average inductor current.

$$V_o \cdot I_o + I_{Lrms}^2 \cdot r_L = V_s \cdot I_{Lave}$$

Because we assume a small ripple,

$$I_{Lave} \approx I_{Lrms}$$

$$V_o \cdot \frac{V_o}{R} + \left[\frac{V_o}{R \cdot (1 - D)} \right]^2 \cdot r_L = V_s \cdot \frac{V_o}{R \cdot (1 - D)}$$

Multiply through by $\frac{R}{V_o^2}$

$$1 + \frac{r_L}{[R \cdot (1 - D)]^2} = \frac{V_s}{V_o} \cdot \frac{1}{1 - D}$$

Simplify

$$\frac{V_s}{V_o} = (1 - D) + \frac{r_L}{R \cdot (1 - D)}$$

$$\frac{V_o}{V_s} = \frac{1}{\left[(1 - D) + \frac{r_L}{R \cdot (1 - D)} \right]} = \frac{1 - D}{(1 - D)^2 + \frac{r_L}{R}}$$

Efficiency

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}}$$

$$\eta = \frac{\frac{V_o^2}{R}}{\frac{V_o^2}{R} + I_{Lrms}^2 \cdot r_L} = \frac{\frac{V_o^2}{R}}{\frac{V_o^2}{R} + \left[\frac{V_o}{R \cdot (1 - D)} \right]^2 \cdot r_L}$$

Divide out the $\frac{V_o^2}{R}$

$$\eta = \frac{1}{1 + \frac{r_L}{R \cdot (1 - D)^2}}$$

ECE 320

Energy Systems I

Lesson 33

Power Electronics

Boost Converter

Adafruit.com

Assignment: look up Limor
Fried and Adafruit industries.
Find out the background of the
Minty Boost converter.