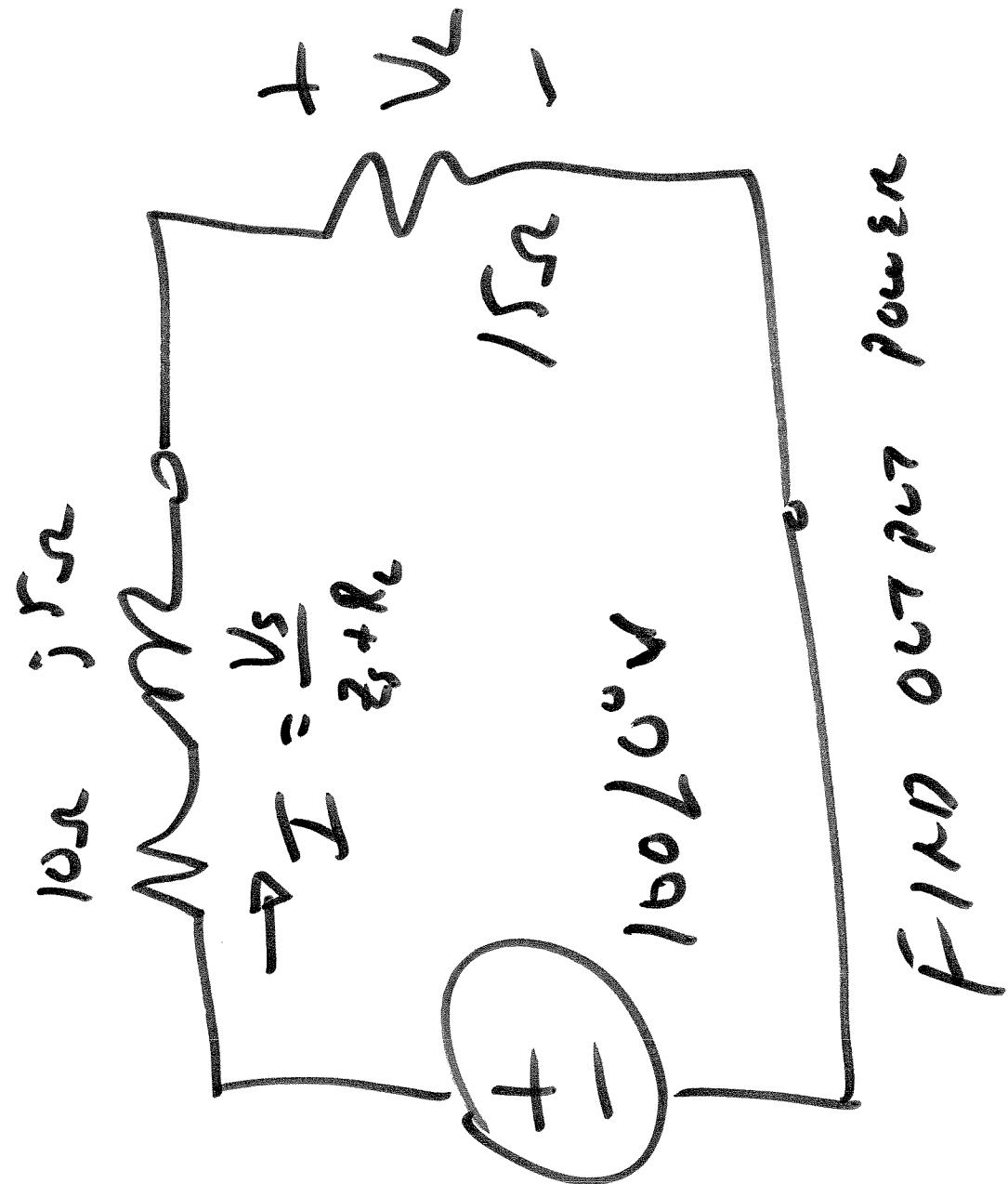


ECE 320 & ECE 329

ENERGY SYSTEMS I
BACKGROUND STUDY IN ENERGY SYSTEMS

SESSION no. 5





$$\text{By } P = R \cdot (V I^x)$$


$$P = \text{Re}(I R \cdot I^*)$$

$$I \cdot I^* = |I|^2$$


$$\Rightarrow P = |I|^2 R$$

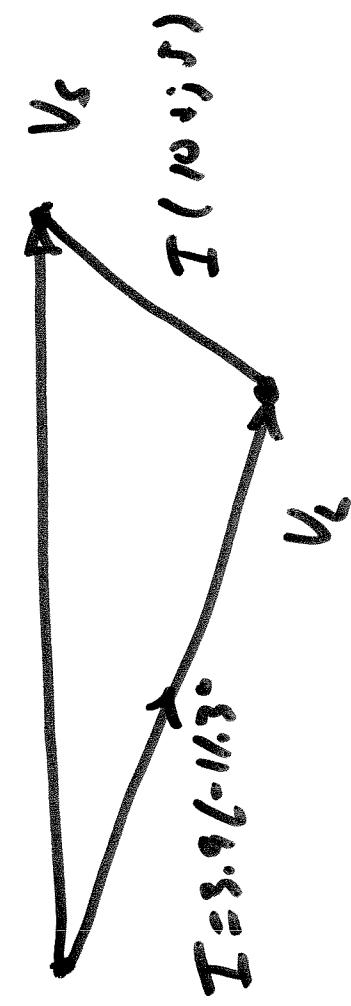

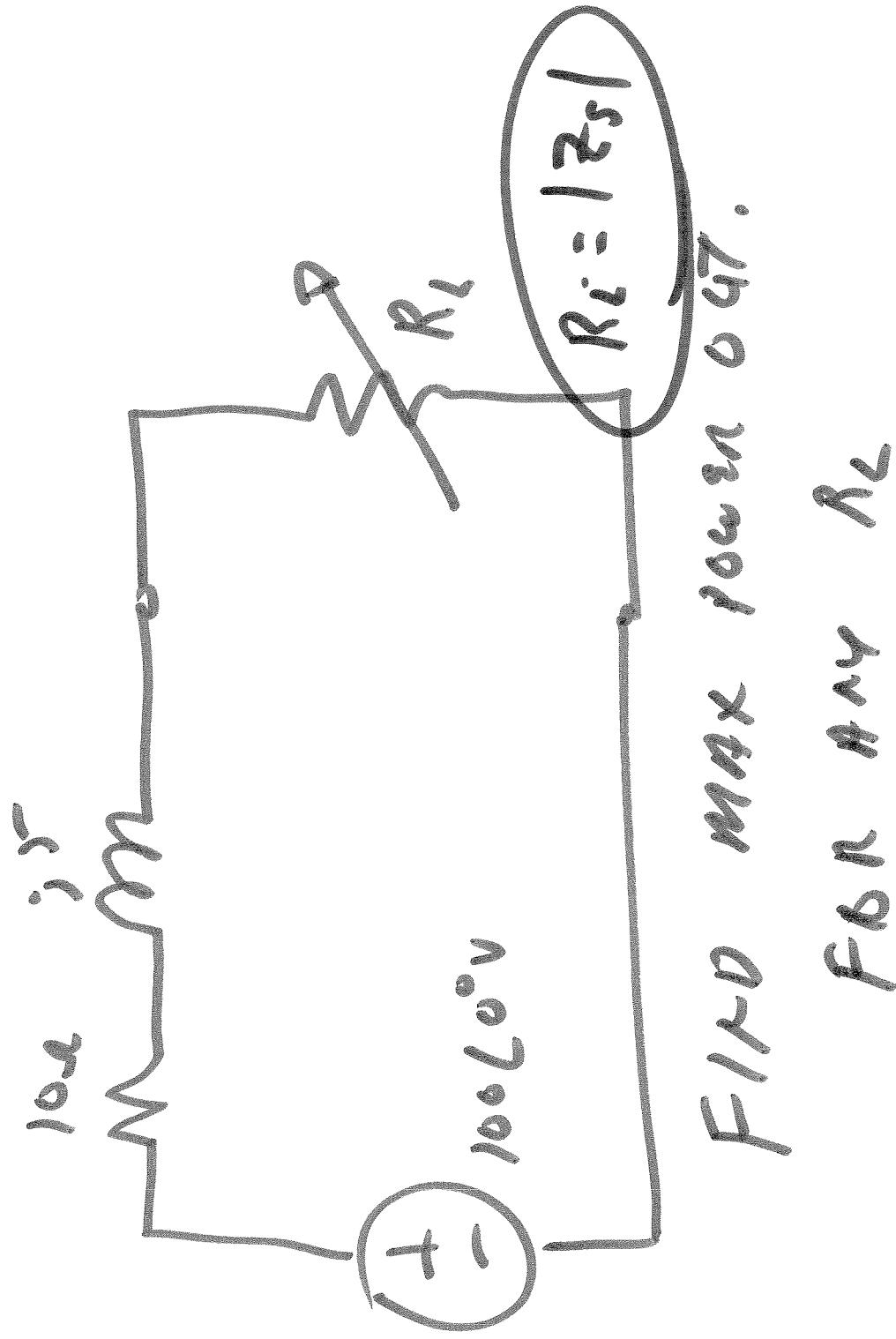

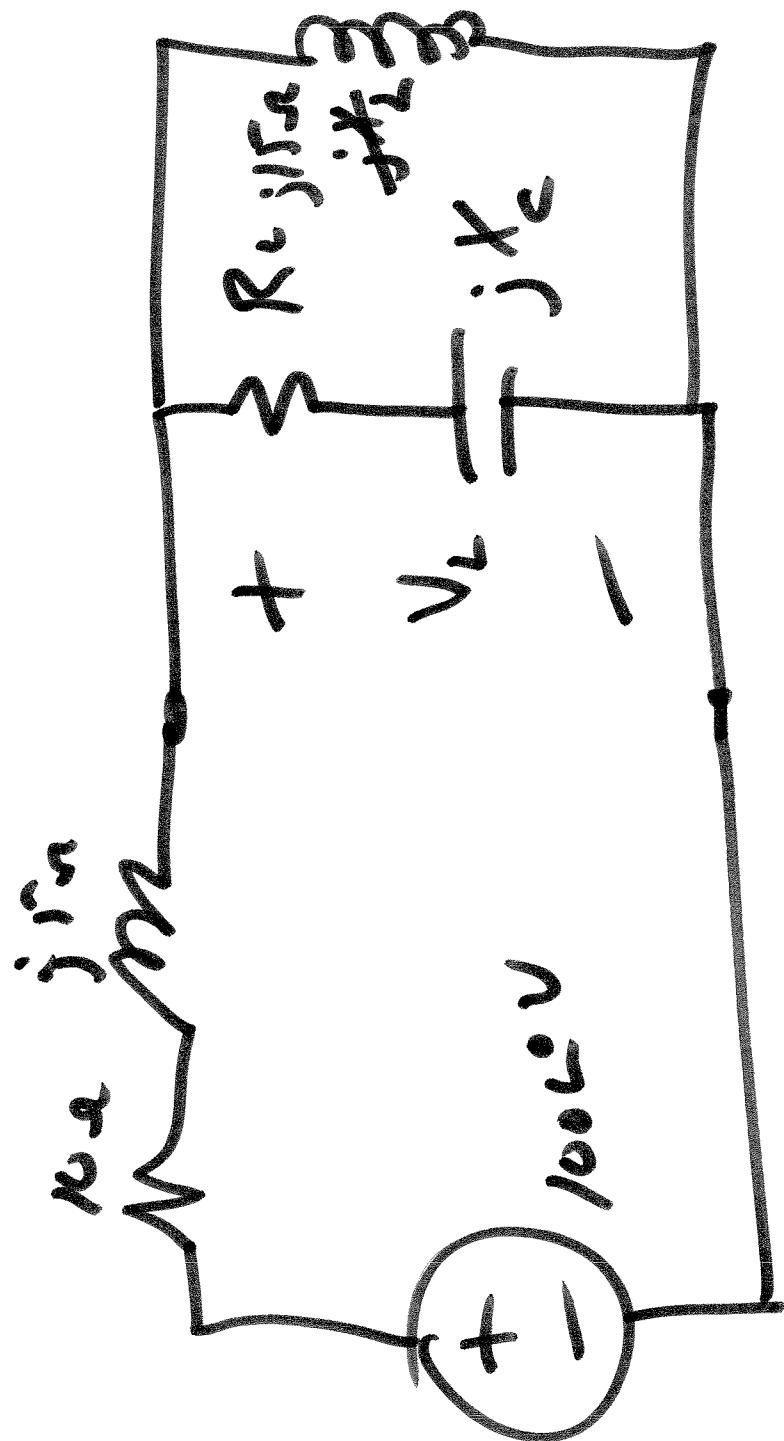
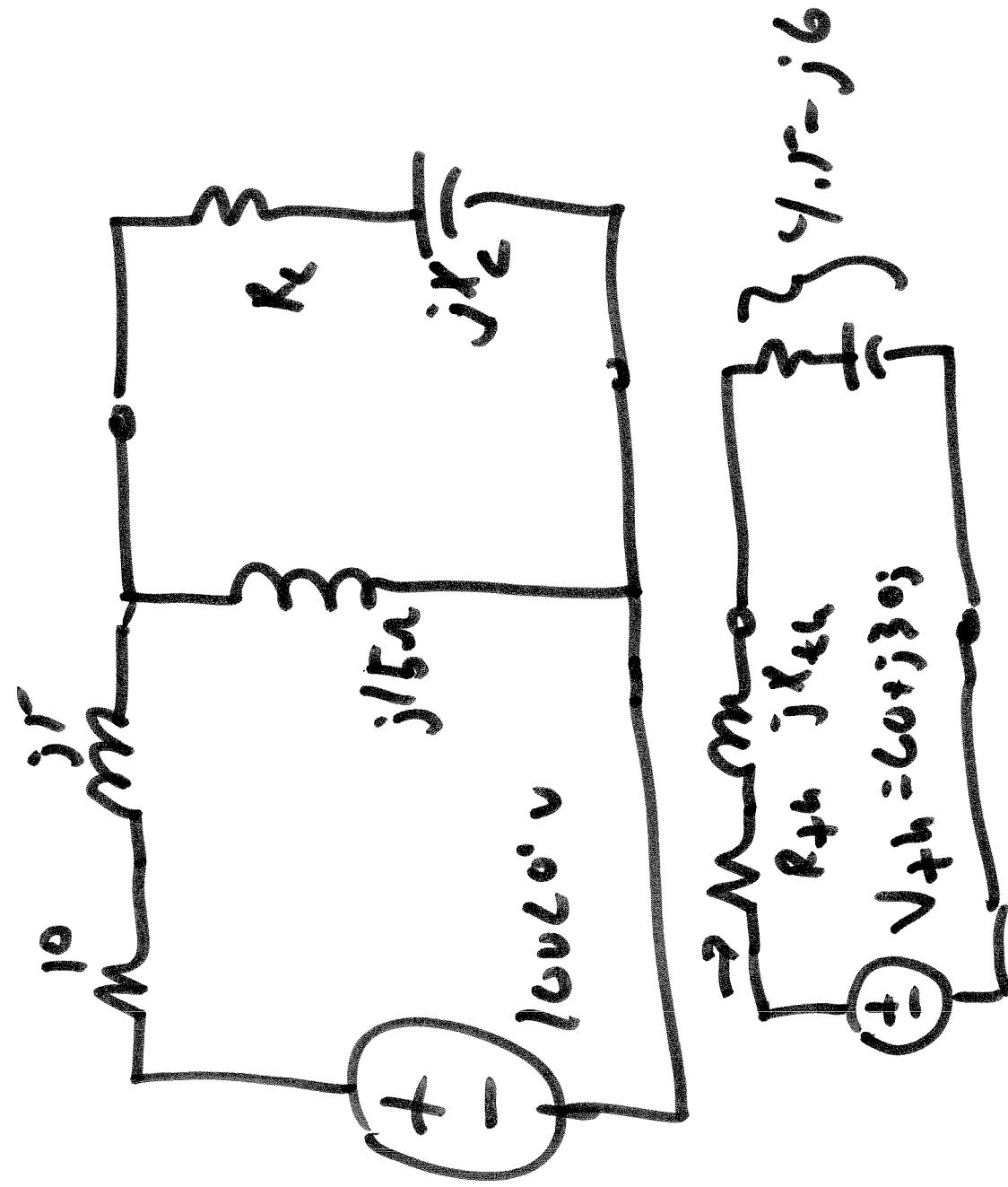
$$\begin{aligned}
 & X_C = -j5\mu\text{F} \quad R_L = 10\Omega \\
 & I = \frac{100e^{j50t}}{j10 + j15} \quad I = 5e^{j50t} \text{ A} \\
 & P_C = (I^2 / jR_1) R_1 = 250 \text{ W}
 \end{aligned}$$



$$V_{th} = (100\text{mV}) \left(\frac{j/15}{10+j/15} \right)$$


$$V_{th} = (60 + j30) \text{V}$$

$$Z_{th} = \frac{(j/15)(10+j/15)}{j/15 + (10+j/15)} = Y_{th} + j6$$


$$I_{max} =$$

$$\frac{600 + j30}{j/15 + (10+j/15)} = 6.22 + j2.22$$

$$\eta_{max} = |I_{max}|^2 / (Y_{th} + j6) = 250 \text{W}$$

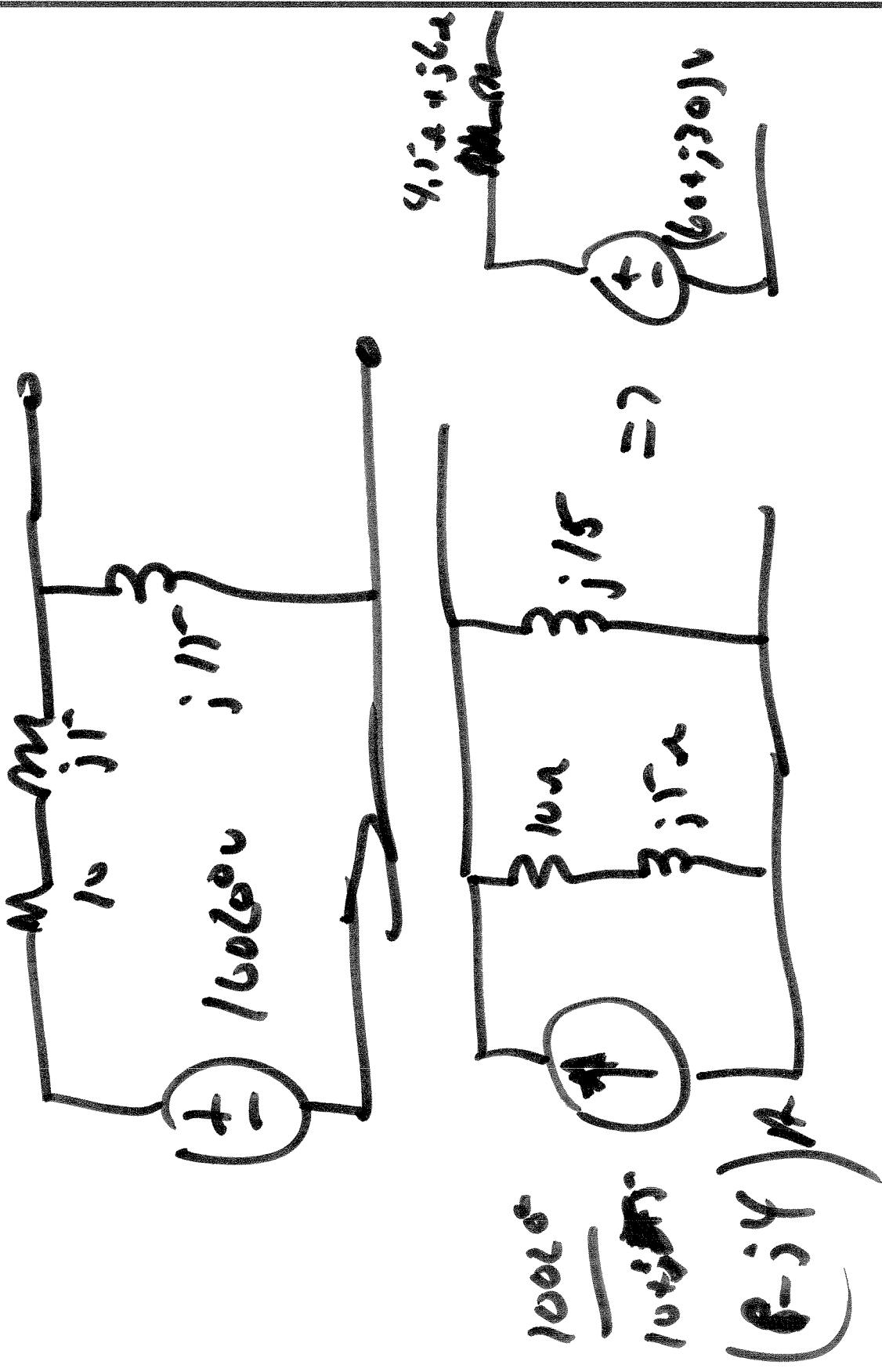

Locals

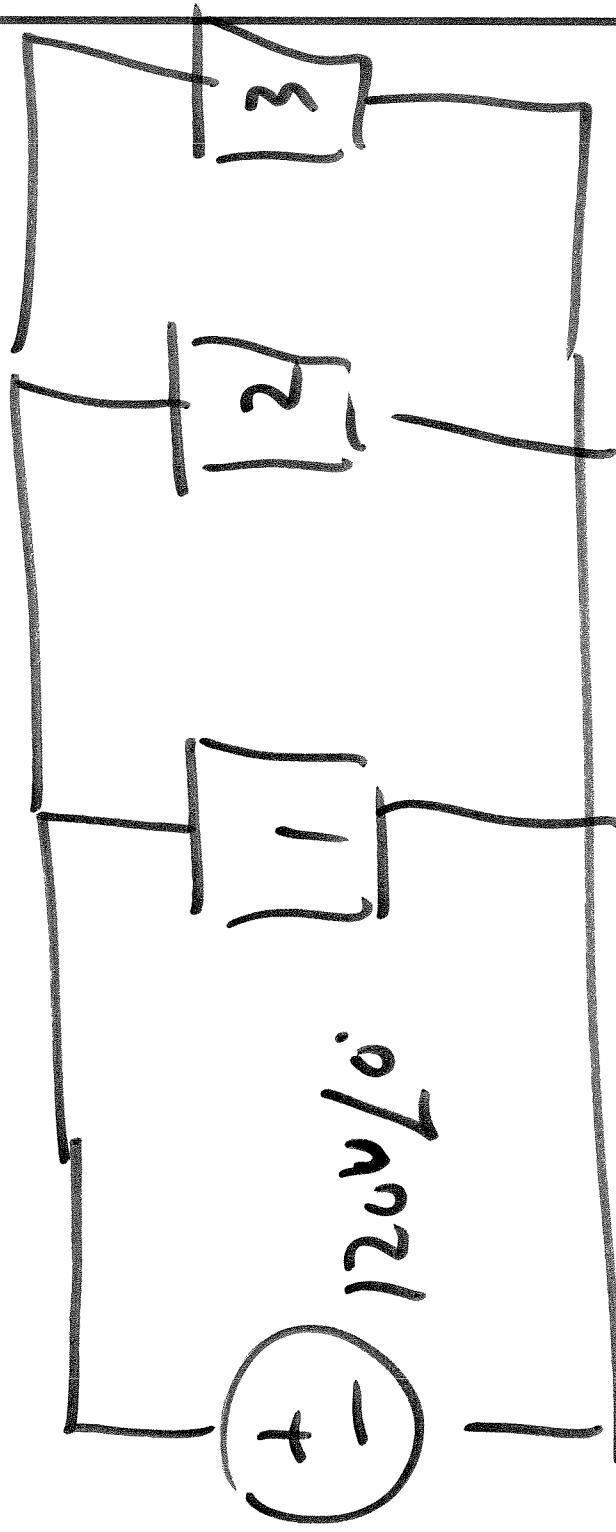

Find P , Φ , S , I for each
load

- Given
- 1: 10 kVA; 0.9 pt. factor
 - 2: 4 kW + j 3 kvar
 - 3: 5 A / 10° inductive (pantry)

$$s \sqrt{P} \alpha$$

$$P_i = (\nu \kappa v n) (0.9) = 9 \text{ kNm}$$

$$Q_i = \sqrt{s_{i2}^2 - P_{i2}} = \sqrt{(\nu \kappa v n)^2 - (9 \text{ kNm})^2}$$

$$Q_i = 4.36 \text{ kNm}$$

$$\Theta_i = \cos^{-1}(0.9)$$

$$T_i = \frac{s_i}{v_i} = \frac{16 \text{ kNm}}{12 \text{ m}} = 83.4 \text{ Nm} = 25.8 \text{ ft-lb}$$

$$P_2 = 4 \text{ kW}$$

$$Q_2 = 3 \text{ kVAR}$$

$$S_2 = \sqrt{P_2^2 + Q_2^2} = 5 \text{ kVA}$$

$$I_2 = \left(\frac{S_2}{V_2} \right)^* =$$

$$\frac{S_{kVA}}{120\text{V}} = 41.67 \angle -36.87^\circ$$

~~$$I_2 = 52^{-10^\circ} \text{ A}$$~~

$$S = V I_2^* = (120 \text{ cos } 10^\circ)(52 \text{ cos } 10^\circ) = 600 \text{ kVA}$$

$$P_1 = 600 \text{ cos } 10^\circ = 591 \text{ W}$$

$$Q_1 = 600 \text{ sin } 10^\circ = 104.3 \text{ VAR}$$

Power output example. For a circuit with a 100V AC source and a $(10+j5)\Omega$ source impedance, find the output power to a load resistance of 15 Ohms.

$$V_S := 100 \cdot V \quad Z_S := (10 + j \cdot 5) \cdot \Omega \quad j := \sqrt{-1}$$

$$|Z_S| = 11.18 \Omega \quad R_L := 15 \cdot \Omega$$

Find current and then power.

$$I := \frac{V_S}{Z_S + R_L} = (3.846 - 0.769i) A$$

$$|I| = 3.922 A \quad \arg(I) = -11.31 \text{ deg}$$

$$P_O := (|I|)^2 \cdot R_L = 230.769 W$$

Checking, find voltage at the load.

$$V_L := V_S \cdot \frac{R_L}{Z_S + R_L} = (57.692 - 11.538i) V$$


$$|V_L| = 58.835 V \quad \arg(V_L) = -11.31 \text{ deg}$$

Or, checking,

$$V_L := I \cdot R_L = (57.692 - 11.538i) V$$

Plot
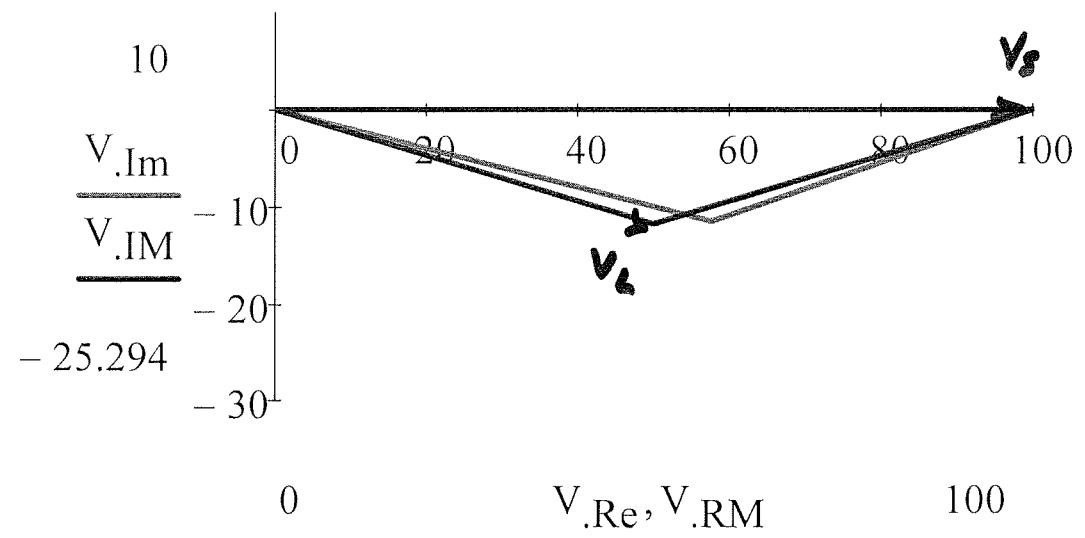
$$V_{Re} := \begin{pmatrix} 0 \\ V_S \\ \operatorname{Re}(V_L) \\ 0 \end{pmatrix} \quad V_{Im} := \begin{pmatrix} 0 \\ 0 \\ \operatorname{Im}(V_L) \\ 0 \end{pmatrix}$$




Max power transfer condition:

$$R_{LM} := |Z_S| = 11.18 \Omega$$

$$V_{LM} := V_s \cdot \frac{R_{LM}}{Z_S + R_{LM}} = (50 - 11.803i) V$$
$$|V_{LM}| = 51.374 V \quad \arg(V_{LM}) = -13.283 \text{ deg}$$

Plot
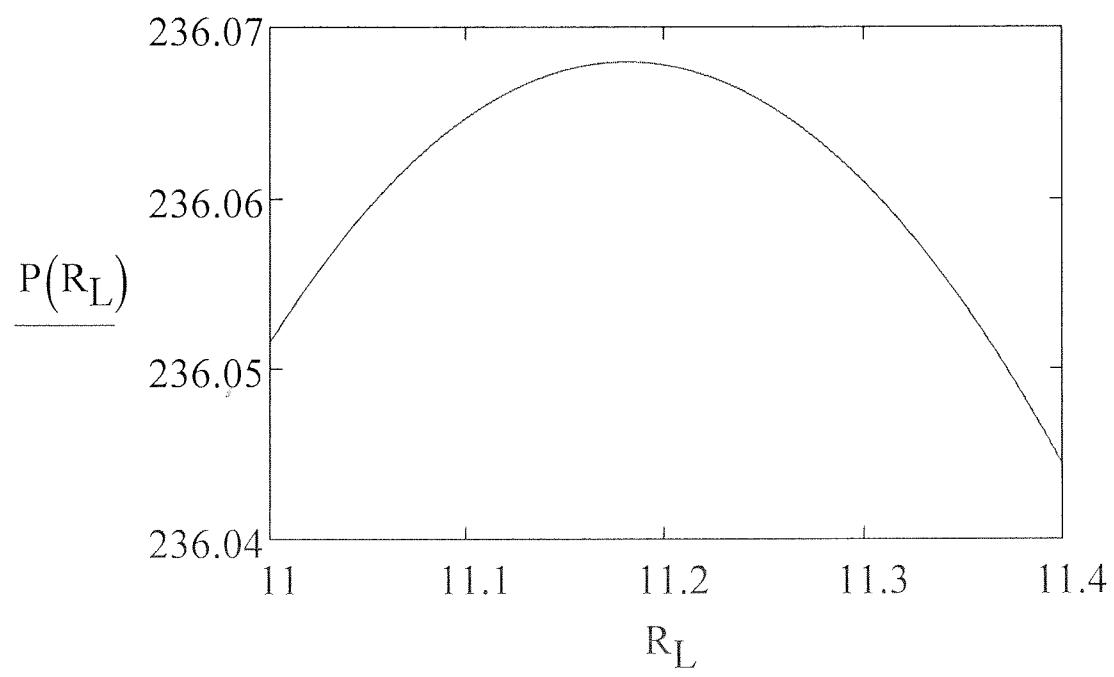
$$V_{RM} := \begin{pmatrix} 0 \\ V_s \\ \operatorname{Re}(V_{LM}) \\ 0 \end{pmatrix} \quad V_{IM} := \begin{pmatrix} 0 \\ 0 \\ \operatorname{Im}(V_{LM}) \\ 0 \end{pmatrix}$$



Max Power Transfer Example. For a circuit with a 100V AC source and a $(10+j5)\Omega$ source impedance, find the output power as a function of load resistance for a resistance only load.


$$V_s := 100 \cdot V \quad Z_s := (10 + j \cdot 5) \cdot \Omega \quad j := \sqrt{-1}$$

Find current and then power.


$$I(R_L) := \frac{V_s}{Z_s + R_L}$$

$$P(R_L) := (|I(R_L)|)^2 \cdot R_L$$

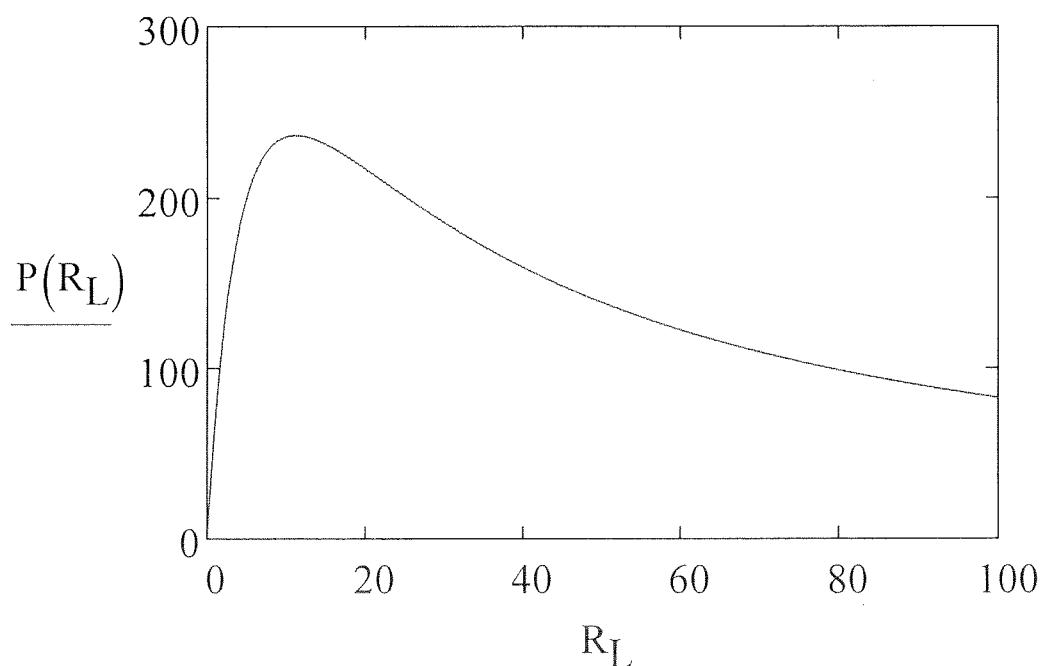Plot, first on a linear scale and then on a semilog scale.



And on the semilog scale

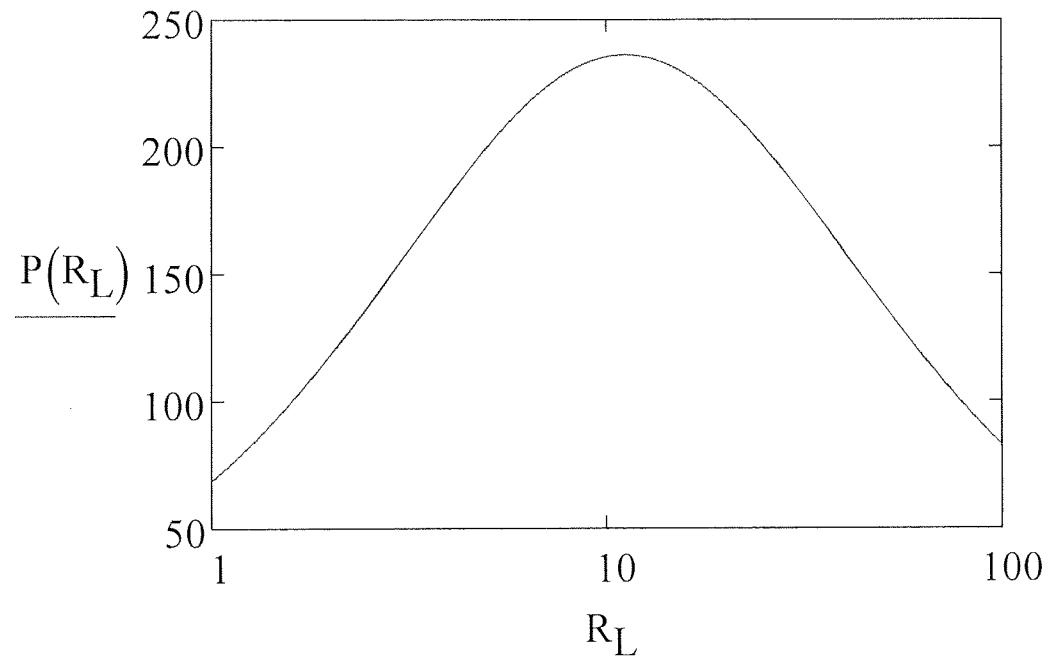

ECE 320

Energy Systems I

Lesson 5

AC Power