

ECE 320
Homework
Ideal DC / DC Converters

Recitation on campus: 9 April 2012
Due on campus: 11 April 2012

From the text handout by Daniel Hart, do the following problems:

1. 6.1 and 6.2
2. Problem 6.7
3. Problem 6.13 There are many answers to this problem; just find one that works.
4. Problem 6.15
5. Problem 6.17
6. Problem 6.20