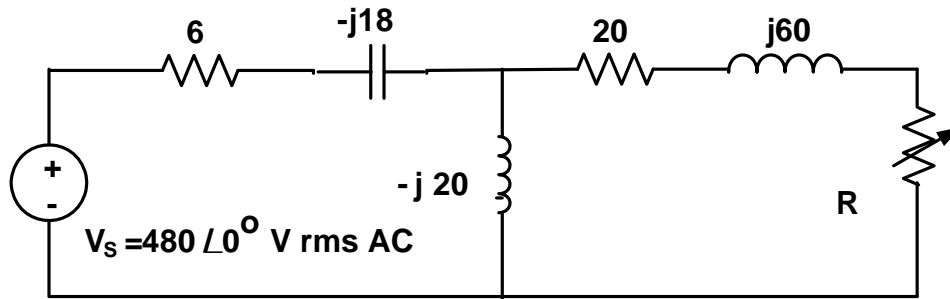


10.34 The variable resistor shown in Figure 10.34 is adjusted until the average power it absorbs is maximum.

- Find R .
- Find the maximum average power.



Units for impedances are Ohms

Figure 10.34

Solve this one by first finding the Thevenin equivalent impedance for the network without load R . Then match the impedance magnitudes.

$$Z_{eq} := (20 \cdot \Omega + j \cdot 60 \cdot \Omega) + \frac{(8 \cdot \Omega - j \cdot 18 \cdot \Omega) \cdot (-j \cdot 20 \cdot \Omega)}{(8 \cdot \Omega - j \cdot 18 \cdot \Omega) + (-j \cdot 20 \cdot \Omega)} \quad Z_{eq} = (22.122 + 50.08i) \Omega$$

$$j := \sqrt{-1}$$

Then match the impedance magnitudes.

$$R_{max} := |Z_{eq}| \quad R_{max} = 54.748 \Omega$$

Find the voltage of the Thevenin circuit and the voltage of the load.

$$V_{th} := (480 \cdot V) \cdot \left(\frac{j \cdot 20 \cdot \Omega}{8 \cdot \Omega - j \cdot 18 \cdot \Omega + j \cdot 20 \cdot \Omega} \right) \quad V_{th} = (282.353 + 1.129i \times 10^3) V$$

$$V_{Rmax} := V_{th} \cdot \left(\frac{R_{max}}{R_{max} + Z_{eq}} \right) \quad V_{Rmax} = (509.073 + 472.732i) V$$

Calculate the load power.

$$P_{max} := \frac{(|V_{Rmax}|)^2}{R_{max}} \quad P_{max} = 8.815 \cdot kW$$

2. Three loads are connected in parallel across a 480V rms line. Load 1 absorbs 12kW and 6.7 kVAr. Load 2 absorbs 4kVA at 0.96 power factor leading. Load 3 absorbs 15kW at 1.00 power factor.

- Find the current in Load 1.
- Load 2 is a combination of a resistance and a capacitance. If these two elements are in parallel with each other, find the resistance and reactance values of each of them.
- Find the real power, reactive power, and apparent power absorbed by the combined three loads.

Restate the given.

$$j_w := \sqrt{-1} \quad \text{kVAr} := \text{kV} \cdot \text{A} \quad \text{leading} := 1$$

$$P_1 := 12 \cdot \text{kW} \quad Q_1 := 6.7 \cdot \text{kVAr} \quad V_L := 480 \cdot \text{V} \quad \text{lagging} := 1$$

$$S_2 := 4.0 \cdot \text{kV} \cdot \text{A} \quad \text{pf}_2 := 0.96 \cdot \text{leading}$$

$$P_3 := 15 \cdot \text{kW} \quad \text{pf}_3 := 1.00$$

Calculate the current in load 1 from the complex power and the terminal voltage.

$$I_1 := \left(\frac{P_1 + j \cdot Q_1}{V_L} \right) = (25 - 13.958i) \text{ A} \quad |I_1| = 28.633 \text{ A} \quad \arg(I_1) = -29.176 \cdot \text{deg}$$

This is the answer for problem 2a.

Find the real and reactive power in load 2.

$$P_2 := S_2 \cdot \text{pf}_2 = 3.84 \cdot \text{kW} \quad Q_2 := -\sqrt{S_2 \cdot S_2 - P_2 \cdot P_2} = -1.12 \cdot \text{kVAr}$$

For parallel connection, each element has the same terminal voltage. Finding the impedance elements:

$$R_2 := \frac{(|V_L|)^2}{P_2} = 60 \Omega \quad X_2 := \frac{(|V_L|)^2}{Q_2} = -205.714 \Omega$$

This is the answer for problem 2b.

Checking, find the current I_2 .

$$\theta_2 := -\arccos(0.96) = -0.284$$

$$I_2 := \left(\frac{S_2}{V_L} \cdot e^{j \cdot \theta_2} \right) = (8 + 2.333i) \text{ A} \quad |I_2| = 8.333 \text{ A} \quad \arg(I_2) = 16.26 \cdot \text{deg}$$

Using Ohm's Law, find the parallel resistance and reactance. If the voltage has a zero phase angle, which we have already set, then the real part of the current will appear in the resistance and the imaginary part of the current will appear in the reactance.

$$R_{2w} := \frac{V_L}{\text{Re}(I_2)} = 60 \Omega \quad X_{2w} := \frac{V_L}{\text{Im}(I_2)} = 205.714 \Omega$$

Collect all the orthogonal components of real and reactive power so we can make a vector addition.

$$P_1 = 12 \cdot \text{kW} \qquad Q_1 = 6.7 \cdot \text{kVAr}$$

$$P_2 = 3.84 \cdot \text{kW} \qquad Q_2 = -1.12 \cdot \text{kVAr}$$

$$P_3 = 15 \cdot \text{kW} \qquad Q_3 := 0 \cdot \text{kVAr} \text{ for a 1.00 power factor}$$

Add the components together as orthogonal components of a vector.

$$P_T := P_1 + P_2 + P_3 = 30.84 \cdot \text{kW} \qquad Q_T := Q_1 + Q_2 + Q_3 = 5.58 \cdot \text{kVAr}$$

$$S_T := P_T + j \cdot Q_T = (30.84 + 5.58i) \cdot \text{kV} \cdot \text{A}$$

$$|S_T| = 31.341 \cdot \text{kV} \cdot \text{A}$$

This is the answer for problem 2c.

Checking, find the currents and add them together. We already have I_1 and I_2 .

$$I_3 := \frac{P_3}{V_L \cdot \text{pf}_3} \cdot e^{j \cdot 0 \cdot \text{deg}} = 31.25 \text{ A}$$

$$I_T := I_1 + I_2 + I_3 = (64.25 - 11.625i) \text{ A}$$

Finally, calculate the total kVA.

$$\underline{S_T} := V_L \cdot \overline{I_T} = (30.84 + 5.58i) \cdot \text{kV} \cdot \text{A}$$

3. A certain load has a voltage of 120V AC at 60 Hertz. It draws 3.0 Amps.


a. Let the voltage and current be in phase. Determine and sketch the power that this load draws as a function of time. Draw the voltage on the same set of axes for reference.

b. Let the power factor be 0.90 lagging; determine and sketch the power that this load draws as a function of time. Draw the voltage on the same set of axes for reference.

The given voltage is rms (not otherwise stated); the current is also rms for the same reason.

$$v(t) := 120 \cdot \sqrt{2} \cdot \cos(\omega_s \cdot t) \cdot V \quad i_a(t) := 3 \cdot \sqrt{2} \cdot \cos(\omega_s \cdot t) \cdot A \quad \omega_s := 2 \cdot \pi \cdot 60 \cdot \frac{\text{rad}}{\text{sec}} = 376.991 \cdot \frac{\text{rad}}{\text{sec}}$$

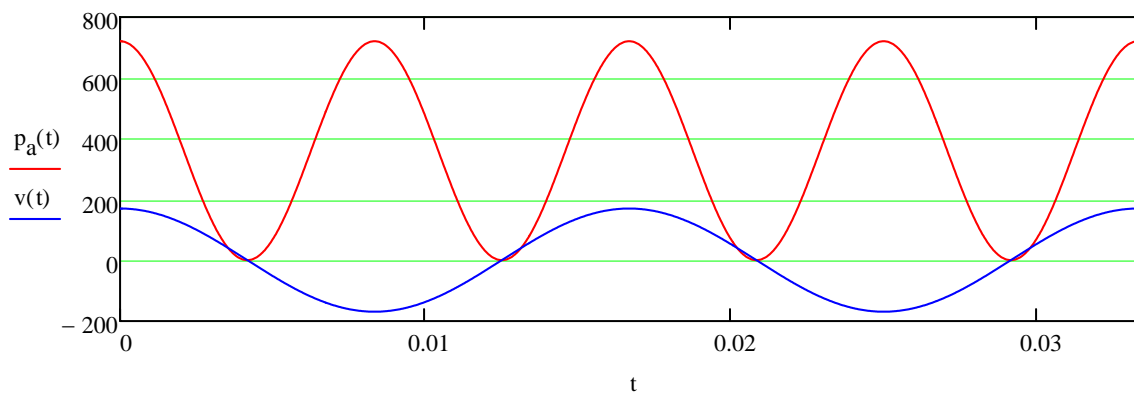
$$p_a(t) := v(t) \cdot i_a(t) \quad P_a := \frac{\omega_s}{2 \cdot \pi} \int_0^{\frac{2 \cdot \pi}{\omega_s}} p_a(t) dt = 360 \text{ W}$$



$$v(t) := 120 \cdot \sqrt{2} \cdot \cos(\omega_s \cdot t) \cdot V \quad i_a(t) := 3 \cdot \sqrt{2} \cdot \cos(\omega_s \cdot t - \theta_{3b}) \cdot A \quad \theta_{3b} := \arccos(0.90) = 25.842 \cdot \text{deg}$$

$$p_a(t) := v(t) \cdot i_a(t) \quad P_{\text{avg}} := \frac{\omega_s}{2 \cdot \pi} \int_0^{\frac{2 \cdot \pi}{\omega_s}} p_a(t) dt = 324 \text{ W}$$

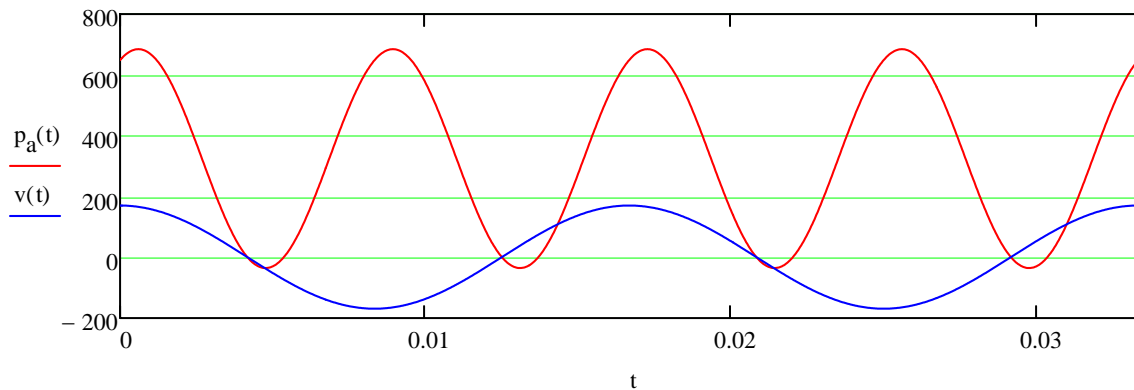See the phase shift and the reduced average value of the power waveform.



Problem 4. (10.37) A factory has an electrical load of 1600 kW at a lagging power factor of 0.80. An additional variable power factor load is to be added to the factory. The new load will add 320 kW to the real power load of the factory. The power factor of the added load is to be adjusted so that the overall power factor of the factory is 0.96 leading.

- Specify the reactive power associated with the added load.
- Does the added load absorb or deliver magnetizing VARs?
- What is the power factor of the additional load?
- Assume that the rms voltage at the factory is 2400V. What is the rms magnitude of the current into the factory before the variable power factor load is added?
- What is the rms magnitude of the current into the factory after the variable power factor load has been added?

$$P_F := 1600 \cdot \text{kW} \quad \text{pf}_F := 0.80 \text{ lagging} \quad P_N := 320 \cdot \text{kW} \quad \text{pf}_{\text{all}} := 0.96 \text{ leading} \quad \begin{matrix} \text{kVAr} := \text{kV} \cdot \text{A} \\ \text{MVA} := 10^6 \cdot \text{V} \cdot \text{A} \end{matrix}$$

Calculate the real and reactive power for the original factory load.

$$S_F := \frac{P_F}{\text{pf}_F} \quad S_F = 2 \times 10^3 \cdot \text{kV} \cdot \text{A} \quad Q_F := \sqrt{S_F^2 - P_F^2} \quad Q_F = 1.2 \times 10^3 \cdot \text{kVAr}$$

Calculate the real and reactive power for the combined load.

$$P_{\text{all}} := P_F + P_N \quad P_{\text{all}} = 1.92 \cdot \text{MW}$$

$$S_{\text{all}} := \frac{P_{\text{all}}}{\text{pf}_{\text{all}}} \quad S_{\text{all}} = 2 \cdot \text{MVA} \quad Q_{\text{all}} := -\sqrt{S_{\text{all}}^2 - P_{\text{all}}^2} \quad Q_{\text{all}} = -0.56 \cdot \text{MVAr}$$

The added reactive power is the difference between the original and combined values thereof.

$$Q_N := Q_{\text{all}} - Q_F \quad Q_N = -1.76 \cdot \text{MVAr} \quad \text{This is the answer to part a.}$$

The added load delivers magnetizing VARs. The added load is capacitive in nature.

Use the definition of power factor to get the new load's power factor. **This is the answer to part b.**

$$S_N := \sqrt{P_N^2 + Q_N^2} \quad S_N = 1.789 \cdot \text{MVA}$$

$$\text{pf}_N := \frac{P_N}{S_N} \quad \text{pf}_N = 0.179 \text{ leading} \quad \text{This is the answer to part c.}$$

Use the equation for real power to find the current, before and after adding the load. $V_F := 2400 \cdot \text{V}$

$$P_F = V_F \cdot I_F \cdot \text{pf}_F \quad I_F := \frac{P_F}{V_F \cdot \text{pf}_F} \quad I_F = 833.333 \text{ A} \quad \text{This is the answer to part d.}$$

$$I_{\text{all}} := \frac{P_{\text{all}}}{V_F \cdot \text{pf}_{\text{all}}} \quad I_{\text{all}} = 833.333 \text{ A} \quad \text{This is the answer to part e.}$$

10.44 If a third resistor is added to a hair dryer circuit, it is possible to design three independent power specifications. If the resistor R3 is added in series with the thermal fuse, then the corresponding LOW, MEDIUM, and HIGH power circuit diagrams are as shown in Figure 10.44. If the three power settings are 600W, 900W, and 1200W, respectively, when connected to a 120V rms supply, what resistor values should be used?

Using a power method, we define the three cases.

$$\text{Guess } R_1 := 10 \cdot \Omega \quad R_2 := 10 \cdot \Omega \quad R_3 := 10 \cdot \Omega$$

Given

$$600 \cdot W = \frac{(120 \cdot V)^2}{R_1 + R_2 + R_3} \quad 900 \cdot W = \frac{(120 \cdot V)^2}{R_2 + R_3} \quad 1200 \cdot W = \frac{(120 \cdot V)^2}{R_3 + \frac{R_1 \cdot R_2}{R_1 + R_2}}$$

$$\begin{pmatrix} R_1 \\ R_2 \\ R_3 \end{pmatrix} := \text{Find}(R_1, R_2, R_3) = \begin{pmatrix} 8 \\ 8 \\ 8 \end{pmatrix} \Omega$$

For those who prefer to see more algebra, we see that rearranging the first two cases leaves a way to find R₁.

$$R_1 + R_2 + R_3 = \frac{(120 \cdot V)^2}{600 \cdot W} \quad R_2 + R_3 = \frac{(120 \cdot V)^2}{900 \cdot W}$$

$$R_1 := \frac{(120 \cdot V)^2}{600 \cdot W} - \frac{(120 \cdot V)^2}{900 \cdot W} \quad R_1 = 8 \Omega$$

The other two expressions give two equations and two unknowns:

$$900 \cdot W = \frac{(120 \cdot V)^2}{R_2 + R_3}$$

$$1200 \cdot W = \frac{(120 \cdot V)^2}{R_3 + \frac{R_1 \cdot R_2}{R_1 + R_2}}$$

$$R_2 + R_3 = 16$$

$$R_3 \cdot (R_1 + R_2) + R_1 \cdot R_2 = 12 \cdot (R_1 + R_2)$$

$$R_3 \cdot R_1 + R_3 \cdot R_2 + R_1 \cdot R_2 = 12 \cdot R_1 + 12 \cdot R_2$$

$$R_2 + R_3 = 16$$

Substitute for R₁.

$$8 \cdot R_3 + R_2 \cdot R_3 + 8 \cdot R_2 - 12 \cdot 8 - 12 \cdot R_2 = 0$$

Simplify again.

$$8 \cdot R_3 + R_2 \cdot R_3 - 4 \cdot R_2 - 96 = 0$$

The two equations simplify to

$$R_2 + R_3 = 16$$

$$8 \cdot R_3 + R_2 \cdot R_3 - 4 \cdot R_2 - 96 = 0$$

Substitute for R2.

$$8 \cdot R_3 + (16 - R_3) \cdot R_3 - 4(16 - R_3) - 96 + 0$$

Simplify into a quadratic equation.

$$8 \cdot R_3 + 16 \cdot R_3 + 4 \cdot R_3 - 96 - R_3^2 - 64 = 0$$

$$R_3^2 - 28 \cdot R_3 + 160 = 0$$

Factor this

$$(R_3 - 20) \cdot (R_3 - 8) = 0$$

Solve for R₂ to find the bogus root.

$$\underline{R_2} := 20 \quad \underline{R_2} := 16 - R_3 = -4$$

$$\underline{R_2} := 8 \quad \underline{R_2} := 16 - R_3 = 8$$

The answer is $R_1 = 8 \Omega$ $R_2 = 8$ $R_3 = 8$

All resistances are positive in this case, making it the realistic solution.

If we fail to see the factors, use the quadratic formula.

$$\underline{R_2} := \frac{28 + \sqrt{28^2 - 4 \cdot 1 \cdot 160}}{2} \quad R_3 = 20$$

$$\underline{R_2} := \frac{28 - \sqrt{28^2 - 4 \cdot 1 \cdot 160}}{2} \quad R_3 = 8$$

All resistances are positive in this case, making it the realistic solution.

$$R_1 = 8 \Omega \quad \underline{R_2} := 8 \cdot \Omega \quad \underline{R_2} := 8 \cdot \Omega$$