

1. (5 points) A small power system is configured as shown in Figure 1. The line reactance is $j0.35$ Ohms. Both ideal transformers have a 5:1 turns ratio. For an output of 1.0MVA, 480V AC rms, 0.94 power factor at full load, find the voltage regulation.

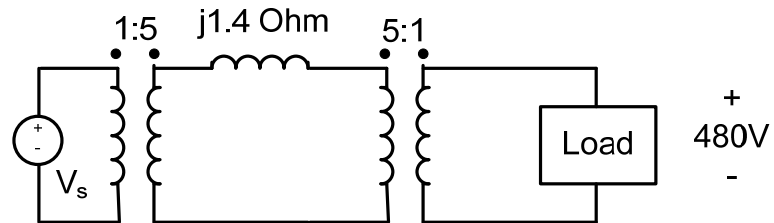


Figure 1. Small Electric Power System.

2. (5 points) A 50kVA, 4160V:480V transformer has the following parameters for its Steinmetz equivalent circuit:

$R_{eq} = 13.8 \text{ Ohms}$	Series winding resistance referred to the high voltage side
$X_{eq} = 41.5 \text{ Ohms}$	Series leakage reactance referred to the high voltage side
$X_M = 92 \text{ Ohms}$	Magnetizing reactance referred to the low voltage side
$R_c = 460 \text{ Ohms}$	Core loss resistance referred to the low voltage side

- a. (1 points) Draw an appropriate equivalent circuit for this transformer. Label each circuit element.
- b. (4 points) When a short circuit test is conducted according to the method prescribed in the textbook, what would you expect the voltage measurement to be?