1. (6 points) For the machine shown on the monitor, identify the four parts indicated:

A. _____ B. ____

C. _____ D. ____

2. (10 points) A <u>separately excited</u> DC motor operated with a terminal voltage of 180V and an armature current of 50A. Its armature resistance is 0.14 Ohms and its field resistance is 300 Ohms. The field voltage, being separately excited, is 240V. Mechanical losses are insignificant. Its saturation curve at 3000 RPM is given on the other side of this page.

a. (5 points) Find its speed of rotation.

b. (2 points) Find Kφ, its machine constant.

c. (3 points) Find its torque.

3. (2 points) If the raise the <u>armature</u> current by adding load, the speed of our separately excited machine will ______. (increase / remain the same / decrease)

4. (2 points) If we raise the <u>field</u> current of our machine by increasing the field voltage, the speed of our separately excited machine will ______. (increase / remain the same / decrease)

