



3. (3 points) Calculate and plot the transistor switch voltage of the same flyback converter in continuous conduction mode.