ECE 404 / 504

T & D Applications of Voltage Sourced Converters

Lesson 10

We can get variable voltage DC from –Vd to +Vd using two power poles in a bidirectional buck converter.

We will now get AC using this same set of ideas.

Peak value is Vd; negative peak is –Vd.

The rms value is Vd.

The amplitude of the fundamental frequency is 4Vd/pi.

What have I been able to do so far?

- *Set the frequency
- * I can get an amplitude; One and only one amplitude so far.

*Set the phase.

Let's go back and look at improving this amplitude. I'd like to be able to set it to something I like.

Peak value is V_d ; negative peak is $-V_d$.

The rms value is (depends on duty cycle): Vd*sqrt(2*d_A)

The amplitude of the fundamental frequency is

(depends on duty cycle). Use an FFT to get the numbers.

What do harmonics do for to us?

*Heat

*Torques...

How can we get the ac pulses that we saw?

*Use two levels dc and compare to a triangle wave.

*Make two buck converter controls and subtract the results.


Next: Three phase waveforms


Harmonics in an AC Pulse Width Modulated Waveform: FFT Example

introduction. FFT Example
$$d_{A} := 0.8 \quad \text{NN} := 10 \quad \text{pts} := 2^{\text{NN}} \quad i := 0, 1 ... \, \text{pts} - 1$$

$$v_{p_{i}} := \begin{vmatrix} 1 & \frac{d_{A}}{2} \\ 1 & \text{if} & \frac{1 - \frac{d_{A}}{2}}{4} \cdot \text{pts} \le i < \frac{1 + \frac{d_{A}}{2}}{4} \cdot \text{pts} \end{vmatrix} \cdot \text{pts}$$
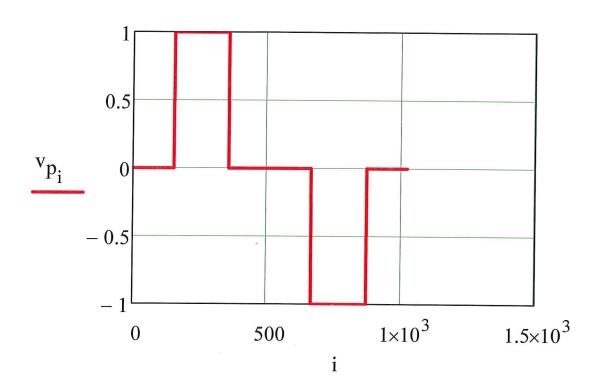
$$v_{fft} := \text{fft} \begin{pmatrix} v_{p} \end{pmatrix}^{\text{therwise}}$$



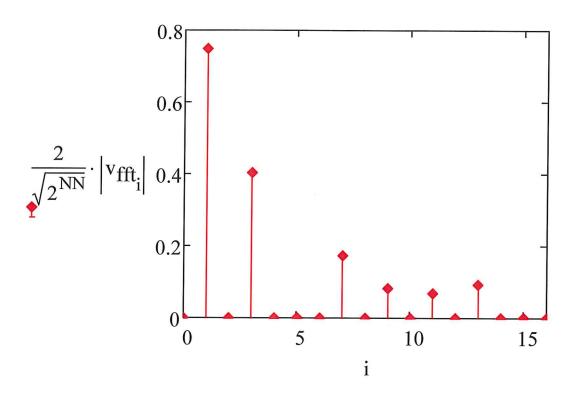

FFT Example

$$d_A := 0.4$$


$$NN := 10$$


$$pts := 2^{NN}$$

$$NN := 10$$
 $pts := 2^{NN}$ $i := 0, 1... pts - 1$

$$v_{p_i} := \begin{bmatrix} 1 & \text{if } 0 \leq i < d_A \cdot \text{pts} \\ 0 & \text{otherwise} \end{bmatrix}$$

$$v_{fft} := fft(v_p)$$

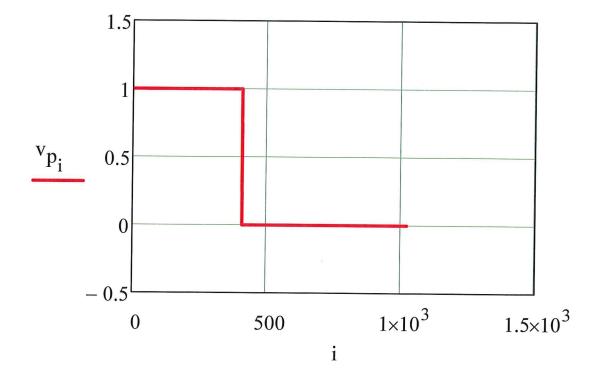

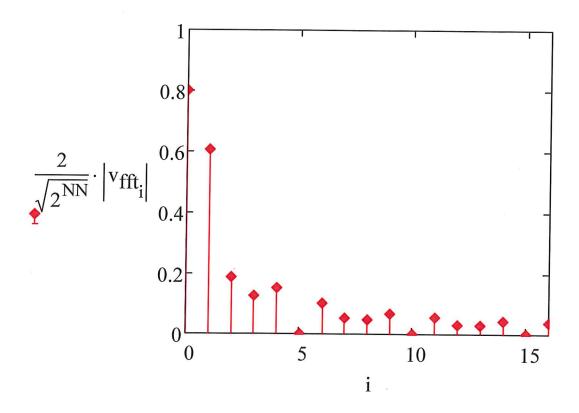

$$v_{fft_1} = 3.012 + 9.211i$$
 $|v_{fft_1}| = 9.691$
 $arg(v_{fft_1}) = 71.895 \cdot deg$
 $\frac{|v_{fft_1}|}{8} = 1.211$
 $\frac{4}{\pi} = 1.273$