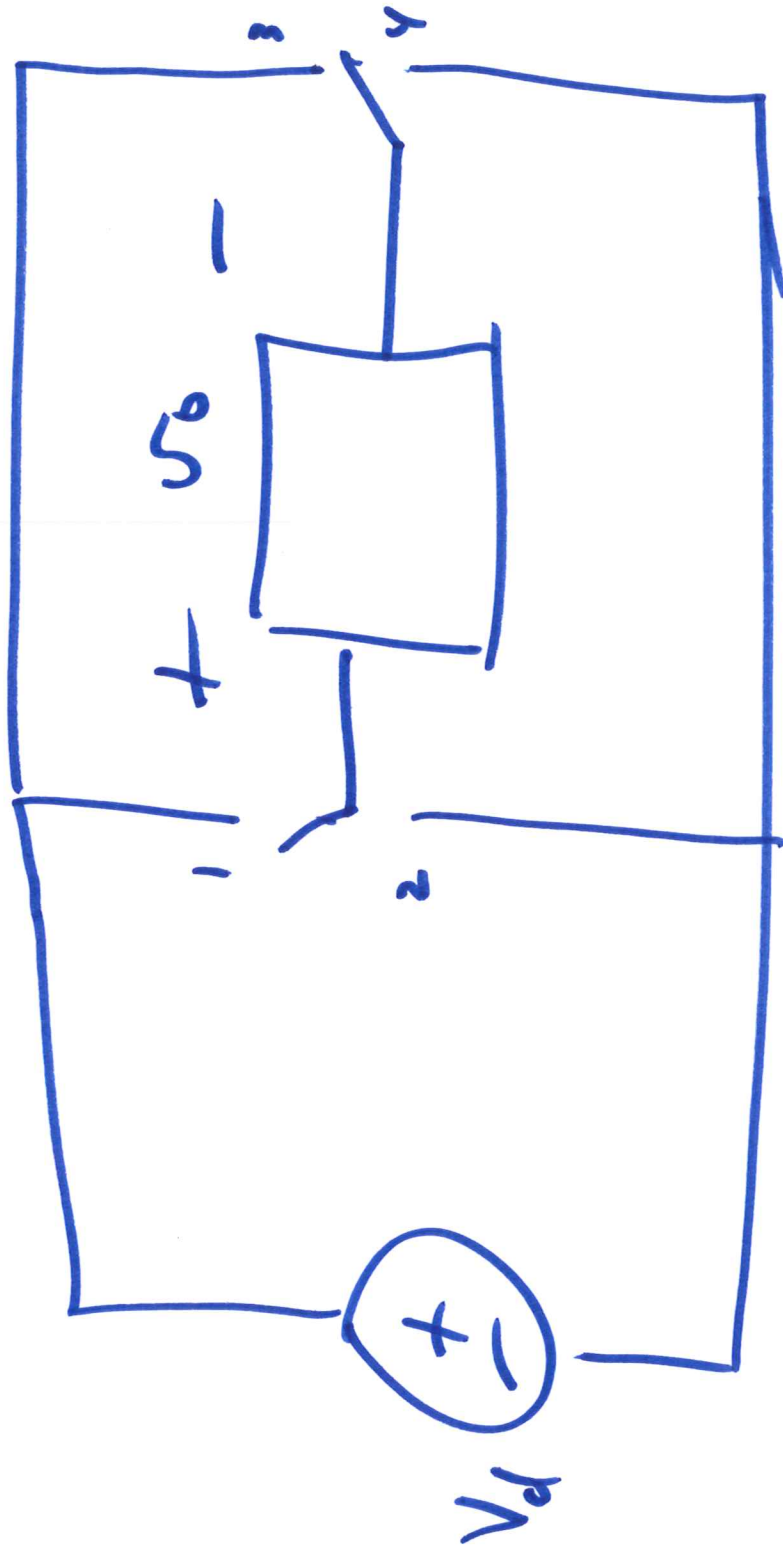



ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS

SESSION no. 10


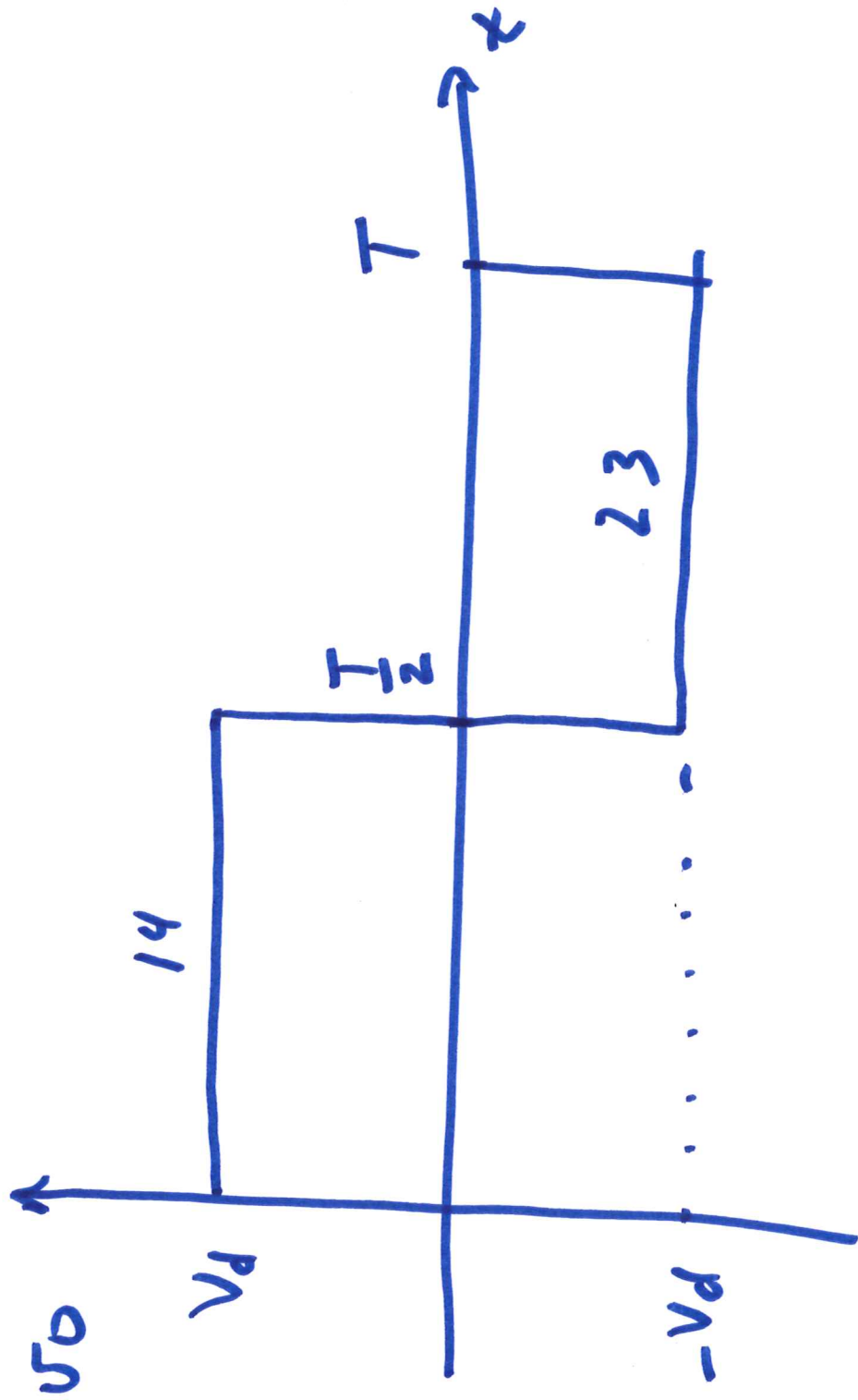
$$\begin{aligned} 1\ 4 &\rightarrow V_o = V_d \\ 2\ 3 &\rightarrow V_o = V_d \\ 1\ 3, 2\ 4 &\rightarrow V_o = 0 \end{aligned}$$



$$\sqrt{2} V_d$$

$$V_d \sqrt{\frac{1}{T} \int_0^T v^2(x) dx}$$

$$\sqrt{\frac{1}{T} \int_0^T \left(V_d^2 dx + \int_{I_2}^T (-V_d)^2 dt \right)}$$

$$\sqrt{\frac{1}{T} \int_0^T V_d^2 dx}$$

$$\sqrt{\frac{1}{T} V_d^2 T}$$

$V_d \sim$

$V_d \sim$

$PN + =$

$$\frac{1}{T}$$

$$\frac{2\pi}{T}$$

$$V_d$$

$$V_d <$$

$$V_{o1} = \frac{4}{\pi} V_d \int_{\pi/2}^{\pi} \sin \omega t \, d\omega$$


$$\omega = \frac{2\pi}{T}$$

$$V_{o1} = \frac{4}{T} \frac{1}{\omega} \left[-V_d \cos \omega t \right]_0^{\pi/2}$$

$$V_{o1} = \frac{2}{\pi} V_d \left(-(-1) - (-1) \right)$$

$$V_{o1} = \frac{4}{\pi} V_d$$

$$\frac{4}{\pi} = 1.28$$

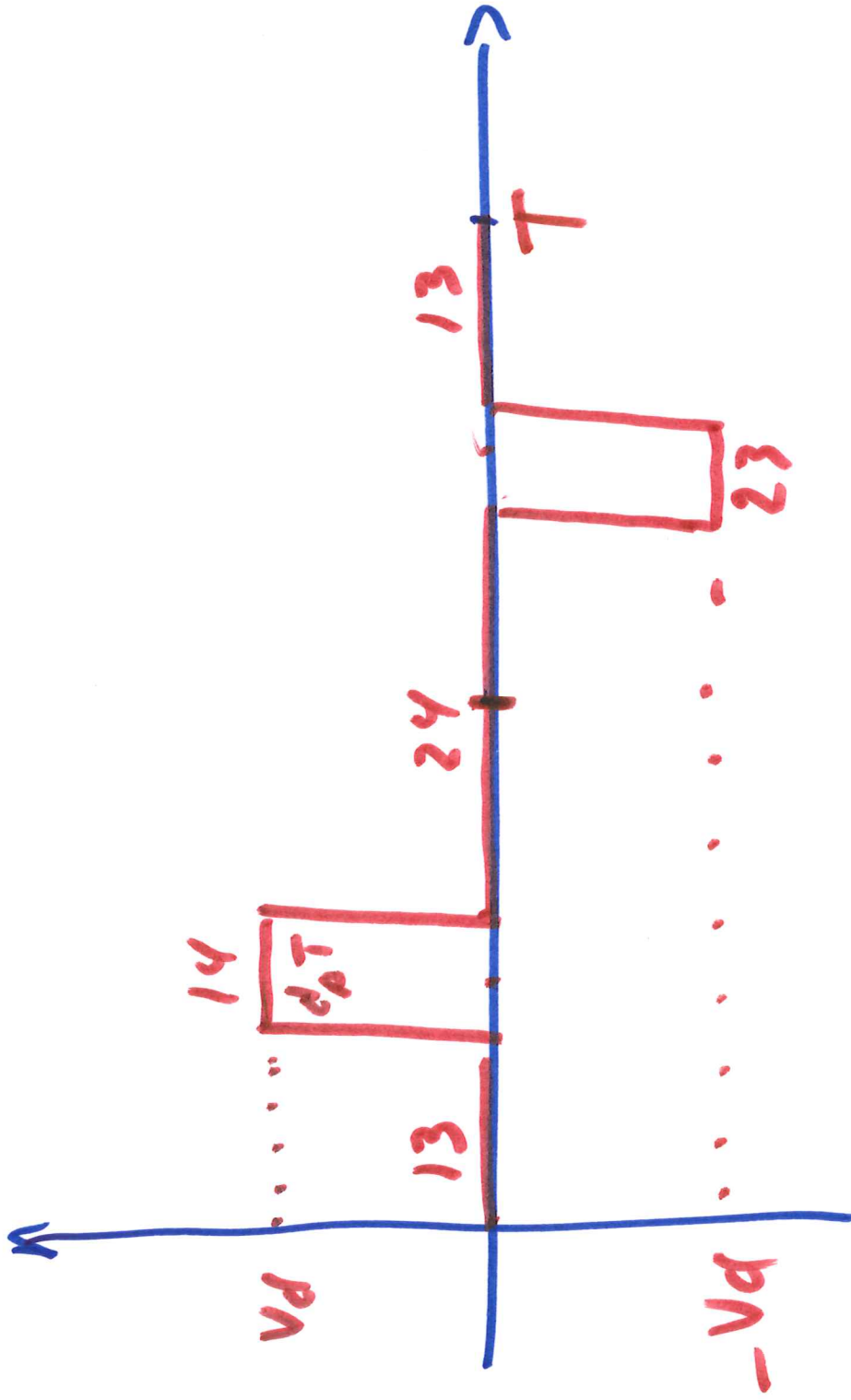

RMS:

$$\sqrt{\frac{1}{T/2} \int_0^{dT} v_d^2 dt + 0}$$

$$\sqrt{\frac{1}{T/2} \int v_d^2 dt}$$


$$\sqrt{2 \text{ clA } v_d^2}$$


$$V_d \sqrt{2dA}$$


$$S = \frac{w_e - w_m}{w_e}$$

LIKES 5 5MACE

$$S_h = \frac{h w_e - w_m}{h w_e}$$

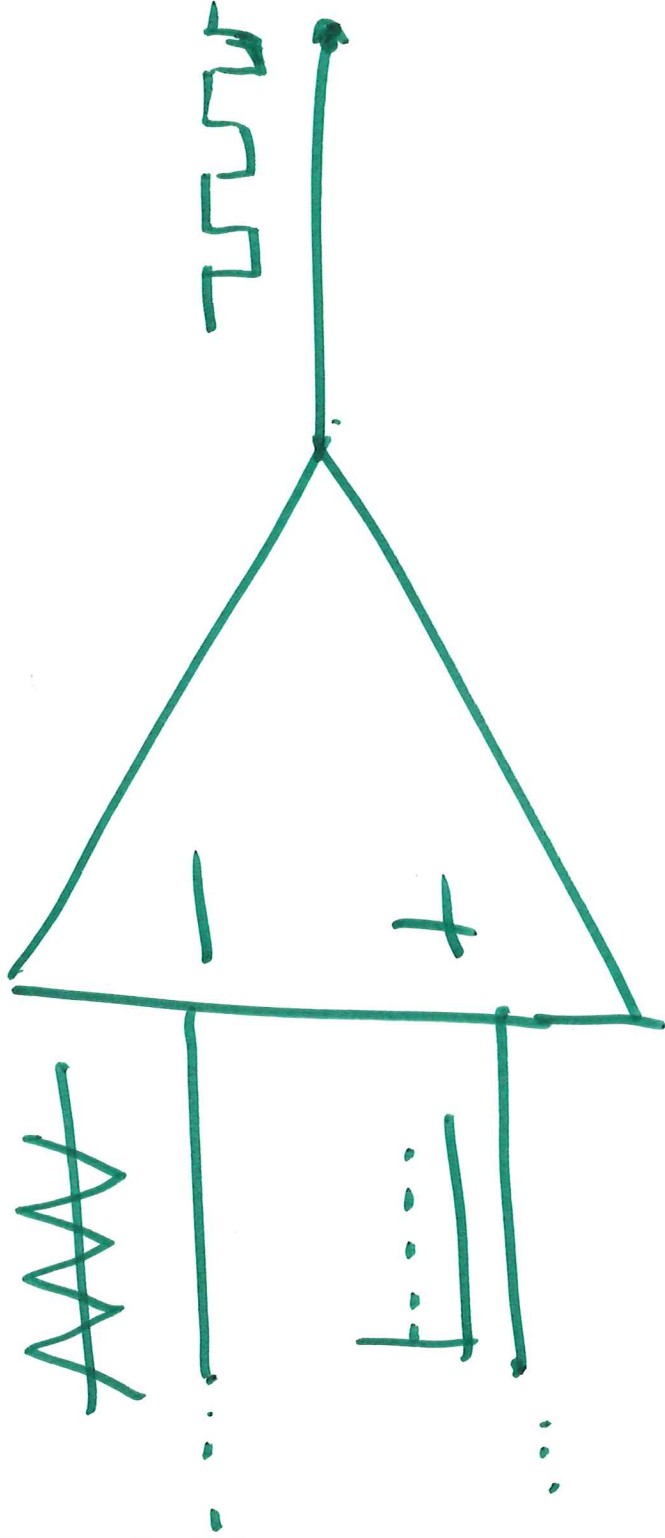

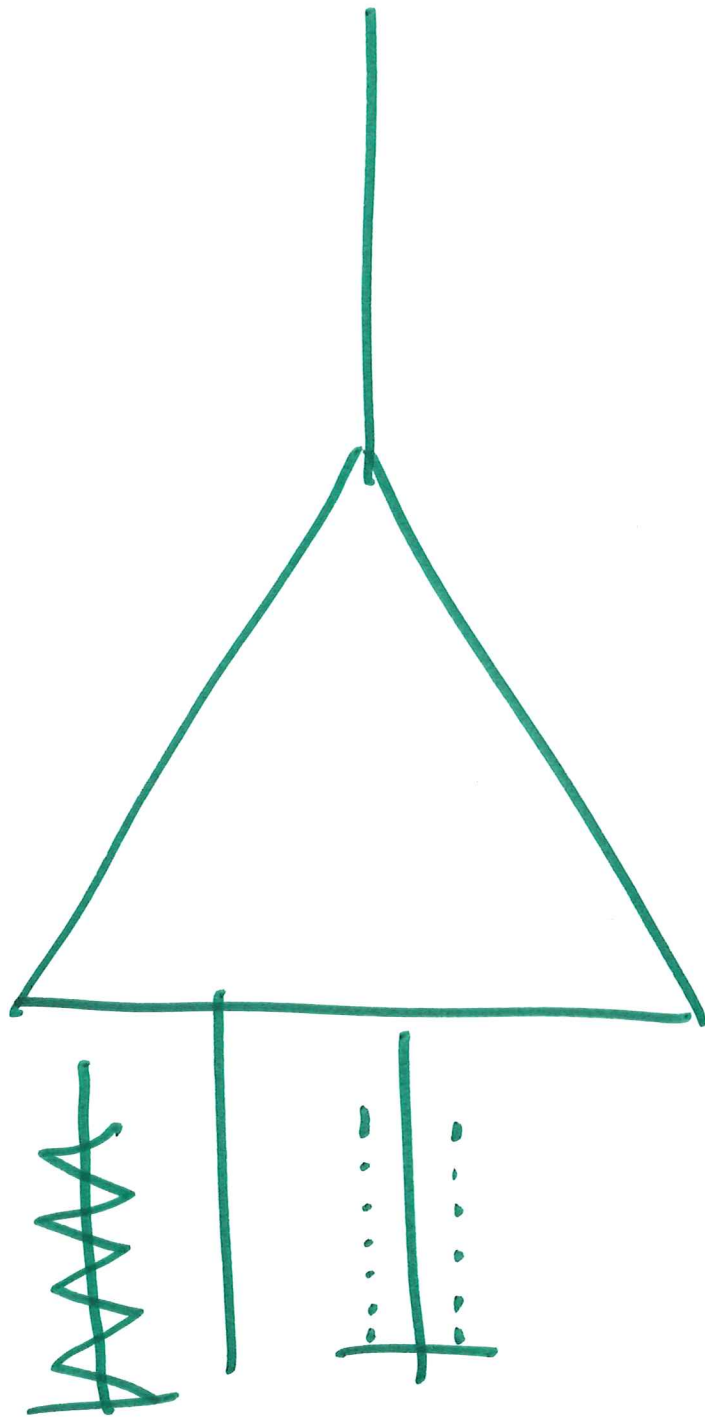

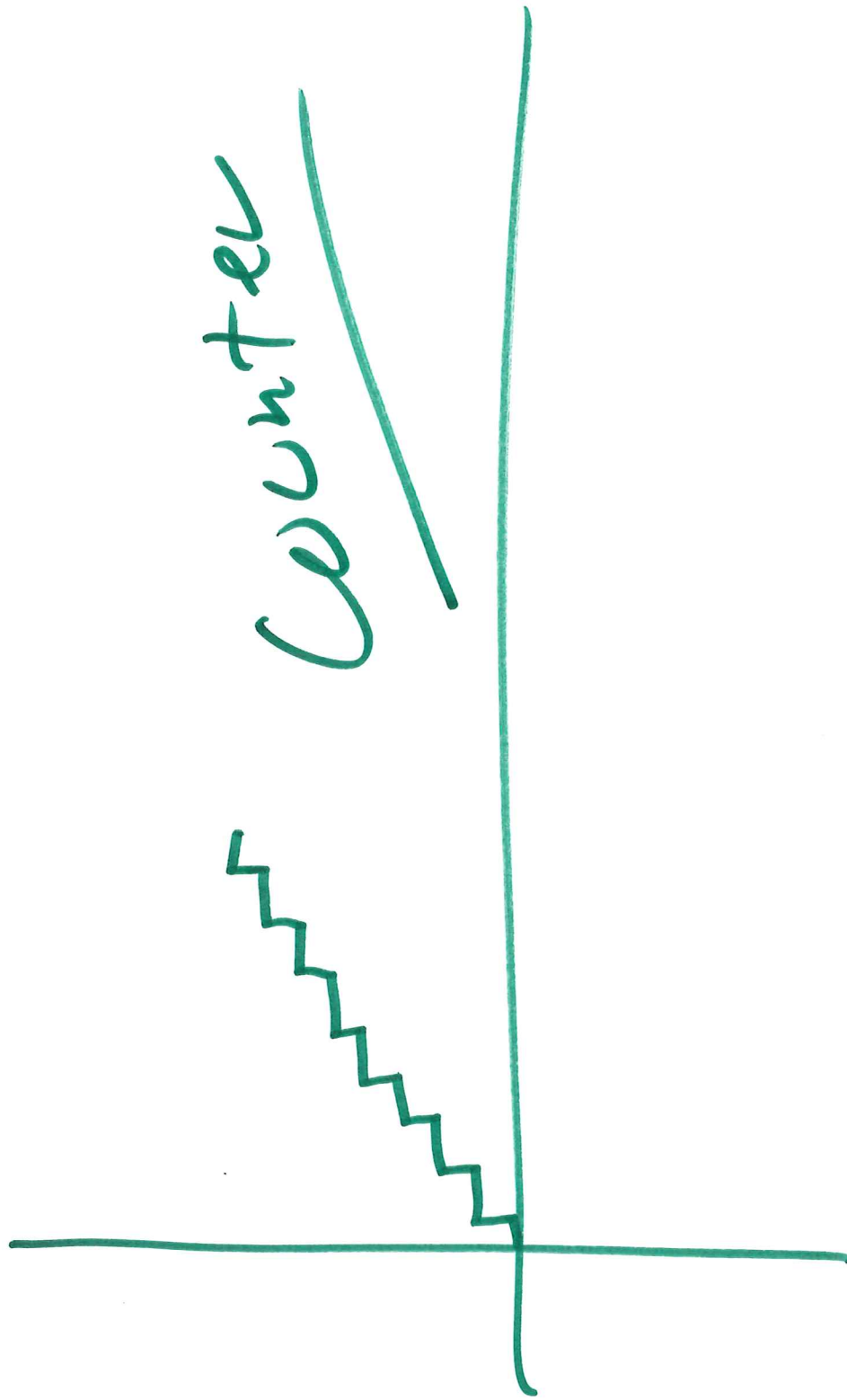

ECE 404 / 504

**T & D Applications of Voltage
Sourced Converters**

Lesson 10

**We can get variable voltage DC
from $-V_d$ to $+V_d$ using two
power poles in a bidirectional
buck converter.**

**We will now get AC using this
same set of ideas.**

Peak value is V_d ; negative peak is $-V_d$.

The rms value is V_d .

The amplitude of the fundamental frequency is $4V_d/\pi$.

What have I been able to do so far?

***Set the frequency**

*** I can get an amplitude; One and only one amplitude so far.**

***Set the phase.**

Let's go back and look at improving this amplitude. I'd like to be able to set it to something I like.

Peak value is V_d ; negative peak is $-V_d$.

The rms value is (depends on duty cycle): $V_d \cdot \sqrt{2 \cdot d_A}$

The amplitude of the fundamental frequency is

(depends on duty cycle). Use an FFT to get the numbers.

What do harmonics do ~~for~~ to us?

***Heat**

***Torques...**

How can we get the ac pulses that we saw?

***Use two levels dc and compare to a triangle wave.**

***Make two buck converter controls and subtract the results.**


Next: Three phase waveforms


Harmonics in an AC Pulse Width Modulated Waveform: FFT Example

$d_A := 0.8$ $NN := 10$ $pts := 2^{NN}$ $i := 0, 1 .. pts - 1$

$$v_{p_i} := \begin{cases} 1 & \text{if } \frac{1 - \frac{d_A}{2}}{4} \cdot pts \leq i < \left(\frac{1 + \frac{d_A}{2}}{4} \right) \cdot pts \\ (-1) & \text{if } \frac{3 - \frac{d_A}{2}}{4} \cdot pts \leq i < \frac{3 + \frac{d_A}{2}}{4} \cdot pts \\ 0 & \text{otherwise} \end{cases}$$

$$v_{fft} := \text{fft}(v_p)$$

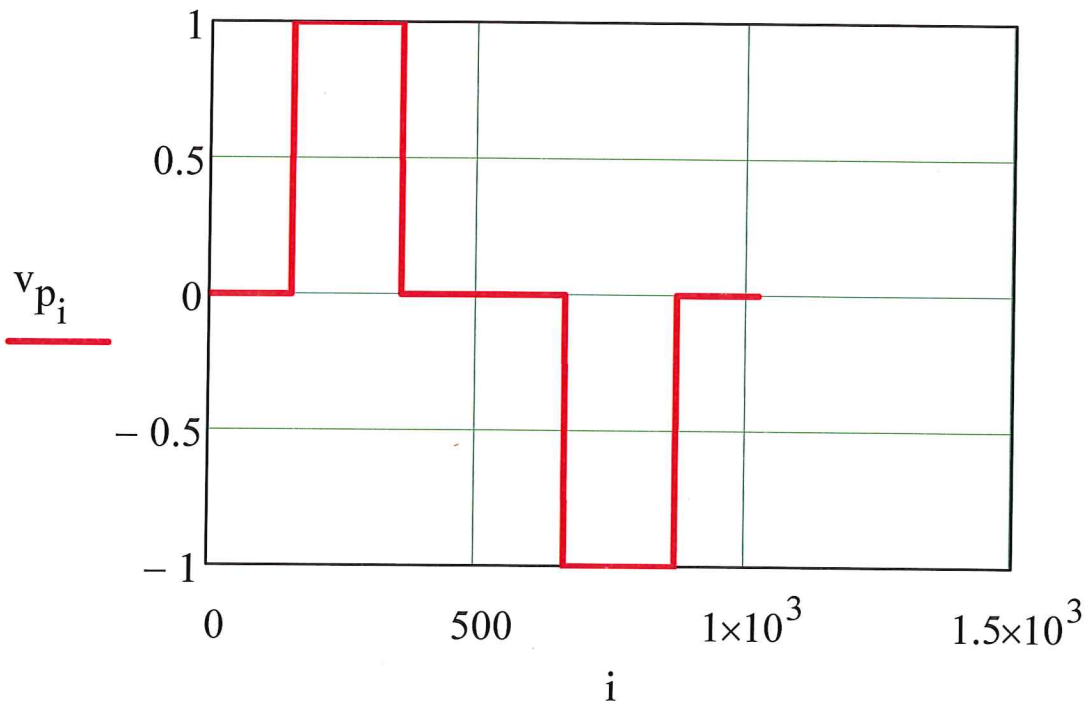

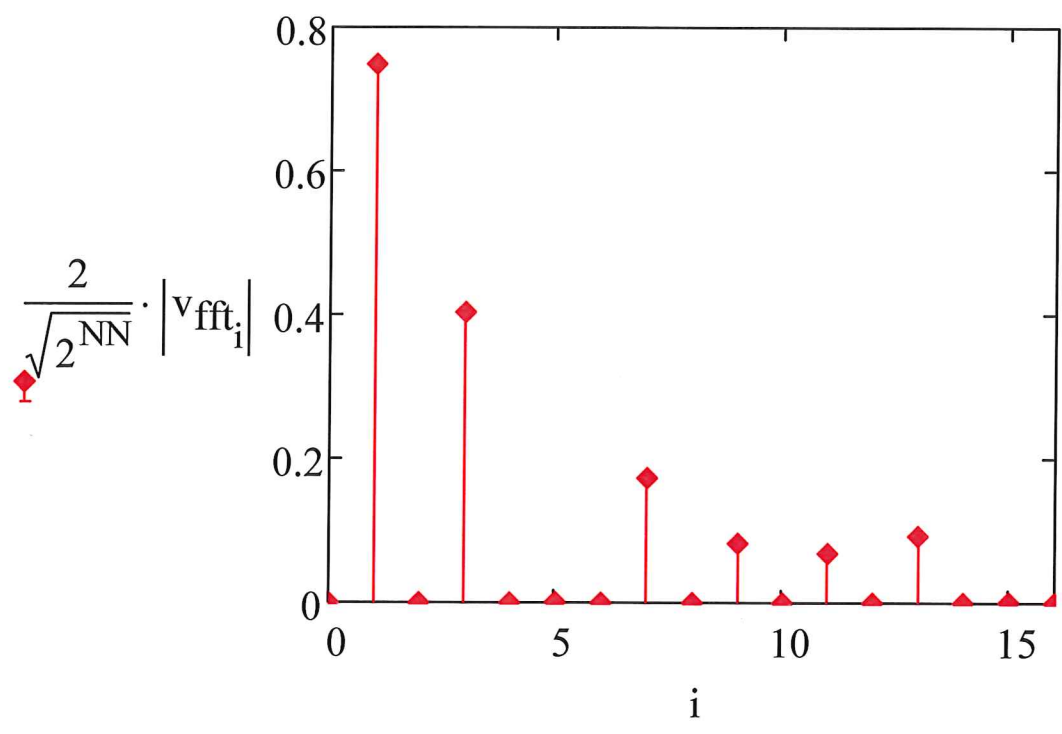


FFT Example


$$d_A := 0.4$$

$$NN := 10 \quad \text{pts} := 2^{NN} \quad i := 0, 1 \dots \text{pts} - 1$$

$$v_{p_i} := \begin{cases} 1 & \text{if } 0 \leq i < d_A \cdot \text{pts} \\ 0 & \text{otherwise} \end{cases}$$

$$v_{\text{fft}} := \text{fft}(v_p)$$

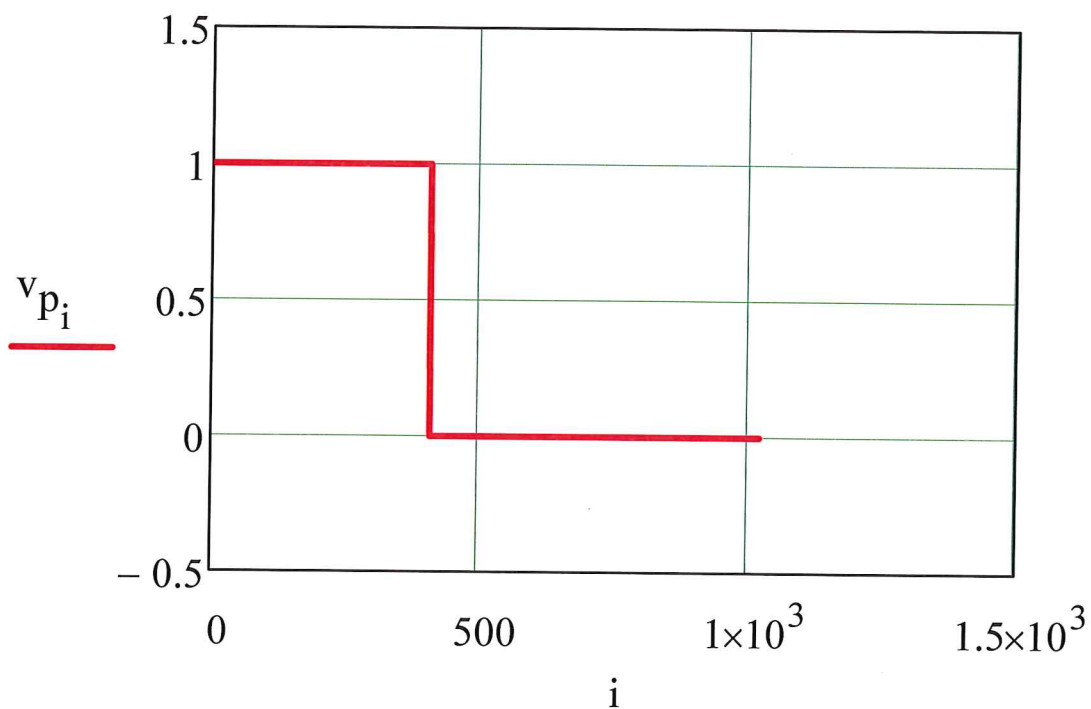

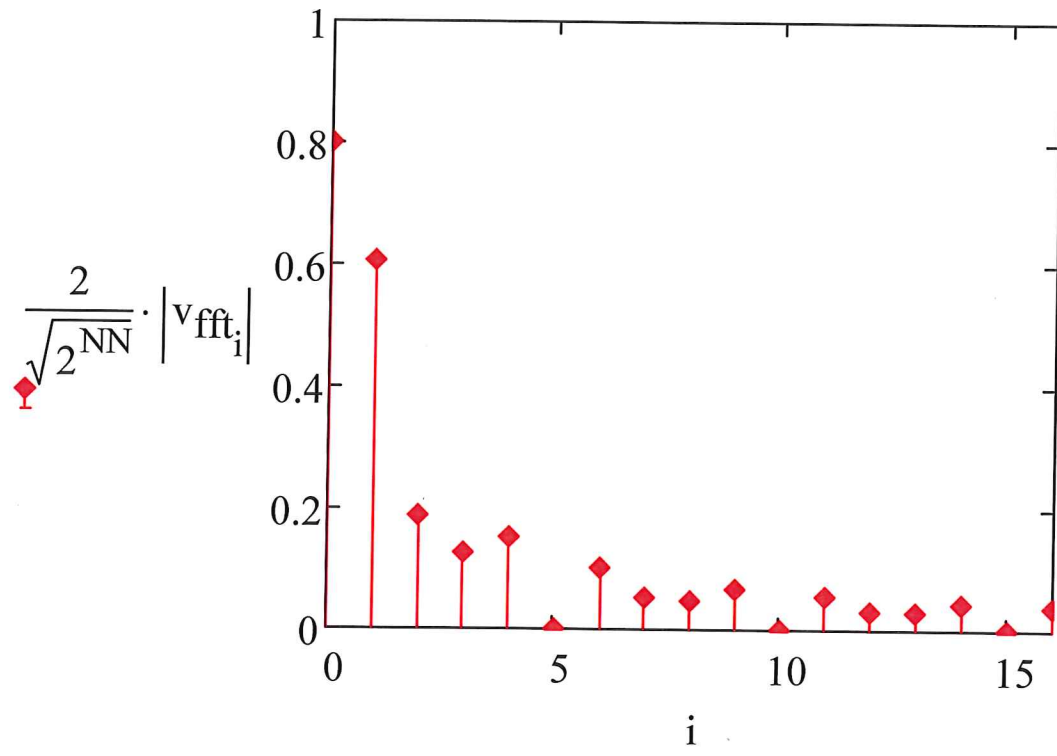

$$v_{\text{fft}_1} = 3.012 + 9.211i$$

$$\left| v_{\text{fft}_1} \right| = 9.691$$

$$\arg(v_{\text{fft}_1}) = 71.895 \cdot \text{deg}$$

$$\frac{\left| v_{\text{fft}_1} \right|}{8} = 1.211$$

$$\frac{4}{\pi} = 1.273$$