

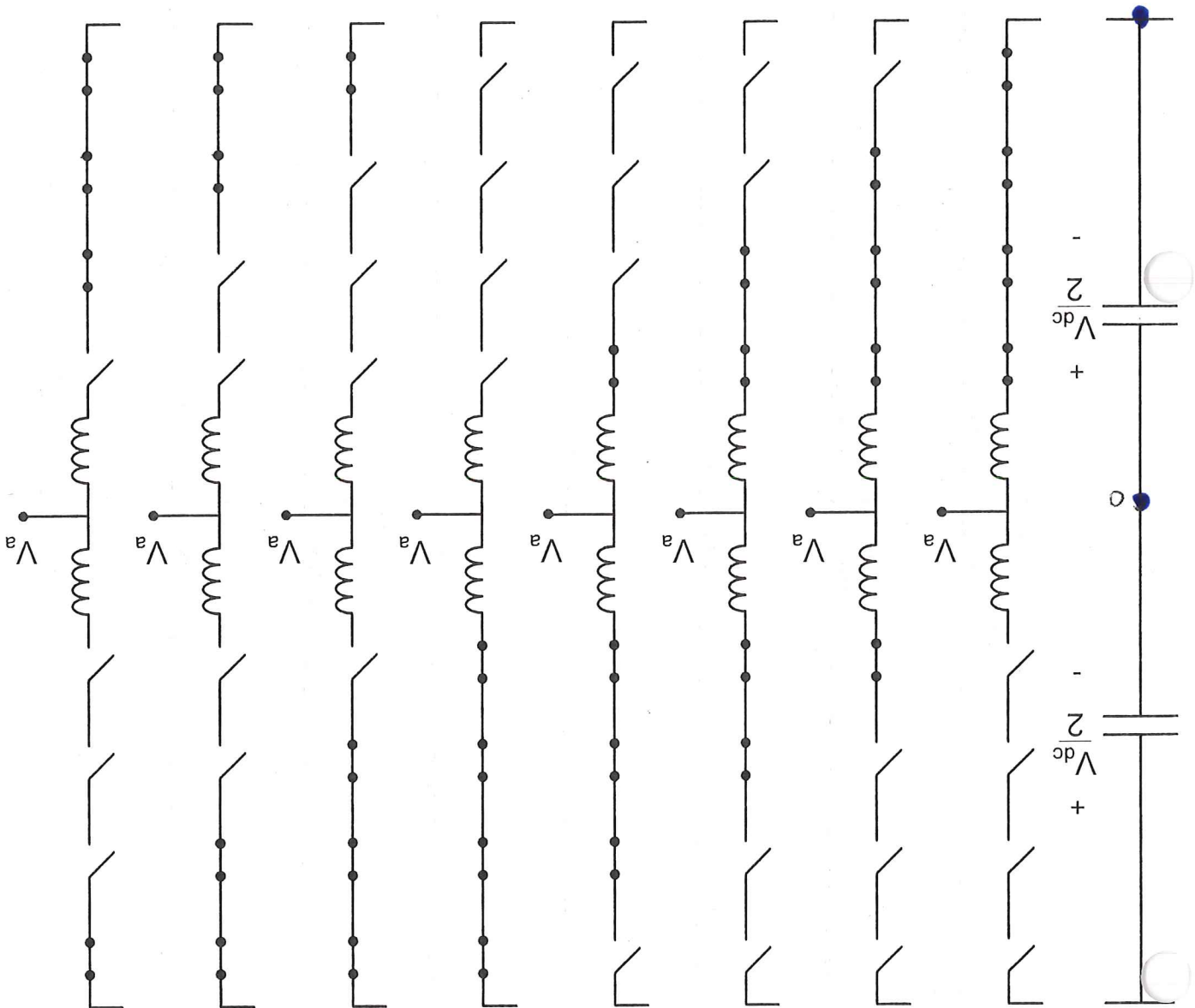


ECE 404-TD / 504-TD


ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS


SESSION no. 18

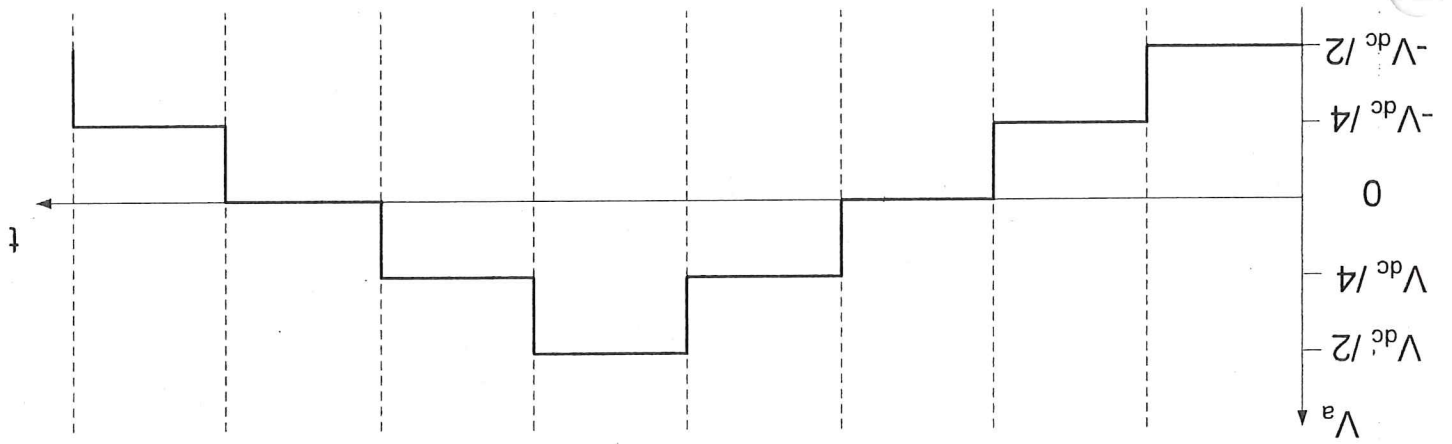

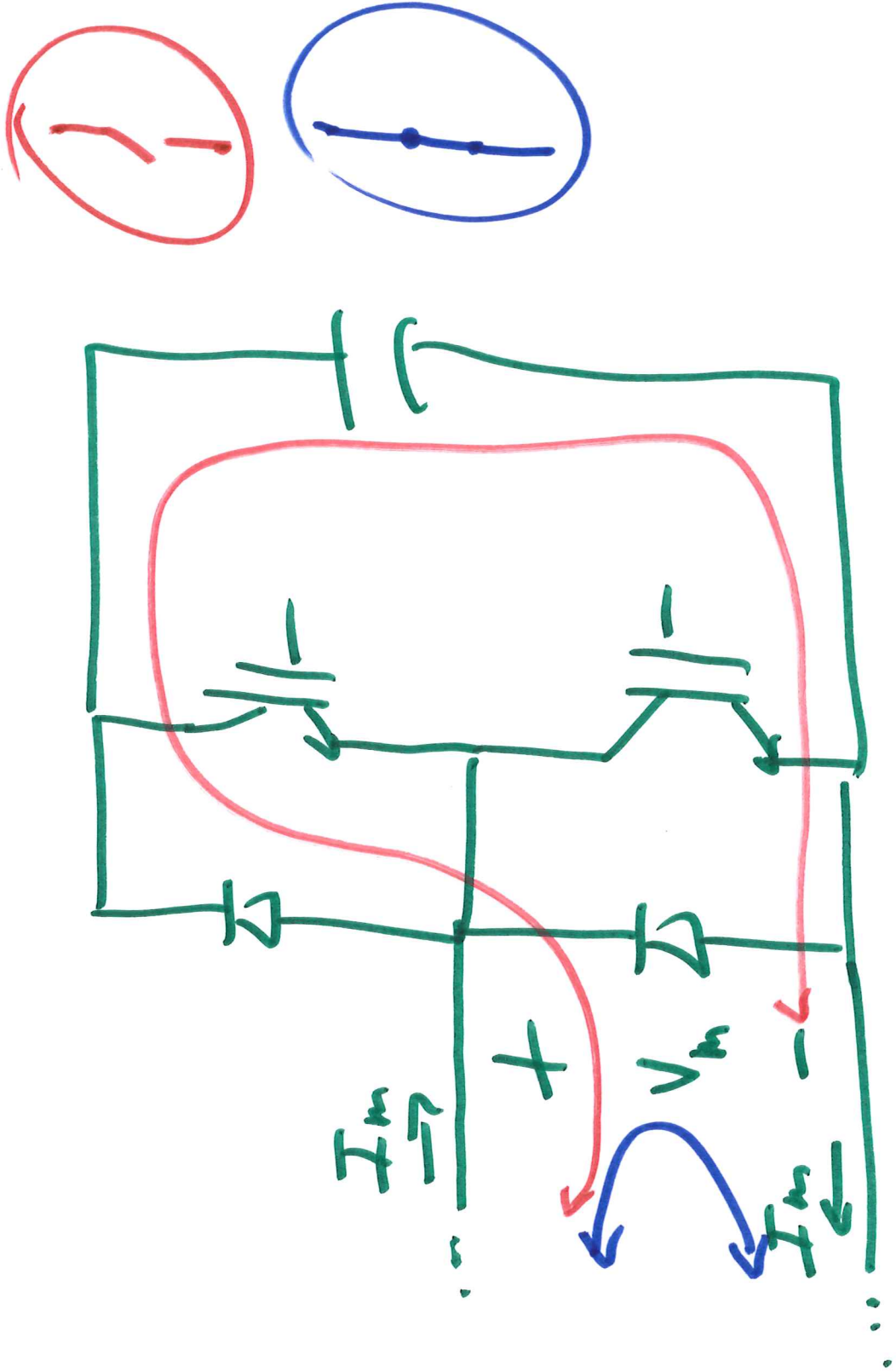

Q = C V

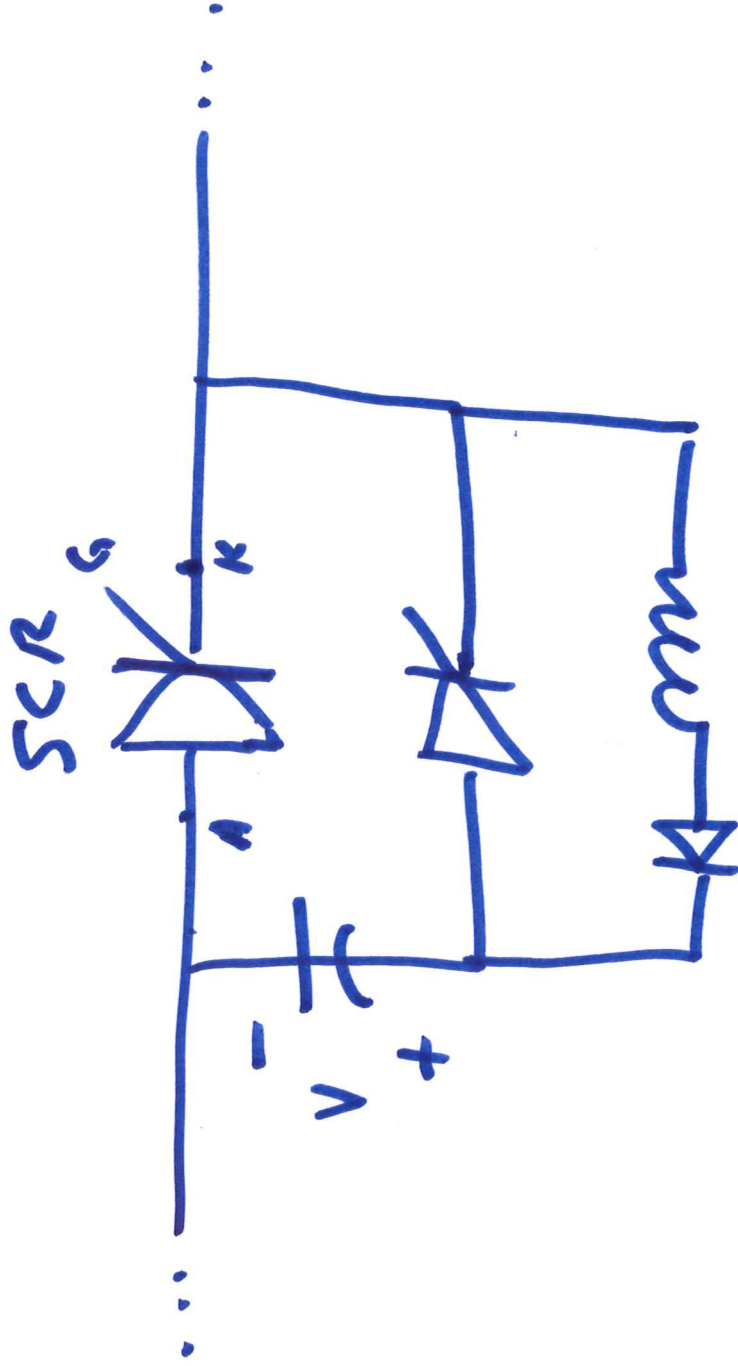

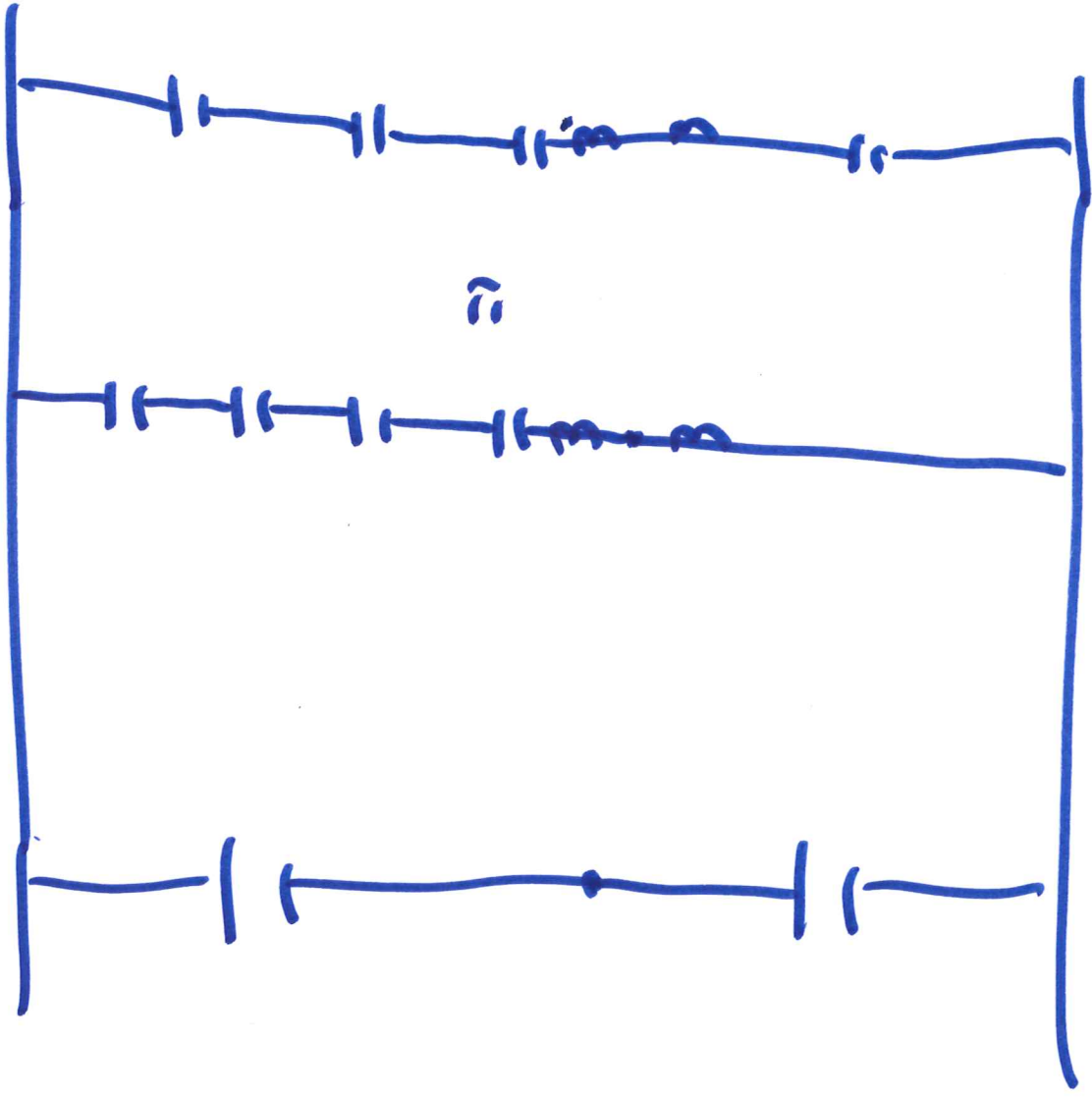

- Modular
- Multilevel
- Converter

Each switch module supports, in this case, $V_{dc}/4$.

Current flows in all switching modules all the time. There is really no such thing as an ON or OFF state here.

Force commutated switching device

Motor drives, power supplies: a switch that turns itself on or off in response to signals/commands.

Force commutated switching device: a switch with circuitry attached to turn it on or off; usually a thyristor (that cannot turn itself off)

The MMC is used to build a stepped voltage. Commercial versions use hundreds of steps. Advantages?

- MUCH higher voltages possible...300 steps, anyone?
- Harmonics? No significant harmonics before 300th?

- Switching frequency? How often does each switch change state? At least once per fundamental frequency cycle.
- Slower switching...what's the advantage? Switching losses!!
 - ☹ More devices
 - ☹ They conduct ALL the time. All of them
- 2-3 level converters have losses of ~2% to 3%; MMC has <1% losses (half bridges; ~1.5% for full bridges) for similarly rated converters, as a practical observation.
- Fault protection? A lot of devices can protect against some pretty severe faults, even those right at the terminals.
- What is the current in each leg of the converter?
- What do the choke coils do for us? They keep the current essentially constant in the short term. They influence the high frequency current harmonics: switching and commutation. Noise and commutation transient reduction, which is periodic and hence harmonic in nature.
- No need for a DC bus capacitor; switching the little capacitors carefully stabilizes the voltage by itself.