

ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS


SESSION no. 20

1. For a four-level NPC converter, find all the available switching states. Let the total dc link voltage be 8.0kV.
 - a. List the switching states in a table showing the voltage across each switch and the components of a space vector representation thereof. You may work in a per unit system of your choice if you prefer.
 - b. Create a plot similar to what was presented in class. Plot all the vectors. Label each vector in the first hexant; that's plenty. You can check your plot using Prof. Corzine's reference.

2. Find and plot one cycle of the dc current that accompanies a three-level space vector PWM that yields a vector of $0.60 V_{dc} \angle 40^\circ$ Volts. The load current is 200 Amps with a power factor of 1.00. A number for V_{dc} is not necessary, but if you want one, make one up and declare it.

3. For a four-level NPC, apply sine-triangle modulation at a 5kHz:50Hz frequency ratio between triangle and sine wave frequencies. Set the sine wave's amplitude at $\frac{3}{4}$ of the sum of the applied triangle wave. Let the dc link voltage be 8kV.
 - a. Plot the triangle waves superimposed on a three phase sine wave.
 - b. Show one (sine) cycle of the resulting pulse width modulation.
 - c. Show a harmonic spectrum that reveals at least the first half dozen nonzero voltage harmonics.

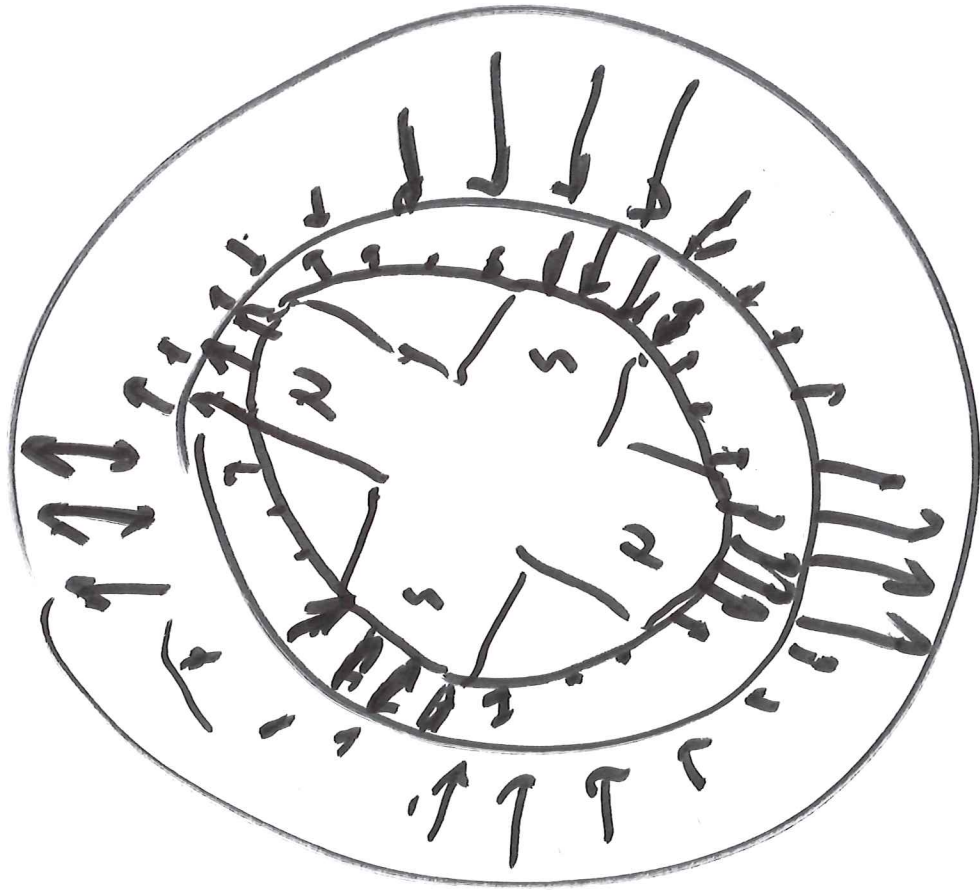4. For a Multimodal Multilevel Converter (MMC) with four-modules in each leg and balanced capacitor voltages of 2kV for each switch and diode,
 - a. Determine the voltage stair step waveform with the ~~same switching losses as the NPC converter of problem 3.~~ **2kV / switch.** Use a fundamental output frequency of 50 Hertz.
 - b. Identify the fundamental and lowest nonzero harmonic output line-to-neutral voltage, magnitude and frequency. Assume the inductors have no voltage drop.
 - c. For a machine load that is modeled as a 50 Hz voltage source of the same amplitude as the fundamental component of the terminal voltage, but lagging three degrees, behind a reactance of 0.35 Ohms at 50 Hz, find the fundamental current and the lowest nonzero current harmonic, magnitude and frequency.





$$s = \text{slip} = \frac{\omega_s - \omega_m}{\omega_s}$$

ECE 404 / 504

**T & D Applications of Voltage
Sourced Converters**

Lesson 20

**NO CLASS Lesson 24; Exam
compensatory time**

Induction Machine...

**2 complete three phase sets of
windings give us 4 poles**

Squirrel cage

Wound rotor

Advantages

- **Ruggedness**
- **Variable speed**
- **Maintenance**
- **Efficiency**
- **Low speed performance**
- **Size and weight**
- **Protection**

Specific advantages:

- **A stable, useful performance AS A GENERATOR with a slight overspeed**
- **Ability to use both stator and rotor as higher bandwidth ports for control, energy I/O, and protection.**

Induction Motor Example

$$j := \sqrt{-1}$$

$$R_1 := 0.02 \quad R_2 := 0.025$$

$$\text{lagging} := 1$$

$$X_1 := 0.06 \quad X_2 := 0.04 \quad X_m := 3.5$$

$$V_1 := 1.00 \quad \omega_s := 1.00$$

Find current input.

$$s := 0.025$$

$$\frac{V_m - V_1}{R_1 + j \cdot X_1} + \frac{V_m}{j \cdot X_m} + \frac{V_m}{\frac{R_2}{s} + j \cdot X_2} = 0$$

This V_m is the air gap voltage.

$$V_m := \frac{\left(\frac{V_1}{R_1 + j \cdot X_1} \right)}{\frac{1}{R_1 + j \cdot X_1} + \frac{1}{j \cdot X_m} + \frac{R_2}{s} + j \cdot X_2} = 0.964 - 0.051i$$

Input Current is

$$I_1 := \frac{V_1 - V_m}{R_1 + j \cdot X_1} = 0.951 - 0.288i \quad |I_1| = 0.994$$
$$\arg(I_1) = -16.852 \cdot \text{deg}$$

Find torque.

$$I_2 := \frac{V_m}{\frac{R_2}{s} + j \cdot X_2} = 0.96 - 0.09i$$

$$\text{torque} := \frac{(|I_2|)^2 \cdot R_2}{s \cdot \omega_s} = 0.93$$

Power in, power out, and efficiency.

$$P_{\text{in}} := \text{Re}(V_1 \cdot \overline{I_1}) = 0.951$$

$$P_{\text{out}} := (|I_2|)^2 \cdot R_2 \cdot \frac{(1-s)}{s} = 0.907$$

$$\eta := \frac{P_{\text{out}}}{P_{\text{in}}} = 95.3\%$$

Power Factor

$$\text{pf} := \frac{P_{\text{in}}}{|V_1| \cdot |\overline{I_1}|} = 0.957 \cdot \text{lagging}$$


Now let's generalize the equations over a range of slip or rotor speed.

$$\underline{V}_m(\text{slip}) := \frac{\left(\frac{V_1}{R_1 + j \cdot X_1} \right)}{\frac{1}{R_1 + j \cdot X_1} + \frac{1}{j \cdot X_m} + \frac{1}{\frac{R_2}{\text{slip}} + j \cdot X_2}}$$


$$\underline{I}_1(\text{slip}) := \frac{V_1 - V_m(\text{slip})}{R_1 + j \cdot X_1}$$

$$\omega(\text{slip}) := \omega_s \cdot (1 - \text{slip}) \quad \text{Rotor Speed}$$

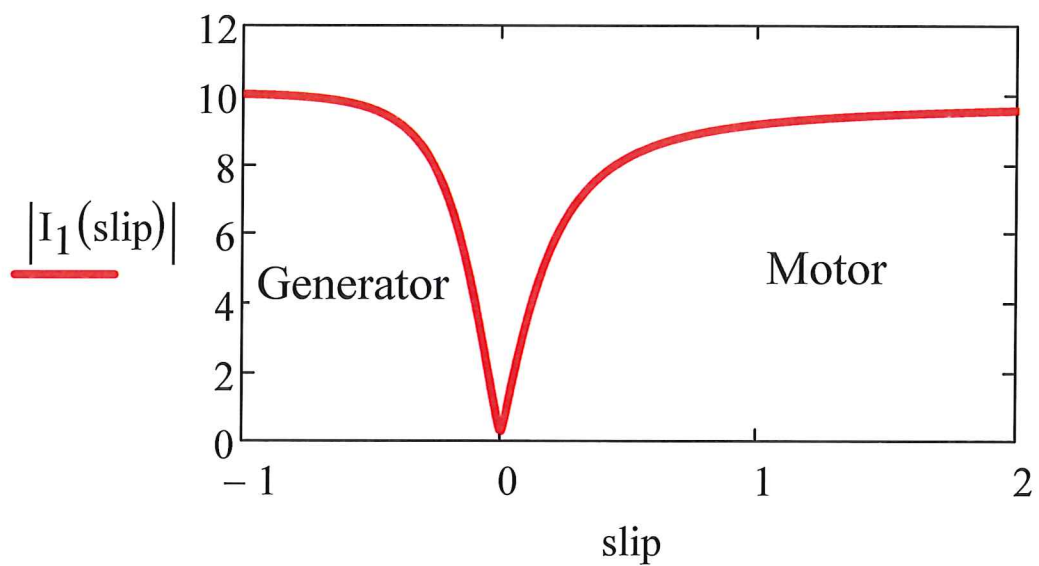Find current input for a range of slip...




...and rotor speed

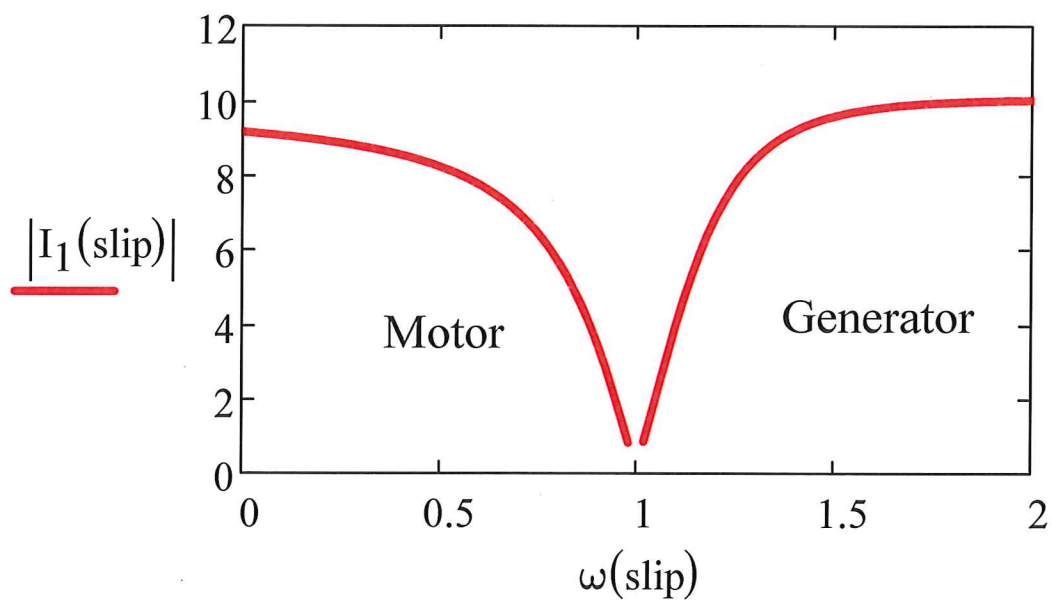

torque

$$\underline{I_2}(\text{slip}) := \frac{V_m(\text{slip})}{\frac{R_2}{\text{slip}} + j \cdot X_2}$$

$$\text{torque}(\text{slip}) := \frac{(|I_2(\text{slip})|)^2 \cdot R_2}{\text{slip} \cdot \omega_s}$$

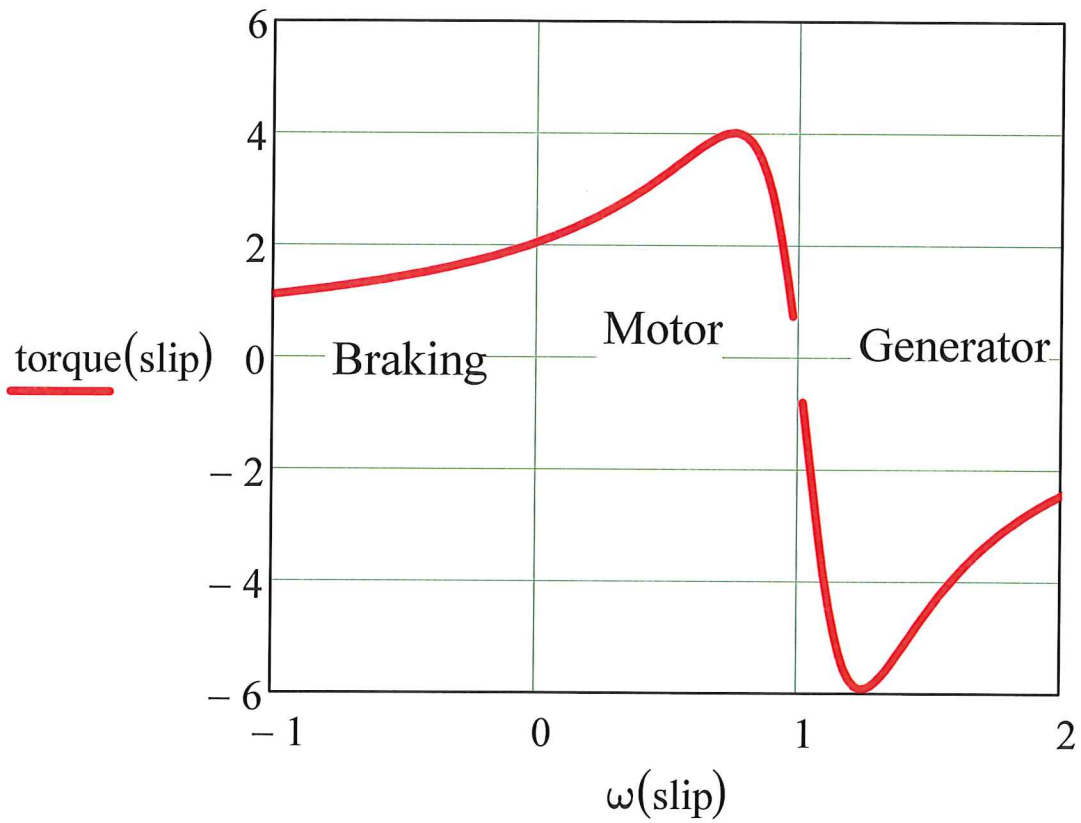


Power in, power out, and efficiency

$$P_{\text{in}}(\text{slip}) := \operatorname{Re}\left(V_1 \cdot \overline{I_1(\text{slip})}\right)$$

$$P_{\text{out}}(\text{slip}) := \left(|I_2(\text{slip})|\right)^2 \cdot R_2 \cdot \frac{(1 - \text{slip})}{\text{slip}}$$
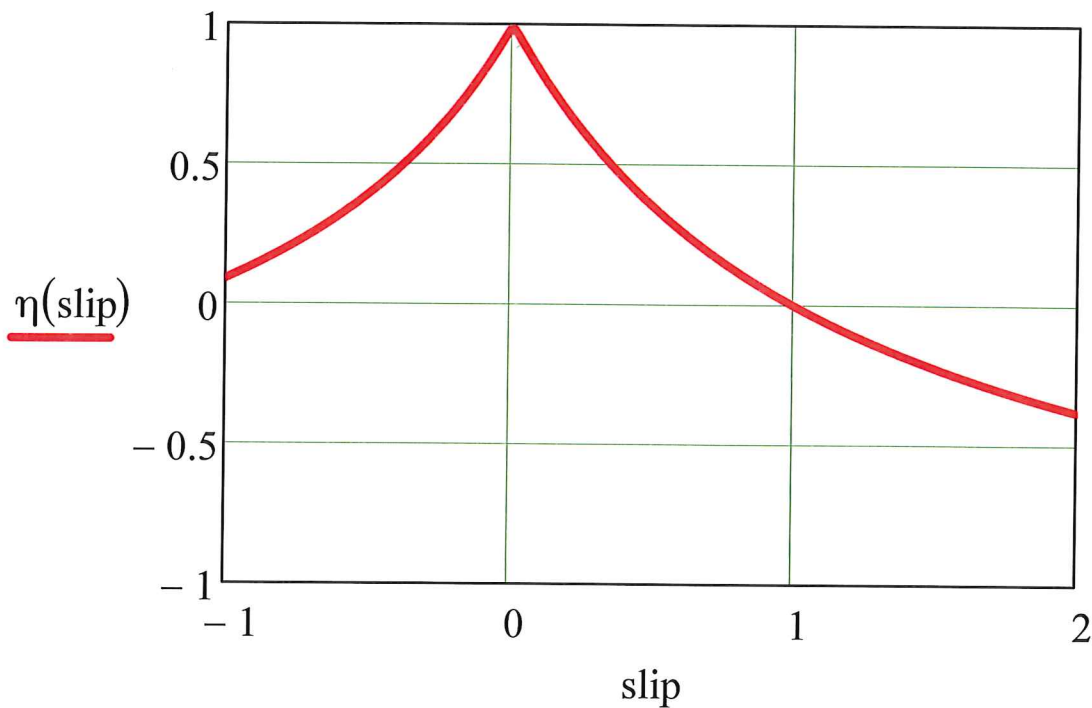
$$\eta(\text{slip}) := \begin{cases} \frac{P_{\text{out}}(\text{slip})}{P_{\text{in}}(\text{slip})} & \text{if } \text{slip} > 0 \\ \frac{P_{\text{in}}(\text{slip})}{P_{\text{out}}(\text{slip})} & \text{if } \text{slip} < 0 \end{cases}$$



Power factor

$$\text{pf}(\text{slip}) := \frac{|P_{\text{in}}(\text{slip})|}{|V_1| \cdot |I_1(\text{slip})|}$$

