

ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS

SESSION no. 23

$$R_{PS} = 0.48$$
$$\frac{dc}{dW}$$


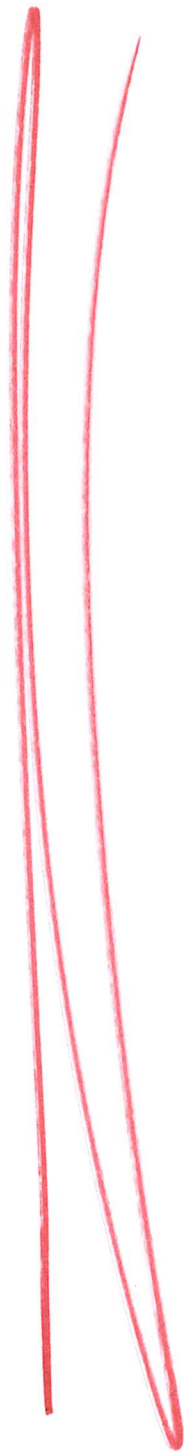
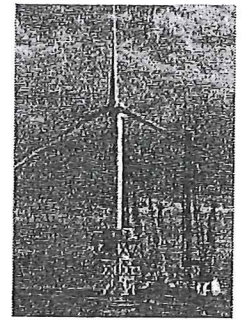
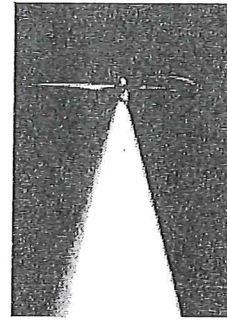


Table 1-10. Examples of commercial DFIG WECS

Parameter	Model		
	Nordex N100	Vestas V90	Repower 5M
Power rating	2.5 MW	3 MW	5 MW
Turbine diameter	100 m	90 m	126 m
Turbine speed	9.6 ~ 14.9 rpm	8.6 ~ 18.4 rpm	7.7 ~ 12.1 rpm
Wind speed (cut-in/rated/cut-out)	3/13/20 m/s	3.5/15/25 m/s	3.5/14/25 m/s
Generator	6-pole WRIG	4-pole WRIG	6-pole WRIG
Gearbox	Planetary/spur stages	Planetary/helical stages	Planetary/spur stages
Pitch/stall mechanism	Pitch	Pitch	Pitch

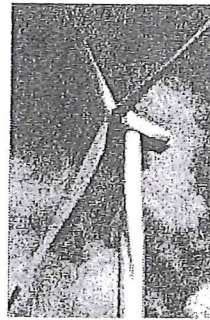

Photos courtesy (from left to right) Nordex, Vestas Wind Systems A/S, and REpower Systems AG.

1.4 WIND ENERGY CONVERSION SYSTEM CONFIGURATIONS


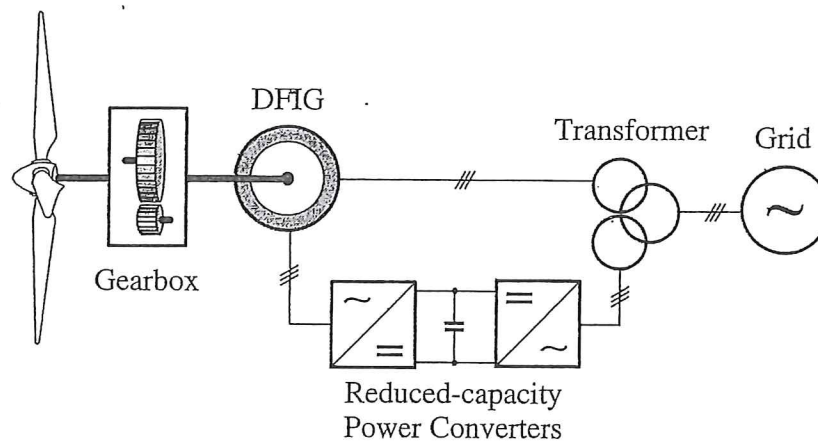


Figure 1-13. Variable-speed configuration with reduced-capacity converters.

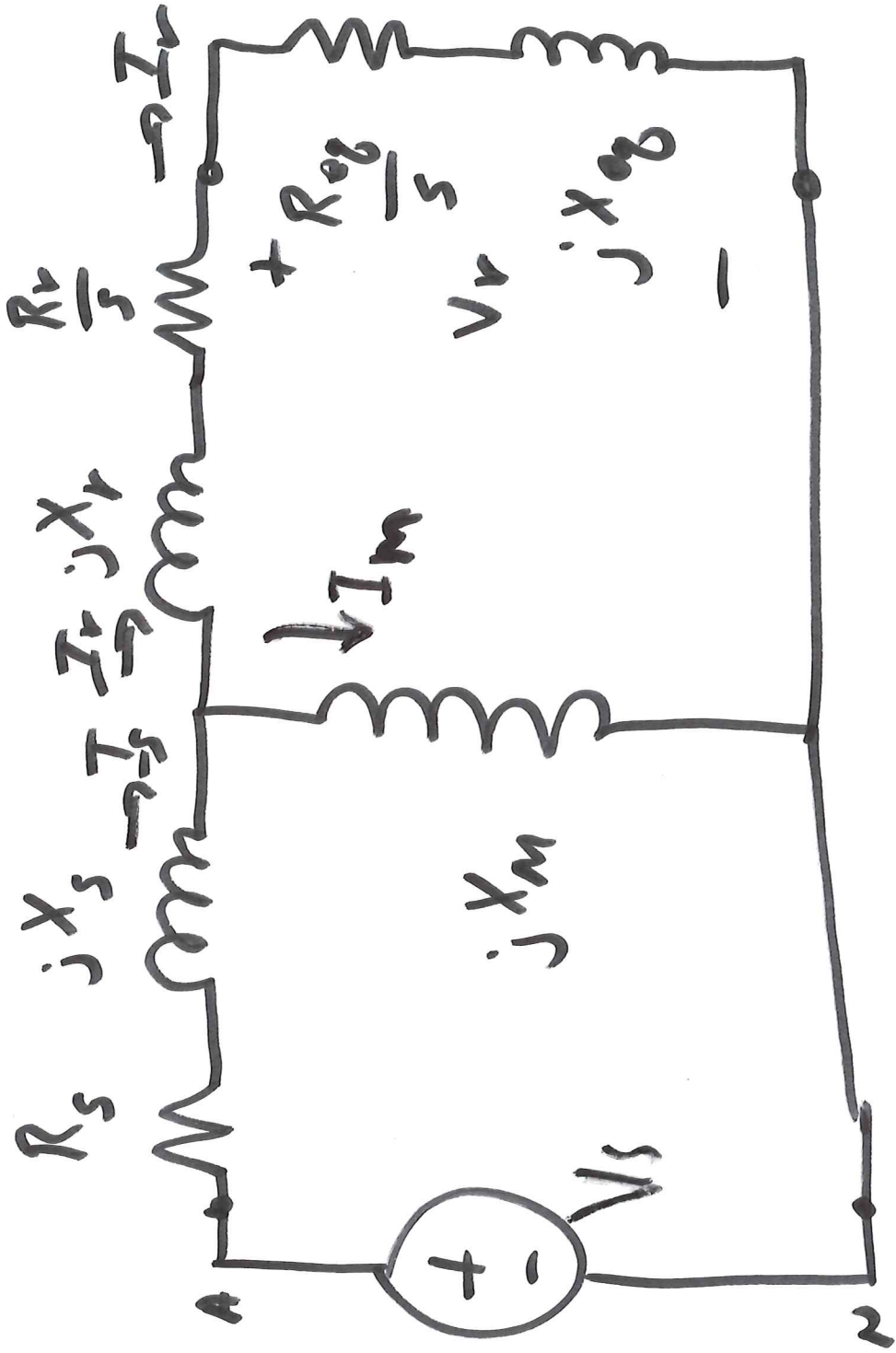

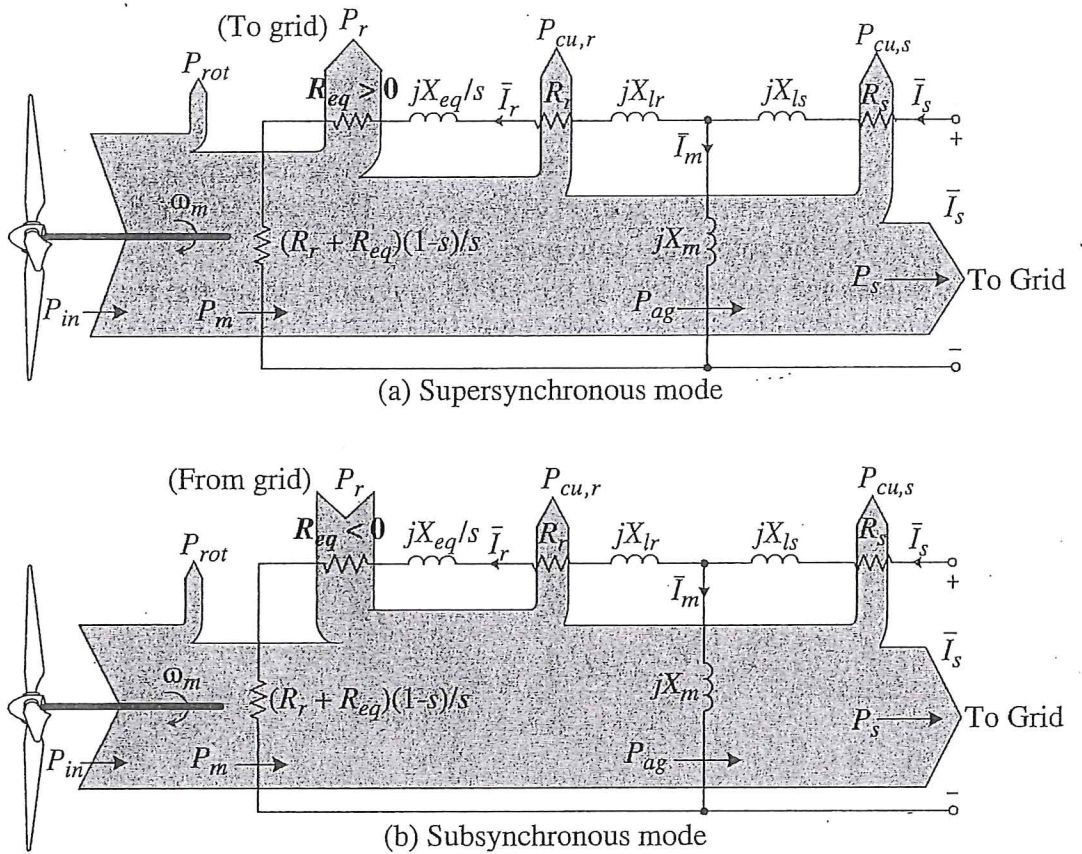


Figure 8-9. Power flow of DFIG with rotor-side converter represented by R_{eq} and X_{eq} .

$$S = \frac{W_s - W_m}{W_s}$$

$$S W_s = W_s - \omega_m$$

~

~

~

slip
discs

SYNCH

MECH

freq
(rotor freq)

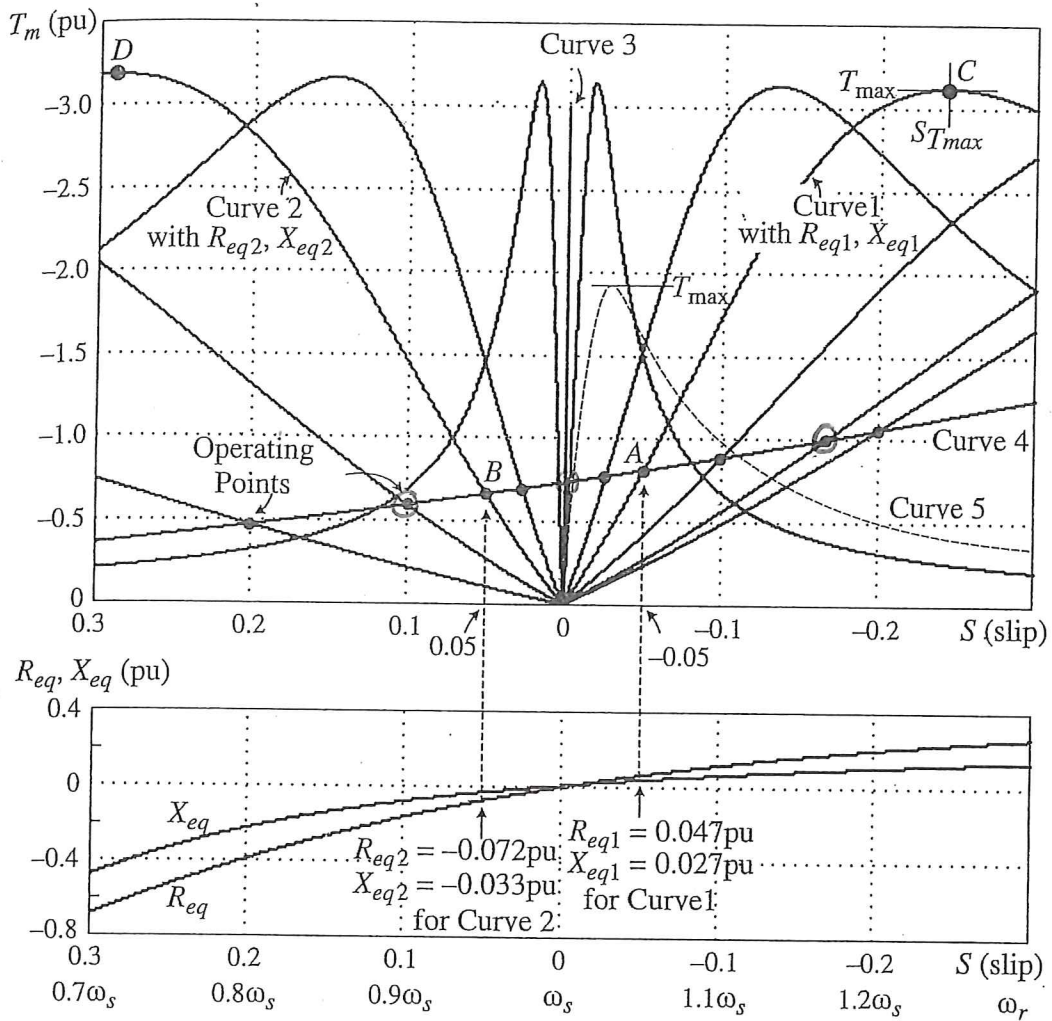


Figure 8-6. Torque-slip characteristics of DFIG wind energy system ($PF_s = 1$).

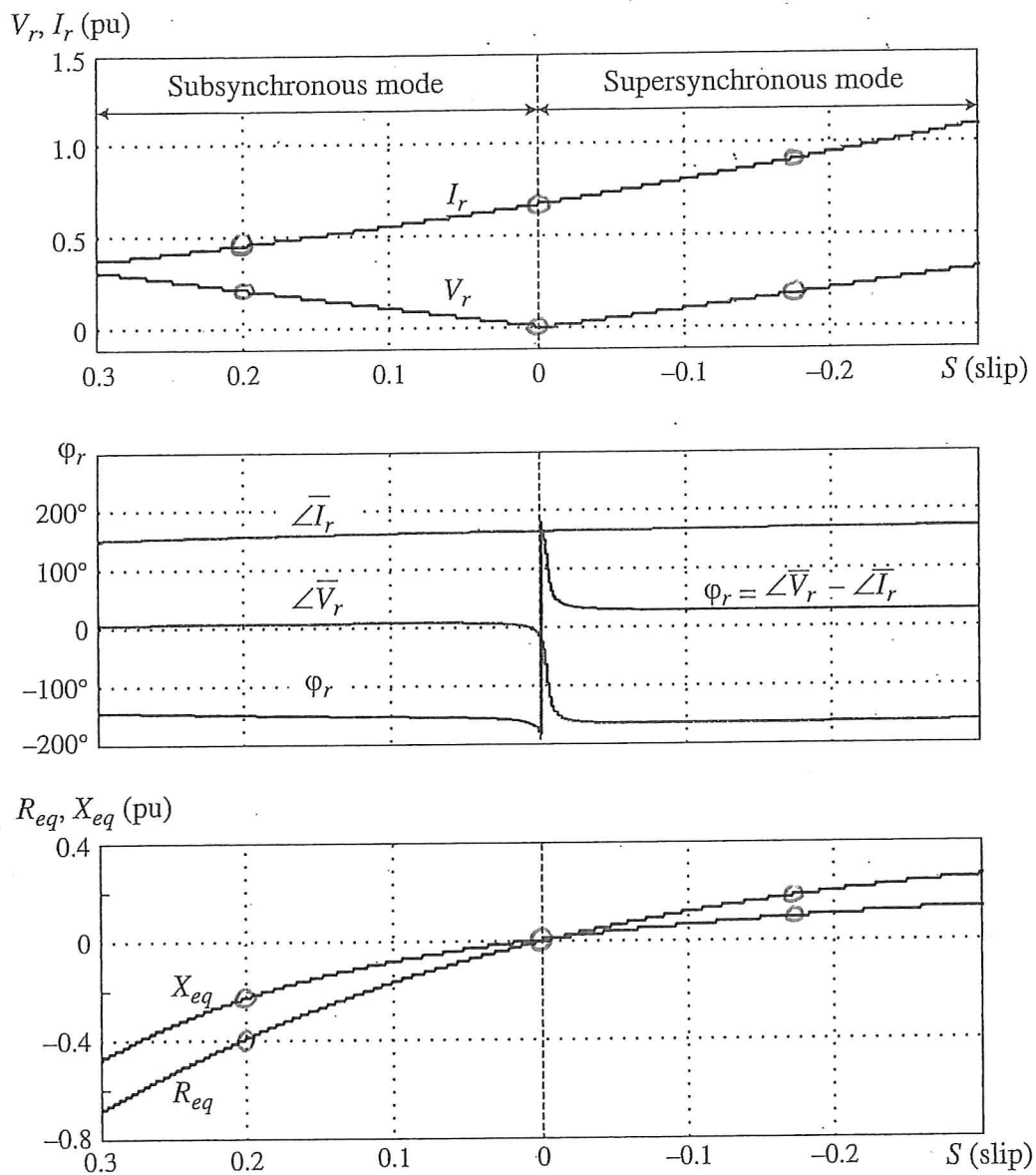


Figure 8-5. Rotor-side converter equivalent impedance ($PF_s = 1$).

Doubly Fed Induction Motor Example

Supersynchronous speed

$$j := \sqrt{-1} \quad m\Omega := 10^{-3} \cdot \Omega$$

Given parameters

$$R_s := 2.65 \cdot m\Omega \quad R_r := 2.63 \cdot m\Omega \quad L_{ls} := 168.7 \cdot \mu H \quad L_{lr} := 133.7 \cdot \mu H \quad L_m := 5.4749 \cdot mH \quad \text{poles} := 4$$

Given operating conditions

$$V_s := \frac{690}{\sqrt{3}} \cdot V \quad T_m := -8185.1 \cdot N \cdot m \quad \omega_s := 2 \cdot \pi \cdot 50 \cdot \frac{\text{rad}}{\text{sec}} \quad \omega_m := \frac{\text{poles}}{2} \cdot 1750 \cdot \frac{\pi}{30} \cdot \frac{\text{rad}}{\text{sec}} = 366.519 \frac{\text{rad}}{\text{sec}}$$

$$\text{pf} := 1.00$$

$$s_w := \frac{\omega_s - \omega_m}{\omega_s} = -0.167$$

From these parameters and operating conditions, calculate the equivalent circuit quantities.

$$I_s := \frac{V_s - \sqrt{V_s^2 - \frac{8 \cdot R_s \cdot T_m \cdot \omega_s}{3 \cdot \text{poles}}}}{2 \cdot R_s} = -1068.2 \text{ A} \quad \theta := \arccos(\text{pf}) = 0 \text{ deg} \quad I_{\text{ref}} := I_s \cdot e^{-j \cdot \theta}$$

$$V_m := V_s - I_s \cdot (R_s + j \cdot \omega_s \cdot L_{ls}) = (401.202 + 56.614i) \text{ V} \quad |V_m| = 405.177 \text{ V} \quad \arg(V_m) = 8.032 \text{ deg}$$

$$I_m := \frac{V_m}{j \cdot \omega_s \cdot L_m} = (32.915 - 233.259i) \text{ A}$$

$$I_r := I_s - I_m = (-1.101 \times 10^3 + 233.259i) \text{ A} \quad |I_r| = 1.126 \times 10^3 \text{ A} \quad \arg(I_r) = 168.04 \text{ deg}$$

$$I_{\text{base}} := 1225.1 \cdot \text{A} \quad I_{\text{rr}} := \frac{|I_r|}{I_{\text{base}}} = 0.919$$

$$V_r := s \cdot V_m - I_r \cdot (R_r + j \cdot s \cdot \omega_s \cdot L_{lr}) = (-65.604 - 17.758i) \text{ V} \quad |V_r| = 67.965 \text{ V} \quad \arg(V_r) = -164.854 \text{ deg}$$

$$V_{\text{base}} := 398.4 \cdot \text{V} \quad V_{\text{rr}} := \frac{|V_r|}{V_{\text{base}}} = 0.171$$

$$Z_{\text{eq}} := \frac{V_r}{I_r} = (0.054 + 0.028i) \Omega \quad R_{\text{eq}} := \text{Re}(Z_{\text{eq}}) = 53.751 \text{ m}\Omega \quad X_{\text{eq}} := \text{Im}(Z_{\text{eq}}) = 27.513 \text{ m}\Omega$$

Steady State Analysis. Supersynchronous Operation.

$$\omega_m = 366.519 \frac{\text{rad}}{\text{sec}} \quad |I_r| = 1125.6 \text{ A} \quad \arg(I_r) = 168.04 \text{ deg}$$

Mechanical power to the generator (Negative means power from mechanical to electrical)

$$P_m := 3 \cdot (|I_r|)^2 \cdot (R_{eq} + R_r) \cdot \frac{(1-s)}{s} = -1500 \text{ kW}$$

Power delivered through the rotor and converter (Positive means power from machine to converter)

$$P_r := 3 \cdot (|I_r|)^2 \cdot R_{eq} = 204.29 \text{ kW}$$

Losses (Rotor and Stator)

$$P_{I2Rr} := 3 \cdot (|I_r|)^2 \cdot R_r = 9.996 \text{ kW} \quad P_{I2Rs} := 3 \cdot (|I_s|)^2 \cdot R_s = 9.072 \times 10^3 \text{ W}$$

Power delivered through the stator terminals (Negative means power from machine to grid)

$$P_s := \text{Re}(3 \cdot V_s \cdot \bar{I}_s) = -1.277 \times 10^3 \text{ kW}$$

Power delivered to the grid (stator and rotor components)

$$P_{\text{grid}} := P_s - P_r = -1.481 \times 10^6 \text{ W}$$

Checking losses two ways.

$$P_m - P_{\text{grid}} = -19.067 \text{ kW} \quad P_{I2Rs} + P_{I2Rr} = 19.067 \text{ kW}$$

Energy efficiency steady state

$$\eta := \frac{P_{\text{grid}}}{P_m} = 98.729 \%$$

Synchronous speed

$$j := \sqrt{-1} \quad m\Omega := 10^{-3} \cdot \Omega$$

Given parameters

$$R_s := 2.65 \cdot m\Omega \quad R_r := 2.63 \cdot m\Omega \quad L_{ls} := 168.7 \cdot \mu H \quad L_{lr} := 133.7 \cdot \mu H \quad L_{lm} := 5.4749 \cdot mH \quad poles := 4$$

Given operating conditions

$$V_{ms} := \frac{690}{\sqrt{3}} \cdot V \quad T_{mech} := -6013.5 \cdot N \cdot m \quad \omega_{ms} := 2 \cdot \pi \cdot 50 \cdot \frac{rad}{sec} \quad \omega_{mn} := \omega_s + 10^{-9} \cdot \frac{rad}{sec}$$

$$pf := 1.00$$

$$s := \frac{\omega_s - \omega_m}{\omega_s} = -3.183 \times 10^{-12}$$

$$I_{\theta} := \frac{V_s - \sqrt{V_s^2 - \frac{8 \cdot R_s \cdot T_m \cdot \omega_s}{3 \cdot poles}}}{2 \cdot R_s} = -786.3 \text{ A}$$

$$\theta := \arccos(pf) = 0 \text{ deg}$$

$$I_{\theta} := I_s \cdot e^{-j \cdot \theta}$$

$$V_{mn} := V_s - I_s \cdot (R_s + j \cdot \omega_s \cdot L_{ls}) = (400.455 + 41.671i) \text{ V} \quad |V_m| = 402.618 \text{ V} \quad \arg(V_m) = 5.941 \text{ deg}$$

$$I_{mn} := \frac{V_m}{j \cdot \omega_s \cdot L_m} = (24.228 - 232.824i) \text{ A}$$

$$I_{\omega} := I_s - I_m = (-810.498 + 232.824i) \text{ A}$$

$$|I_r| = 843.276 \text{ A}$$

$$\arg(I_r) = 163.973 \text{ deg}$$

$$I_{base} := 1225.1 \cdot A \quad I_{\omega} := \frac{|I_r|}{I_{base}} = 0.688$$

$$V_{\omega} := s \cdot V_m - I_r \cdot (R_r + j \cdot s \cdot \omega_s \cdot L_{lr}) = (2.132 - 0.612i) \text{ V}$$

$$|V_r| = 2.218 \text{ V} \quad \arg(V_r) = -16.027 \text{ deg}$$

$$Z_{eq} := \frac{V_r}{I_r} = (-2.63 \times 10^{-3} + 7.022i \times 10^{-13}) \Omega$$

$$V_{base} := 398.4 \cdot V$$

$$V_{\omega} := \frac{|V_r|}{V_{base}} = 5.567 \times 10^{-3}$$

$$R_{eq} := \operatorname{Re}(Z_{eq}) = -2.63 \text{ m}\Omega$$

$$X_{eq} := \operatorname{Im}(Z_{eq}) = 7.022 \times 10^{-10} \text{ m}\Omega$$

Steady State Analysis. Synchronous Operation.

$$\omega_m = 314.159 \frac{\text{rad}}{\text{sec}} \quad |I_r| = 843.3 \text{ A} \quad \arg(I_r) = 163.973 \text{ deg}$$

Mechanical power to the generator (Negative means power from mechanical to electrical)

$$P_{\text{mech}} := 3 \cdot (|I_r|)^2 \cdot (R_{\text{eq}} + R_r) \cdot \frac{(1-s)}{s} = -945 \text{ kW}$$

Power delivered through the rotor and converter (Positive means power from machine to converter)

$$P_{\text{mech}} := 3 \cdot (|I_r|)^2 \cdot R_{\text{eq}} = -5.611 \text{ kW}$$

Losses (Rotor and Stator)

$$P_{I_2R_r} := 3 \cdot (|I_r|)^2 \cdot R_r = 5.611 \text{ kW} \quad P_{I_2R_s} := 3 \cdot (|I_s|)^2 \cdot R_s = 4.915 \times 10^3 \text{ W}$$

Power delivered through the stator terminals (Negative means power from machine to grid)

$$P_{\text{mech}} := \text{Re}(3 \cdot V_s \cdot \bar{I}_s) = -939.684 \text{ kW}$$

Power delivered to the grid (stator and rotor components)

$$P_{\text{grid}} := P_s - P_r = -9.341 \times 10^5 \text{ W}$$

Checking losses two ways.

$$P_m - P_{\text{grid}} = -10.526 \text{ kW} \quad P_{I_2R_s} + P_{I_2R_r} = 10.526 \text{ kW}$$

Energy efficiency steady state

$$\eta := \frac{P_{\text{grid}}}{P_m} = 98.886 \%$$

Subsynchronous speed

$$j_w := \sqrt{-1} \quad m\Omega := 10^{-3} \cdot \Omega$$

Given parameters

$$R_{ms} := 2.65 \cdot m\Omega \quad R_{mw} := 2.63 \cdot m\Omega \quad L_{lms} := 168.7 \cdot \mu H \quad L_{lmw} := 133.7 \cdot \mu H \quad L_{mm} := 5.4749 \cdot mH \quad poles := 4$$

Given operating conditions

$$V_{ms} := \frac{690}{\sqrt{3}} \cdot V \quad T_{mm} := -3849 \cdot N \cdot m \quad \omega_{ms} := 2 \cdot \pi \cdot 50 \cdot \frac{rad}{sec} \quad \omega_{mm} := \frac{poles}{2} \cdot 1200 \cdot \frac{\pi}{30} \cdot \frac{rad}{sec} = 251.327 \frac{rad}{sec}$$

$$pf := 1.00$$

$$s := \frac{\omega_s - \omega_m}{\omega_s} = 0.2$$

$$I_{ms} := \frac{V_s - \sqrt{V_s^2 - \frac{8 \cdot R_s \cdot T_m \cdot \omega_s}{3 \cdot poles}}}{2 \cdot R_s} = -504.2 A$$

$$\theta := \arccos(pf) = 0 \text{ deg}$$

$$I_{ms} := I_s \cdot e^{-j \cdot \theta}$$

$$V_{mw} := V_s - I_s \cdot (R_s + j \cdot \omega_s \cdot L_{ls}) = (399.708 + 26.722i) V \quad |V_m| = 400.6 V \quad \arg(V_m) = 3.825 \text{ deg}$$

$$I_{mw} := \frac{V_m}{j \cdot \omega_s \cdot L_m} = (15.536 - 232.39i) A$$

$$I_w := I_s - I_m = (-519.737 + 232.39i) A$$

$$|I_r| = 569.326 A$$

$$\arg(I_r) = 155.909 \text{ deg}$$

$$I_{base} := 1225.1 \cdot A$$

$$I_{mw} := \frac{|I_r|}{I_{base}} = 0.465$$

$$V_{mw} := s \cdot V_m - I_r \cdot (R_r + j \cdot s \cdot \omega_s \cdot L_{lr}) = (83.261 + 9.099i) V \quad |V_r| = 83.756 V \quad \arg(V_r) = 6.237 \text{ deg}$$

$$V_{base} := 398.4 \cdot V$$

$$V_{mw} := \frac{|V_r|}{V_{base}} = 0.21$$

$$Z_{eq} := \frac{V_r}{I_r} = (-0.127 - 0.074i) \Omega$$

$$R_{eq} := \operatorname{Re}(Z_{eq}) = -126.983 \text{ m}\Omega \quad X_{eq} := \operatorname{Im}(Z_{eq}) = -74.285 \text{ m}\Omega$$

Steady State Analysis. Subsynchronous Operation.

$$\omega_m = 251.327 \frac{\text{rad}}{\text{sec}} \quad |I_r| = 569.3 \text{ A} \quad \arg(I_r) = 155.909 \text{ deg}$$

Mechanical power to the generator (Negative means power from mechanical to electrical)

$$P_{\text{mech}} := 3 \cdot (|I_r|)^2 \cdot (R_{\text{eq}} + R_r) \cdot \frac{(1-s)}{s} = -484 \text{ kW}$$

Power delivered through the rotor and converter (Positive means power from machine to converter)

$$P_{\text{mech}} := 3 \cdot (|I_r|)^2 \cdot R_{\text{eq}} = -123.477 \text{ kW}$$

Losses (Rotor and Stator)

$$P_{\text{I2Rr}} := 3 \cdot (|I_r|)^2 \cdot R_r = 2.557 \text{ kW} \quad P_{\text{I2Rs}} := 3 \cdot (|I_s|)^2 \cdot R_s = 2.02 \text{ kW}$$

Power delivered through the stator terminals (Negative means power from machine to grid)

$$P_{\text{stator}} := \text{Re}(3 \cdot V_s \cdot \bar{I}_s) = -602.578 \text{ kW}$$

Power delivered to the grid (stator and rotor components)

$$P_{\text{grid}} := P_s - P_r = -479.1 \text{ kW}$$

Checking losses two ways.

$$P_m - P_{\text{grid}} = -4.578 \text{ kW} \quad P_{\text{I2Rs}} + P_{\text{I2Rr}} = 4.578 \text{ kW}$$

Energy efficiency steady state

$$\eta := \frac{P_{\text{grid}}}{P_m} = 99.053 \%$$

ECE 404 / 504

**T & D Applications of Voltage
Sourced Converters**

Lesson 23

**Due: Friday 8 March on
campus; Monday 11 March off
campus Engr Outreach**

Doubly Fed Induction

**Generator : Induction machine
with three phase windings on**

**both stator and rotor; same
number of poles on each;**

**Doubly fed machine has
become popular for wind
turbines; typically 30% or less
of the energy goes through the
variable speed drive**

**Stator: Energy from machine
through transformer to grid**

**Rotor: Energy from machine
through converter and
transformer to grid**

**Power flow: Stator to grid
unidirectional; rotor to grid
bidirectional ; rotor power is
typically <30% of stator power**

SLIP!!

**There is no class on Friday
(next lesson). Compensatory
time for the exam. Engr
Outreach, there will be no
video posted on Friday.**