

ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF  
VOLTAGE SOURCE CONVERTERS

SESSION no. 27

## Simulation studies using Power Converters

- Start Simple

- As develop model do small pieces and test them
- AC System equivalent
  - verify against known conditions

- start out with
  - simple equivalent impedance with voltage sources
  - (not detailed generation)
- compare power flow results
- compare short circuit results

- then start adding more details to controls
- then start adding more

behavioral system

known inputs

inputs w/ time delay

→ Predictions

- open loop controls

model

A - simple, non-swirling

## 2. Power converter model

### B. - Build a switching model of converter

- again open loop
- control with very
- Simple AC/DC systems
- compare to results for non switching converters with same AC/DC system
- switching model needs to reach steady state

- once confident in this model

then

① somewhat more complicated

AC/DC system to match

(a) → added complexity to

(b) one at a time

wire  
non  
switched

Diagram

- Again - match to  
non-switched model

(2) Then add detail to controls


- more detail in
- synchronization
- ~~activation~~
- other control logic
- checks along the way for reasonable performance

(3) Then add more to the AC system - in steps

## Non-switching models of voltage sourced converters

### 1. Fundamental Component model

→ 3Ø bridge converter

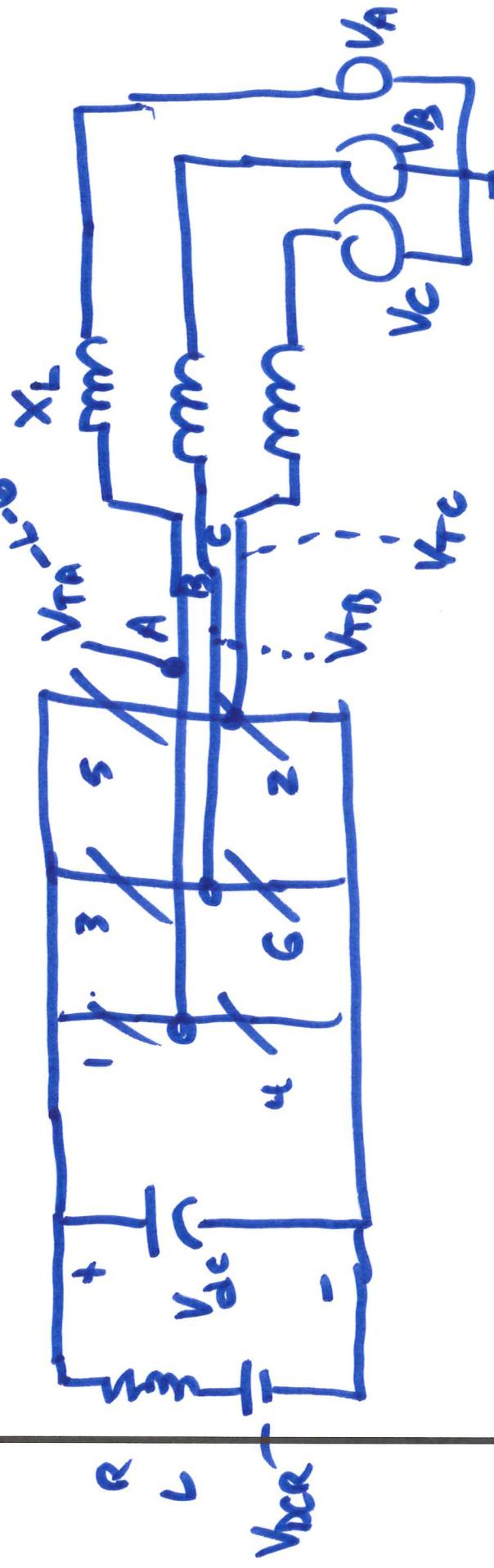

$$V_{TA}(t) = V_{TAN}(t) + \cancel{V_{TAN3}(t)} + \dots + \cancel{V_{TAn}(t)}$$

- concentrate  
on fundamental

component

- Transfers

use P  
P + Q

for power

system commands

- all multiples of 3 = 0
- central to switch should have symmetry to eliminate even harmonics
- most of harmonics around or above modulation frequency

$$i_a(t) = \underbrace{i_{A1}(t)}_{\text{Point of interest}} + \sum_{i=2}^n i_{hi}$$

$\bar{S}_{AC30_1} = 3 \bar{V}_{ta} \bar{I}_A^* = 3 \bar{V}_{ta} \left( \frac{\bar{V}_{ta} - \bar{V}_A}{jX_L} \right)^*$

phasor

$P_{30} = \operatorname{Re} \left( 3 \bar{V}_{ta} \left( \frac{\bar{V}_{ta} - \bar{V}_A}{jX_L} \right)^* \right)$


$= \frac{3 |V_{ta}| |V_A|}{X_L} \sin(\theta_{Vta} - \theta_{VA})$

$\delta = 0 \rightarrow \theta_{VA} = 0$


## control scheme for power converter

- $|V_{tar}|$  from modulation index
  - $\theta_{tar}$  from reference waveform
  - $\omega$  →  $|V_{tar}| \cos(\omega t + \theta_{tar})$
- ↑  
synchronization with power system

AC side equivalent

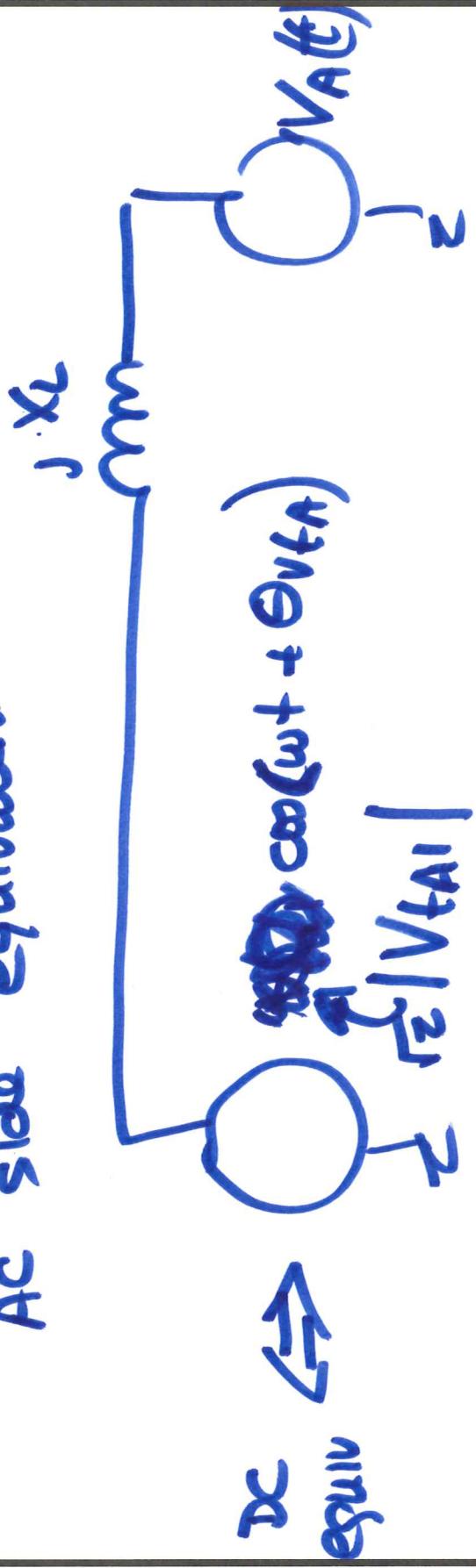

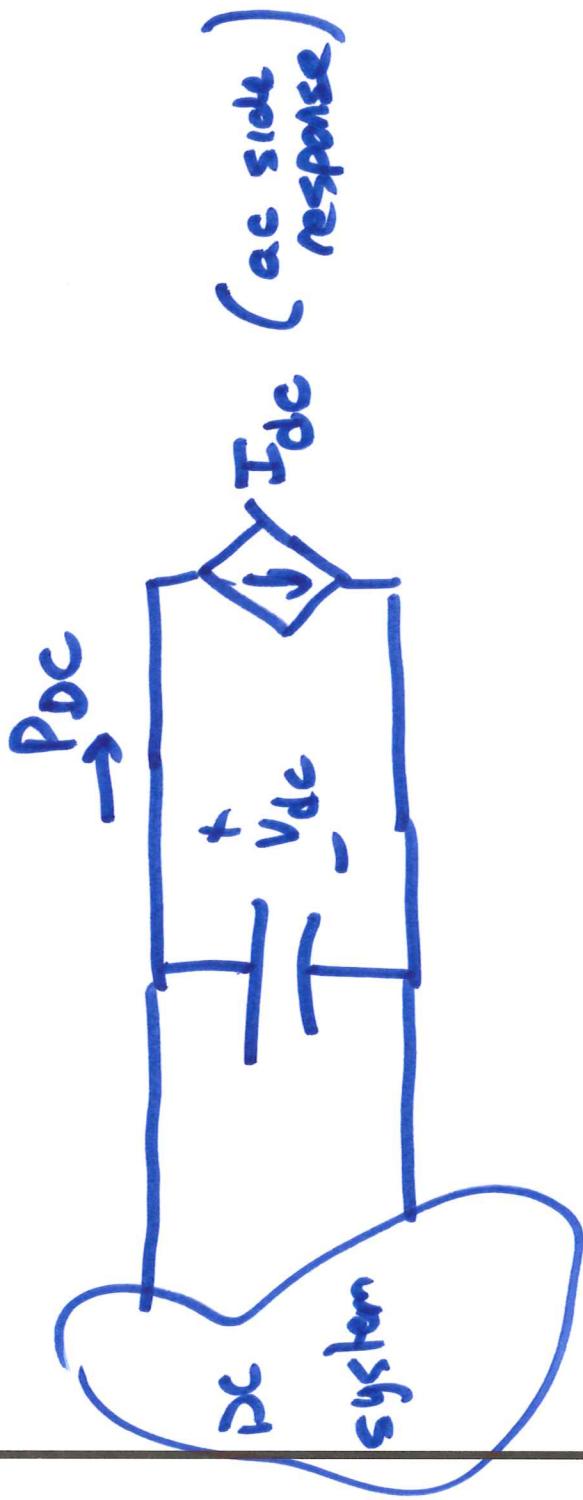Now we need to represent DC side  
plus interaction ---



$$P_{dc} = V_{dc} I_{dc}$$

$$P_{AC} = \frac{3 |V_{tan}| |I_{tan}|}{X} \sin(\theta_{tan} - \theta_{in})$$

$\exists$  use igniter converter losses  $P_{dc} = P_{AC}$   
 $\exists$  we can add later

$$V_{dc} \pi_{dc} = \frac{3 |V_{ext}| |V_A|}{x} \sin(\theta_{ext} - \theta_{vn})$$

$$- |V_{ext}| = m \cdot \kappa V_{dc}$$

↑  
modulation  
index from  
switching  
scheme

$\kappa$  - represents fundamental component  
scaling of  $V_{dc}$  w/ topology dependent

$$\text{3Ø bridge } \kappa = \frac{\sqrt{2}}{\pi}$$

$$|V_{EA1}| = m \frac{\sqrt{2}}{\pi} V_{dc}$$

- substitute  $\rightarrow$

divide both sides by  $V_{dc}$

$$I_{dc} = 3m \frac{\sqrt{2}}{\pi} |V_A| \sin(\theta_{vEA} - \theta_{VA}) / X_L$$