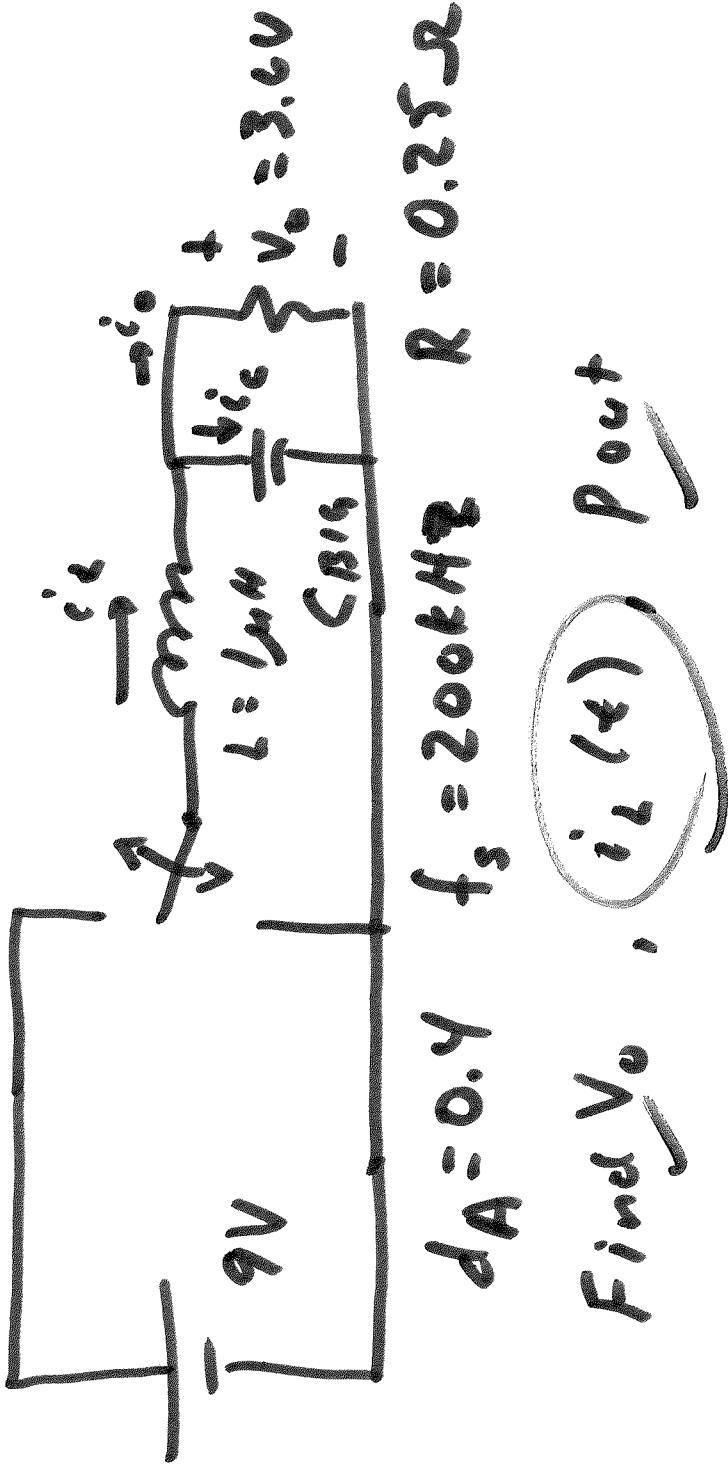


ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS

SESSION no. 3



$$d_A = 0.4 \quad f_s = 2000 \text{ Hz} \quad R = 0.25\Omega$$


Find v_o , $i_2(t)$, P_{out}

$$i_L(t) + v_L(t) -$$
$$\rightarrow \text{Comm} - \dots$$

$$\begin{bmatrix} qv \\ 0v \end{bmatrix}$$

$$\begin{bmatrix} 3.6v \\ 3.6v \end{bmatrix}$$

$$i_L(t) = \frac{1}{L} \int v_L(t) dt$$

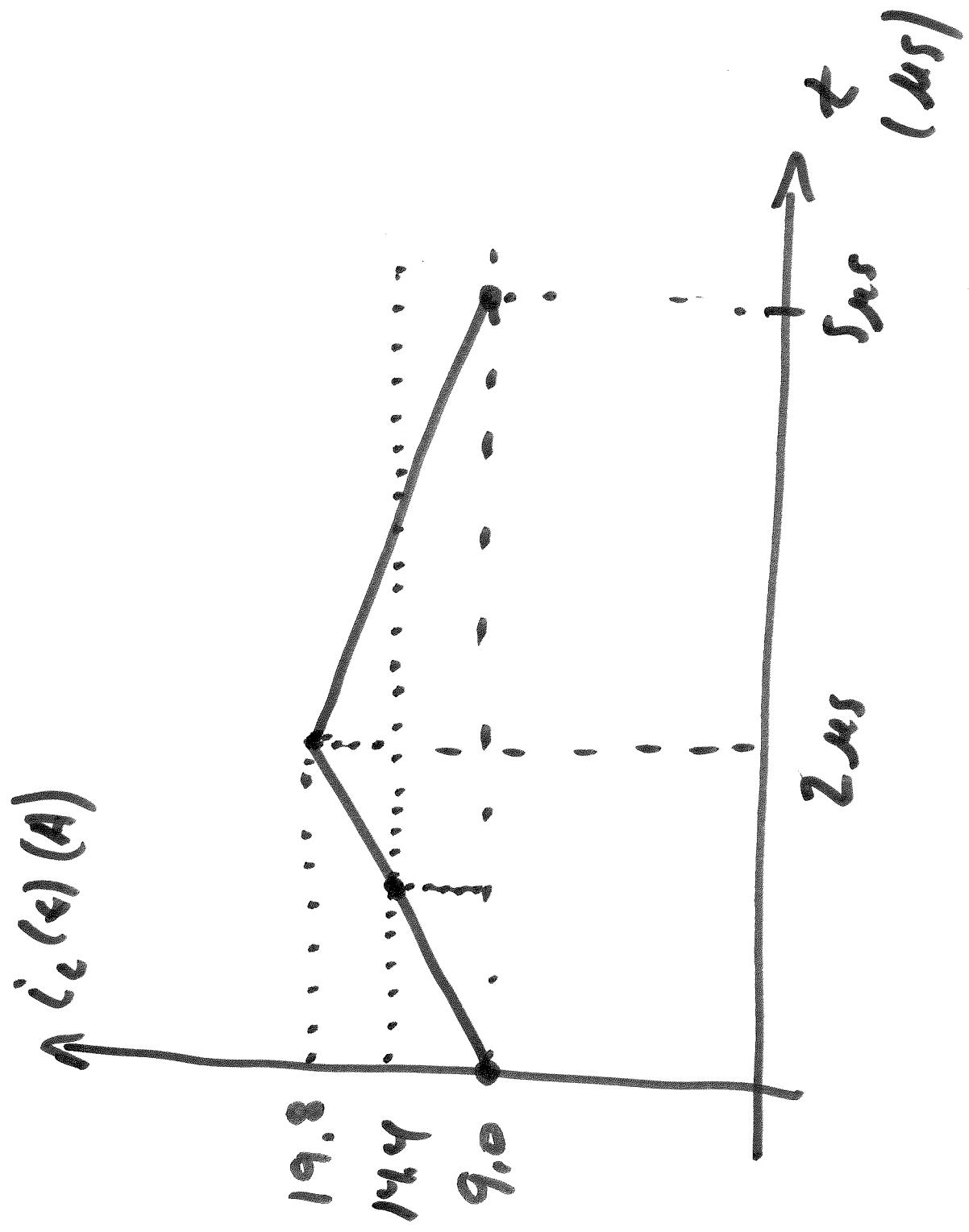

$$i_L(2\mu_1) = i_L(\partial\mu_1) + \frac{1}{L} \left((V_{in} - V_o) \right) dt$$

$$L = 1 \text{ mH}$$

$$V_{in} = 9V$$

$$V_o = 3.6V$$


$$i_L(2\mu_1) = i_L(\partial\mu_1) + 10.8 \text{ A}$$

$$i_L = i_C + i_o$$
$$i_L - i_C = 0 + \frac{3.6V}{0.2\text{ mN}}$$
$$i_o = 14.4 A$$


$$i_{C1,4}(A) = i_C(0) + \frac{10.3A}{2}$$

$$i_L(0) = \underline{\underline{9.0\ A}}$$

D10 DΣ

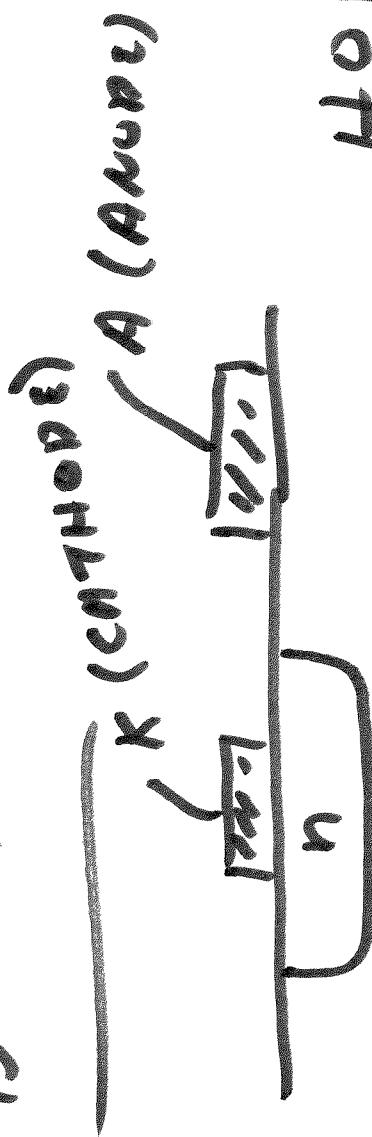


HORIZONAL

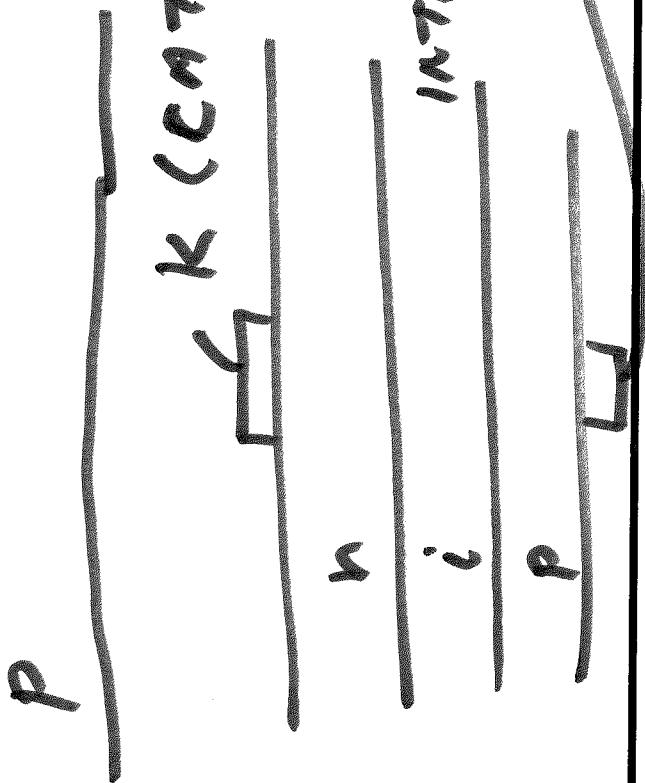


VΣ K71CAC

P10D4

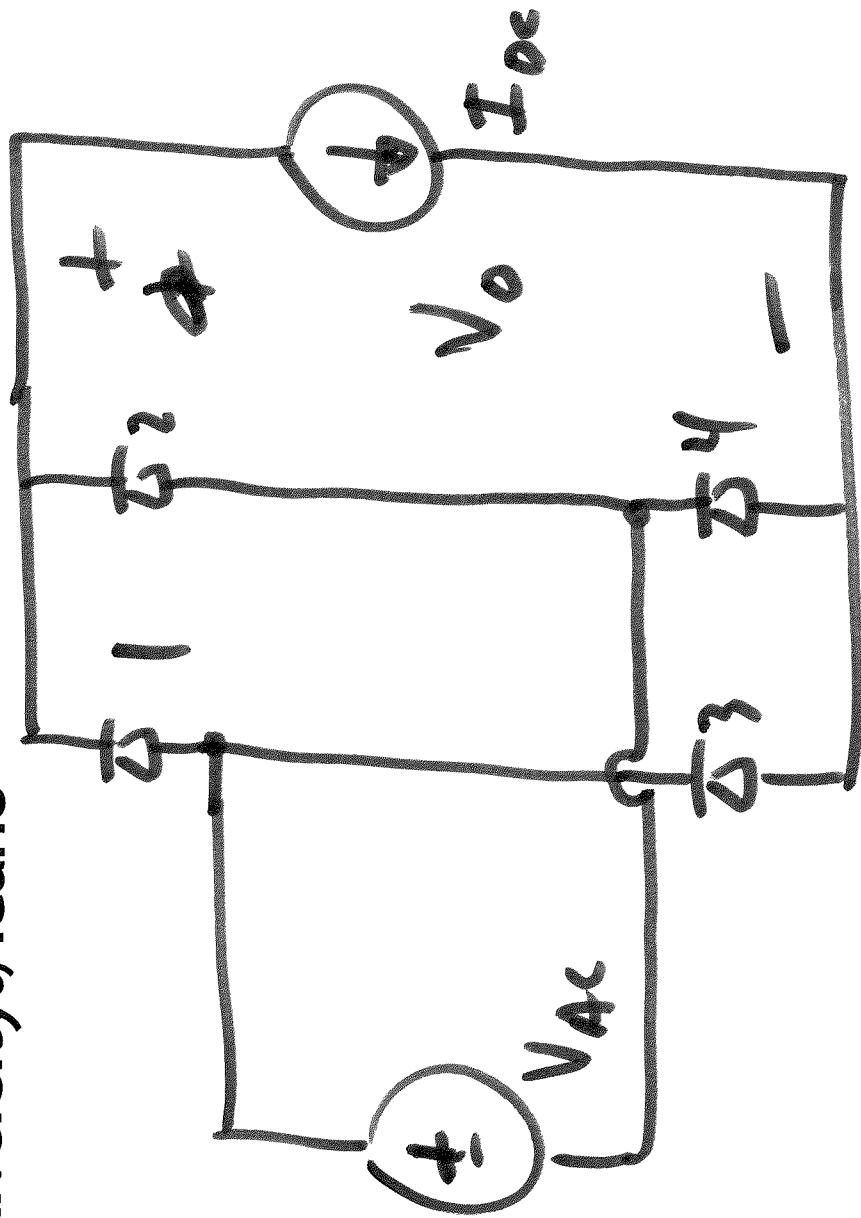
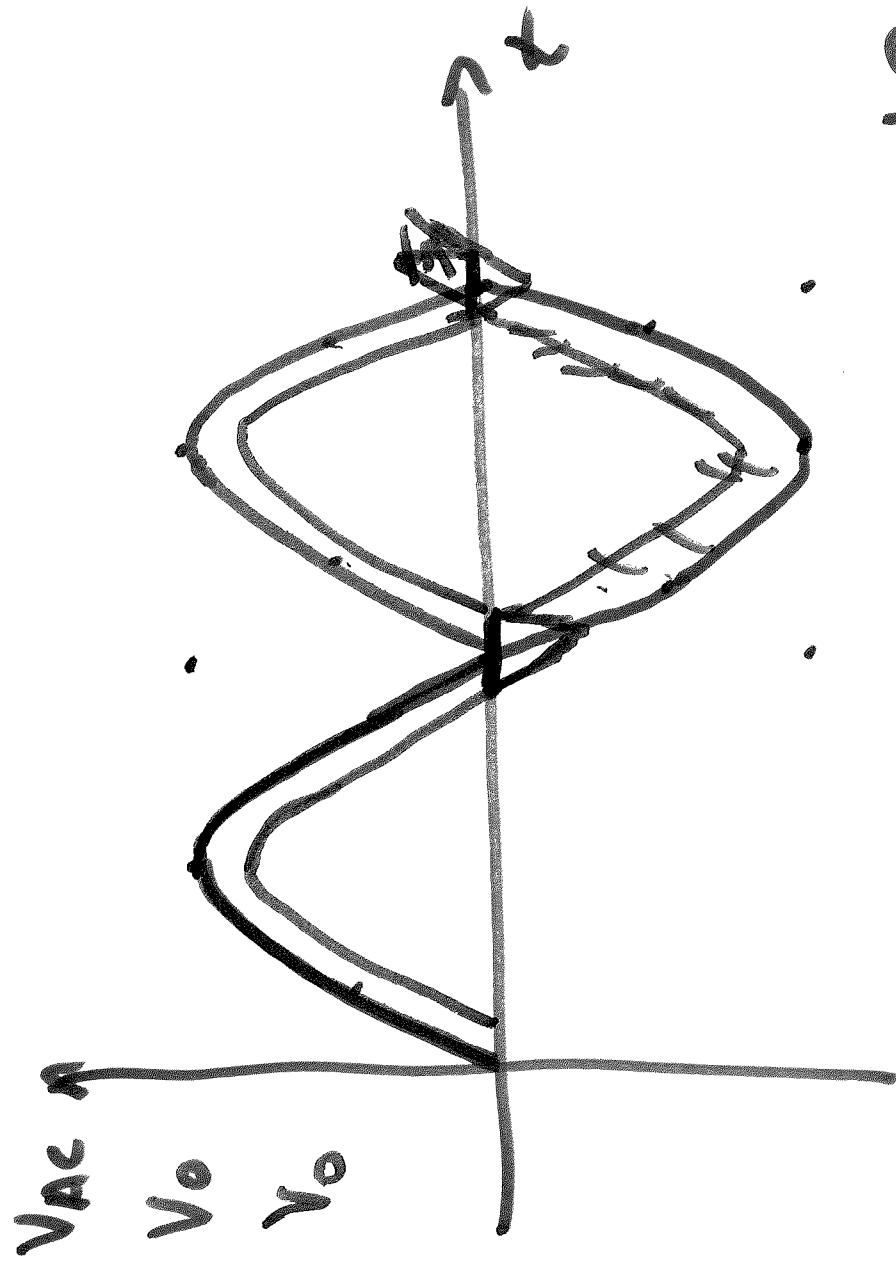
$$I_{AC} + V_{AC}(\omega t) = 12\sqrt{2} \sin \omega t$$
$$I_{DC} = 2.0 \text{ A}$$



$I \propto \text{exp}(V)$
0.7 V

ECE 404 / 504

T & D Applications of Voltage Sourced Converters

Lesson 3

The inductor current is a ramp: Integrate the constant voltage over time and scale it...we get a ramp.

Let's build a biposition switch from available components.

Switching component types:

Uncontrolled switch: The rest of the circuit determines the switch state. Example: diode

Forward bias: try to place a positive voltage on the diode...it will conduct.

Reverse bias: try to place a negative current in the diode...it will block.

Semicontrolled switch: example: thyristor (silicon controlled rectifier SCR) SCR conducts when it has a positive (forward) voltage AND a trigger pulse; it blocks like a diode (try to reverse the current)

Controlled: conducts and blocks in response to commands. Example: MOSFET, Insulated Gate Bipolar Transistor (IGBT), Gate Turn-off Thyristor (GTO), others...

Diode (Power diode)

- ☺ Greater voltage capacity
- ☺ Greater current capacity
- ☹ Intrinsic region has more voltage drop and power loss
- ☹ Resistance term in series in the model