

ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS

SESSION no. 34

ECE 404/504: Homework #5


Due Session 37 (April 17)

1. Implement an averaged model of a three VSC with an AC source voltage of 2.4kV (L-L), $R = 0.096 \Omega$, $L = 3.82\text{mH}$ ($X/R = 15$) and a switching frequency of 3600Hz.
- A. Determine V_{dc} if the maximum amplitude of the modulating function is 0.8 and the maximum reactive power the converter can supply is 4MVAR while transferring 0 MW (both measured at the source side of the R-L). Round up to nearest 10 V.
 - C. Generate open loop modulating functions ($m_a(t)$, $m_b(t)$, and $m_c(t)$) such that $P=4\text{MW}$ and $Q=0$. Verify that the converter supplies this using averaged models.
 - D. Generate open loop modulating functions such that $P=3.71\text{MW}$ and $Q=1.5\text{MVAR}$. Verify that the converter supplies this.
 - E. Generate open loop modulating functions such that $P=3.71\text{MW}$ and $Q=-1.5\text{MVAR}$. Verify that the converter supplies this.
 - F. Generate open loop modulating functions such that $P=-3.71\text{MW}$ and $Q=-1.5\text{MVAR}$. Verify that the converter supplies this.
 - G. ECE 504 students, implement using a switching model. Compare ac currents to those from the averaged models and the fundamental component of converter terminal voltages to averaged model results.
2. Now the VSC from problem 1 has a closed loop control scheme implemented in the synchronously rotating d-q reference frame. Assume that the source voltage is constant.
- A. Determine the i_{dref} and i_{qref} such that $P=4\text{MW}$ and $Q=0$.
 - B. Determine the i_{dref} and i_{qref} such that $P=3.71\text{MW}$ and $Q=1.5\text{MVAR}$.
 - C. Determine the i_{dref} and i_{qref} such that $P=3.71\text{MW}$ and $Q=-1.5\text{MVAR}$.
 - D. Determine the i_{dref} and i_{qref} such that $P=3.71\text{MW}$ and $Q=-1.5\text{MVAR}$.
 - E. ECE 504 students implement cases A-D using closed loop control in your EMT program using averaged models.

Assume PLL $\rightarrow V_{sq} = 0$

1/1
134
1/11


1/3
1/5
1/3

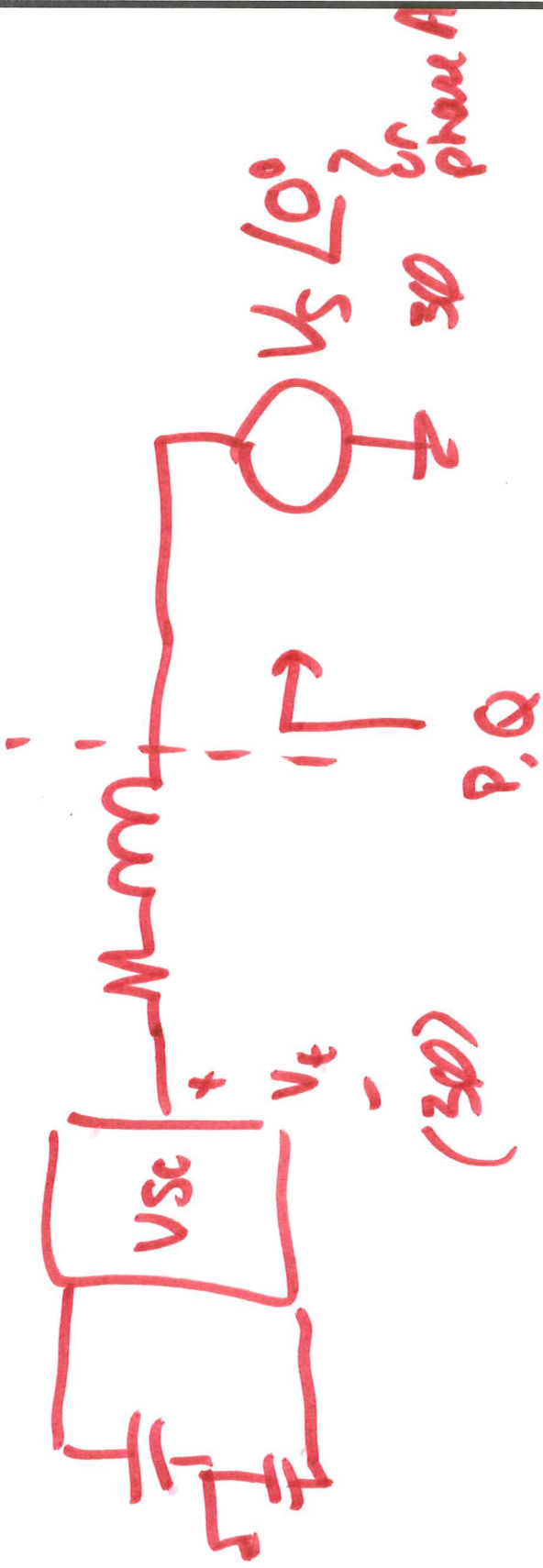


$$\left(1 + \frac{m_A}{2}\right) i_A = I_{PA}$$

$$\left(1 - \frac{m_A}{2}\right) i_A = I_{NA}$$

• Current commands

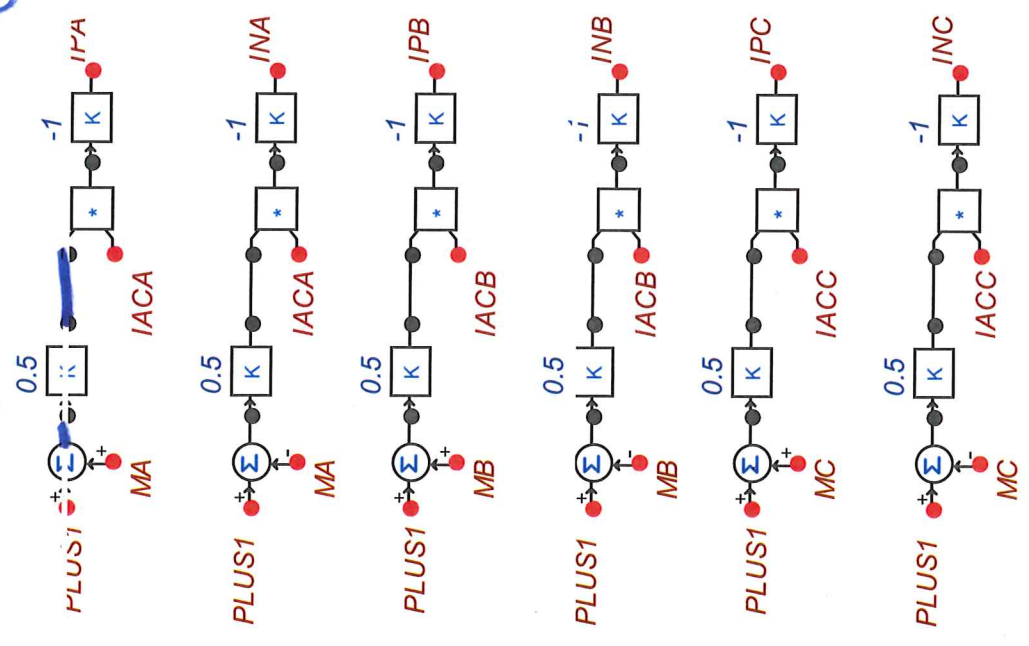



• Voltage command

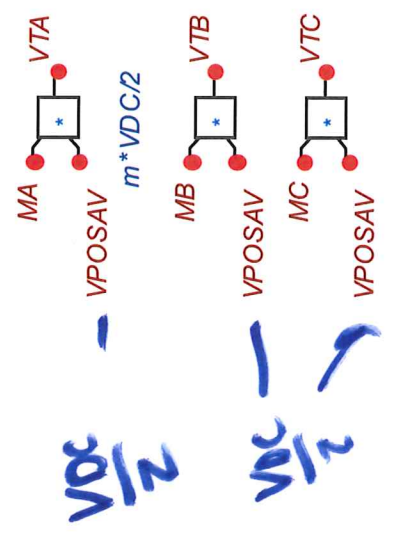

specify magnitude of m

- Generate modulating functions

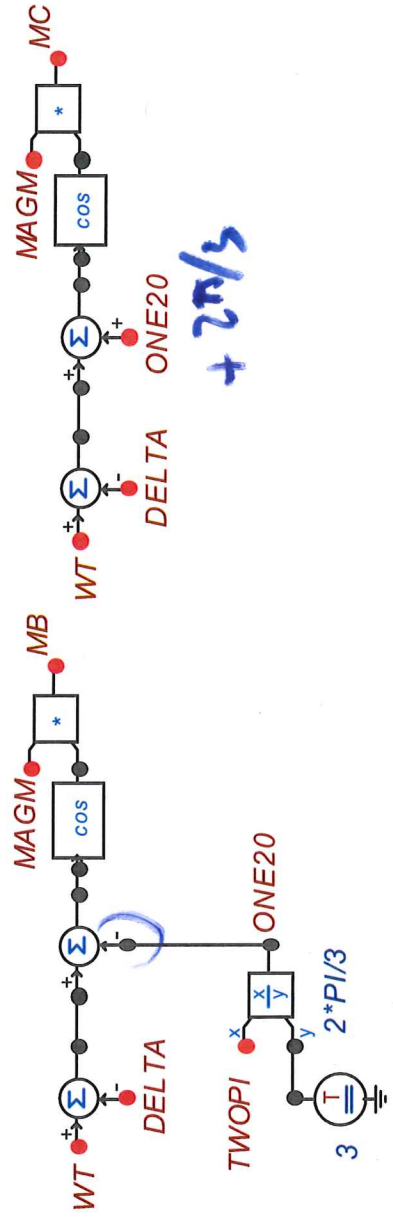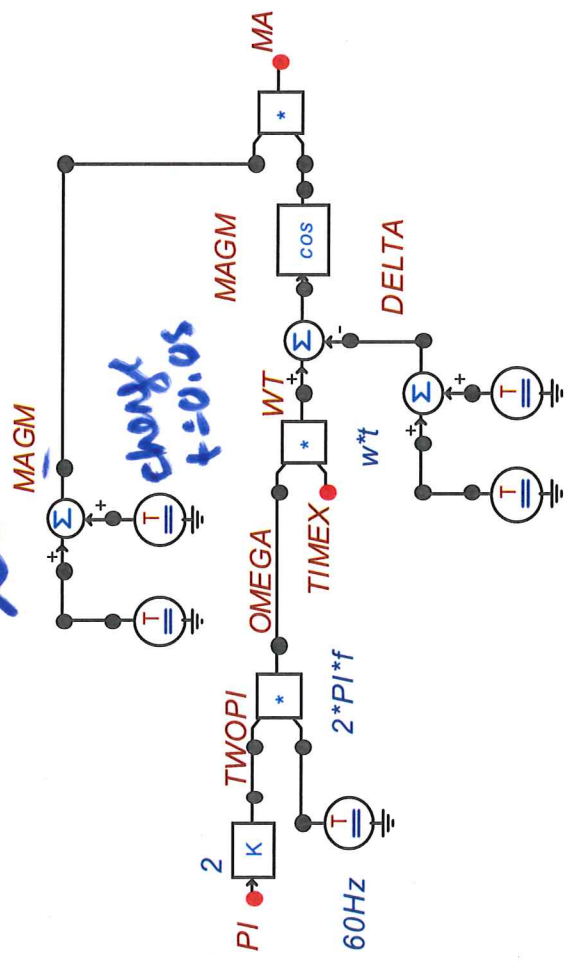
$$M_A(t) = M_{AGM} \cdot \cos(\omega t - \alpha)$$



+ 2PI/3


L34 7/11

Phase A currents

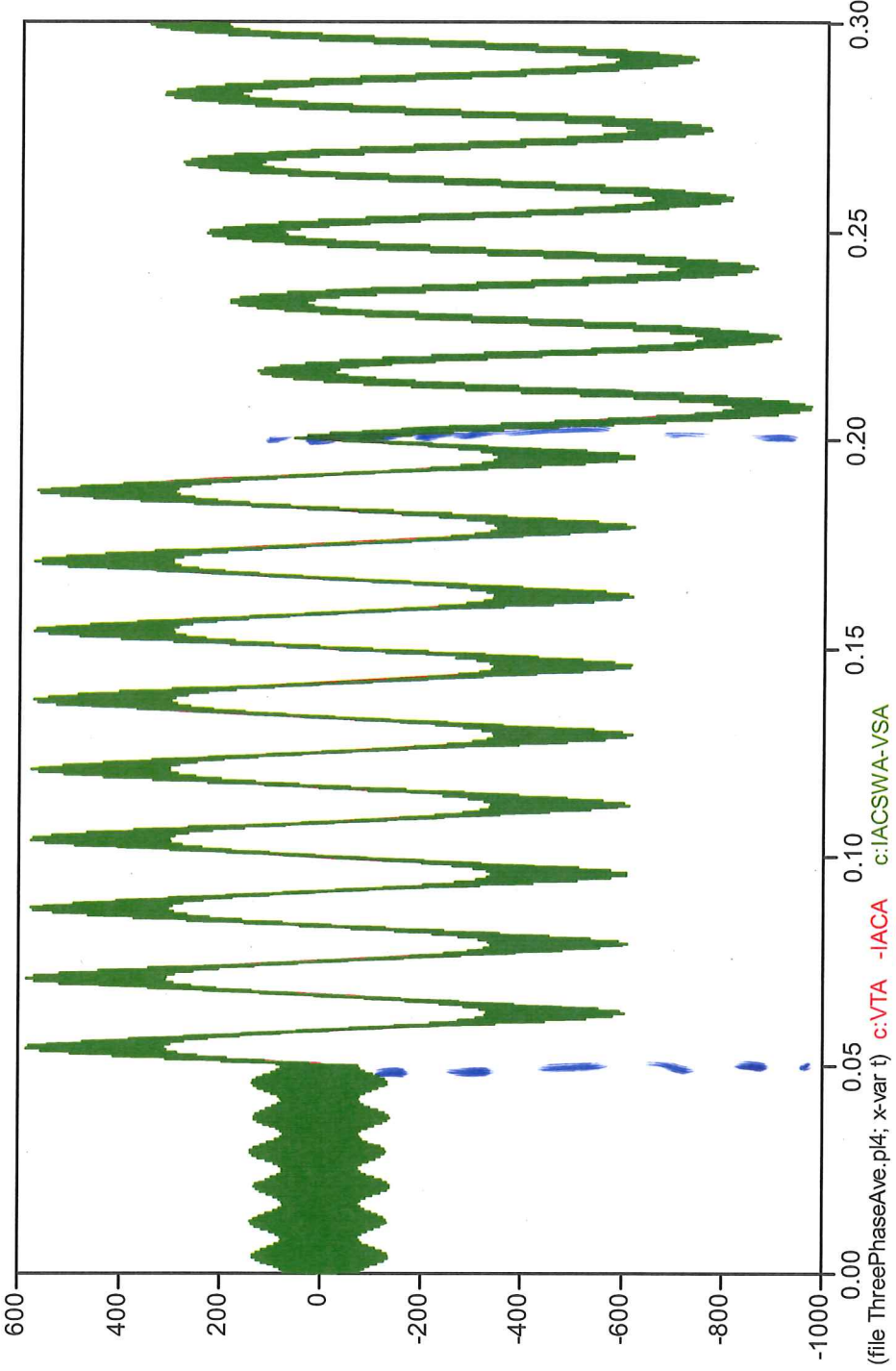


L34 8/11

Positive side DC currents

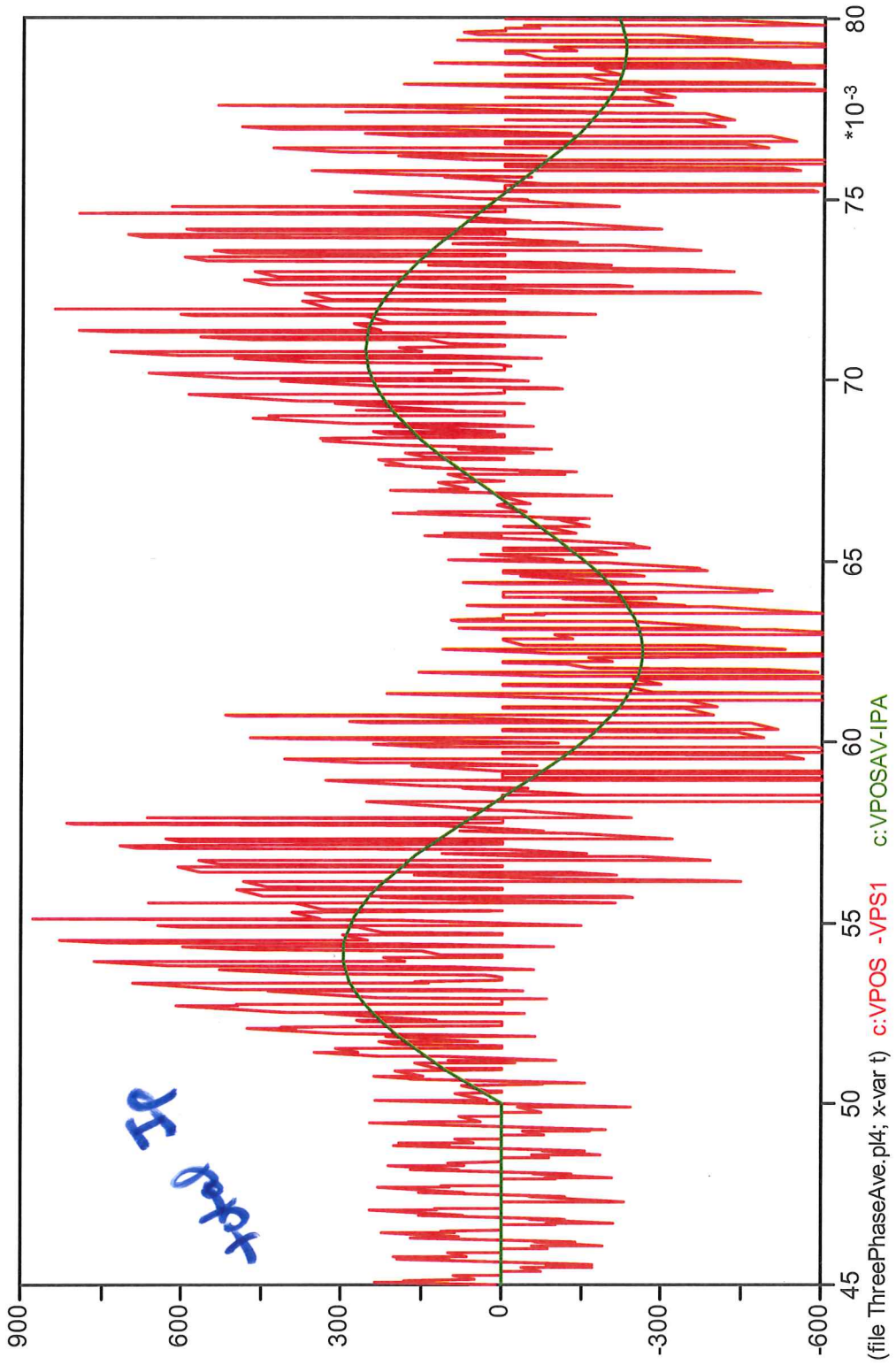

L34 9/11

University of Idaho

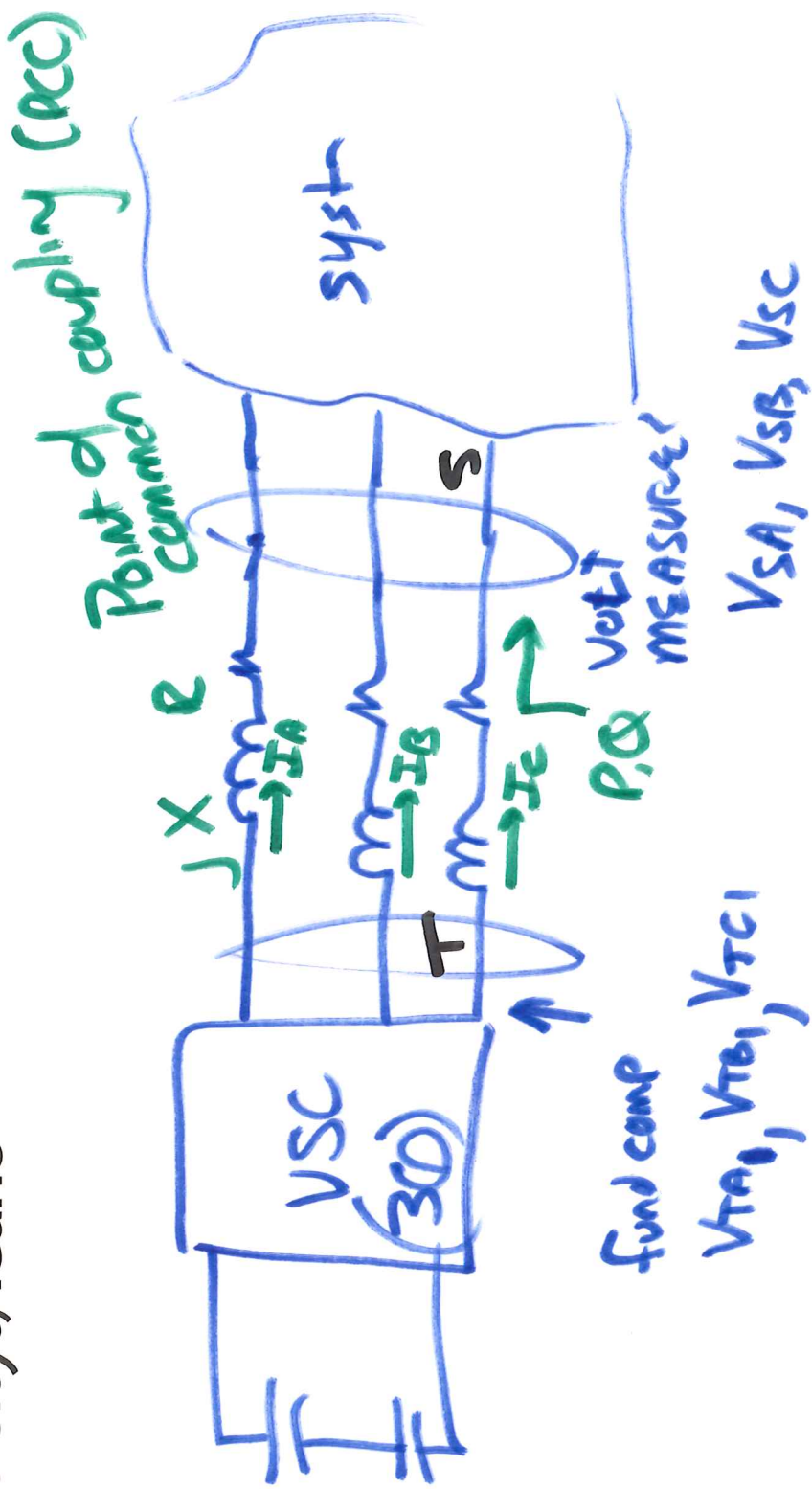

for now balanced 3 ϕ

Regulate P, Q at PCC

L34 16/11

University of Idaho

If R small compared to X

$$X/R > 10$$

↑ polarity of I_A coming from ↑

$$-P_{ST} = 3 \cdot \text{Re}(\dot{V}_{S0nA} \dot{I}_A)$$

$$-S_{ST} = 3 \dot{V}_{SA} \dot{I}_A^*$$

$$= 3 \dot{V}_{SA} \left(\frac{V_T - V_{SA}}{Z + jX} \right)^* \approx 0$$

$$\left[\begin{array}{l} V_A \angle \delta \\ V_{SA} \angle 0 \end{array} \right]$$

$$-P_{ST} = \frac{3 |V_{SA}| |V_{TA}| \sin(\delta - 0)}{X} = P_{TS}$$

Similarly

$$-Q_{ST} = \frac{-|V_{SA}|^2 + |V_{SA}||V_{TA}| \cos(\delta-0)}{X}$$

≠ Q_{TS} because of Q "absorbed" in inductor