

ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS

SESSION no. 36


University of Idaho

L36 1/11


• HW due date (HW5)

→ lecture 39, April 22

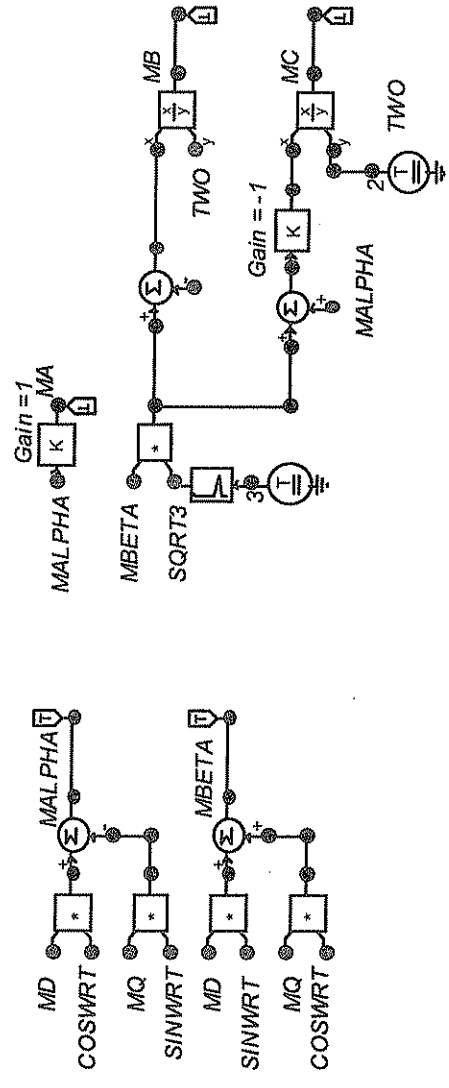Convert MD and MQ alpha-beta
and then to ABC domain



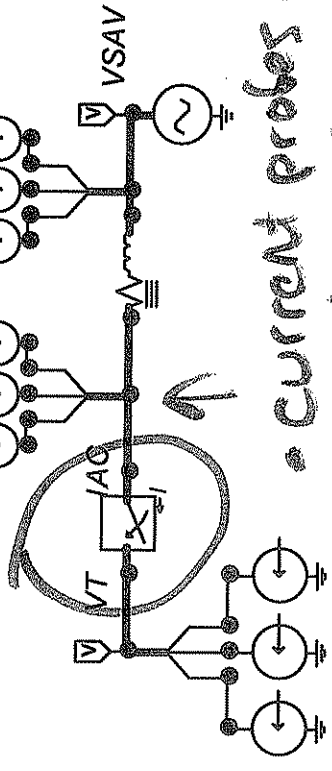current for
probes - TACS voltage problem (Veg)



- current probes - connected to node with switch coming from TACS that
- TACS interprets current as ~~being~~ polarity node into switch regardless of network polarity

Problem 1 on homework

- with open loop control
- and P, Q calculated neglecting

Resistance

→ The calculated V_e/V_s

will not give precise

match of P, Q in ATP

or EMTOC

$K_p \rightarrow$ Proportional gain

K_i - integral gain

IF τ_d, τ_i, τ_d are constant in steady state

$$\frac{K_i}{K_p} = \frac{R_s}{L_s}$$

$$\text{Out} \approx \tau_d \tau_i \tau_d \text{ OVs}$$

$$\frac{K_p}{L_s} = \tau_i$$

τ_i Time constant of desired response \rightarrow Book users SMS

U36 5/11

University of Idaho

IF in synch ref


frame \rightarrow change

$\omega_0 L$ in cross

coupling term in
control loop

Closed Loop Controls

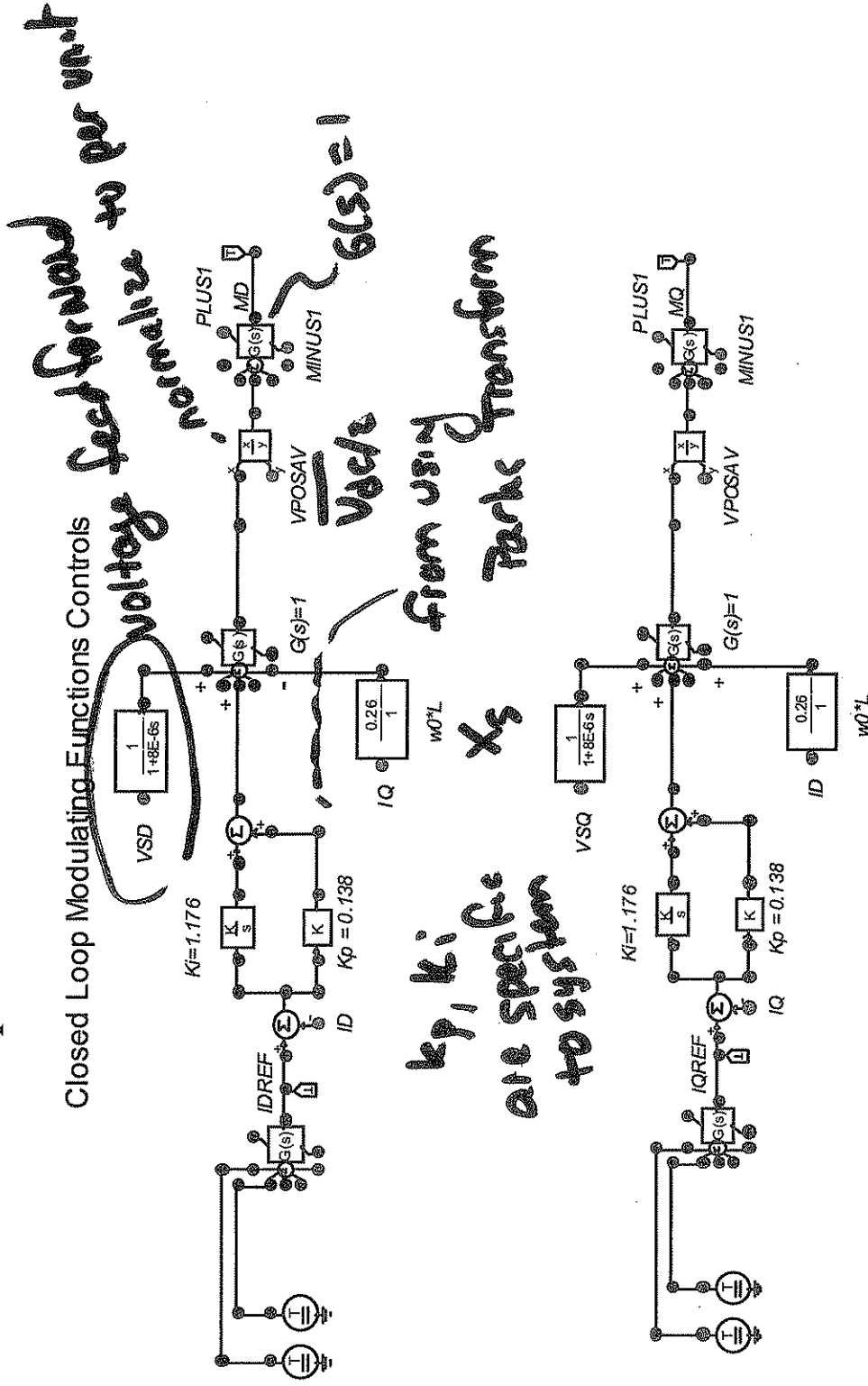Closed Loop Modulating Functions Controls





Convert MD and MQ alpha-beta and then to ABC domain

$$\text{Gain} = \frac{1}{\omega L}$$

L36 7/11


University of Idaho

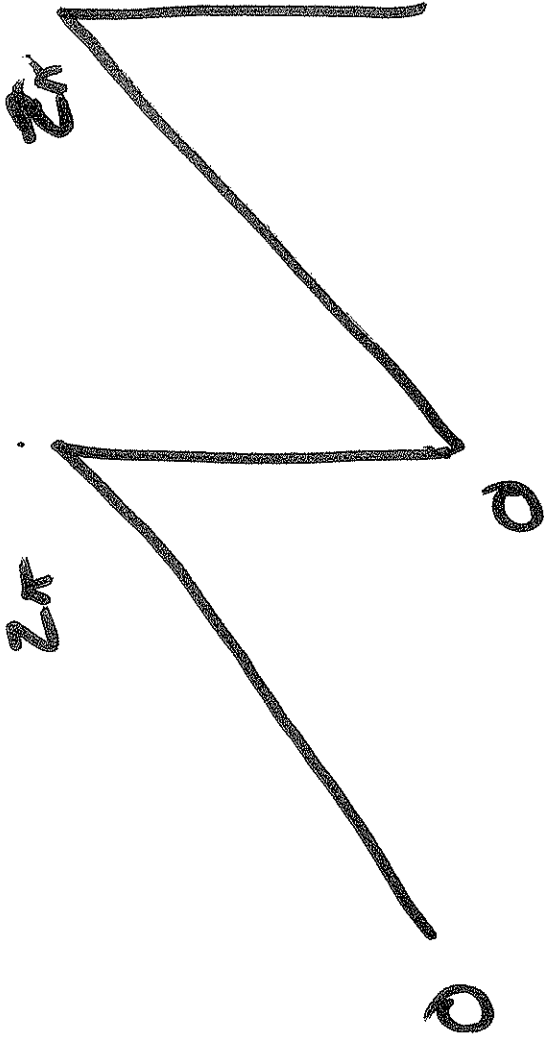

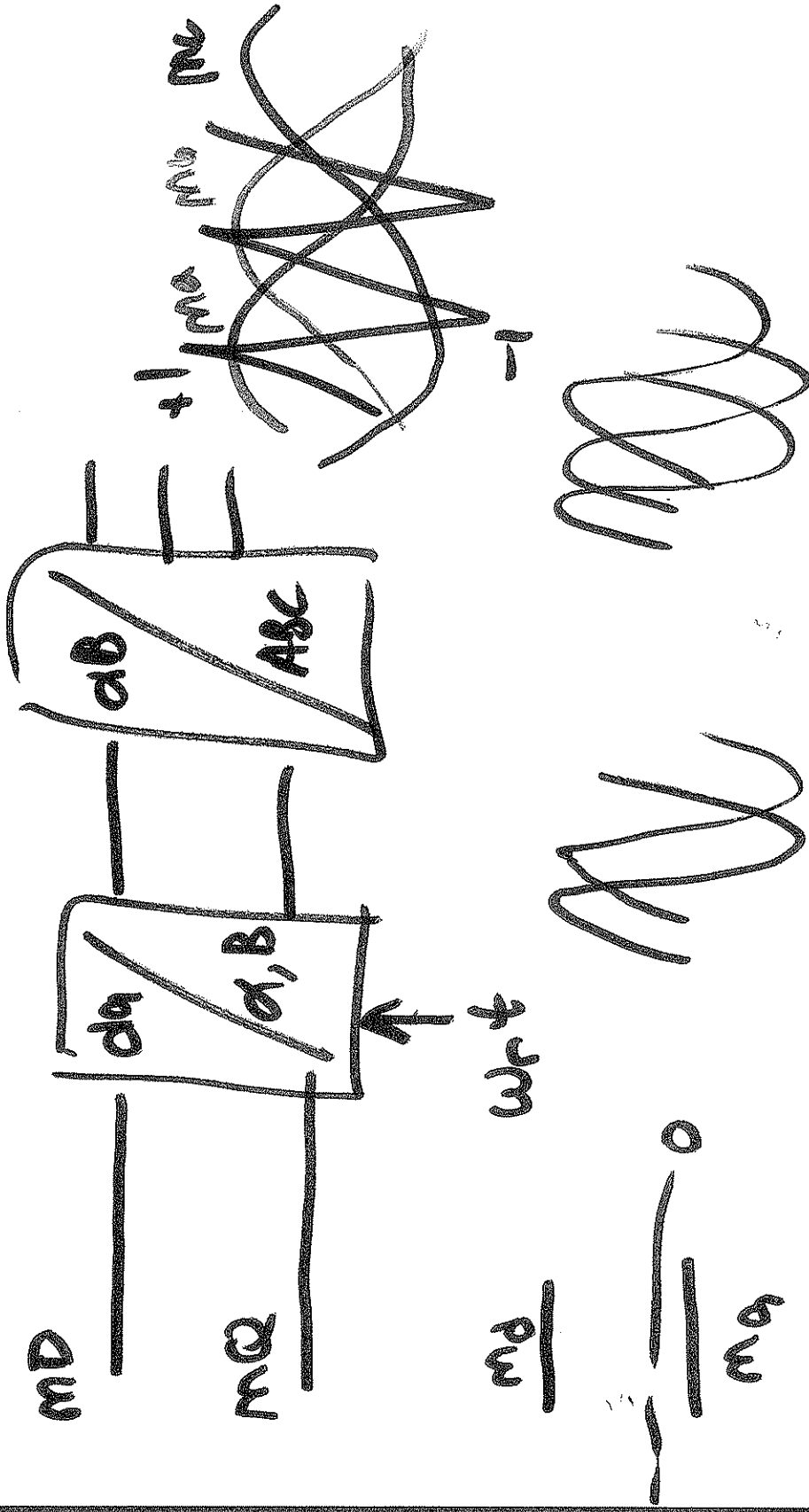


136 9/11

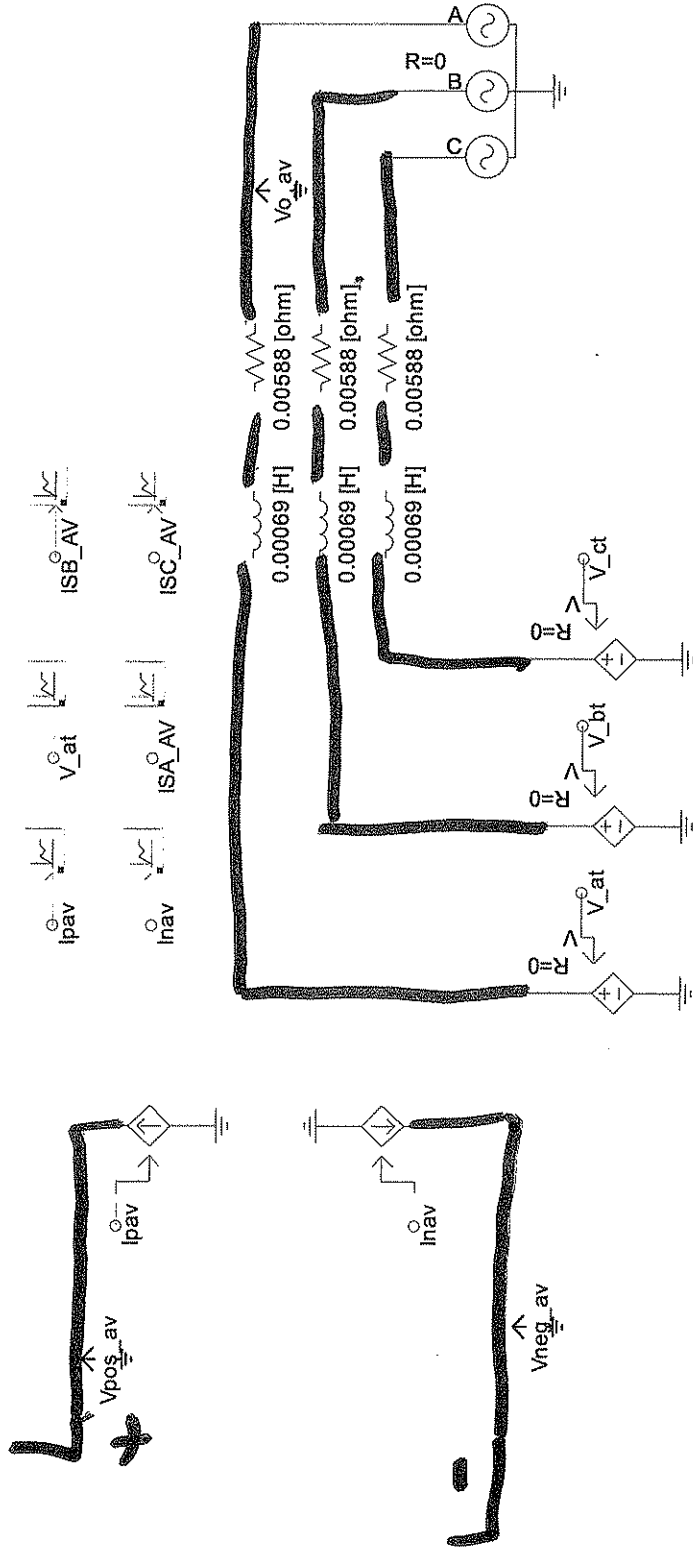- Averaged Model Power Circuit (note DC links tied to switching model to reduce node count)



236 16/11


• Create Open-loop Modulating Functions

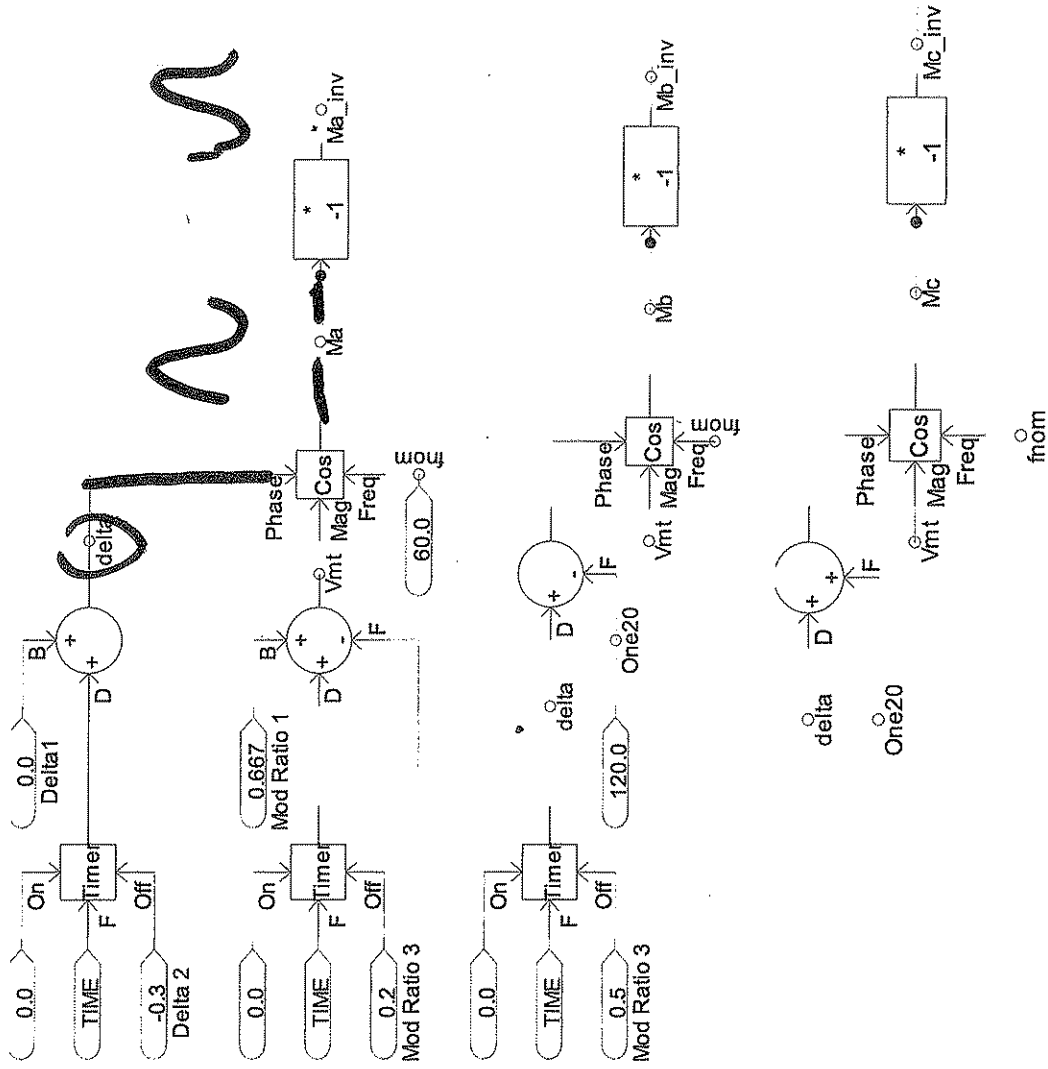

L36 11/14

PSCAD/EMTDC Implementation of Three Phase Averaged Models

- Switching circuit

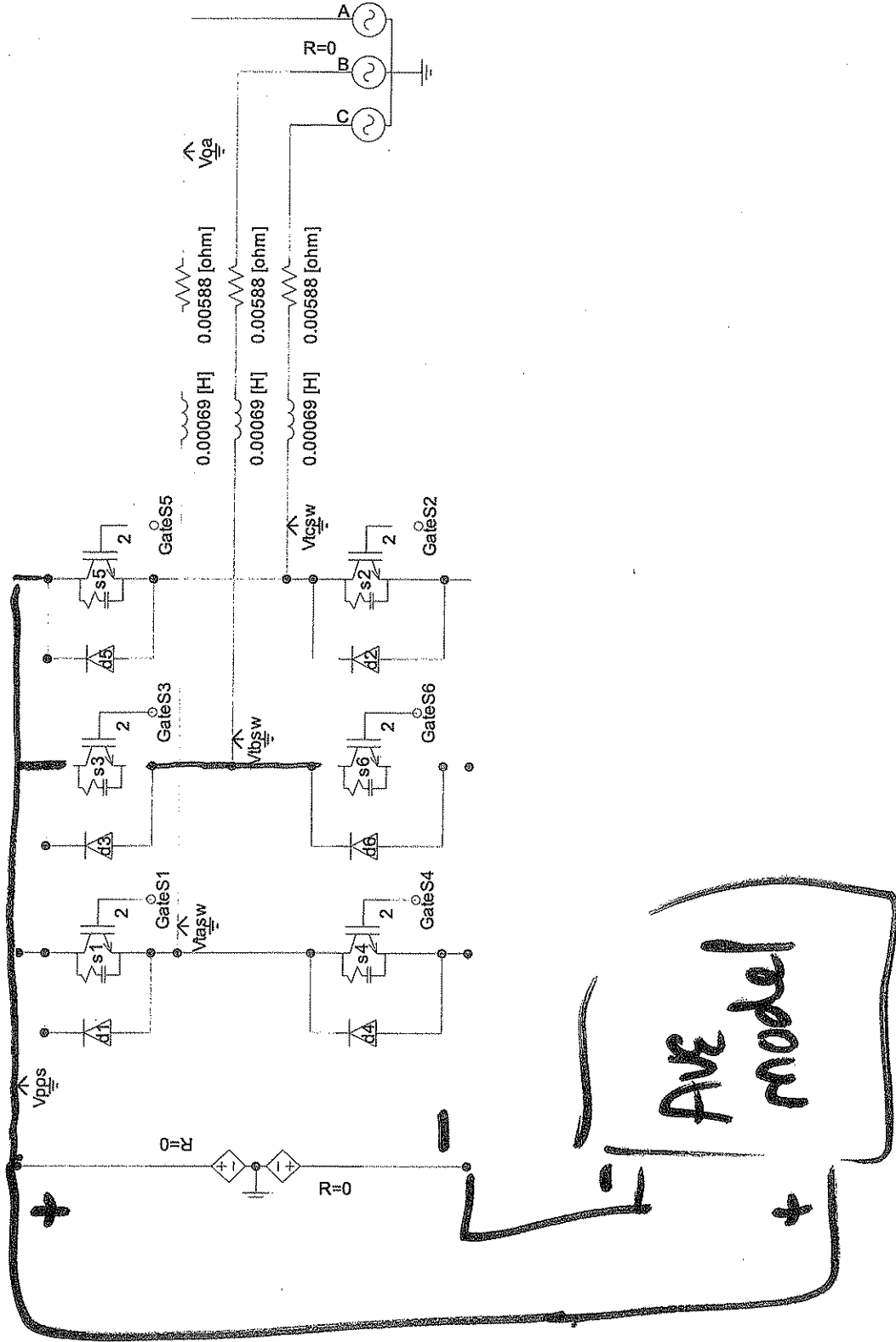

Ave
model