

ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF  
VOLTAGE SOURCE CONVERTERS

SESSION no. 36


L36 1/0

University of Idaho


- HW due date (HW5)  
→ lecture 39, April 22

L36 2/11

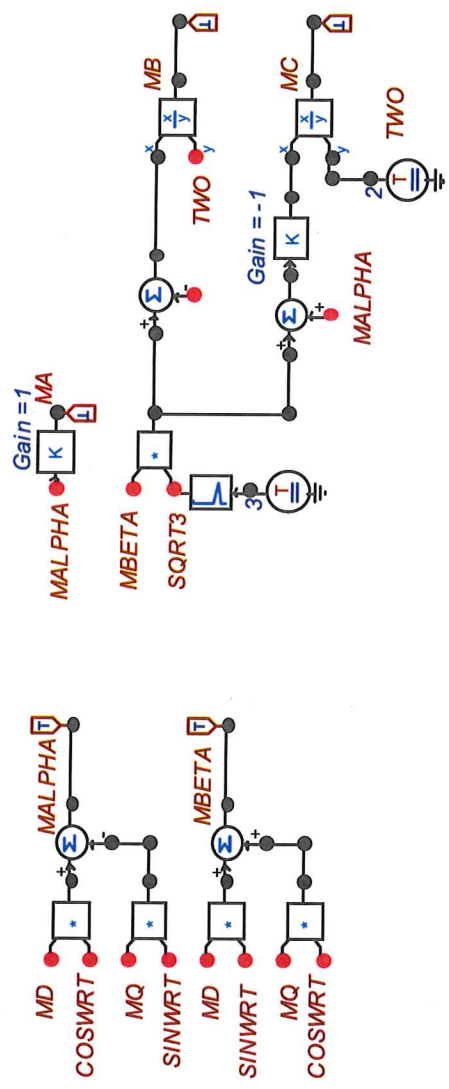Convert MD and MQ alpha-beta  
and then to ABC domain



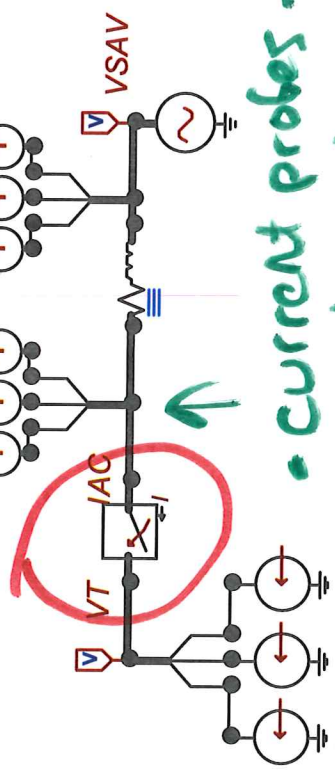current for TACS voltage (V<sub>ag</sub>)  
probes TACS - voltage problem



- current probes - connected to node with switch coming from
- TACS interprets current as ~~being~~ that node into switch regardless of network polarity

## Problem 1 on homework

- with open loop control and  $P, Q$  calculated neglecting Resistance

→ The calculated  $V_t/V_s$

will not give precise

match of  $P, Q$  in ATP

on EMTDC

$K_p \rightarrow$  Proportional gain

$K_i$  - integral gain

IF  $\tau_d, \tau_i$  are constant in steady state

$$\frac{K_i}{K_p} = \frac{R_s}{L_s}$$



$$\frac{K_p}{L_s} = \frac{1}{\tau_i}$$

$\tau_i$  Time constant of desired response  $\rightarrow$  Book using 5ms

If in synch ref


frame  $\rightarrow$  change

$\omega_0 L$  in cross

coupling term in  
control loop

LB36 6/11

### Closed Loop Controls

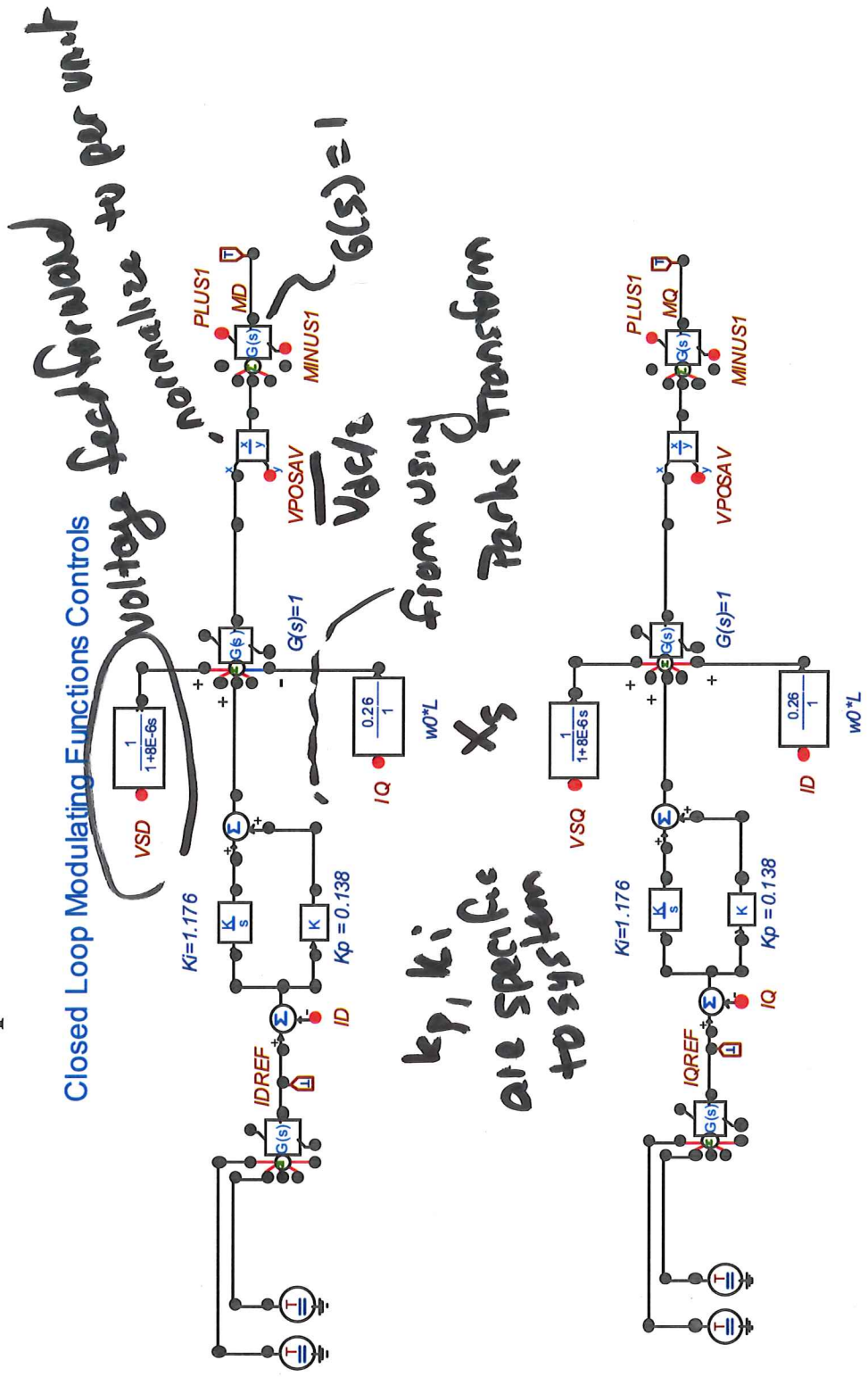


Convert MD and MQ alpha-beta  
and then to ABC domain

Gain = 1




L36 7/11

University of Idaho

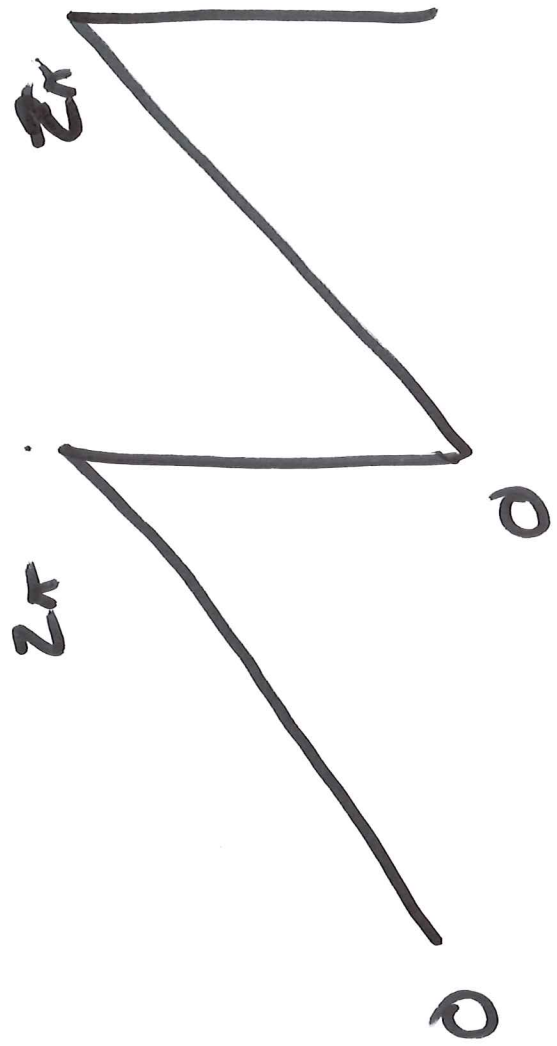




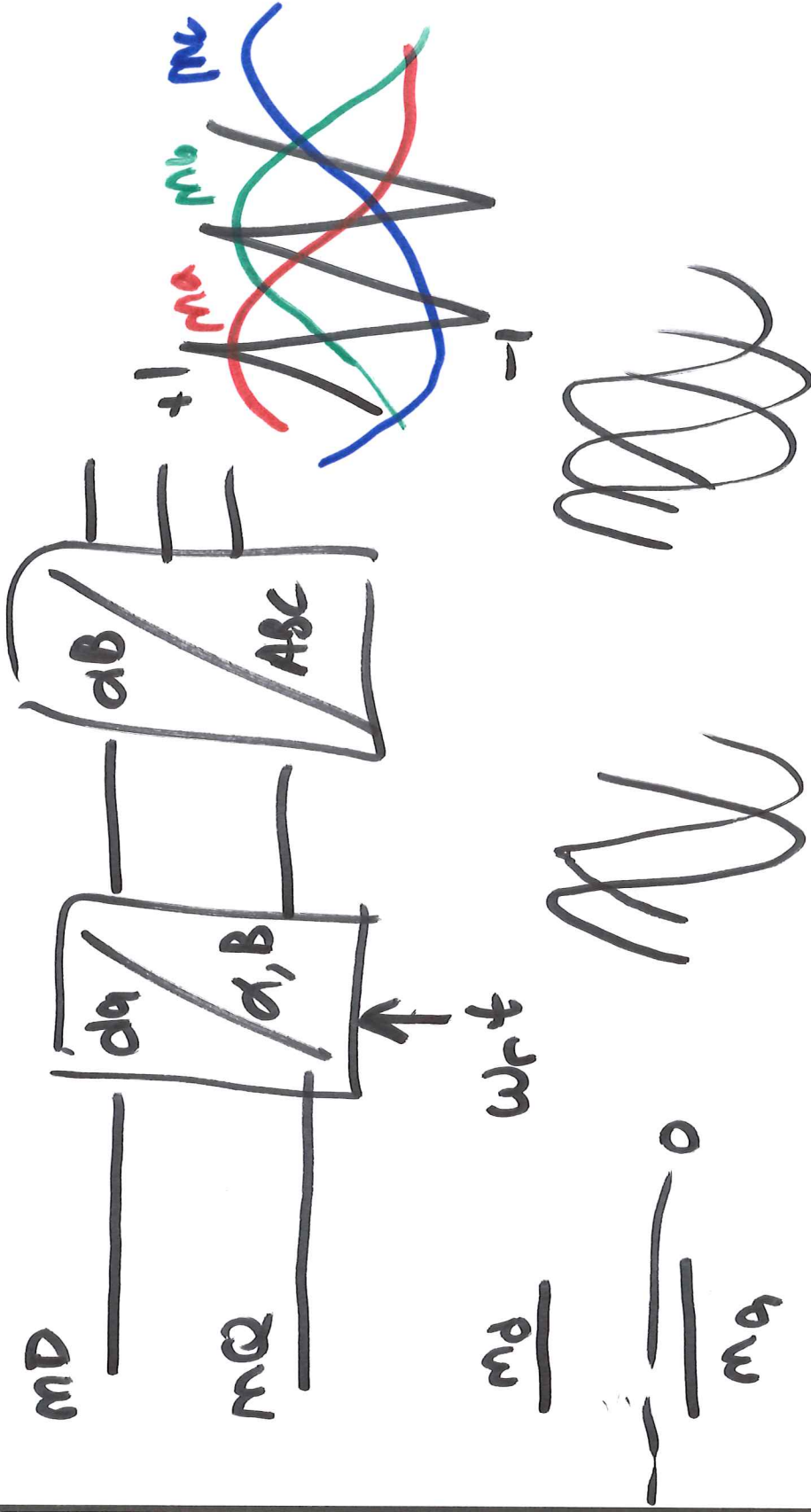


136 9/11

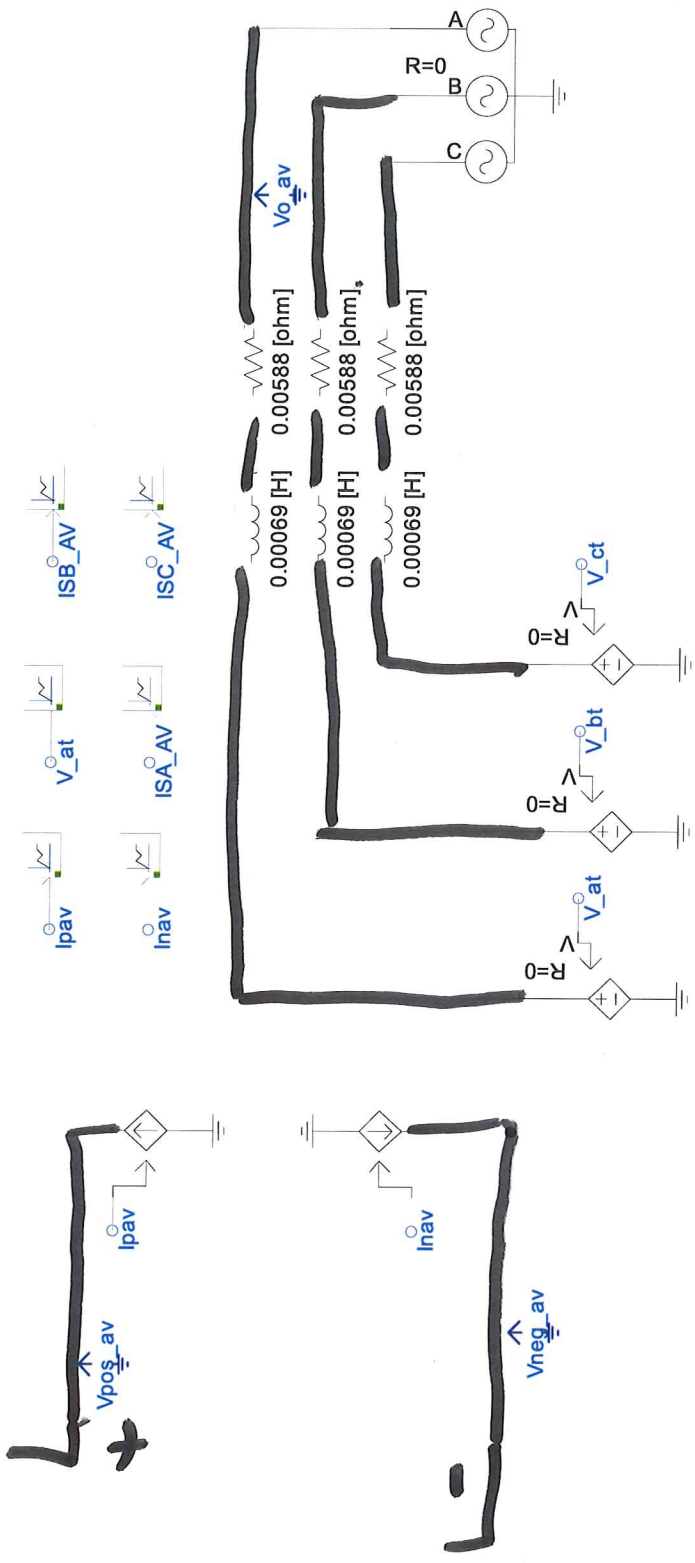- Averaged Model Power Circuit (note DC links tied to switching model to reduce node count)



236 16/11

• Create Open-loop Modulating Functions

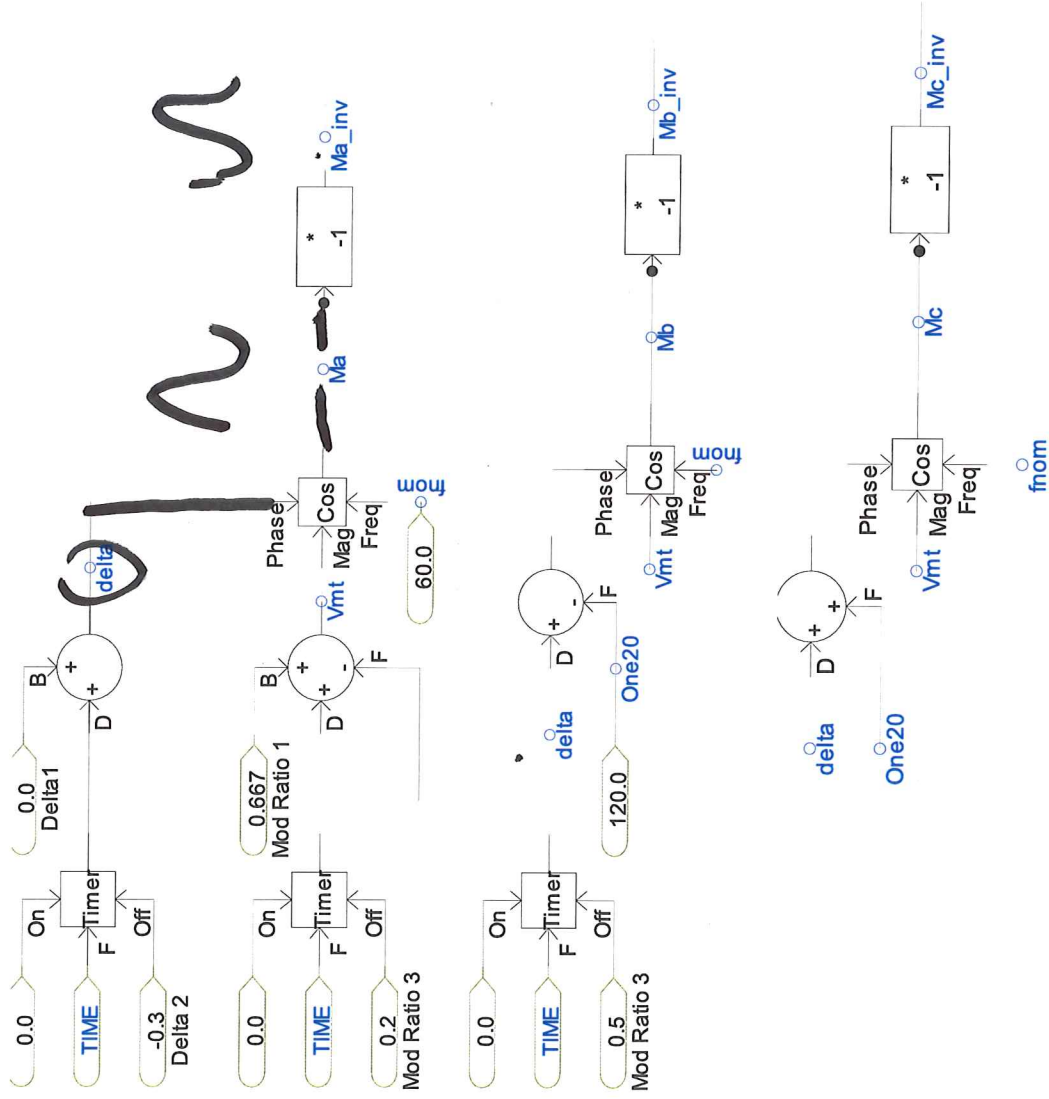

L36 11/6

### PSCAD/EMTDC Implementation of Three Phase Averaged Models

- Switching circuit

