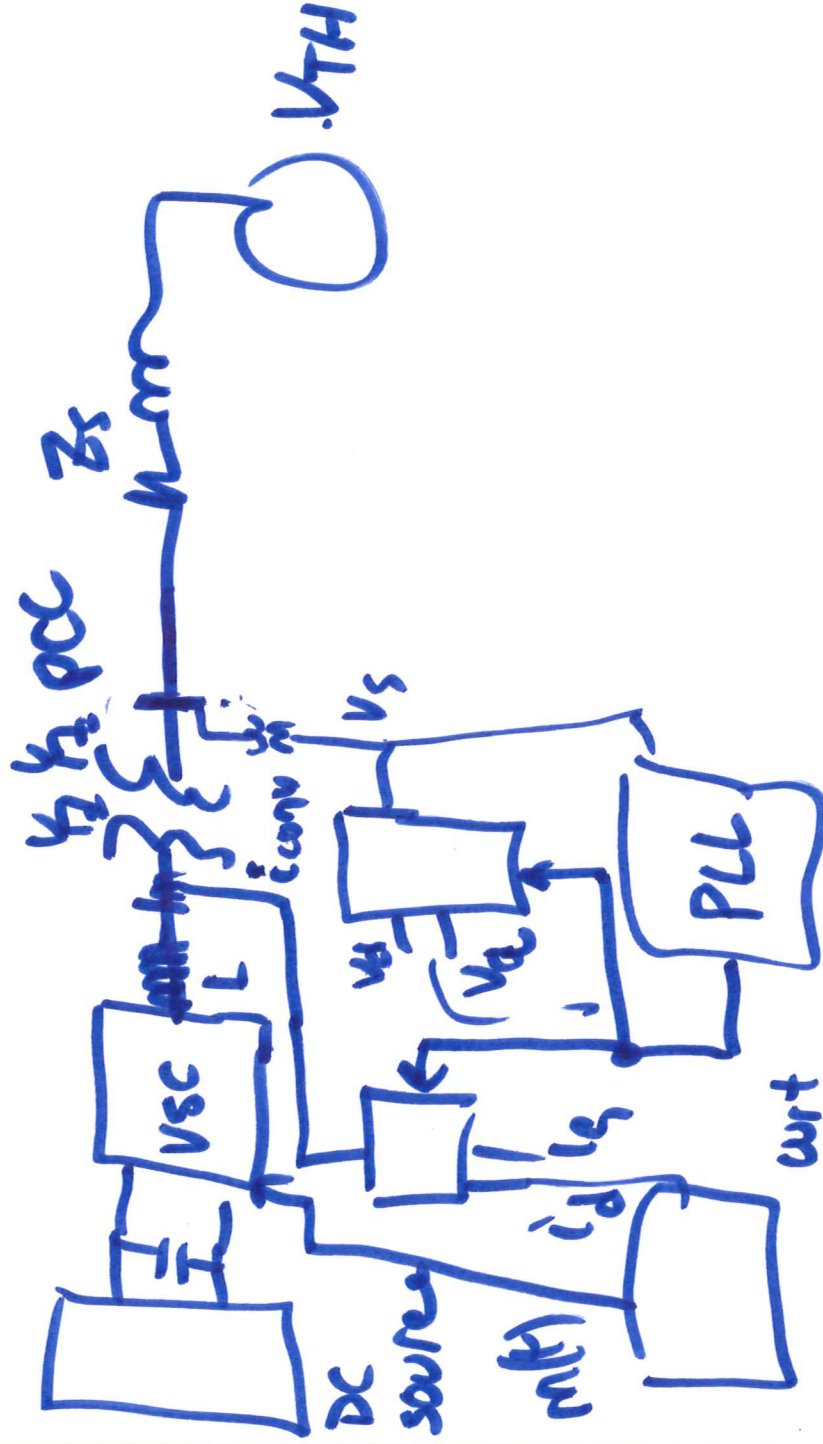


ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF
VOLTAGE SOURCE CONVERTERS

SESSION no. 43

- Current control in response to external faults




If there is a fault on ac system beyond the PCC

- V_s will be reduced on faulted phase (on phases)
- V_s will exhibit unbalance if fault is unbalanced

Impact on control?

- If stay with const P, Q
 - converter will increase currents to maintain P, Q

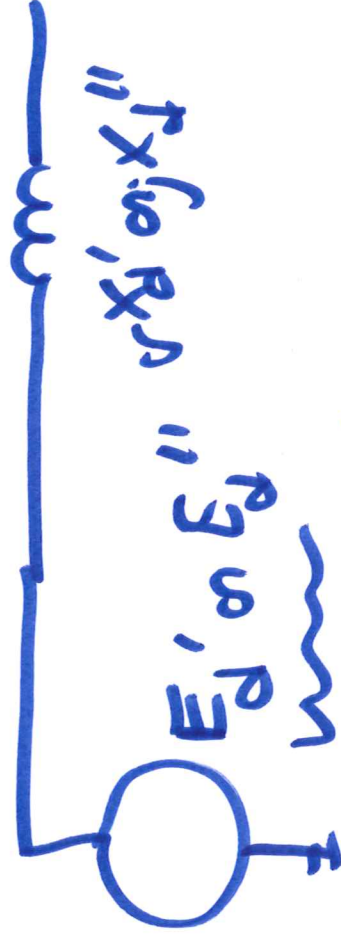- will not behave like a synchronous generator
- not a fixed magnitude / angle internal source



slowly time varying - stay at Prefault value due to field constant

- Supply large currents
- angle of currents dictated

$$I_f = \frac{E'}{Z_f}$$

↓
impedance of fault path
seen by the machine

Voltage source converter does
not do this, in any normal
control mode.

~~Low~~ Converter cap supply large currents

- Problem with synch ref frame

trans form

→ Negative sequence becomes
120 Hz oscillation in

V_d, V_q

converter control options/challenges

challenge 1. maintaining synchronism

→ PLL uses synch ref frame

→ transformation & PI control

→ regulate $V_{sq} \rightarrow 0$

and determine w.t of system

Unbalanced fault

negative sequence voltage

maps to 120Hz

→ PLL need filter to block 120Hz
in transformed domain (8.3.5)

2. Need to do some form of current regulation that does not directly respond to maintaining constant P & pf $Q=0$

3. Grid codes require Low Voltage ride through \rightarrow converter control could be designed to supply reactive power

regulate $|V|$ at PCC or fixed leading

Pf

~~3/18~~

4. Current regulation options

(A) I_d , I_q based?

- could have some unbalance in output
- some ripple at 120Hz

(B) Current regulated PWM to guarantee balanced currents (balanced references)

→ balanced currents better
for dc bus voltage ripple