

ECE 404-TD / 504-TD

ST: T&D APPLICATIONS OF  
VOLTAGE SOURCE CONVERTERS

SESSION no. 8

$$\text{m}\Omega := 10^{-3} \cdot \Omega$$

Problem 2

$$V_i := 12 \cdot \text{V} \quad V_o := 5 \cdot \text{V} \quad P_o := 100 \cdot \text{W} \quad d_A := 0.50 \quad f_s := 100 \cdot \text{kHz} \quad t_r := 100 \cdot \text{ns} \quad t_f := 100 \cdot \text{ns}$$



$$I_o := \frac{P_o}{V_o} = 20 \text{ A} \quad T_s := \frac{1}{f_s} = 10 \mu\text{s} \quad V_d := 1.00 \cdot \text{V} \quad R_{ds\_on} := 50 \cdot \text{m}\Omega \quad t_{vf} := 0 \cdot \text{s} \quad t_{vr} := 0 \cdot \text{s}$$

The problem is overspecified. The duty cycle is correct, but can be calculated from the other information.

$$V_a := d_A \cdot (V_i - I_o \cdot R_{ds\_on}) + (1 - d_A) \cdot (-V_d) = 5 \text{ V}$$


Draw the waveforms.

$$i_m := \begin{pmatrix} 0 \cdot \text{A} \\ I_o \\ I_o \\ I_o \\ I_o \\ 0 \cdot \text{A} \end{pmatrix} \quad i_d := \begin{pmatrix} I_o \\ 0 \cdot \text{A} \\ 0 \cdot \text{A} \\ 0 \cdot \text{A} \\ 0 \cdot \text{A} \\ I_o \end{pmatrix} \quad v_m := \begin{pmatrix} V_i + V_d \\ V_i + V_d \\ I_o \cdot R_{ds\_on} \\ I_o \cdot R_{ds\_on} \\ V_i + V_d \\ V_i + V_d \end{pmatrix} \quad v_d := \begin{pmatrix} -V_d \\ -V_d \\ V_i - I_o \cdot R_{ds\_on} \\ V_i - I_o \cdot R_{ds\_on} \\ -V_d \\ -V_d \end{pmatrix} \quad t_b := \begin{pmatrix} 0 \cdot \text{s} \\ t_r \\ t_r + t_{vf} \\ d_A \cdot T_s \\ d_A \cdot T_s + t_{vr} \\ d_A \cdot T_s + t_f + t_{vr} \end{pmatrix}$$

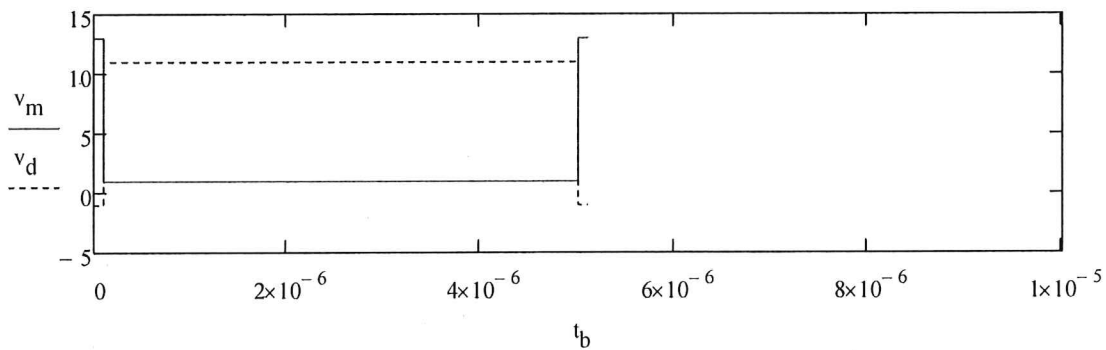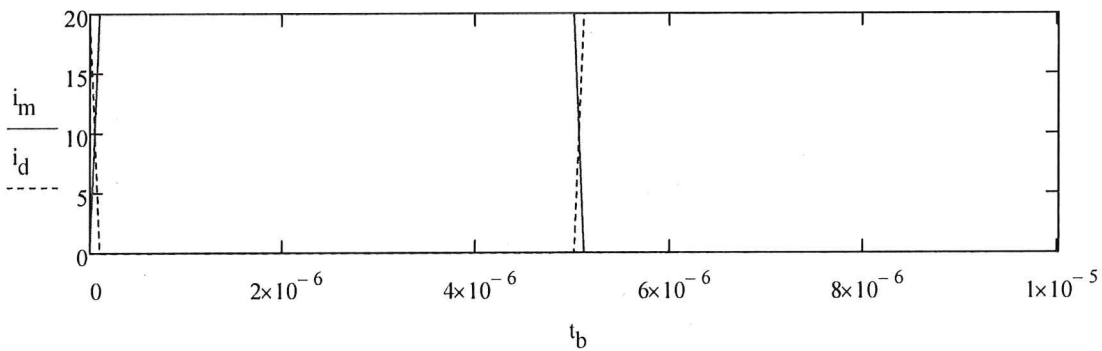

$$p_m := \begin{pmatrix} v_{m0} \cdot i_{m0} \\ v_{m1} \cdot i_{m1} \\ v_{m2} \cdot i_{m2} \\ v_{m3} \cdot i_{m3} \\ v_{m4} \cdot i_{m4} \\ v_{m5} \cdot i_{m5} \end{pmatrix} = \begin{pmatrix} 0 \\ 260 \\ 20 \\ 20 \\ 260 \\ 0 \end{pmatrix} \text{ W}$$
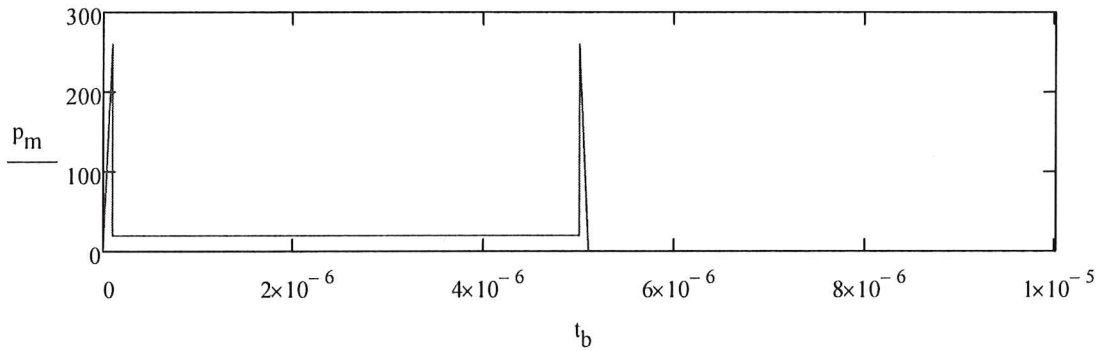
$$p_d := \begin{pmatrix} v_{d0} \cdot i_{d0} \\ v_{d1} \cdot i_{d1} \\ v_{d2} \cdot i_{d2} \\ v_{d3} \cdot i_{d3} \\ v_{d4} \cdot i_{d4} \\ v_{d5} \cdot i_{d5} \end{pmatrix} = \begin{pmatrix} -20 \\ 0 \\ 0 \\ 0 \\ 0 \\ -20 \end{pmatrix} \text{ W}$$




$$P_d := (1 - d_A) \cdot V_d \cdot I_o = 10 \text{ W}$$


Reference


$$d_A \cdot I_o^2 \cdot R_{ds\_on} = 10 \text{ W}$$


$$P_m := d_A \cdot I_o^2 \cdot R_{ds\_on} + \frac{V_i \cdot I_o}{2} \cdot (t_r + t_f) \cdot f_s = 12.4 \text{ W}$$

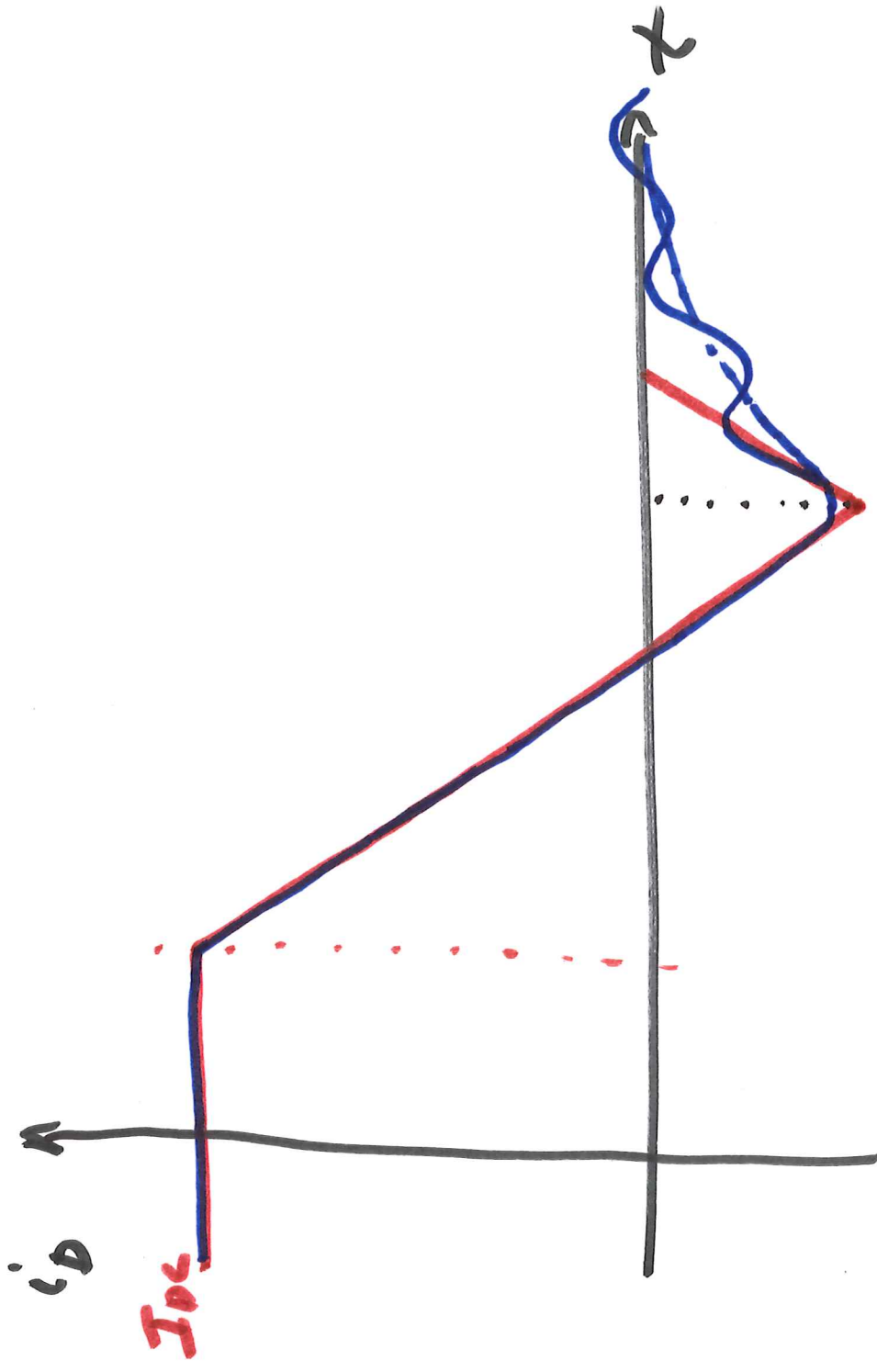
$$\frac{V_i \cdot I_o}{2} \cdot (t_r + t_f) \cdot f_s = 2.4 \text{ W}$$



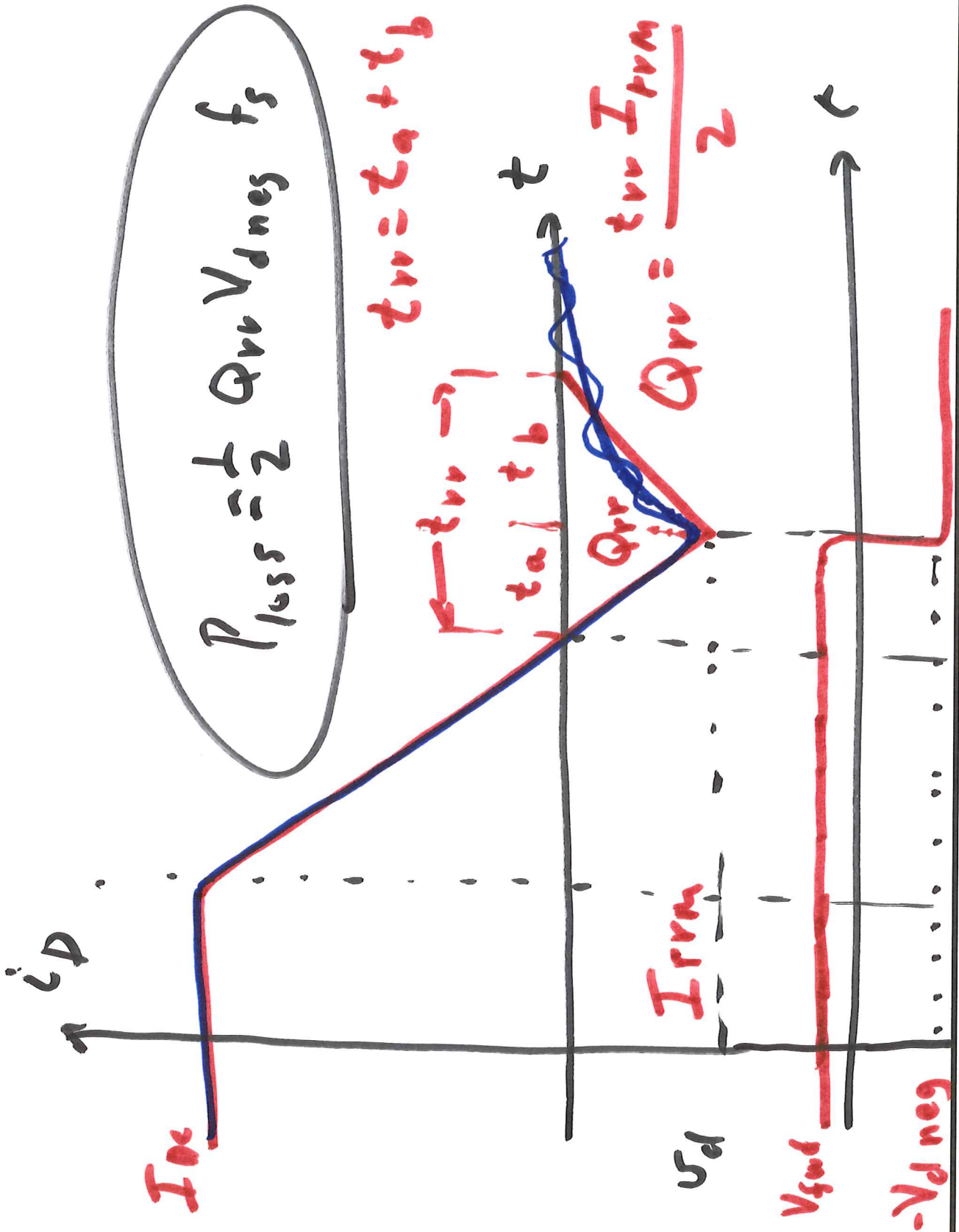

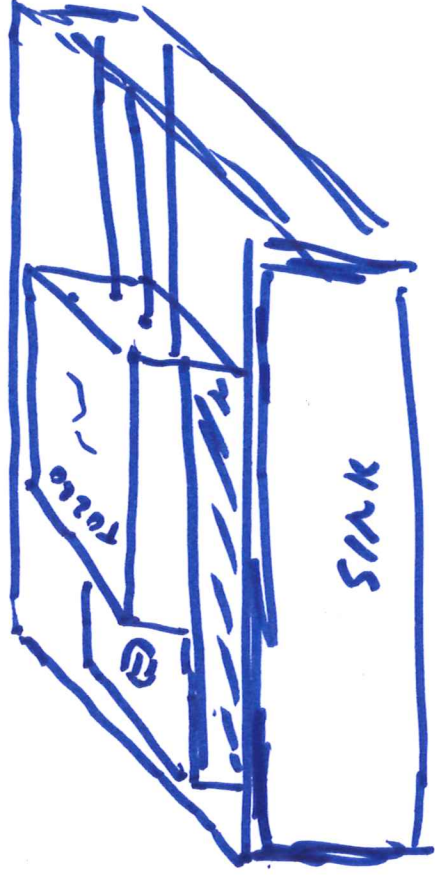

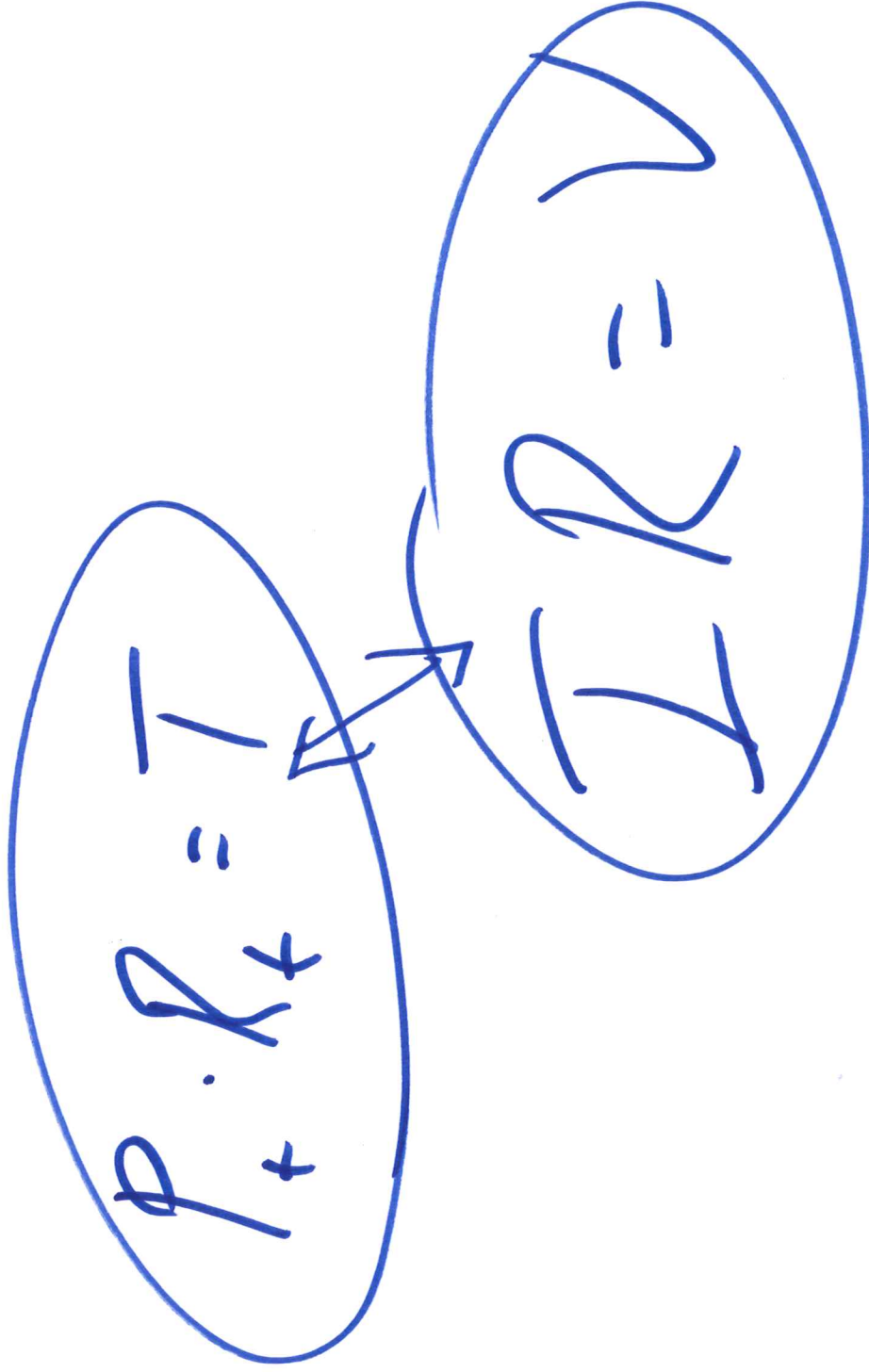

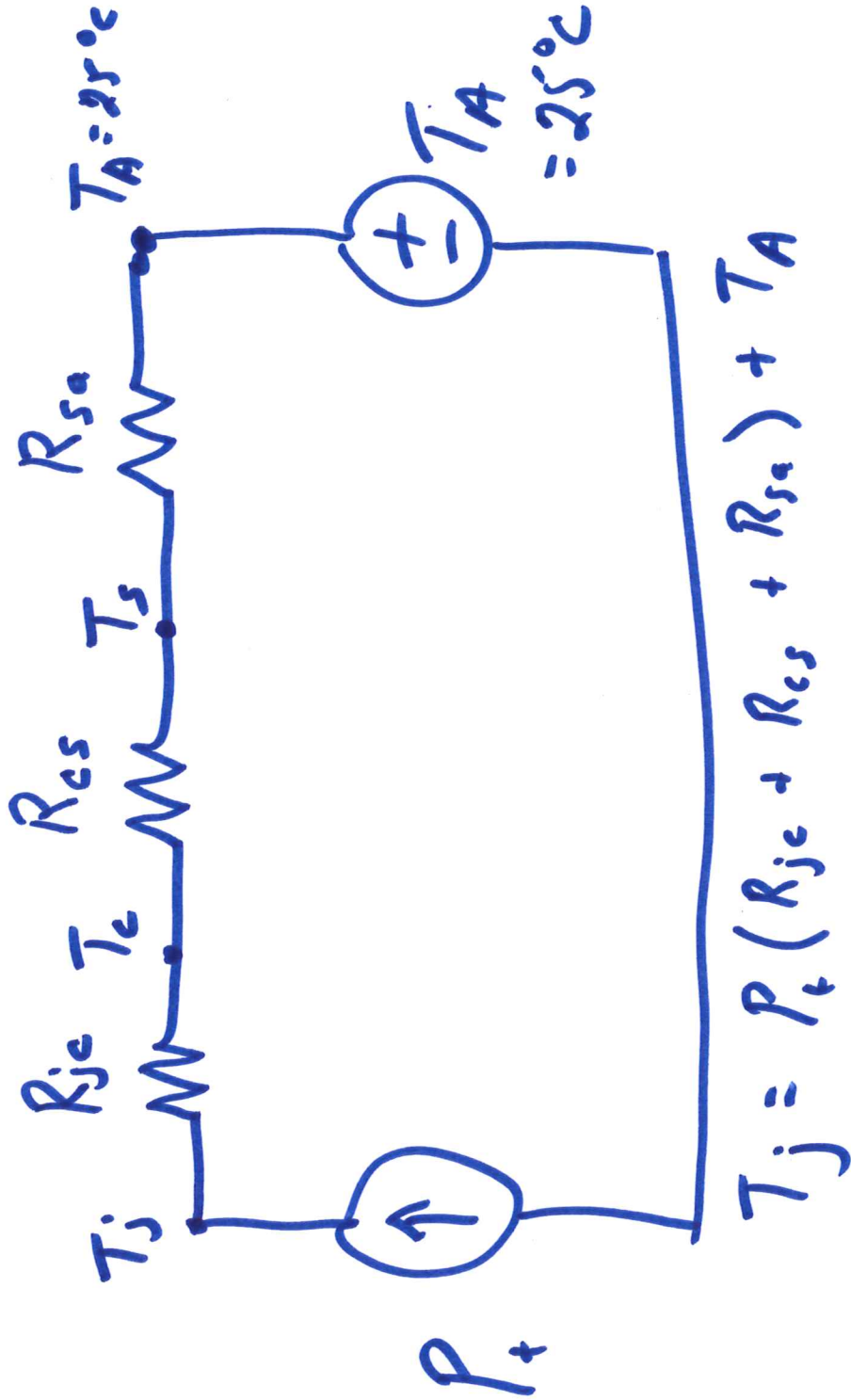

$$T_j = P_t (R_{jc} + R_{cs} + R_{sc}) + T_A$$

---

---





# IRF630 IRF630FP

N-channel 200V - 0.35Ω - 9A TO-220/TO-220FP  
Mesh overlay™ II Power MOSFET

## General features

Type	V <sub>DSS</sub>	R <sub>DS(on)</sub>	I <sub>D</sub>
IRF630	200V	<0.40Ω	9A
IRF630FP	200V	<0.40Ω	9A


- Extremely high dv/dt capability
- Very low intrinsic capacitances
- Gate charge minimized

## Description


This power MOSFET is designed using the company's consolidated strip layout-based MESH OVERLAY™ process. This technology matches and improves the performances compared with standard parts from various sources.

## Applications

- Switching application

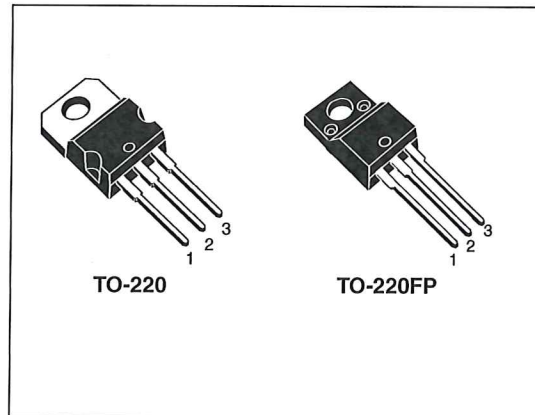

## Internal schematic diagram

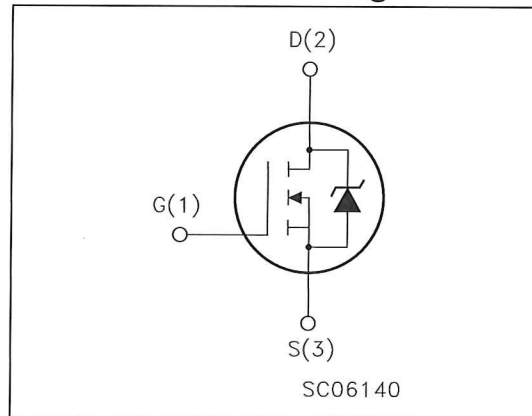

## Order codes

Part number	Marking	Package	Packaging
IRF630	IRF630	TO-220	Tube
IRF630FP	IRF630FP	TO-220FP	Tube

## Contents

<b>1</b>	<b>Electrical ratings</b> .....	<b>3</b>
<b>2</b>	<b>Electrical characteristics</b> .....	<b>4</b>
	2.1 Electrical characteristics (curves) .....	6
<b>3</b>	<b>Test circuit</b> .....	<b>9</b>
<b>4</b>	<b>Package mechanical data</b> .....	<b>10</b>
<b>5</b>	<b>Revision history</b> .....	<b>13</b>

# 1 Electrical ratings

**Table 1. Absolute maximum ratings**

Symbol	Parameter	Value		Unit
		TO-220	TO-220FP	
$V_{DS}$	Drain-source voltage ( $V_{GS} = 0$ )	200		V
$V_{DGR}$	Drain-gate voltage ( $R_{GS} = 20\text{ k}\Omega$ )	200		V
$V_{GS}$	Gate-source voltage	$\pm 20$		V
$I_D$	Drain current (continuous) at $T_C = 25^\circ\text{C}$	9	9 <sup>(1)</sup>	A
$I_D$	Drain current (continuous) at $T_C = 100^\circ\text{C}$	5.7	5.7 <sup>(1)</sup>	A
$I_{DM}^{(2)}$	Drain current (pulsed)	36	36 <sup>(1)</sup>	A
$P_{TOT}$	Total dissipation at $T_C = 25^\circ\text{C}$	75	30	W
	Derating factor	0.6	0.24	W/ $^\circ\text{C}$
$dv/dt^{(3)}$	Peak diode recovery voltage slope	5		V/ns
$V_{ISO}$	Insulation withstand voltage (DC)	--	2000	V
$T_J$ $T_{stg}$	Operating junction temperature Storage temperature	-65 to 150 150		$^\circ\text{C}$

- Limited only by maximum temperature allowed
- Pulse width limited by safe operating area
- ISD  $\leq 9\text{A}$ ,  $di/dt \leq 300\text{A}/\mu\text{s}$ ,  $V_{DD} \leq V(\text{BR})\text{DSS}$ ,  $T_J \leq T_{JMAX}$

**Table 2. Thermal data**


Symbol	Parameter	Value		Unit
		TO-220	TO-220FP	
$R_{thj-case}$	Thermal resistance junction-case Max	1.67	4.17	$^\circ\text{C}/\text{W}$
$R_{thj-a}$	Thermal resistance junction-ambient Max	62.5		$^\circ\text{C}/\text{W}$
$R_{thc-sink}$	Thermal resistance case-sink typ	0.5		$^\circ\text{C}/\text{W}$
$T_I$	Maximum lead temperature for soldering purpose	300		$^\circ\text{C}$

**Table 3. Avalanche characteristics**

Symbol	Parameter	Value	Unit
$I_{AR}$	Avalanche current, repetitive or not-repetitive (pulse width limited by $T_J$ Max)	9	A
$E_{AS}$	Single pulse avalanche energy (starting $T_J = 25^\circ\text{C}$ , $I_d = I_{AR}$ , $V_{dd} = 50\text{V}$ )	160	mJ

**TO-220 MECHANICAL DATA**

DIM.	mm.			inch		
	MIN.	TYP.	MAX.	MIN.	TYP.	MAX.
A	4.40		4.60	0.173		0.181
b	0.61		0.88	0.024		0.034
b1	1.15		1.70	0.045		0.066
c	0.49		0.70	0.019		0.027
D	15.25		15.75	0.60		0.620
E	10		10.40	0.393		0.409
e	2.40		2.70	0.094		0.106
e1	4.95		5.15	0.194		0.202
F	1.23		1.32	0.048		0.052
H1	6.20		6.60	0.244		0.256
J1	2.40		2.72	0.094		0.107
L	13		14	0.511		0.551
L1	3.50		3.93	0.137		0.154
L20		16.40			0.645	
L30		28.90			1.137	
øP	3.75		3.85	0.147		0.151
Q	2.65		2.95	0.104		0.116

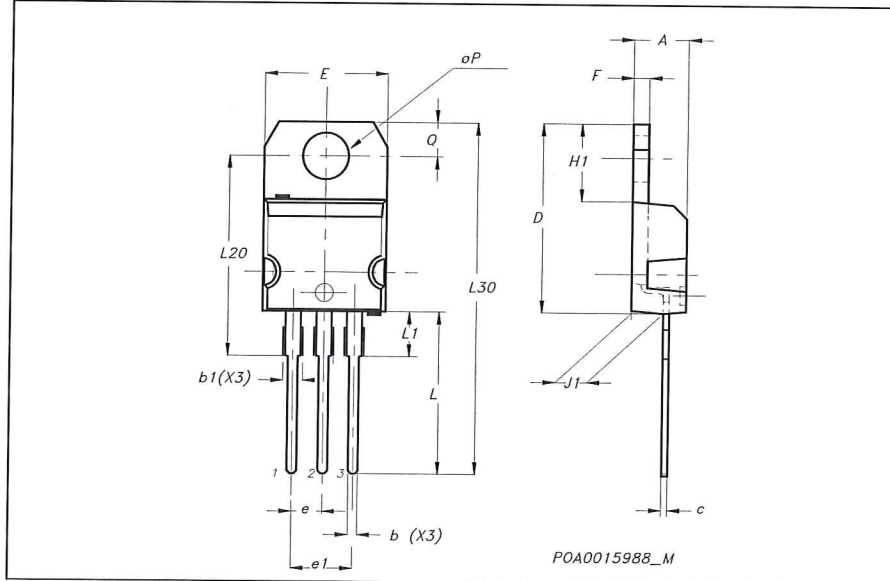

**ECE 404 / 504**

**T & D Applications of Voltage  
Sourced Converters**

**Lesson 8**

**The course materials will be on the course website, as given in the syllabus. Outreach will no longer post the same thing on their website. Your videos will still be on the Outreach website.**

# **Diode Reverse Recovery**

**Heat sinking**

**Electromechanical analogs:  
use circuit concepts to solve  
problems that have little to do  
with circuits.**

**Energy...charge**

**Power...current**

**Thermal resistance...resistance**

## **Temperature...voltage**

**We generate thermal power from our switches...MOSFETs and diodes, for example. The heat so generated must go somewhere. We want to choose that somewhere.**

**\*Heat is generated in a semiconductor junction. (pn junction).**

**\*It flows from junction through the silicon to the device's case.**

**\*From the case, the heat flows into the heat sink, should we choose to use one.**

**\*From the heat sink, the heat flows out into the ambient.**