

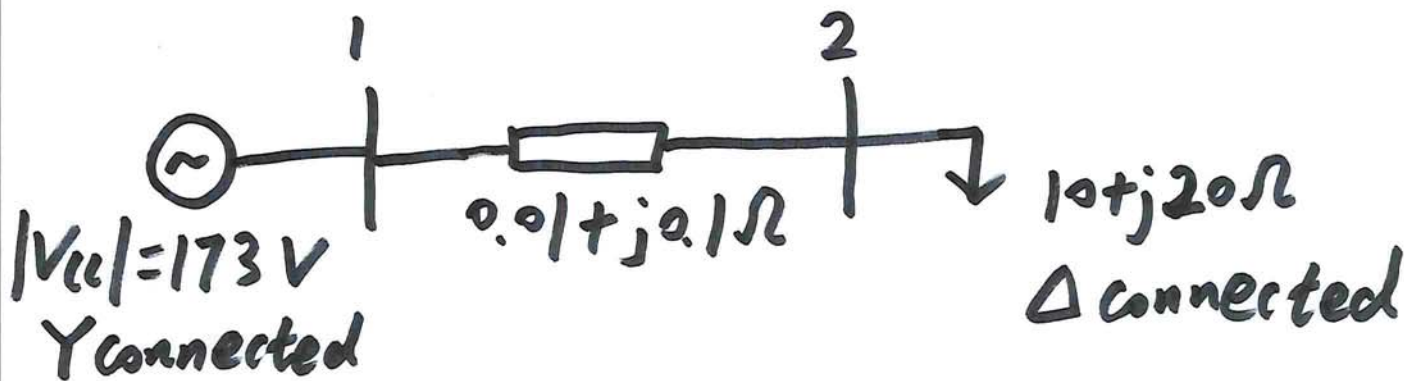
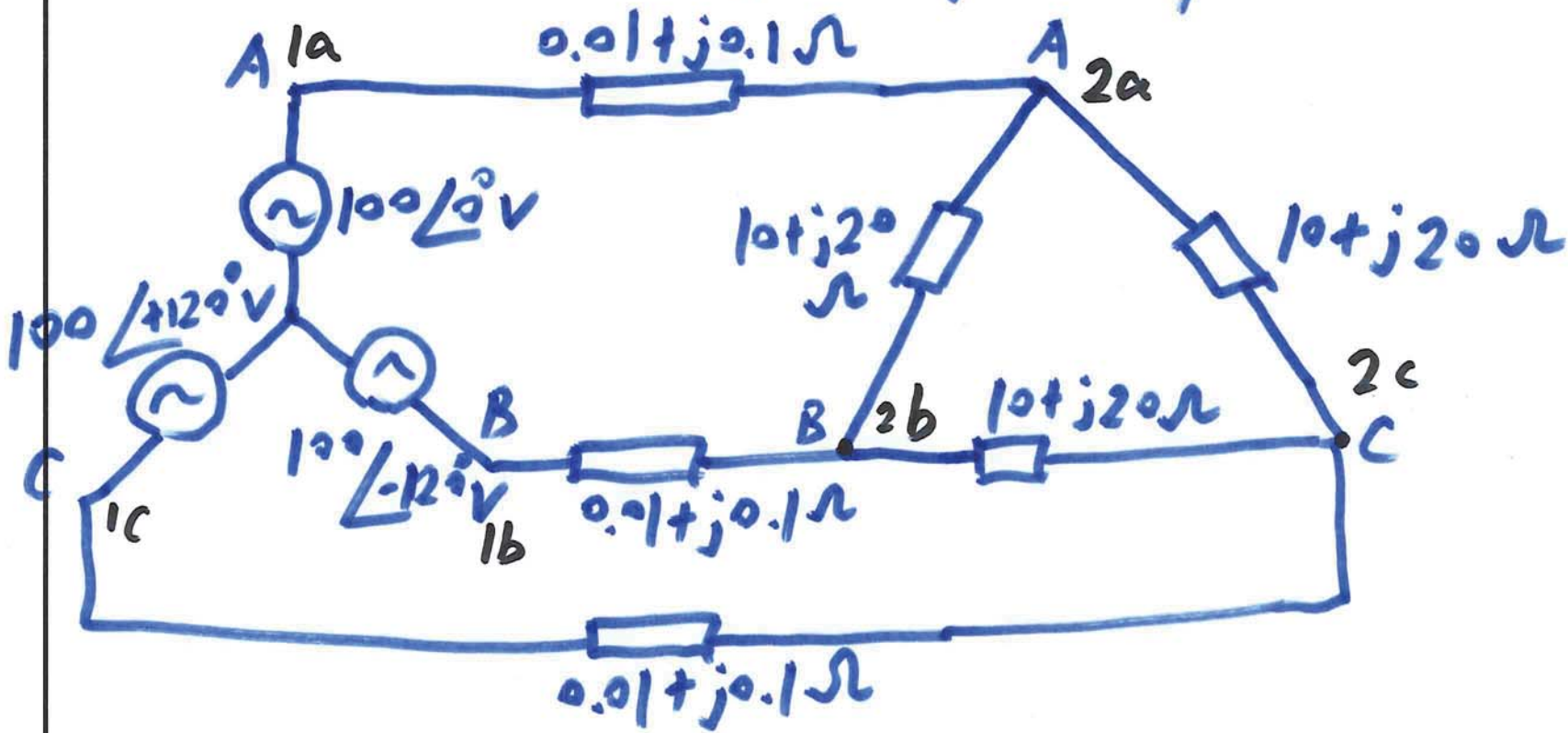
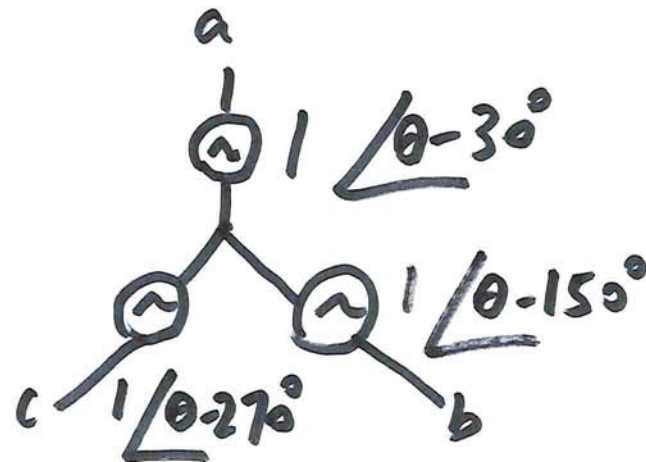
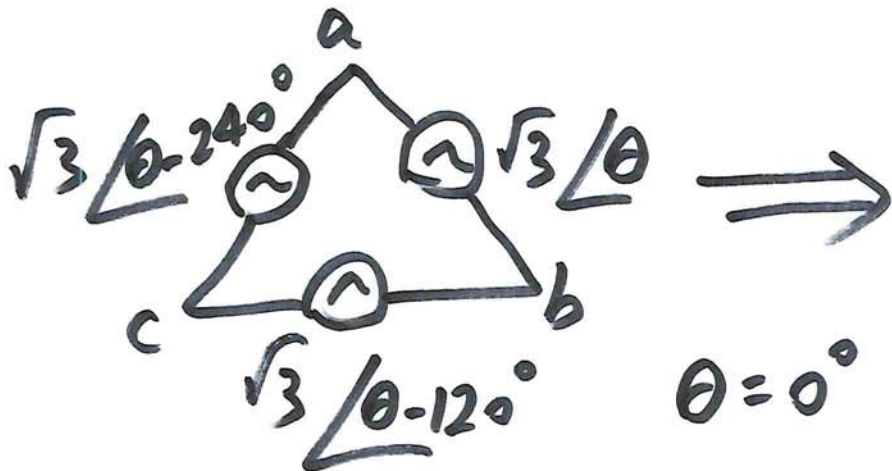


ECE 420


One-line diagram for 3-phase circuit

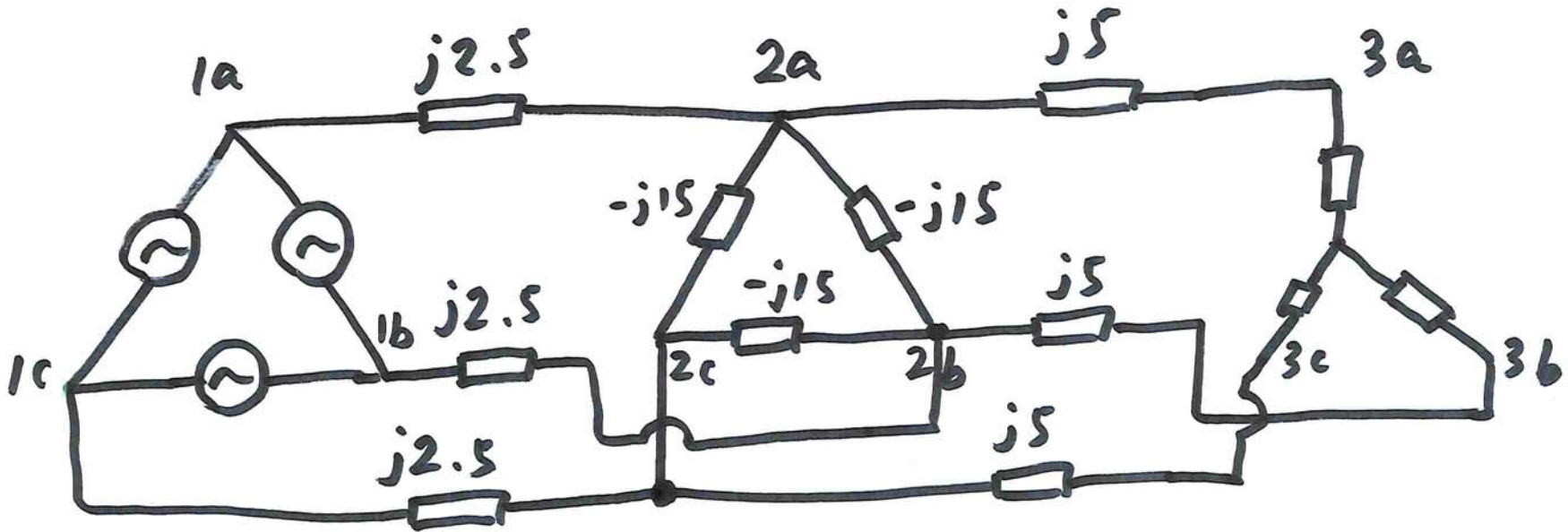

ECE 420

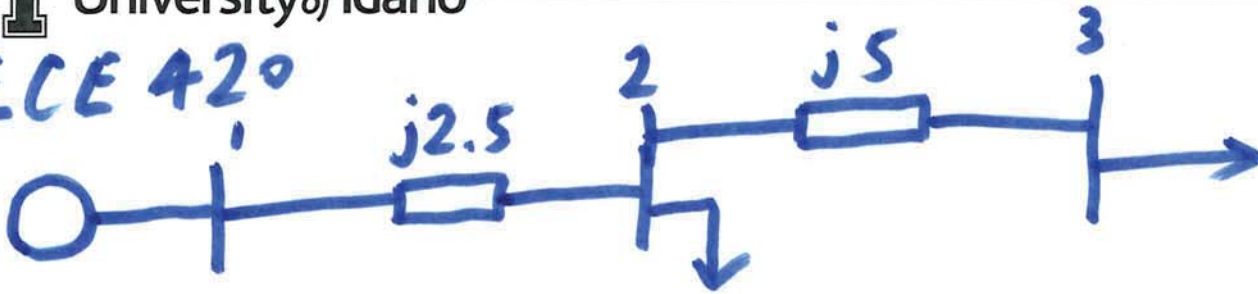

Per phase analysis for 3-phase circuits

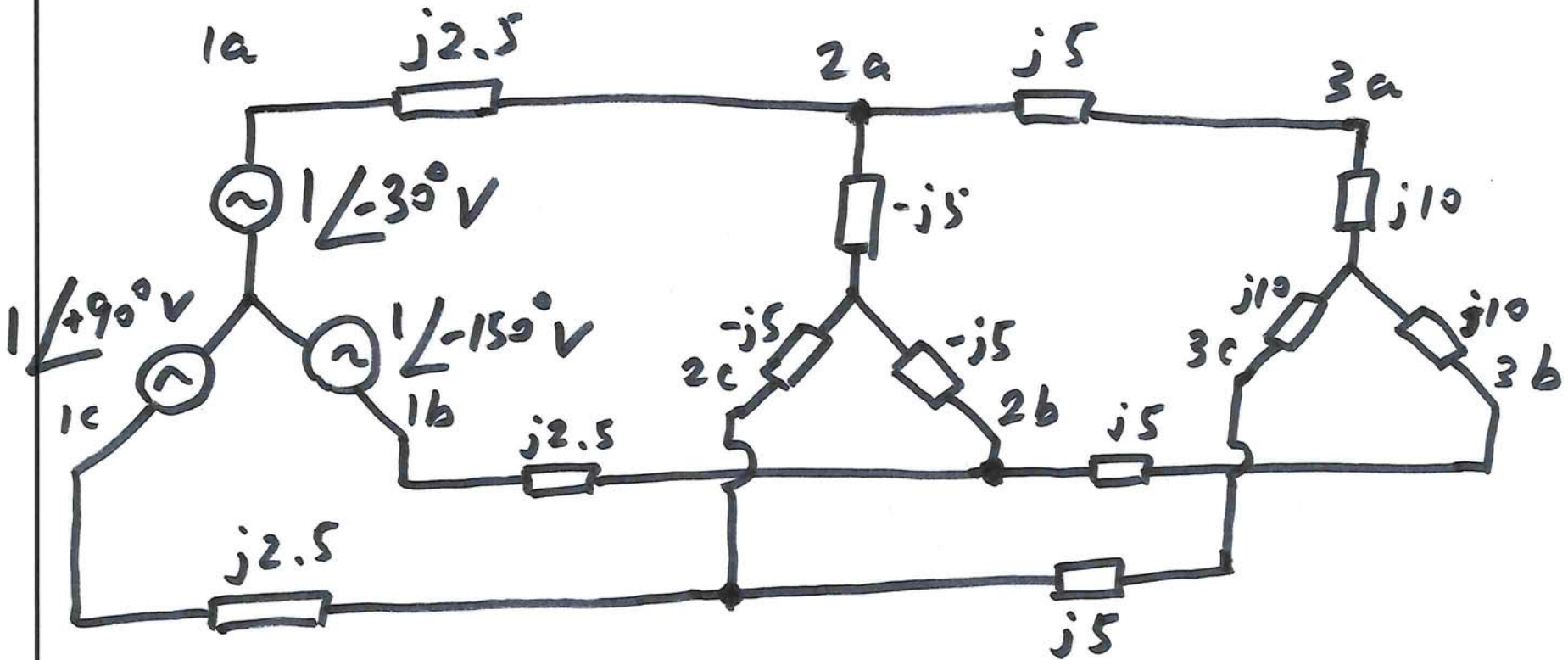

Per phase equivalent circuit

