

$Z_{bl} = 12000 \Omega$   
 $Z_{bl} = 9 \Omega$

$R_{c, \text{pu}} = \frac{160 \text{ k}\Omega}{12000 \Omega} = 13.33$   
 $R_{c, \text{pu}} = \frac{144 \Omega}{9 \Omega} = 16$

$$V_b, I_b, S_b, Z_b$$


$$V_b, I_b \Rightarrow S_b = V_b I_b$$

$$Z_b = \frac{V_b}{I_b}$$

$$S_b = 100 \text{ MVA}$$

$$V_b, S_b \Rightarrow I_b = \frac{S_b}{V_b}$$
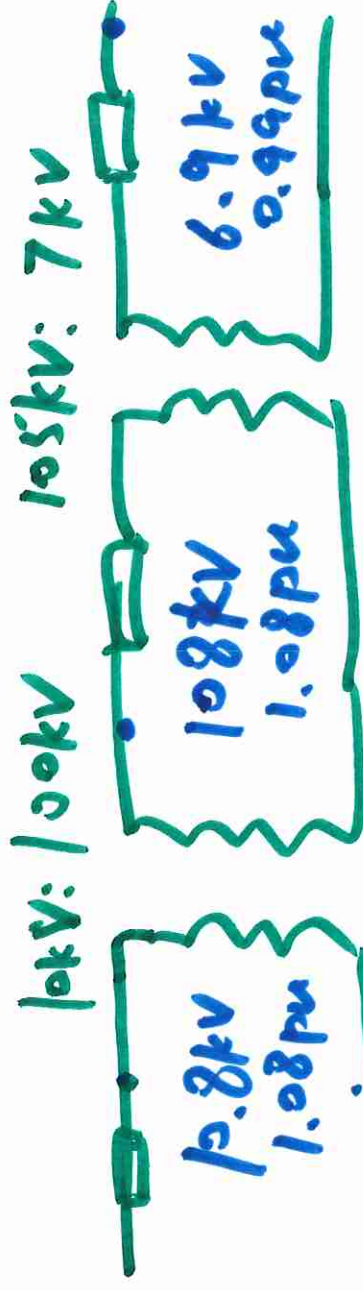
$$Z_b = \frac{V_b}{I_b} = \frac{V_b^2}{S_b}$$



$$V_{br} = 10kV$$

$$V_{br} = V_{br} \frac{10k}{10k}$$

$$V_{br} = V_{br} \frac{100k}{10k} \cdot \frac{7k}{105k}$$

$$Z_{br} = \frac{V_{br}^2}{S_b}$$

$$Z_{br} = \frac{10^2}{100}$$

$$Z_{br} = \frac{1119^2}{S_b}$$