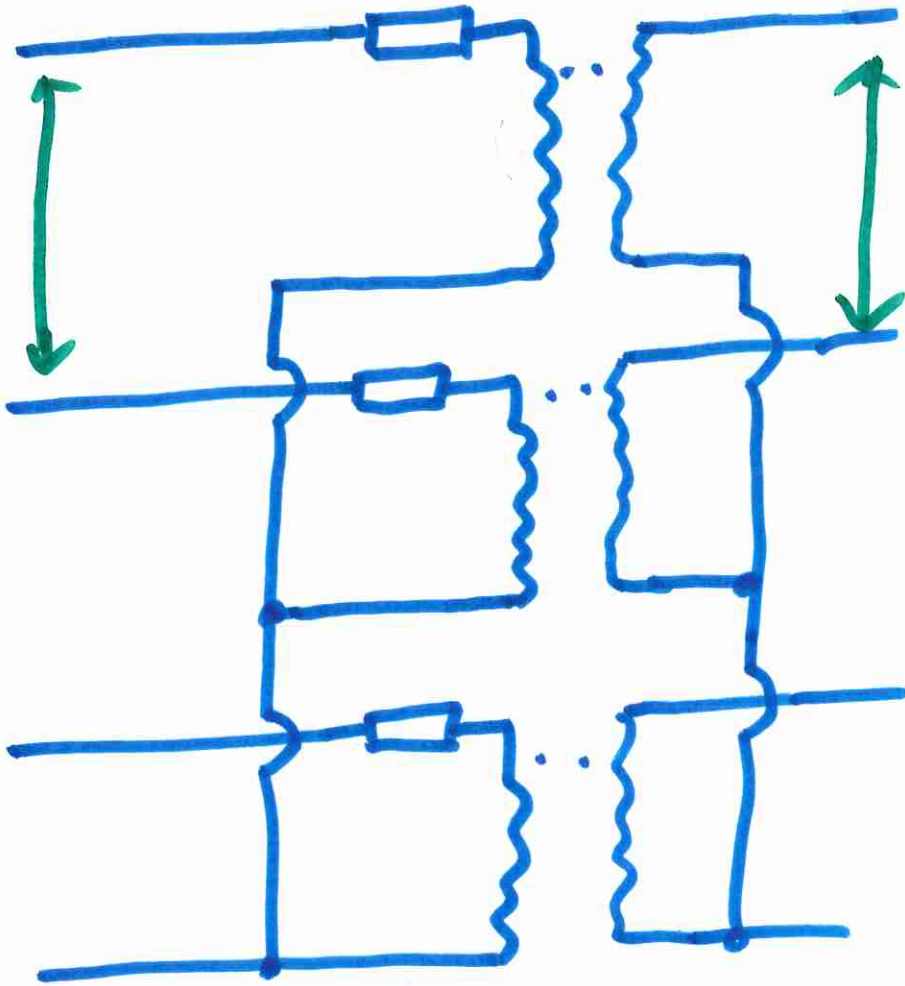


Y-Y

34.5 kV: 11 kV
line-line line-line $S_{3\phi, \text{rating}} = 600$
MVA

$R_{eq} + jX_{eq}$



$$Z_{\phi, b} = \frac{V_{\phi, b}^2}{S_{\phi, b}}$$

~~$V_{ll, b} = 34.5 \text{ kV}$~~

$$V_{ll, b} = 34.5 \text{ kV}$$

$$V_{\phi, b} = \frac{34.5}{\sqrt{3}} V_{ll, b} / \sqrt{3}$$


$$S_{\phi, b} = S_{3\phi, b} / 3$$

$$Z_{\phi, b} = \frac{(V_{ll, b} / \sqrt{3})^2}{S_{3\phi, b} / 3} = \frac{V_{ll, b}^2}{S_{3\phi, b}}$$

$\Delta-Y$

34.5 kV: 11 kV
l-l l-l

$S_{3\phi,b} = 600 \text{ MVA}$

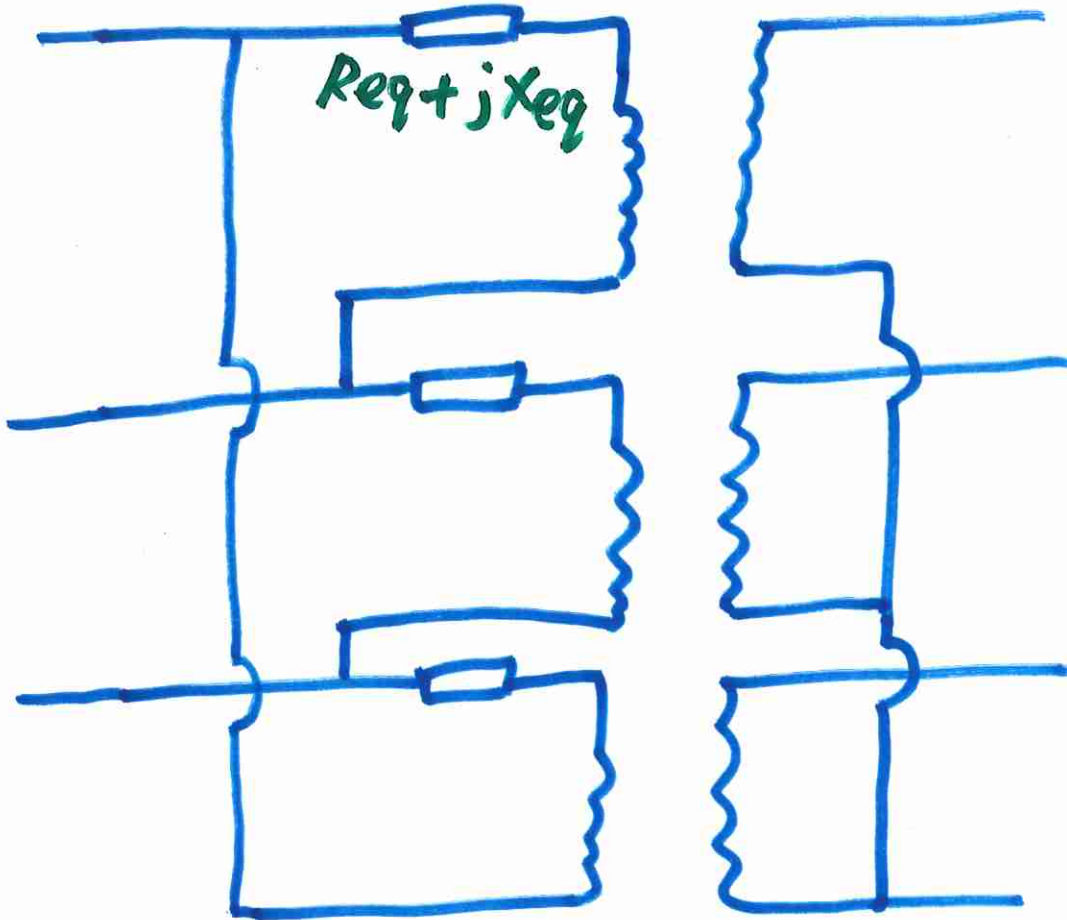

$$Z_{\phi,b} = \frac{V_{\phi,b}^2}{S_{\phi,b}}$$

$$V_{\phi,b} = V_{ll,b}$$

$$S_{\phi,b} = S_{3\phi,b} / 3$$

$$Z_{\phi,b} = \frac{V_{ll,b}^2}{S_{3\phi,b} / 3} = \frac{3 V_{ll,b}^2}{S_{3\phi,b}}$$