

ECE 523  
Symmetrical Components

Session 10

L10 1/15

ORIGIN := 0

$Z_{1\text{thev}}(0.5) = 0.2167i \text{ pu}$       $Z_1(0.5)_{4,4} = 0.2167i \text{ pu}$

The diagonal elements on the bus impedance matrix are the Thevenin impedance looking out from that node/bus in the system

**Three Phase Fault**

pre fault voltage 1.0

$I_{f3\text{ph}}(M) := \frac{V_f}{Z_1(M)_{4,4}}$

$|I_{f3\text{ph}}(0.5)| = 4.6154 \text{ pu}$

$\arg(I_{f3\text{ph}}(0.5)) = -90 \cdot \text{deg}$

From above:  $I_{3\text{ph}}(0.5) = -4.6154i$

STEP 1

$\Delta V1(M) := Z_1(M) \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{f3\text{ph}}(M) \end{pmatrix}$

STEP 2

$\begin{pmatrix} -0.1332 + 0.0769i \\ -0.2308 \\ -0.6154 \\ -0.3553 + 0.2051i \\ -1 \end{pmatrix}$


fault current

$|\Delta V1(0.5)| = \begin{pmatrix} 0.1538 \\ 0.2308 \\ 0.6154 \\ 0.4103 \\ 1 \end{pmatrix} \cdot \text{pu}$


$\arg(\Delta V1(0.5)) = \begin{pmatrix} 150 \\ 180 \\ -180 \\ 150 \\ -180 \end{pmatrix} \cdot \text{deg}$



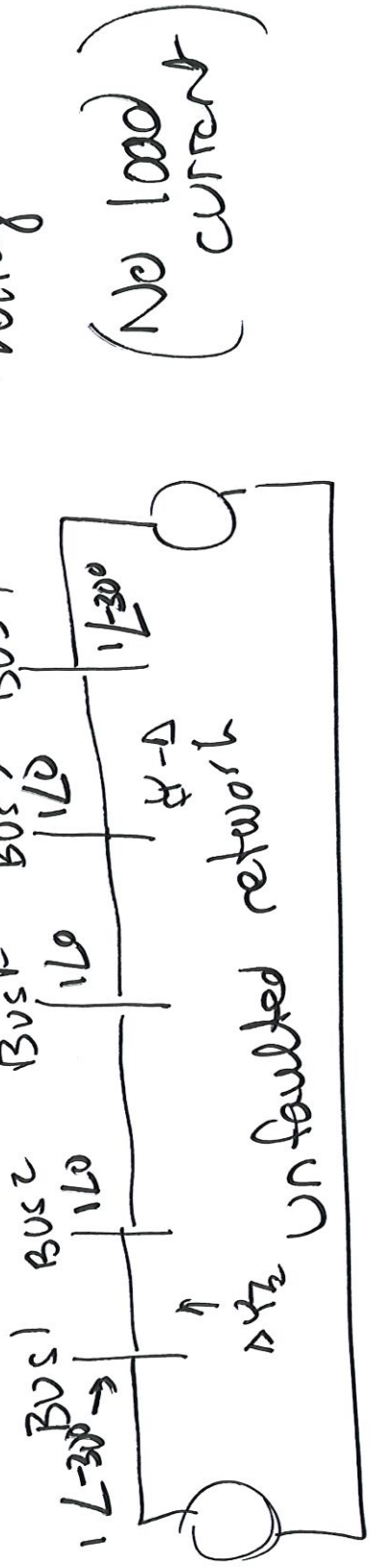Prefault (un faulted network) ← Prefault voltage



Pure faulted network

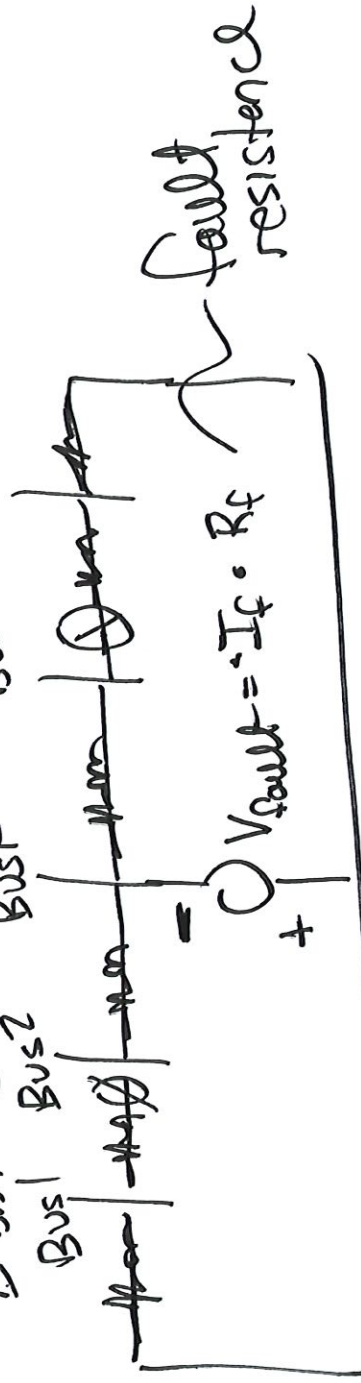

$V_{\text{new}} = V_{\text{prefault}} + \Delta V_i \rightarrow \text{Depend on transfer impedances (all depend } Z_{BUS})$

L10 3/15 LA 17/17

**Z BUS Matrix Approach**

Easiest Approach is to Create Ybus Matrix. Modified for Fault Calculations:

Transformer Phase Shift:

$$Y_1(M) := \begin{bmatrix} \frac{1}{jX_{G11}} + \frac{1}{Z_{T11}} & \frac{-1 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T11}} & 0 & 0 & 0 & 0 \\ \frac{-1 \cdot e^{j \cdot 30 \text{deg}}}{Z_{T11}} & \frac{1}{Z_{T11}} + \frac{1}{M \cdot Z_{L11}} & 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{Z_{T21}} + \frac{1}{(1-M) \cdot Z_{L11}} & \frac{1}{Z_{T21}} & \frac{-1 \cdot e^{j \cdot 30 \text{deg}}}{Z_{T21}} & 0 \\ 0 & 0 & \frac{-1 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T21}} & \frac{1}{Z_{T21}} + \frac{1}{jX_{G21}} & 0 & 0 \\ 0 & \frac{-1}{M \cdot Z_{L11}} & \frac{-1}{(1-M) \cdot Z_{L11}} & \frac{-1}{(1-M) \cdot Z_{L11}} & 0 & \frac{1}{M \cdot Z_{L11}} + \frac{1}{(1-M) \cdot Z_{L11}} \end{bmatrix}$$

BUS 1    BUS 2    BUS 3    BUS 4    BUS F

BUS 1    BUS 2    BUS 3    BUS 4    BUS F

$[I] = [Y][V]$

$Z_1(M) := Y_1(M)^{-1}$

$$Z_1(0.5) = \begin{bmatrix} 0.0474i & 0.0231 + 0.04i & 0.0103 + 0.0178i & 0.0137i & 0.0167 + 0.0289i \\ -0.0231 + 0.04i & 0.0692i & 0.0308i & -0.0103 + 0.0178i & 0.05i \\ -0.0103 + 0.0178i & 0.0308i & 0.2359i & -0.0786 + 0.1362i & 0.1333i \\ 0.0137i & 0.0103 + 0.0178i & 0.0786 + 0.1362i & 0.1937i & 0.0444 + 0.077i \\ -0.0167 + 0.0289i & 0.05i & 0.1333i & -0.0444 + 0.077i & 0.2167i \end{bmatrix} \quad \begin{matrix} I \\ V = [Z] I \end{matrix}$$

Z BUS 4.4

L10 4/15

- For now, assume initially flat voltage profile, but with transformer phase shifts added

$$V1(M) := \begin{pmatrix} 1.0e^{-j \cdot 30 \text{deg}} \\ 1.0 \\ 1.0 \\ 1.0 \cdot e^{-j \cdot 30 \text{deg}} \\ 1.0 \end{pmatrix} + \Delta V1(M) \quad V1(0.5) = \begin{pmatrix} 0.7328 - 0.4231i \\ 0.7692 \\ 0.3846 \\ 0.5107 - 0.2949i \\ 0 \end{pmatrix}$$

low side

$$V_{B1}(M) := V1(M)_0 \quad |V_{B1}(0.5)| = 0.8462 \text{ pu} \quad \arg(V_{B1}(0.5)) = -30 \text{ deg}$$

$$V_{B4}(M) := V1(M)_3 \quad |V_{B4}(0.5)| = 0.5897 \text{ pu} \quad \arg(V_{B4}(0.5)) = -30 \text{ deg}$$

- Both balanced 3 phase.

$$I = \frac{V_i - V_j}{Z_{ij}}$$

From above:

$$|V_{bus1}(0.5)| = 0.8462 \quad \arg(V_{bus1}(0.5)) = -30 \text{ deg}$$

$$|V_{bus4}(0.5)| = 0.5897 \quad \arg(V_{bus4}(0.5)) = -30 \text{ deg}$$

$$|I_S(0.5)| = 3.0769 \text{ pu} \quad \arg(I_S(0.5)) = -120 \text{ deg}$$

$$|I_R(0.5)| = 1.5385 \text{ pu} \quad \arg(I_R(0.5)) = -120 \text{ deg}$$

STEPS

$$I_S(M) := \frac{V_S \cdot e^{-j \cdot 30 \text{deg}} - V1(M)_0}{jX_{G11}}$$

$$I_R(M) := \frac{V_R \cdot e^{-j \cdot 30 \text{deg}} - V1(M)_3}{jX_{G21}}$$

Can calculate current in any branch

L10 5/13

$$|I_{srcS}(0.5)| = 3.0769 \quad \arg(I_{srcS}(0.5)) = -120 \cdot \text{deg}$$

$$|I_{srcR}(0.5)| = 1.5385 \quad \arg(I_{srcR}(0.5)) = -120 \cdot \text{deg}$$

Alternate:


$$I_{SA}(M) := \frac{V1(M)_0 - V1(M)_1 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T11}} \quad |I_{SA}(0.5)| = 3.0769 \cdot \text{pu} \quad \arg(I_{SA}(0.5)) = -120 \cdot \text{deg}$$

$$I_{RA}(M) := \frac{V1(M)_3 - V1(M)_2 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T21}} \quad |I_{RA}(0.5)| = 1.5385 \cdot \text{pu} \quad \arg(I_{RA}(0.5)) = -120 \cdot \text{deg}$$

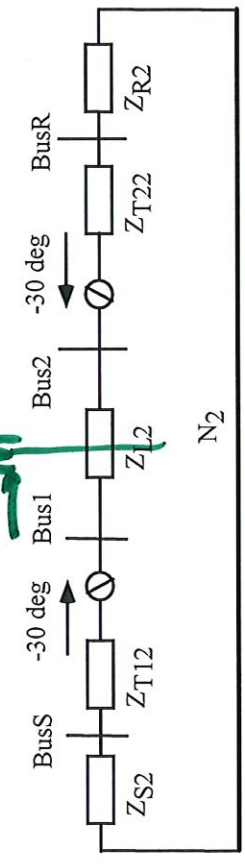**Negative Sequence Ybus**

- All of the impedance values are the same in this case.
- Only change is in the Δ-Y phase shifts.
- Equivalent circuit looks the same, but no sources.

- Negative sequence per unit, per phase, equivalent circuit:



L10 6/15

opposite pos  
of sep.

$$Y_2(M) := \begin{bmatrix} \frac{1}{jX_{G12}} + \frac{-1 \cdot e^{j \cdot 30 \text{deg}}}{Z_{T12}} & 0 & 0 & 0 \\ \frac{-1 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T12}} & \frac{1}{Z_{T12}} + \frac{1}{M \cdot Z_{L12}} & 0 & \frac{-1}{M \cdot Z_{L12}} \\ 0 & 0 & \frac{1}{Z_{T22}} + \frac{1}{(1-M) \cdot Z_{L12}} & \frac{-1 \cdot e^{-j \cdot 30 \text{deg}}}{Z_{T22}} \\ 0 & 0 & \frac{-1 \cdot e^{j \cdot 30 \text{deg}}}{Z_{T22}} & \frac{1}{Z_{T22}} + \frac{1}{jX_{G22}} \\ 0 & \frac{-1}{M \cdot Z_{L12}} & \frac{-1}{(1-M) \cdot Z_{L12}} & \frac{1}{M \cdot Z_{L12}} + \frac{1}{(1-M) \cdot Z_{L12}} \end{bmatrix}$$

$$Z_2(M) := Y_2(M)^{-1}$$

$$Z_2(0.5) = \begin{bmatrix} 0.0474i & -0.0231 + 0.04i & -0.0103 + 0.0178i & 0.0137i & -0.0167 + 0.0289i \\ 0.0231 + 0.04i & 0.0692i & 0.0308i & 0.0103 + 0.0178i & 0.05i \\ 0.0103 + 0.0178i & 0.0308i & 0.2359i & 0.0786 + 0.1362i & 0.1333i \\ 0.0137i & -0.0103 + 0.0178i & -0.0786 + 0.1362i & 0.1937i & -0.0444 + 0.077i \\ 0.0167 + 0.0289i & 0.05i & 0.1333i & 0.0444 + 0.077i & 0.2167i \end{bmatrix}$$



Don't do  $Z_c(0)$  or  $Z_c(1)$   $m = 10^{-10}$   
 $m=1$  or  $m=0$  causes a divide by 0  $m = 0.99999...$

L10 7/15

$$\underline{Y_0(M)} := \begin{bmatrix} \frac{1}{Z_{G10}} & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{Z_{T10}} + \frac{1}{M \cdot Z_{L10}} & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{Z_{T20}} + \frac{1}{(1-M) \cdot Z_{L10}} & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{Z_{G20}} & 0 \\ 0 & \frac{-1}{M \cdot Z_{L10}} & \frac{-1}{(1-M) \cdot Z_{L10}} & 0 & \frac{1}{M \cdot Z_{L10}} + \frac{1}{(1-M) \cdot Z_{L10}} \end{bmatrix}$$

$$Z_0(M) := Y_0(M)^{-1}$$

$$Z_0(0.5) = \begin{pmatrix} 2.5 + 0.025i & 0 & 0 & 0 & 0 \\ 0 & 0.0247i & 0.0017i & 0 & 0.0132i \\ 0 & 0.0017i & 0.1243i & 0 & 0.063i \\ 0 & 0 & 0 & 13.3333 + 0.0667i & 0 \\ 0 & 0.0132i & 0.063i & 0 & 0.4881i \end{pmatrix}$$


$$Z_{0\text{thev}}(0.5) = 0.4881\text{ipu}$$

$$Z_0(0.5)_{4,4} = 0.4881\text{ipu}$$


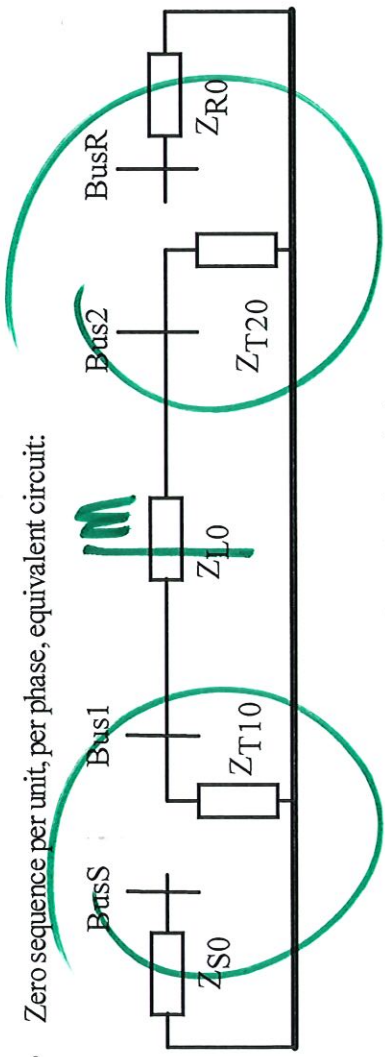
### Zero Sequence Ybus

- Impedance values differ
- Model the transformer zero sequence connections
- Different looking equivalent circuit.
- Zero sequence per unit, per phase, equivalent circuit:



- Thevenin equivalent impedance by brute force circuit analysis:

$$Z_{0left}(M) := Z_{T10} + Z_{L10} \cdot M$$

- Note that generator impedances are not present due to transformer connections

$$Z_{0right}(M) := Z_{L10} \cdot (1 - M) + Z_{T20}$$


$$Z_{0equiv}(M) := \left[ \frac{1}{Z_{T10} + Z_{L10} \cdot M} + \frac{1}{Z_{L10} \cdot (1 - M) + Z_{T20}} \right]^{-1}$$

- More compactly:  $Z_{0thev}(M) := \left( \frac{1}{Z_{0left}(M)} + \frac{1}{Z_{0right}(M)} \right)^{-1}$

L10 9/15

### ECE 523: Fault Analysis Using Powerworld

*Slack bus*

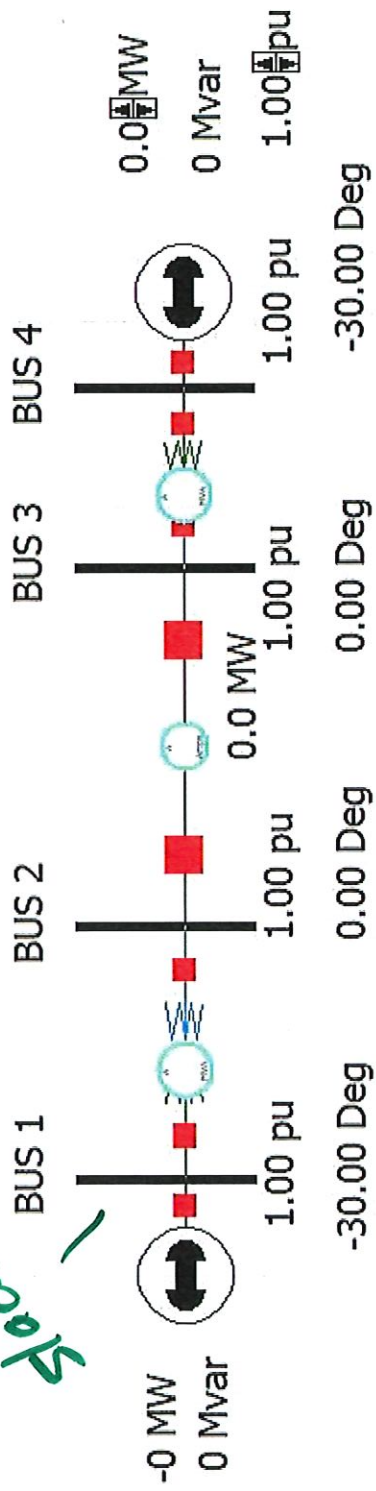

- Set slack bus angle such that the faulted line is at 30 deg

Maintainer \_\_\_\_\_

Bus Information    Display    Attached Device

Bus Voltage		
Voltage (p.u.)	1.0000	
Angle (degrees)	-30.000	

System Slack Bus

L10 10/15

- Transformer phase shift

Branch Options

Transformer Number	From Bus	To Bus	Circuit	Find
1	BUS 1	2	1	Finc
Name	BUS 1	BUS 2		Finc
Area Name	1 (1)	1 (1)		Finc
Nominal kV	13.80	115.0		<input checked="" type="checkbox"/> Fror
Labels ...	no labels		<input checked="" type="checkbox"/> Default Owner	

Display Parameters Transformer Control Fault Info Owner, Area, Zone, Sub Cl

Transformer Information

Off-nominal Turns Ratio	1.00000	Automatic Control Type	No Automatic Control
Phase Shift (degrees)	-30.0	Transformer Control is	No Automatic Control

Edit Integer Tap Positions

Change Automatic Control Options...

- Transformer connection

L10 11/15

Transformer

From Bus: 1 To Bus: 2 Circuit: 1

Number: 1

Name: BUS 1

Area Name: 1 (1)

Nominal kV: 13.80

Find By Numbers Find By Names Find ...

From End Metered

Default Owner (Same as From Bus)

Labels ... no labels

Display Parameters Transformer Control Fault Info Owner, Area, Zone, Sub Custom Stability Geography

Treat as open circuit in zero sequence

Zero Sequence Impedance

R:	0.000000
X:	0.025000
C:	0.000000

Ground Impedance

R:	0.000000
X:	0.000000
R2:	0.000000
X2:	0.000000

Secondary Zero Sequence Imp

R2:	0.000000
X2:	0.000000

Zero Sequence Line Shunt Admittance

From G:	0.000000
From B:	0.000000
To G:	0.000000
To B:	0.000000

Neutral Impedance

Neutral R:	0.000000
Neutral X:	0.000000

R and X are values on the From side or R2 and X2 are values on the To side

Configuration: Delta-Grounded Wye

Note: Configuration only determines the grounding of the transformer windings. Phase shifters must be entered as part of the Transformer Control data.

- Getting fault Ybus: (fault at 50% of the line)

L10 12/15

ECE 523:  
Symmetrical Components

Name	Bus 1	Bus 2	Bus 3	Bus 4	Bus 5
BUS 1	0.00 - j60.00	20.00 + j34.64			
BUS 2	-20.00 + j34.64	0.00 - j44.00	0.00 + j0.00		-0.00 + j4.00
BUS 3	0.00 + j0.00	0.00 + j0.00	0.00 - j11.50	-3.75 + j6.50	-0.00 + j4.00
BUS 4			3.75 + j6.50	0.00 - j11.25	
FaultPt		-0.00 + j4.00	-0.00 + j4.00		0.00 - j8.00

neg seq bus volt

seq


Bus voltages

Name	Phase Volt A	Phase Ang A	Phase Volt B	Phase Ang B	Phase Volt C	Phase Ang C	Seq. Volt +	Seq. Angle +	Seq. Volt -	Seq. Angle -	Seq. Volt 0	Seq. Angle 0
BUS 1	0.84615	-30	0.84615	-150	0.84615	90	0.8462	-30	0	90	0	90
BUS 2	0.76923	0	0.76923	-120	0.76923	120	0.7692	0	0	90	0	90
BUS 3	0.38462	0	0.38462	-120	0.38462	120	0.3846	0	0	90	0	90
BUS 4	0.58974	-30	0.58974	-150	0.58974	90	0.5897	-30	0	90	0	90
FaultPt	0	0	0	-120	0	120	0	0	0	90	0	90

faulted branch replaced

Branch currents:

From Name	To Name	Phase Cur A From	Phase Ang A From	Phase Cur B From	Phase Ang B From	Phase Cur C From	Phase Ang C From	Seq. Cur + From	Seq. Angle + From	Seq. Cur - From	Seq. Angle - From	Seq. Cur 0 From	Seq. Angle 0 From
BUS 1	BUS 2	3.07692	-120	3.07692	3.07692	3.07692	3.07692	3.07692	0	3.07692	0	3.07692	-119.99998
BUS 2	BUS 3	0	0	0	0	0	0	0	0	0	0	0	0
BUS 2	FaultPt	3.07692	-90	3.07692	3.07692	3.07692	3.07692	3.07692	30	3.07692	30	3.07692	-89.99996
BUS 4	BUS 3	1.53846	-120	1.53846	1.53846	1.53846	1.53846	1.53846	0	1.53846	0	1.53846	-119.99995
FaultPt	BUS 3	1.53846	90	1.53846	1.53846	1.53846	1.53846	1.53846	-150	1.53846	-150	1.53846	90.00004

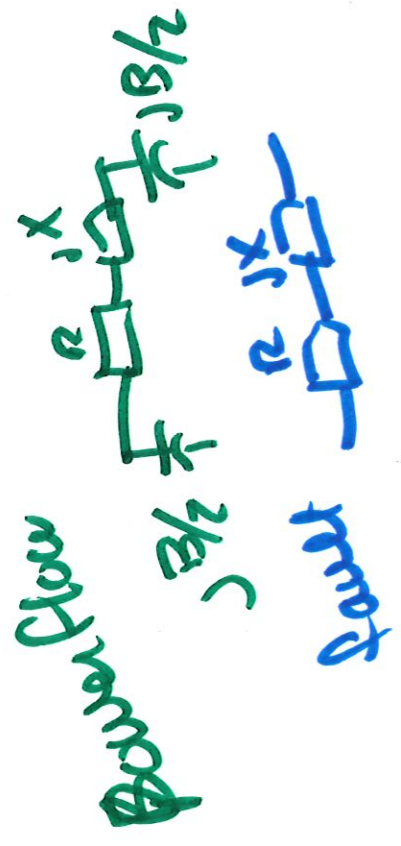

# Analysis of unbalanced faults

1. Shunt faults
  - with or w/o fault resistance
  - with and w/o load flow
2. Series faults
3. Simultaneous faults

# Conducting the Analysis

- Pos, neg, zero sequence equiv circuits

$$\rightarrow Y_{BUS1}, Y_{BUS2}, Y_{BUS0} \rightarrow \underbrace{\quad}_{Z_{BUS}} \rightarrow (Y_{BUS2})^{-1} = Z_{BUS}$$

- Perform all steps of fault analysis in sequence domain  $\rightarrow$  results back to ABC

# Each fault type

→ Boundary conditions for that fault

→ convert to sequence domain

→ find formula/equiv ckt for fault current calculation in sequence domain

→ once we have fault currents

do circuit analysis for rest of ckt in sequence domain