


Unbalanced Fault Analysis Examples

pu := 1 MVA := 1000kW

$$a := 1e^{j \cdot 120\text{deg}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

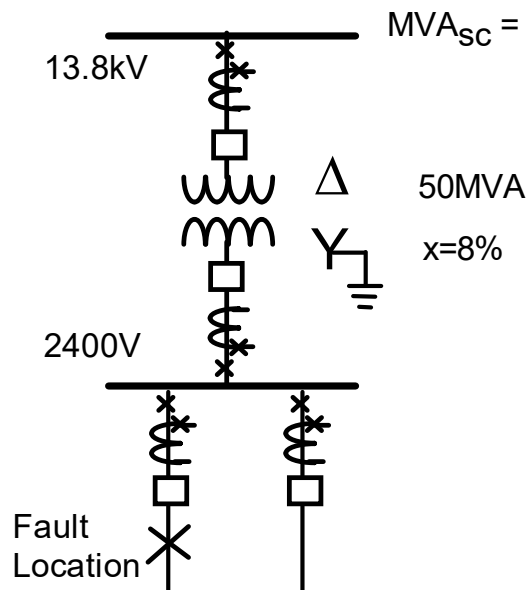Compare the per unit phase currents seen on the HV side of the transformer below with those seen by at the fault location for three phase, SLG and LL faults the left side feeder. Assume wye connected CT's.



Use transformer ratings as the per unit base.

$$V_{hi} := 13.8\text{kV} \quad V_{lo} := 2400\text{V}$$

$$X_{xfmr_pu} := 0.08\text{pu}$$

$$MVA_{rated} := 50\text{MVA} \quad S_B := 50\text{MVA}$$

$$MVA_{sc} := 300\text{MVA}$$

$$X_{src_pu} := \frac{(1.0\text{pu})^2}{\left(\frac{MVA_{sc}}{S_B}\right)} \quad X_{src_pu} = 0.17 \cdot \text{pu}$$

$$V_{src} := 1.0\text{pu}$$




Sequence Impedances for Faults:

$$X_1 := X_{src_pu} + X_{xfmr_pu} \quad X_1 = 0.25 \cdot \text{pu} \quad X_2 := X_1$$

$$X_{\text{ground}} := 0 \text{ pu}$$

$$X_0 := X_{\text{xfmr_pu}} + 3 \cdot X_{\text{ground}}$$

Sequence Networks:

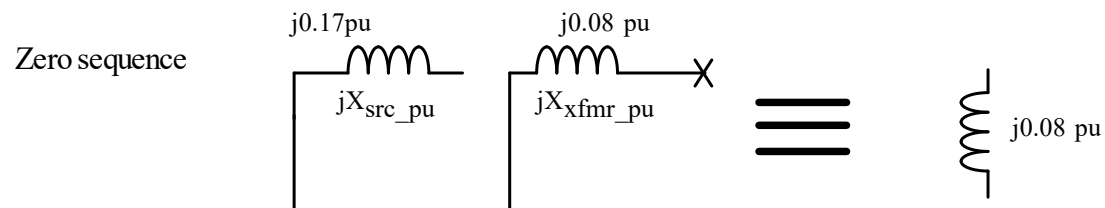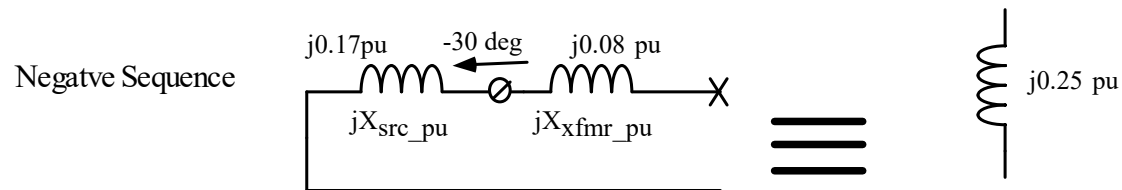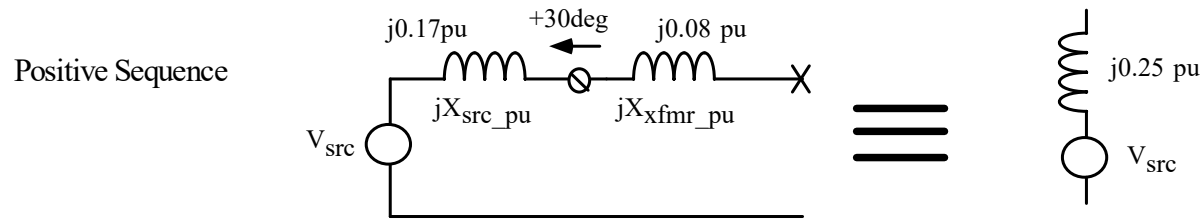

Three phase fault:

$$I_{f_3\phi} := \frac{V_{\text{src}}}{jX_1} \quad I_{f_3\phi} = -4.05i \cdot \text{pu}$$

Per unit current magnitudes will be the same on the low side as they are on the high side. But there will be a plus 30 degree shift.

$$I_{f_abc3ph} := I_{f_3\phi} \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix}$$

$$\overrightarrow{|I_{f_abc3ph}|} = \begin{pmatrix} 4.05 \\ 4.05 \\ 4.05 \end{pmatrix}$$

$$\overrightarrow{\arg(I_{f_abc3ph})} = \begin{pmatrix} -90 \\ 150 \\ 30 \end{pmatrix} \cdot \text{deg}$$

$$I_{HV_abc3ph} := I_{f_3\phi} \cdot e^{j \cdot 30 \text{deg}} \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix}$$

$$\overrightarrow{|I_{HV_abc3ph}|} = \begin{pmatrix} 4.05 \\ 4.05 \\ 4.05 \end{pmatrix}$$

$$\overrightarrow{\arg(I_{HV_abc3ph})} = \begin{pmatrix} -60 \\ 180 \\ 60 \end{pmatrix} \cdot \text{deg}$$

Voltage at the fault point:

$$V_{af} := V_{src} - j \cdot X_1 \cdot I_{f_3\phi} \quad V_{af} = 0 \cdot \text{pu}$$

Line to Line fault:

$$I_{0_LLf} := 0 \text{pu} \quad R_f := 0 \text{pu}$$

$$I_{1_LLf} := \frac{V_{src}}{j \cdot X_1 + j \cdot X_2 + R_f} \quad I_{1_LLf} = -2.03i \cdot \text{pu}$$

$$I_{2_LLf} := -I_{1_LLf}$$

$$I_{abc_LLf} := A_{012} \cdot \begin{pmatrix} I_{0_LLf} \\ I_{1_LLf} \\ I_{2_LLf} \end{pmatrix}$$

$$\overrightarrow{|I_{abc_LLf}|} = \begin{pmatrix} 0 \\ 3.51 \\ 3.51 \end{pmatrix} \cdot \text{pu}$$

$$\arg(I_{abc_LLf_1}) = 180 \cdot \text{deg}$$

$$\arg(I_{abc_LLf_2}) = 0 \cdot \text{deg}$$

Now move the currents from the low side to the high side (note, you must transform the sequence currents):

$$I_{1_LLH} := I_{1_LLf} \cdot e^{j \cdot 30 \text{deg}} \quad I_{0_LLH} := 0 \text{pu}$$

$$I_{2_LLH} := I_{2_LLf} \cdot e^{-j \cdot 30 \text{deg}}$$

$$I_{abc_LLh} := A_{012} \cdot \begin{pmatrix} I_{0_LLH} \\ I_{1_LLH} \\ I_{2_LLH} \end{pmatrix}$$

$$\overrightarrow{|I_{abc_LLh}|} = \begin{pmatrix} 2.03 \\ 4.05 \\ 2.03 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(I_{abc_LLh})} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

Phase B per unit current is larger on the high side of the transformer than on the low side.

Voltage at the fault point:

$$V_{1_LL} := V_{\text{src}} - j \cdot X_1 \cdot I_{1_LLf} \quad |V_{1_LL}| = 0.5 \cdot \text{pu} \quad \arg(V_{1_LL}) = 0 \cdot \text{deg}$$

$$V_{2_LL} := 0 - j \cdot X_2 \cdot I_{2_LLf} \quad |V_{2_LL}| = 0.5 \cdot \text{pu} \quad \arg(V_{2_LL}) = 0 \cdot \text{deg}$$

$$V_{0_LL} := 0 - j \cdot X_0 \cdot I_{0_LLf} \quad |V_{0_LL}| = 0 \cdot \text{pu}$$

$$V_{abc_LL} := A_{012} \cdot \begin{pmatrix} V_{0_LL} \\ V_{1_LL} \\ V_{2_LL} \end{pmatrix}$$

$$\overrightarrow{|V_{abc_LL}|} = \begin{pmatrix} 1 \\ 0.5 \\ 0.5 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(V_{abc_LL})} = \begin{pmatrix} 0 \\ 180 \\ 180 \end{pmatrix} \cdot \text{deg}$$

Voltage at the 13.8kV Bus

$$V_{1_LLHV} := V_{src} \cdot e^{j \cdot 30 \text{deg}} - j \cdot X_{src_pu} \cdot I_{1_LLH} \quad |V_{1_LLHV}| = 0.66 \cdot \text{pu} \quad \arg(V_{1_LLHV}) = 30 \cdot \text{deg}$$

$$V_{2_LLHV} := 0 - j \cdot X_{src_pu} \cdot I_{2_LLH} \quad |V_{2_LLHV}| = 0.34 \cdot \text{pu} \quad \arg(V_{2_LLHV}) = -30 \cdot \text{deg}$$

$$V_{0_LLHV} := 0 \quad |V_{0_LLHV}| = 0 \cdot \text{pu}$$

$$V_{abc_LLHV} := A_{012} \cdot \begin{pmatrix} V_{0_LLHV} \\ V_{1_LLHV} \\ V_{2_LLHV} \end{pmatrix}$$

$$\overrightarrow{|V_{abc_LLHV}|} = \begin{pmatrix} 0.88 \\ 0.32 \\ 0.88 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(V_{abc_LLHV})} = \begin{pmatrix} 10.61 \\ -90 \\ 169.39 \end{pmatrix} \cdot \text{deg}$$

Single Line to Ground fault:

$$I_{0_SLGf} := \frac{V_{src}}{j \cdot X_1 + j \cdot X_2 + j \cdot X_0 + 3 \cdot R_f} \quad I_{0_SLGf} = -1.74i \cdot pu$$

$$I_{1_SLGf} := I_{0_SLGf} \quad I_{2_SLGf} := I_{0_SLGf}$$

$$I_{abc_SLGf} := A_{012} \cdot \begin{pmatrix} I_{0_SLGf} \\ I_{1_SLGf} \\ I_{2_SLGf} \end{pmatrix}$$

$\overrightarrow{|I_{abc_SLGf}|} = \begin{pmatrix} 5.23 \\ 0 \\ 0 \end{pmatrix} \cdot pu$

$\overrightarrow{\arg(I_{abc_SLGf})} = \begin{pmatrix} -90 \\ 18.43 \\ 18.43 \end{pmatrix} \cdot deg$

Now move the currents from the low side to the high side:

$$I_{1_SLGH} := I_{1_SLGf} \cdot e^{j \cdot 30deg} \quad I_{0_SLGH} := 0pu$$

$$I_{2_SLGH} := I_{2_SLGf} \cdot e^{-j \cdot 30deg}$$

$$I_{abc_SLGH} := A_{012} \cdot \begin{pmatrix} I_{0_SLGH} \\ I_{1_SLGH} \\ I_{2_SLGH} \end{pmatrix}$$

$\overrightarrow{|I_{abc_SLGH}|} = \begin{pmatrix} 3.02 \\ 0 \\ 3.02 \end{pmatrix} \cdot pu$

Currents are lower on the high side
and appear as a L-L fault not SLG

$$\overrightarrow{\arg(I_{abc_SLGh})} = \begin{pmatrix} -90 \\ 90 \\ 90 \end{pmatrix} \cdot \text{deg}$$

Voltage at the fault point:

$$V_{1_SLG} := V_{src} - j \cdot X_1 \cdot I_{1_SLGf} \quad |V_{1_SLG}| = 0.57 \cdot \text{pu} \quad \arg(V_{1_SLG}) = 0 \cdot \text{deg}$$

$$V_{2_SLG} := 0 - j \cdot X_2 \cdot I_{2_SLGf} \quad |V_{2_SLG}| = 0.43 \cdot \text{pu} \quad \arg(V_{2_SLG}) = 180 \cdot \text{deg}$$

$$V_{0_SLG} := 0 - j \cdot X_0 \cdot I_{0_SLGf} \quad |V_{0_SLG}| = 0.14 \cdot \text{pu} \quad \arg(V_{0_SLG}) = 180 \cdot \text{deg}$$

$$V_{abc_SLG} := A_{012} \cdot \begin{pmatrix} V_{0_SLG} \\ V_{1_SLG} \\ V_{2_SLG} \end{pmatrix}$$

$$\overrightarrow{|V_{abc_SLG}|} = \begin{pmatrix} 0 \\ 0.89 \\ 0.89 \end{pmatrix} \cdot \text{pu}$$

$$\arg(V_{abc_SLG_1}) = -103.59 \cdot \text{deg}$$

$$\arg(V_{abc_SLG_2}) = 103.59 \cdot \text{deg}$$

Voltage on 13.kV bus

$$V_{1_SLGHV} := \left(V_{src} \cdot e^{j \cdot 30 \text{deg}} - j \cdot X_{src_pu} \cdot I_{1_SLGH} \right) \quad |V_{1_SLGHV}| = 0.71 \cdot \text{pu} \quad \arg(V_{1_SLGHV}) = 30 \cdot \text{deg}$$

$$V_{2_SLGHV} := \left(0 - j \cdot X_{src_pu} \cdot I_{2_SLGH} \right) \quad |V_{2_SLGHV}| = 0.29 \cdot \text{pu} \quad \arg(V_{2_SLGHV}) = 150 \cdot \text{deg}$$


$$V_{0_SLGHV} := 0 - j \cdot X_{src_pu} \cdot I_{0_SLGH} \quad |V_{0_SLGHV}| = 0 \cdot \text{pu}$$

$$V_{abc_SLGHV} := A_{012} \cdot \begin{pmatrix} V_{0_SLGHV} \\ V_{1_SLGHV} \\ V_{2_SLGHV} \end{pmatrix}$$

$\overrightarrow{|V_{abc_SLGHV}|} = \begin{pmatrix} 0.62 \\ 1 \\ 0.62 \end{pmatrix} \cdot pu$

$\overrightarrow{\arg(V_{abc_SLGHV})} = \begin{pmatrix} 54.06 \\ -90 \\ 125.94 \end{pmatrix} \cdot deg$

• **Example with two sources:**

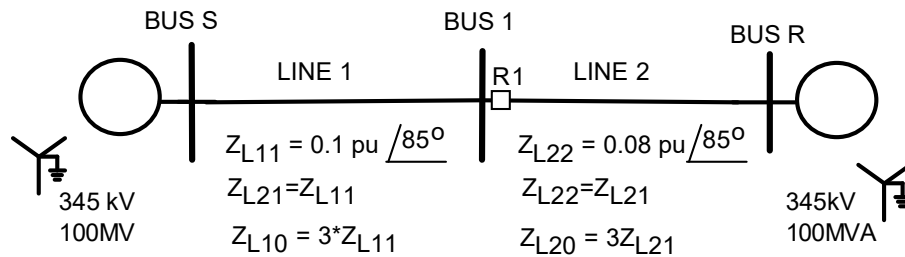

$V_S = 1.0 pu @ 0 deg$
 $Z_{S1} = j0.03 pu$
 $Z_{S2} = Z_{S1}$
 $Z_{S0} = 3 * Z_{S1}$

Per unit line impedances
calculated with SB=100MVA
and VB=345kV LL

$V_R = 1.0 pu at 0 deg$
 $Z_{R1} = j0.06 pu$
 $Z_{R2} = Z_{R1}$
 $Z_{R0} = 3 * Z_{R1}$

$Z_{S1} := j \cdot 0.03 pu$

$Z_{L11} := 0.1 pu \cdot e^{j \cdot 85 deg}$

$Z_{L21} := 0.08 pu \cdot e^{j \cdot 85 deg}$

$Z_{S2} := Z_{S1}$

$Z_{L10} = 0.01 + 0.1i$

$Z_{L20} = 0.01 + 0.08i$

$$Z_{S0} := 3Z_{S1}$$

$$Z_{L12} := Z_{L11}$$

$$Z_{L22} := Z_{L21}$$

$$Z_{R1} := j \cdot 0.06 \text{ pu}$$

$$Z_{L10} := 3 \cdot Z_{L11}$$

$$Z_{L20} := 3 \cdot Z_{L21}$$

$$Z_{R2} := Z_{R1}$$

$$Z_{L10} = 0.03 + 0.3i$$

$$Z_{L20} = 0.02 + 0.24i$$

$$Z_{R0} := 3Z_{R1}$$

- For faults on Line 2:

$$Z_{L2_1_thev}(n) := \left[\frac{1}{Z_{S1} + Z_{L11} + n \cdot Z_{L21}} + \frac{1}{(1-n) \cdot Z_{L21} + Z_{R1}} \right]^{-1}$$

$$Z_{L2_2_thev}(n) := \left[\frac{1}{Z_{S2} + Z_{L12} + n \cdot Z_{L22}} + \frac{1}{(1-n) \cdot Z_{L22} + Z_{R2}} \right]^{-1}$$

$$Z_{L2_0_thev}(n) := \left[\frac{1}{Z_{S0} + Z_{L10} + n \cdot Z_{L20}} + \frac{1}{(1-n) \cdot Z_{L20} + Z_{R0}} \right]^{-1}$$

- **3 phase faults:** $V_f := 1$

$$I_{f1}(m) := \frac{V_f}{Z_{L2_1_thev}(m)}$$

$$I_{left_1}(m) := \frac{I_{f1}(m) \cdot [(1-m) \cdot Z_{L21} + Z_{R1}]}{Z_{S1} + Z_{L11} + m \cdot Z_{L21} + [(1-m) \cdot Z_{L21} + Z_{R1}]}$$

$$V_{R1_1}(m) := V_f - I_{\text{left_1}}(m) \cdot (Z_{S1} + Z_{L11})$$

$$|I_{\text{left_1}}(0.5)| = 5.89 \cdot \text{pu}$$

$$\arg(I_{\text{left_1}}(0.5)) = -85.88 \cdot \text{deg}$$

$$|V_{R1_1}(0.5)| = 0.24 \cdot \text{pu}$$

$$\arg(V_{R1_1}(0.5)) = -0.88 \cdot \text{deg}$$

- **SLG faults:**

$$I_{f0}(m) := \frac{V_f}{Z_{L2_1_thev}(m) + Z_{L2_2_thev}(m) + Z_{L2_0_thev}(m)}$$

$$I_{f1}(m) := I_{f0}(m)$$

$$I_{f2}(m) := I_{f0}(m)$$

$$I_{\text{left_1}}(m) := \frac{I_{f1}(m) \cdot [(1 - m) \cdot Z_{L21} + Z_{R1}]}{Z_{S1} + Z_{L11} + m \cdot Z_{L21} + [(1 - m) \cdot Z_{L21} + Z_{R1}]}$$

$$I_{\text{left_2}}(m) := \frac{I_{f2}(m) \cdot [(1 - m) \cdot Z_{L22} + Z_{R2}]}{Z_{S2} + Z_{L12} + m \cdot Z_{L22} + [(1 - m) \cdot Z_{L22} + Z_{R2}]}$$

$$I_{\text{left_0}}(m) := \frac{I_{f0}(m) \cdot [(1 - m) \cdot Z_{L20} + Z_{R0}]}{Z_{S0} + Z_{L10} + m \cdot Z_{L20} + [(1 - m) \cdot Z_{L20} + Z_{R0}]}$$

$$V_{R1_1}(m) := V_f - I_{\text{left_1}}(m) \cdot (Z_{S1} + Z_{L11})$$

$$V_{R1_2}(m) := 0 - I_{\text{left_2}}(m) \cdot (Z_{S2} + Z_{L12})$$

$$V_{R1_0}(m) := 0 - I_{\text{left_0}}(m) \cdot (Z_{S0} + Z_{L10})$$

$$V_{ABC_R1}(m) := A_{012} \cdot \begin{pmatrix} V_{R1_0}(m) \\ V_{R1_1}(m) \\ V_{R1_2}(m) \end{pmatrix} \quad \overrightarrow{|V_{ABC_R1}(0.5)|} = \begin{pmatrix} 0.24 \\ 1.18 \\ 1.18 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(V_{ABC_R1}(0.5))} = \begin{pmatrix} -0.88 \\ -132.89 \\ 132.99 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC_R1}(m) := A_{012} \cdot \begin{pmatrix} I_{\text{left_0}}(m) \\ I_{\text{left_1}}(m) \\ I_{\text{left_2}}(m) \end{pmatrix} \quad \overrightarrow{|I_{ABC_R1}(0.5)|} = \begin{pmatrix} 3.53 \\ 0 \\ 0 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(I_{ABC_R1}(0.5))} = \begin{pmatrix} -85.88 \\ 49.05 \\ 49.05 \end{pmatrix} \cdot \text{deg}$$

• **DLG faults:**

$$I_{f1}(m) := \frac{V_f}{Z_{L2_1_thev}(m) + \left(\frac{1}{Z_{L2_2_thev}(m)} + \frac{1}{Z_{L2_0_thev}(m)} \right)^{-1}}$$

$$I_{f2}(m) := -I_{f1}(m) \cdot \left(\frac{Z_{L2_0_thev}(m)}{Z_{L2_2_thev}(m) + Z_{L2_0_thev}(m)} \right)$$

$$I_{f0}(m) := -I_{f1}(m) \cdot \left(\frac{Z_{L2_2_thev}(m)}{Z_{L2_2_thev}(m) + Z_{L2_0_thev}(m)} \right)$$

$$I_{\text{left_1}}(m) := \frac{I_{f1}(m) \cdot [(1-m) \cdot Z_{L21} + Z_{R1}]}{Z_{S1} + Z_{L11} + m \cdot Z_{L21} + [(1-m) \cdot Z_{L21} + Z_{R1}]}$$

$$I_{\text{left}_2}(m) := \frac{I_{f2}(m) \cdot [(1 - m) \cdot Z_{L22} + Z_{R2}]}{Z_{S2} + Z_{L12} + m \cdot Z_{L22} + [(1 - m) \cdot Z_{L22} + Z_{R2}]}$$

$$I_{\text{left}_0}(m) := \frac{I_{f0}(m) \cdot [(1 - m) \cdot Z_{L20} + Z_{R0}]}{Z_{S0} + Z_{L10} + m \cdot Z_{L20} + [(1 - m) \cdot Z_{L20} + Z_{R0}]}$$

$$V_{R1_1}(m) := V_f - I_{\text{left}_1}(m) \cdot (Z_{S1} + Z_{L11})$$

$$V_{R1_2}(m) := 0 - I_{\text{left}_2}(m) \cdot (Z_{S2} + Z_{L12})$$

$$V_{R1_0}(m) := 0 - I_{\text{left}_0}(m) \cdot (Z_{S0} + Z_{L10})$$

$$V_{ABC_R1}(m) := A_{012} \cdot \begin{pmatrix} V_{R1_0}(m) \\ V_{R1_1}(m) \\ V_{R1_2}(m) \end{pmatrix} \quad \overrightarrow{|V_{ABC_R1}(0.5)|} = \begin{pmatrix} 1.22 \\ 0.24 \\ 0.24 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(V_{ABC_R1}(0.5))} = \begin{pmatrix} 0.05 \\ -120.88 \\ 119.12 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC_R1}(m) := A_{012} \cdot \begin{pmatrix} I_{\text{left}_0}(m) \\ I_{\text{left}_1}(m) \\ I_{\text{left}_2}(m) \end{pmatrix} \quad \overrightarrow{|I_{ABC_R1}(0.5)|} = \begin{pmatrix} 0 \\ 5.25 \\ 5.25 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(I_{ABC_R1}(0.5 + 10^{-15}))} = \begin{pmatrix} 93.58 \\ 170.22 \\ 18.02 \end{pmatrix} \cdot \text{deg}$$

- Adding the 10^{-15} avoided a divide by 0 problem in angle calculation