


ECE 523  
Symmetrical Components

Session 11

# Single Line to Ground Fault (SLG)

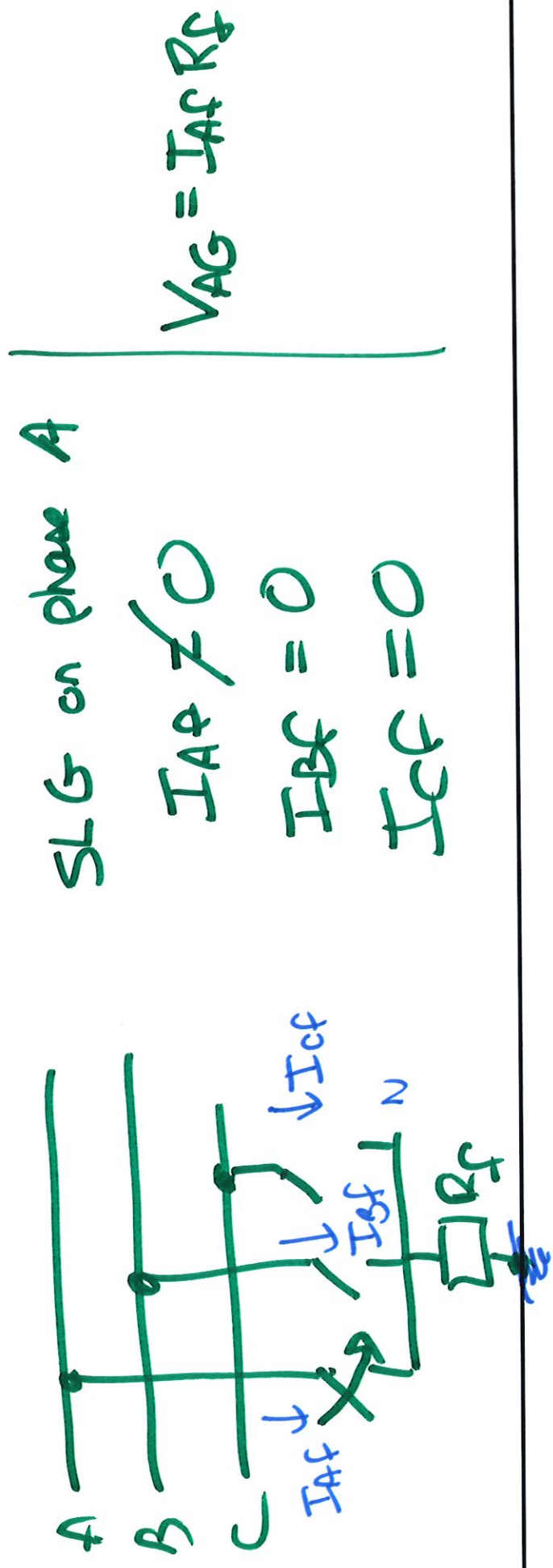
(1) Boundary conditions

→ fault currents at fault location (not same as line currents)





Grounded System - closed to ground point

$V_{AG} = V_{AN}$  Prefault



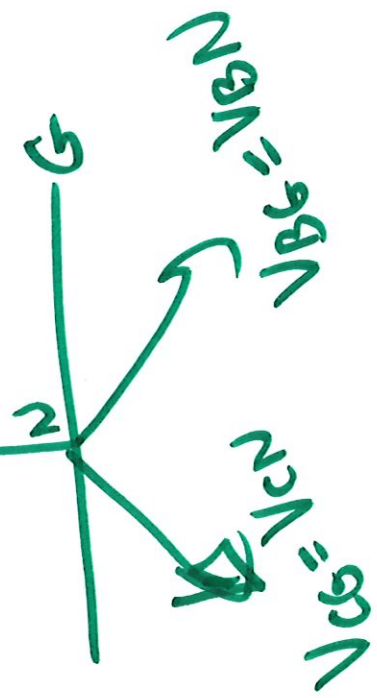


$I_A \cdot R_F$  SLG Fault on A

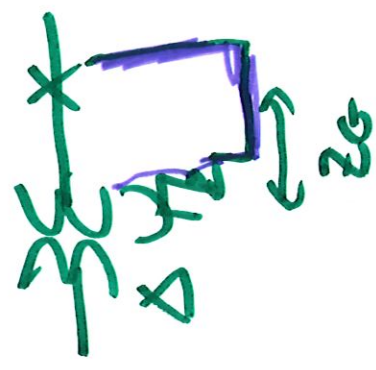
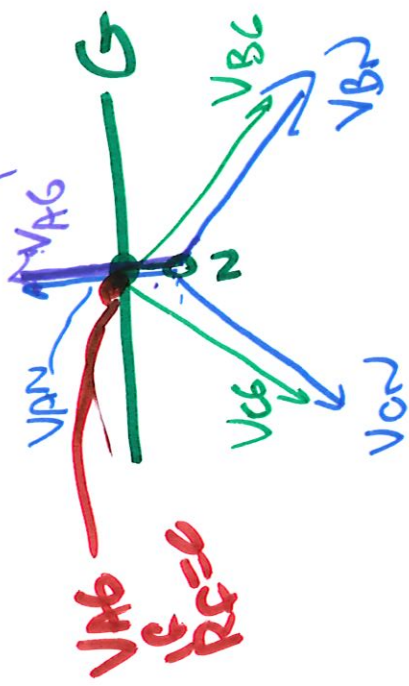


# ungrounded system

SLG Prefault

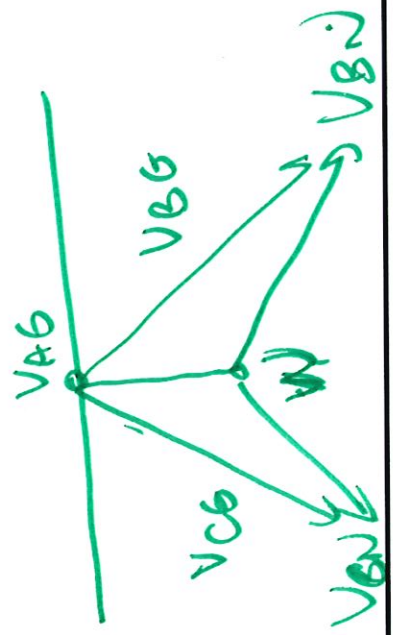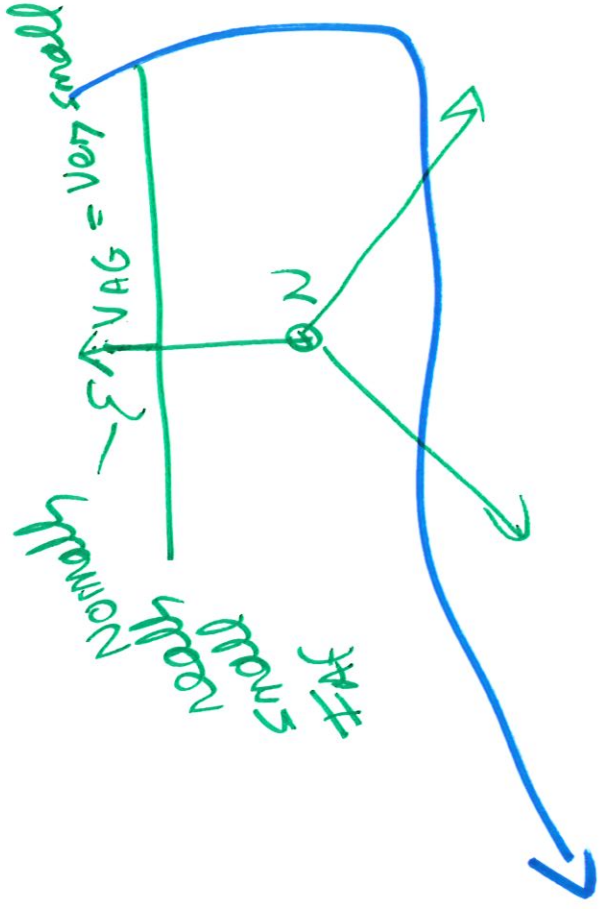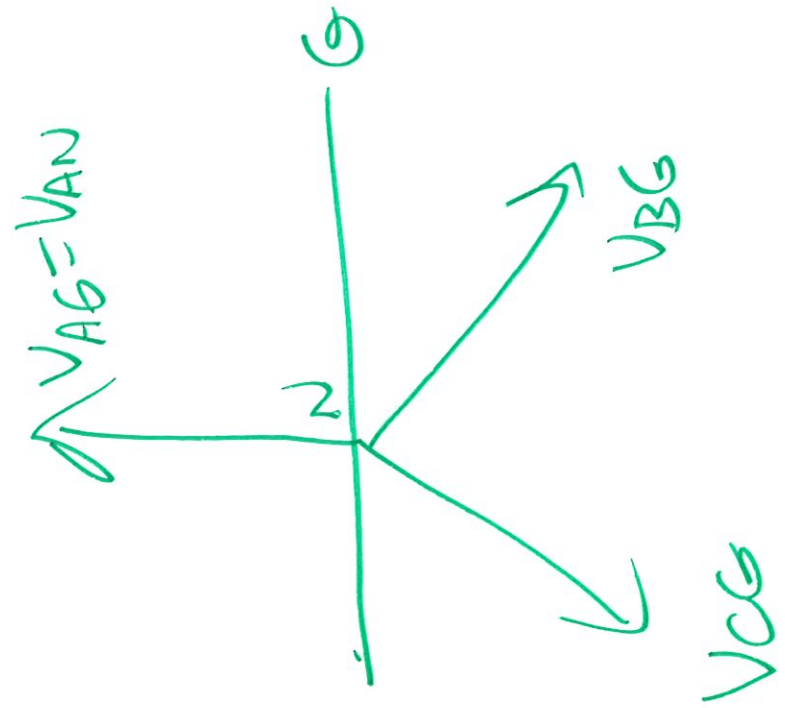


Grounded

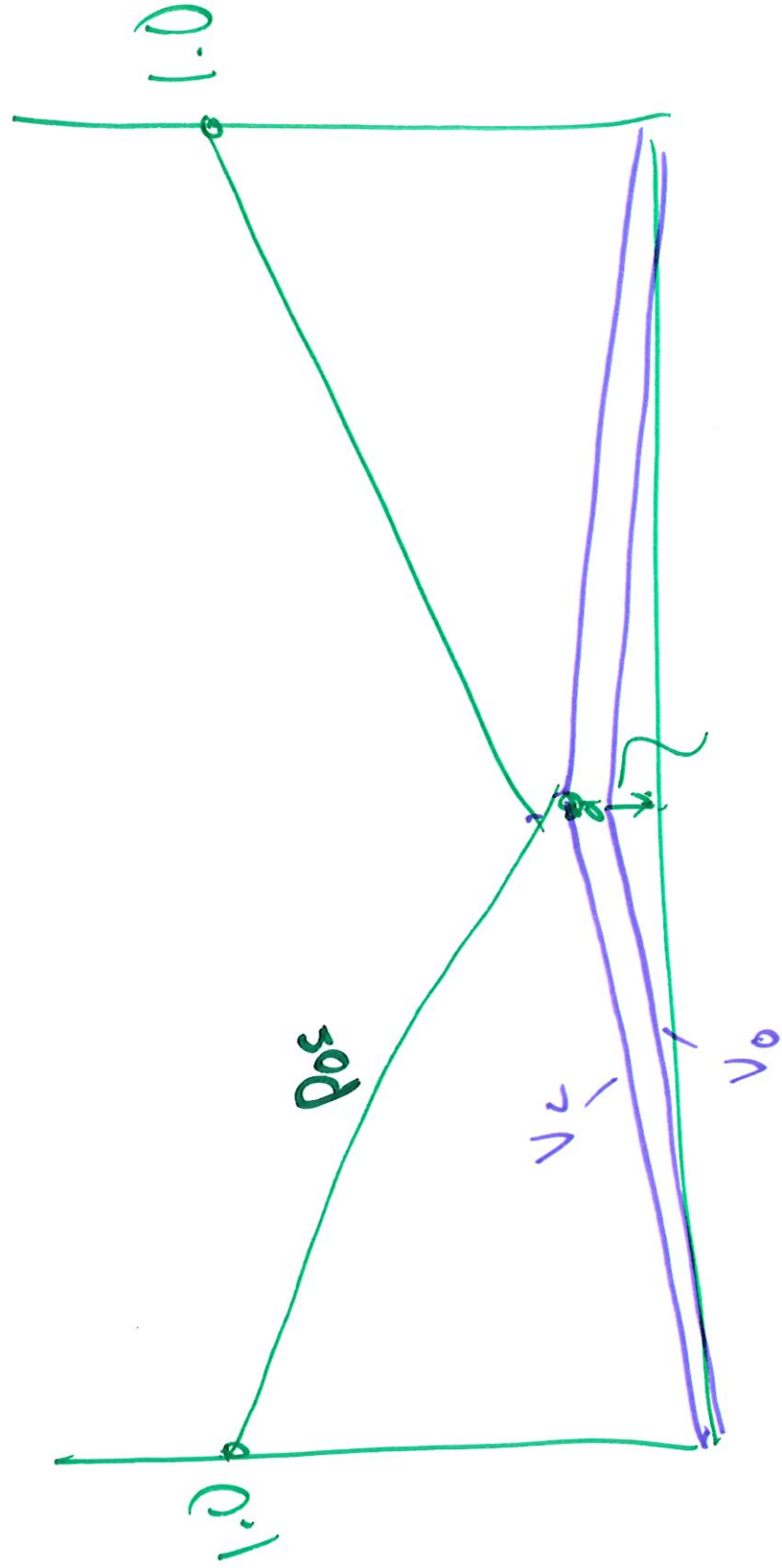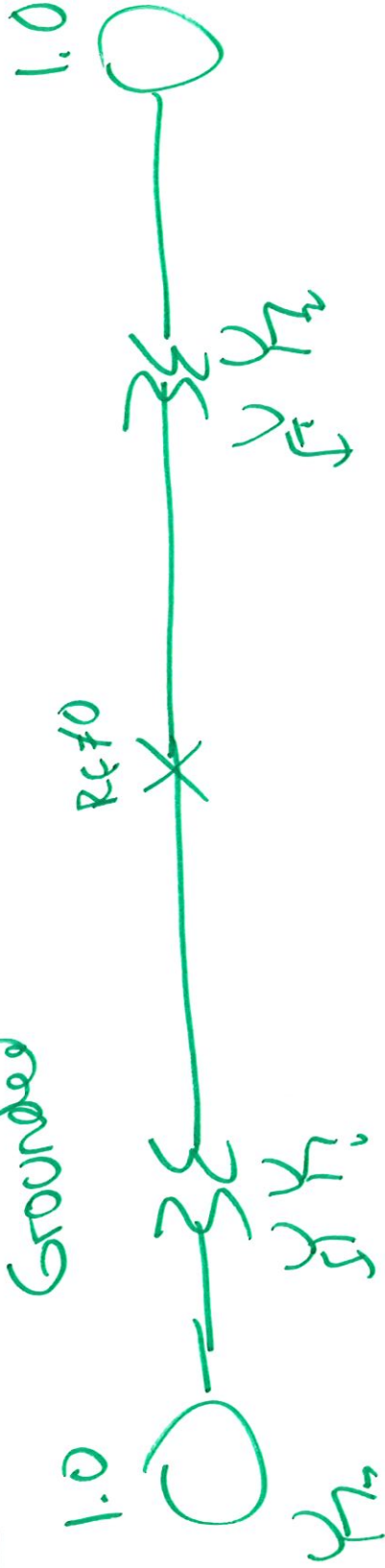



Ungrounded

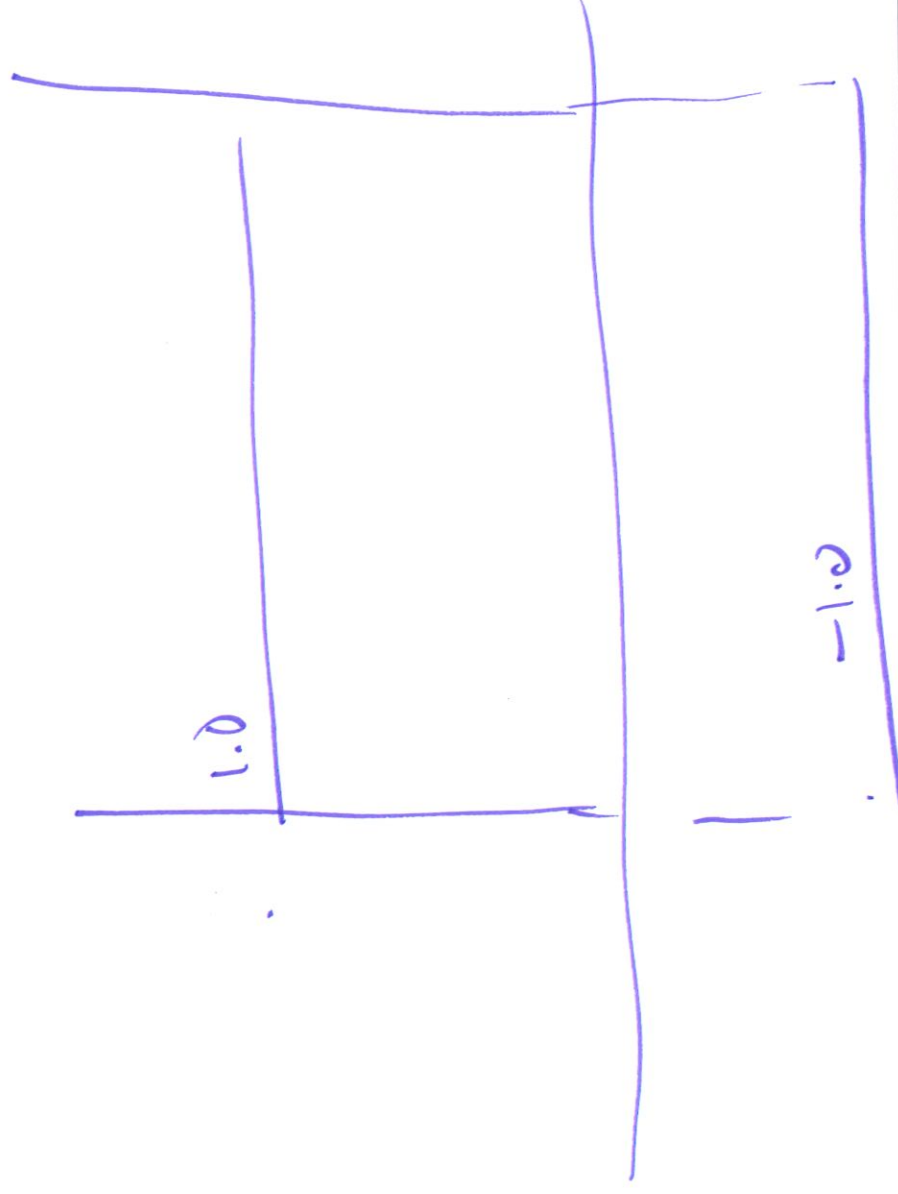

SLG - general case

$$I_{Bf} = I_{Cf} = 0$$

$$I_{Af} \neq 0$$

$$V_{AG} = I_{Af} \cdot Z_f$$

$\Rightarrow$  Symmetrical components domain

$$(V_{A0} + V_{A1} + V_{A2}) = (I_{A0} + I_{A1} + I_{A2}) \cdot R_f$$

voltage equations

$$\begin{bmatrix} I_{A0} \\ I_{A1} \\ I_{A2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \begin{bmatrix} I_{Af} \\ 0 \\ 0 \end{bmatrix}$$

current constraints

$$\begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_{Af} \\ 0 \\ 0 \end{bmatrix}$$


$$I_{AO} = \frac{I_{AF}}{3} = I_A = I_{A2}$$

$$(V_{AO} + V_{A1} + V_{A2}) = 3 I_{AO} R_f$$


connect sequence networks based on this

Pos seq equiv - Thevenin equiv


Neg seq

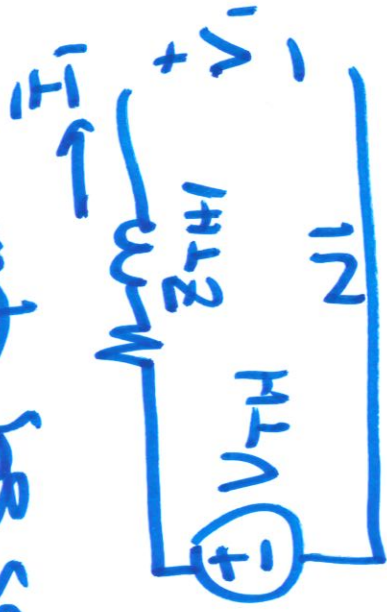


Zero seq

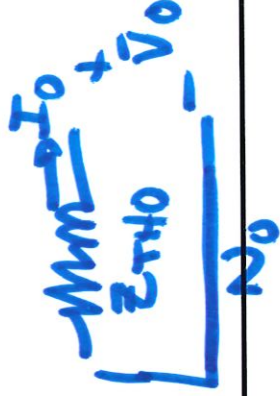



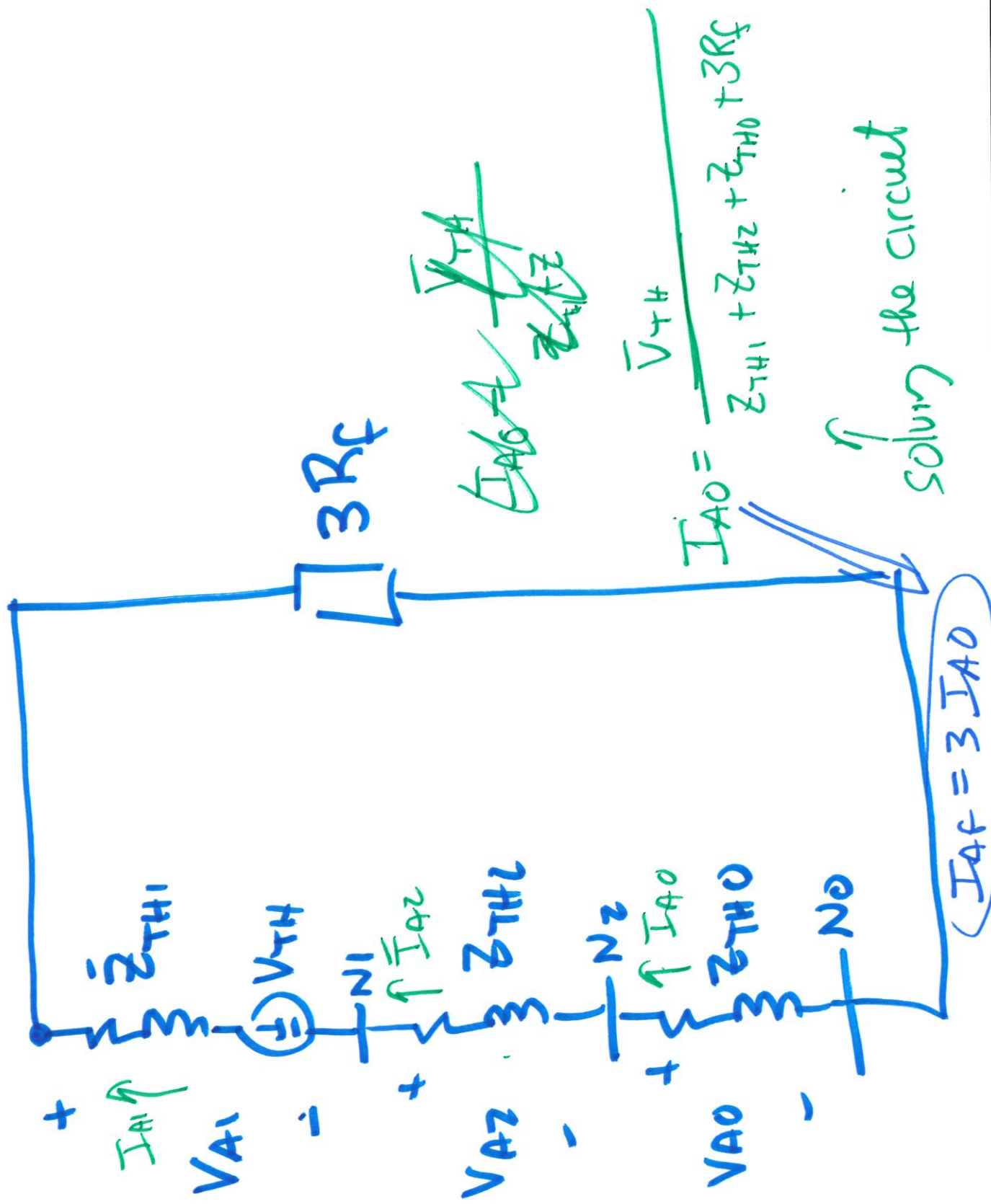

ungrounded system

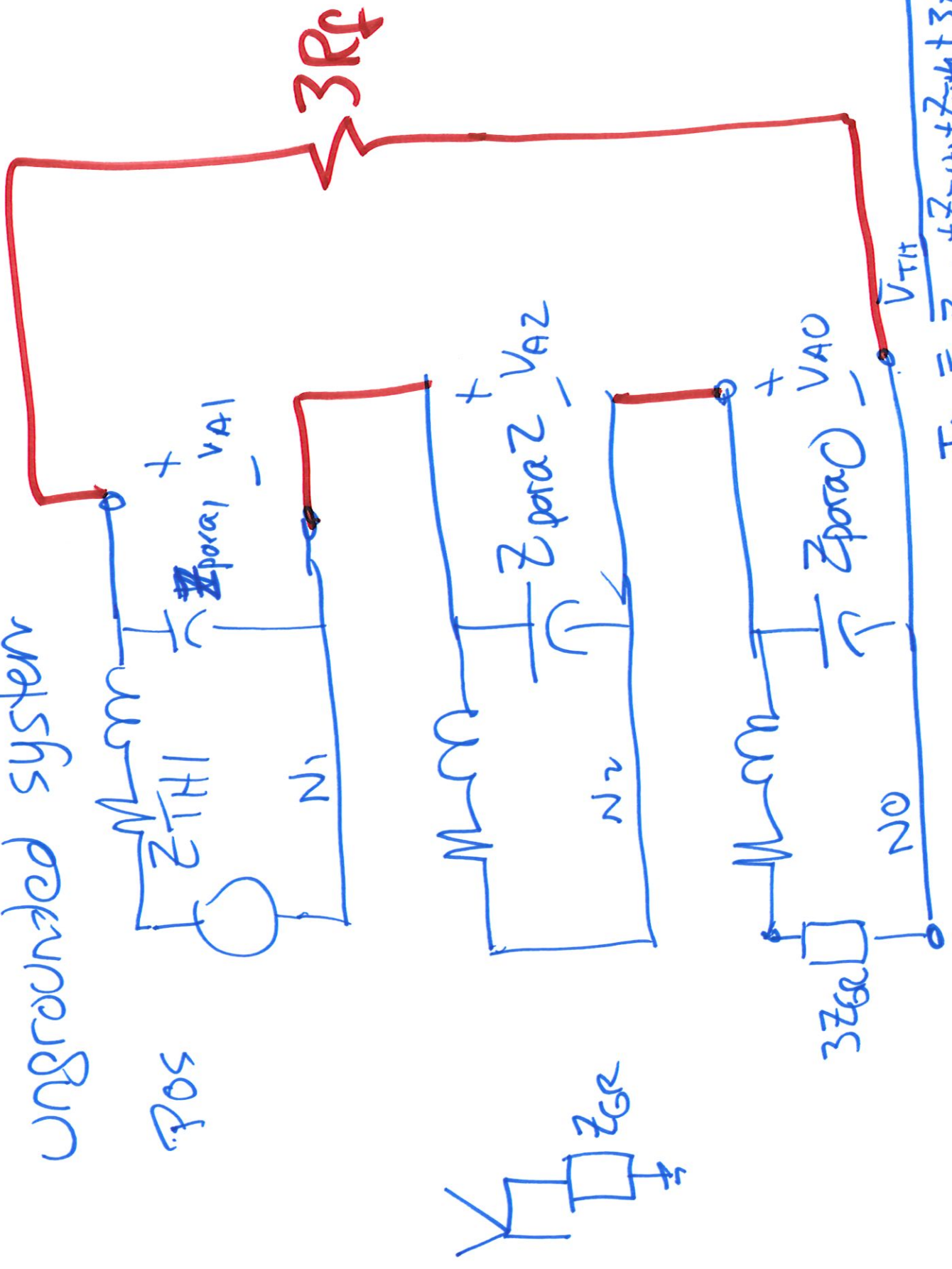


### Unbalanced Fault Analysis Examples

$pu := 1$      $MVA := 1000kW$

$a := 1e^{j \cdot 120deg}$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

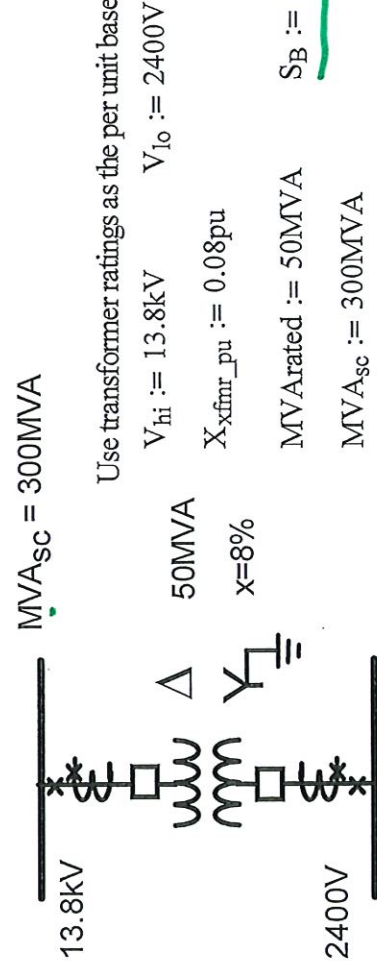Compare the per unit phase currents seen on the HV side of the transformer below with those seen by at the fault location for three phase, SLG and LL faults the left side feeder. Assume wye connected CT's.



$MVA_{sc} = 300MVA$

Use transformer ratings as the per unit base.

$V_{hi} := 13.8kV$      $V_{lo} := 2400V$

$X_{xfmr\_pu} := 0.08pu$

$MVA_{rated} := 50MVA$      $S_B := 50MVA$

$MVA_{sc} := 300MVA$

$X_{src\_pu} := \frac{(1.0pu)^2 \cdot \left( \frac{MVA_{sc}}{S_B} \right)}{\text{convert to per unit}}$

$X_{src\_pu} = 0.17 \cdot pu$


$V_{src} := 1.0pu$

Sequence Impedances for Faults:

$X_1 := X_{src\_pu} + X_{xfmr\_pu}$

$X_2 := X_1$

$X_0 := 0.25 \cdot pu$

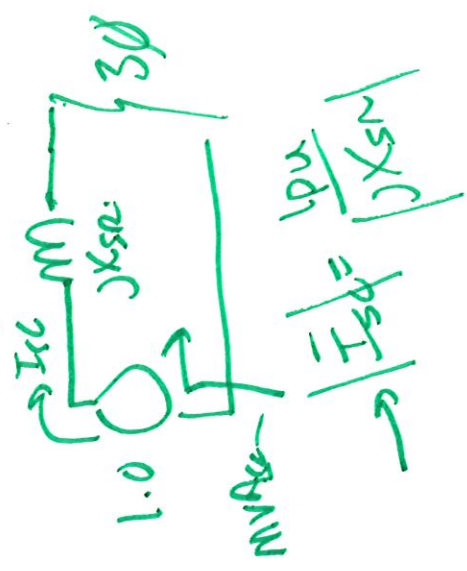


$MVA_{sc} = V \cdot I_{sc}$   
 $= 1 \cdot pu \cdot I_{sc}$   
 $= (1pu)^2$   
 $= \frac{1}{jX_{sc}}$

LU 1/15


$$X_{\text{ground}} := 0 \text{ pu}$$

$$X_0 := X_{\text{xfrm}} \text{ pu} + 3 \cdot X_{\text{ground}}$$


**Sequence Networks:**

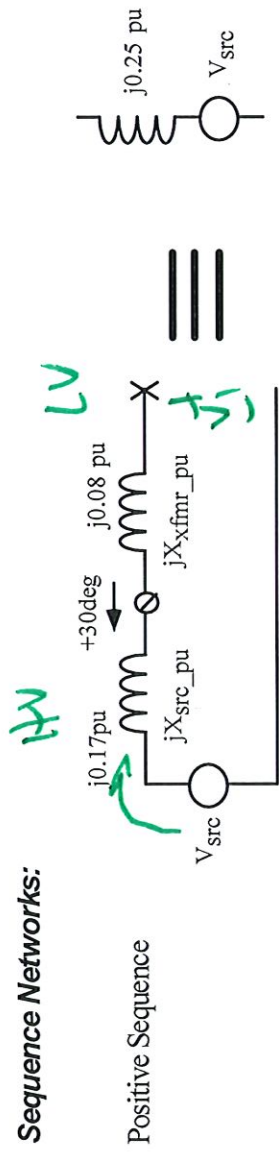

Positive Sequence

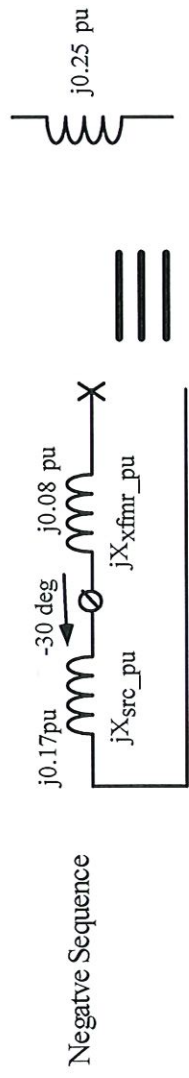

Negative Sequence

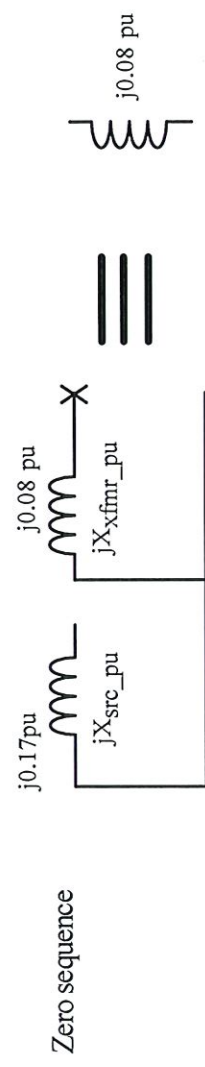

Zero sequence

**Three phase fault:**

$$I_{f_{3\phi}} := \frac{V_{\text{src}}}{jX_1}$$

$$I_{f_{3\phi}} = -4.05j \text{ pu}$$



Per unit current magnitudes will be the same on the low side as they are on the high side. But there will be a plus 30 degree shift.

$$I_{f\_abc3ph} := I_{f\_3\phi} \cdot \begin{pmatrix} 1 \\ 2 \\ a \end{pmatrix}$$

$$|I_{f\_abc3ph}| = \begin{pmatrix} 4.05 \\ 4.05 \\ 4.05 \end{pmatrix}$$

$$\arg(I_{f\_abc3ph}) = \begin{pmatrix} -90 \\ 150 \\ 30 \end{pmatrix} \cdot \text{deg}$$

$$I_{HV\_abc3ph} := I_{f\_3\phi} \cdot e^{j \cdot 30 \text{deg}} \cdot \begin{pmatrix} 1 \\ 2 \\ a \end{pmatrix}$$

$$|I_{HV\_abc3ph}| = \begin{pmatrix} 4.05 \\ 4.05 \\ 4.05 \end{pmatrix}$$

$$\arg(I_{HV\_abc3ph}) = \begin{pmatrix} -60 \\ 180 \\ 60 \end{pmatrix} \cdot \text{deg}$$

$V_{af} = 0$   
 $= I_f \cdot R_f = 0$

Voltage at the fault point:

$$V_{af} := V_{src} - j \cdot X_1 \cdot I_{f\_3\phi}$$

**Line to Line fault:**

$$I_{0\_LLf} := 0 \text{ pu} \quad R_f := 0 \text{ pu}$$

$$I_{1\_LLf} := \frac{V_{src}}{j \cdot X_1 + j \cdot X_2 + R_f} \quad I_{1\_LLf} = -2.03i \text{ pu}$$

$$I_{2\_LLf} := -I_{1\_LLf}$$

$$I_{abc\_LLf} := A_{012} \cdot \begin{pmatrix} I_{0\_LLf} \\ I_{1\_LLf} \\ I_{2\_LLf} \end{pmatrix}$$

$$|I_{abc\_LLf}| = \begin{pmatrix} 0 \\ 3.51 \\ 3.51 \end{pmatrix} \text{ pu}$$

L11 13/15

**Single Line to Ground fault:**

$R_f = 0$

$$I_0\_SLGf := \frac{V_{src}}{j \cdot X_1 + j \cdot X_2 + j \cdot X_0 + 3 \cdot R_f} \quad I_0\_SLGf = -1.74i \cdot pu$$

$$I_1\_SLGf := I_0\_SLGf \quad I_2\_SLGf := I_0\_SLGf$$

$\begin{pmatrix} I_0\_SLGf \\ I_1\_SLGf \\ I_2\_SLGf \end{pmatrix}$	=	$\begin{pmatrix} 5.23 \\ 0 \\ 0 \end{pmatrix} \cdot pu$
$\arg(I_{abc\_SLGf})$	=	$\begin{pmatrix} -90 \\ 18.43 \\ 18.43 \end{pmatrix} \cdot deg$


Now move the currents from the low side to the high side:

$$I_1\_SLGH := I_1\_SLGf \cdot e^{j \cdot 30deg} \quad I_0\_SLGH := 0pu$$

$$I_2\_SLGH := I_2\_SLGf \cdot e^{-j \cdot 30deg}$$

$\begin{pmatrix} I_0\_SLGH \\ I_1\_SLGH \\ I_2\_SLGH \end{pmatrix}$	=	$\begin{pmatrix} 3.02 \\ 0 \\ 3.02 \end{pmatrix} \cdot pu$
---	---	--

HV LV  
3E  
Δ YZ

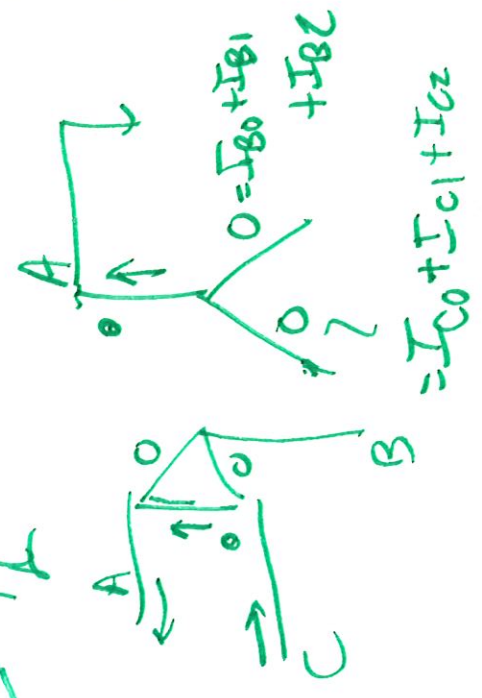

Currents are lower on the high side and appear as a L-L fault not SLG

$$\arg(I_{abc\_SLGH}) = \begin{pmatrix} -90 \\ 90 \\ 90 \end{pmatrix} \cdot \text{deg}$$

Voltage at the fault point:  $-2 \text{ pu}$

$$V_1\_SLG := V_{src} - (j \cdot X_1) \cdot I_1\_SLGf \quad |V_1\_SLG| = 0.57 \text{ pu} \quad \arg(V_1\_SLG) = 0 \cdot \text{deg}$$

$$V_2\_SLG := 0 - j \cdot X_2 \cdot I_2\_SLGf \quad |V_2\_SLG| = 0.43 \text{ pu} \quad \arg(V_2\_SLG) = 180 \cdot \text{deg}$$

$$V_0\_SLG := 0 - j \cdot X_0 \cdot I_0\_SLGf \quad |V_0\_SLG| = 0.14 \text{ pu} \quad \arg(V_0\_SLG) = 180 \cdot \text{deg}$$

$$V_1 + V_2 + V_0 = 3 \angle -90^\circ$$

$$V_{abc\_SLG} := A_{012} \cdot \begin{pmatrix} V_0\_SLG \\ V_1\_SLG \\ V_2\_SLG \end{pmatrix}$$

$$|V_{abc\_SLG}| = \begin{pmatrix} 0 \\ 0.89 \\ 0.89 \end{pmatrix} \cdot \text{pu}$$

$$\arg(V_{abc\_SLG_1}) = -103.59 \cdot \text{deg}$$

$$\arg(V_{abc\_SLG_2}) = 103.59 \cdot \text{deg}$$

$V_{abc\_SLG}$  is not a fault

Voltage on 13.8 kV bus

$$V_1\_SLGHV := (V_{src} \cdot e^{j \cdot 30 \text{deg}} - j \cdot X_{src\_pu} \cdot I_1\_SLGH) \quad |V_1\_SLGHV| = 0.71 \text{ pu} \quad \arg(V_1\_SLGHV) = 30 \cdot \text{deg}$$

$$V_2\_SLGHV := (0 - j \cdot X_{src\_pu} \cdot I_2\_SLGH) \quad |V_2\_SLGHV| = 0.29 \text{ pu} \quad \arg(V_2\_SLGHV) = 150 \cdot \text{deg}$$

$$V_0\_SLGHV := 0 - j \cdot X_{src\_pu} \cdot I_0\_SLGH \quad |V_0\_SLGHV| = 0 \cdot \text{pu}$$

