
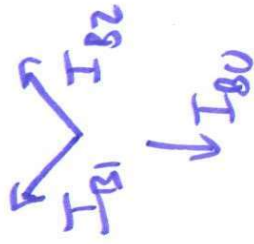



ECE 523
Symmetrical Components

Session 13

Zero sequence model

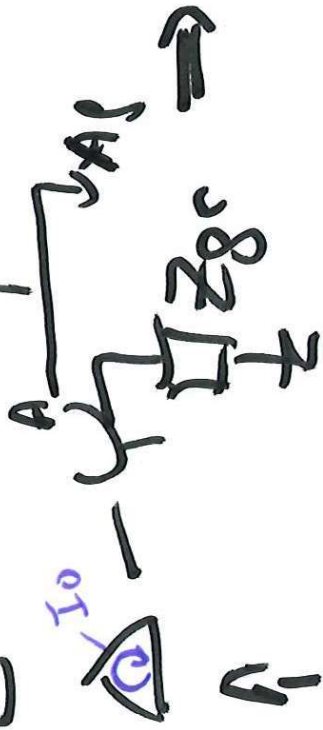

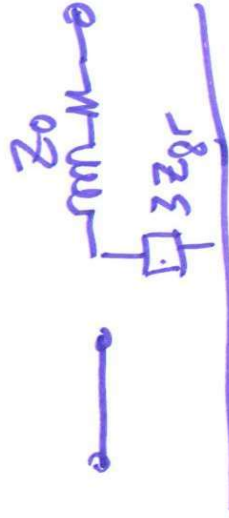- no connection to ground
- I_0 circulates in Δ side or



SLG Fault:

fault + fault point
- pre-fault fault point

$$I_{0_SLG}(M, R_f) := \frac{V_f}{Z_1(M)_{4,4} + Z_2(M)_{4,4} + Z_0(M)_{4,4} + 3 \cdot R_f}$$

$$|I_{0_SLG}(0.5, 0)| = 1.0853$$

$$\arg(I_{0_SLG}(0.5, 0)) = -90 \text{ deg}$$

Then equiv at fault point

$$I_{1_SLG}(M, R_f) := I_{0_SLG}(M, R_f)$$

$$I_{2_SLG}(M, R_f) := I_{0_SLG}(M, R_f)$$

$$I_{ABC_SLG}(M, R_f) := A_{012} \cdot \begin{pmatrix} I_{0_SLG}(M, R_f) \\ I_{1_SLG}(M, R_f) \\ I_{2_SLG}(M, R_f) \end{pmatrix}$$

$$|I_{ABC_SLG}(0.5, 0)| = \begin{pmatrix} 3.2558 \\ 0 \\ 0 \end{pmatrix} \cdot \text{pu}$$

$$\arg(I_{ABC_SLG}(0.5, 0)) = \begin{pmatrix} -90 \\ 18.4349 \\ 18.4349 \end{pmatrix} \text{ deg}$$

- Angles meaningless when magnitude is 0

- Now find voltages in each sequence component)

$$\Delta V_{1_SLG}(M, R_f) := Z_1(M) \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{1_SLG}(M, R_f) \end{pmatrix}$$


-I₁ fault

$$|\Delta V_{1_SLG}(0.5, 0)| = \begin{pmatrix} 0.0362 \\ 0.0543 \\ 0.1447 \\ 0.0965 \\ 0.2351 \end{pmatrix}$$

$$\arg(\Delta V_{1_SLG}(0.5, 0)) = \begin{pmatrix} 150 \\ 180 \\ -180 \\ 150 \\ 180 \end{pmatrix} \text{ deg}$$



Substation

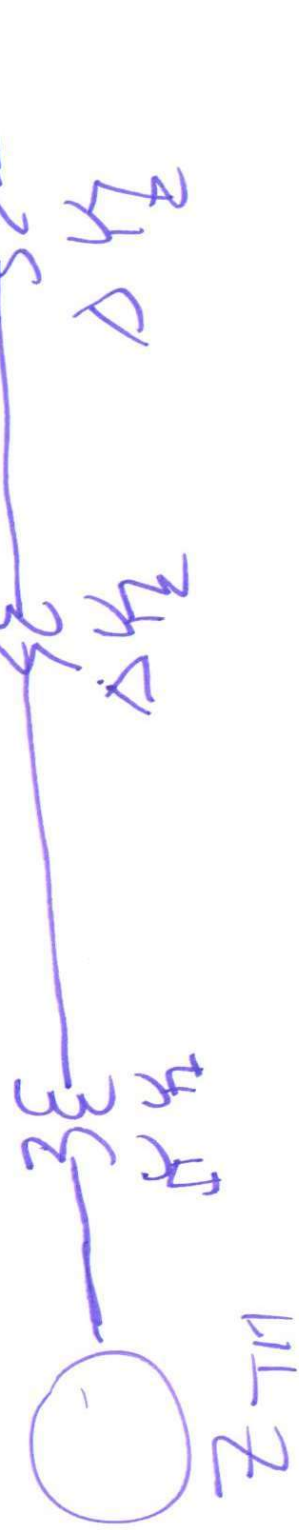

Simplify $\rightarrow Z_f = 0$

$(F_{BF} \cdot Z_f = 0)$
 $V_{B6} = V_{CG}$

$$V_1 = \frac{1}{3} [V_{A6} + aV_{B6} + a^2V_{B6}]$$

$$V_2 = \frac{1}{3} [V_{A6} + a^2V_{B6} + aV_{B6}] = V_1$$

$$V_1 = V_2$$

$$I_1 = -I_2$$



$$\underline{I}_1 = \frac{V_{TH}}{Z_{1TH} + Z_{2TH}}$$

$$\underline{I}_2 = -\underline{I}_1$$

$$\underline{I}_0 = 0 \quad V_0 = 0$$

$$Z_f \neq 0$$

$$V_{B6} - V_{CG} = Z_f \cdot I_{Bf}$$

In terms of A reference symmetrical components

$$V_{B1} = a^2 V_{A1}$$

$$V_{C1} = a V_{A1}$$

$$V_{B2} = a V_{A2}$$

$$(V_{B6} - V_{CG}) = (V_{A0} - V_{A0}) + V_{A1} (a^2 - a) + V_{A2} (a - a^2)$$

$$= Z_f \begin{pmatrix} I_{A0} \\ 0 \\ I_{B1} \end{pmatrix} + a^2 I_{A1} + a I_{A2} - a I_{A1}$$

$$= Z_f (I_{A1} (a^2 - a))$$


$$V_{BG} - V_{C6} = Z_f I_B f$$

$$\downarrow$$

$$\cancel{(a^2 - a)} (V_{A1} - V_{A2}) = \cancel{(a^2 - a)} I_{A1} \cdot Z_f$$

$$(V_{A1} - V_{A2}) = I_{A1} Z_f$$

$$I_{A1} = -I_{A2}$$

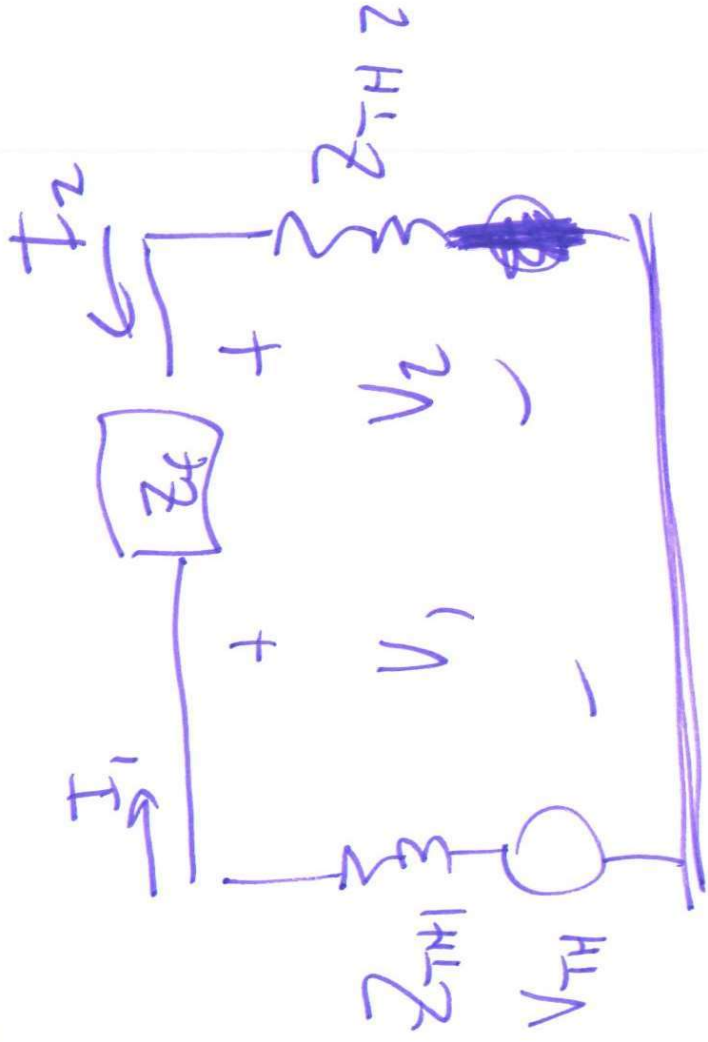

$$I_1 = \frac{V_{TH}}{Z_{TH} + Z_L + Z_L}$$

From Name	To Name	Phase Cur A From	Phase Ang A From	Phase Cur B From	Phase Ang B From	Phase Cur C From	Phase Ang C From
BUS S	BUS 1	1.25318	-90	1.25318	90	0	0
BUS 1	BUS 2	0	0	0	0	0	0
BUS 1	FaultPt	2.0197	-90	0.15086	90	0.15086	90
BUS R	BUS 2	0.62659	-90	0.62659	90	0	0
FaultPt	BUS 2	1.23615	90	0.15086	90	0.15086	90

Good match with calculations above.

LL Fault:

$$I_{1_LL}(M, R_f) := \frac{V_f}{Z_1(M)_{4,4} + Z_2(M)_{4,4} + R_f}$$

$$I_{2_LL}(M, R_f) := -I_{1_LL}(M, R_f)$$

$$I_{0_LL} := 10^{-15}$$

Approximately zero, works better with MathCAD.

$$I_{ABC_LL}(M, R_f) := A_{012} \cdot \begin{pmatrix} I_{0_LL} \\ I_{1_LL}(M, R_f) \\ I_{2_LL}(M, R_f) \end{pmatrix}$$

M, Rf

$$|I_{1_LL}(0.5, 0)| = 2.3077$$

$$\arg(I_{1_LL}(0.5, 0)) = -90 \cdot \text{deg}$$

$$\overrightarrow{\arg(I_{ABC_LL}(0.5, 0))} = \begin{pmatrix} 0 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$


$$\overrightarrow{|I_{ABC_LL}(0.5, 0)|} = \begin{pmatrix} 0 \\ 3.997 \\ 3.997 \end{pmatrix} \cdot \text{pu}$$

$$\frac{I_B}{I_1} = -\sqrt{3}$$

$$V_{\text{ABCB1.LL}}(M, R_f) := A_{012} \cdot \begin{pmatrix} V_{0LL}(M, R_f)_1 \\ V_{1LL}(M, R_f)_1 \\ V_{2LL}(M, R_f)_1 \end{pmatrix} \quad \left| \overrightarrow{V_{\text{ABCB1.LL}}(0.5, 0)} \right| = \begin{pmatrix} 1 \\ 0.8329 \\ 0.8329 \end{pmatrix} \cdot \text{pu} \quad \arg(V_{\text{ABCB1.LL}}(0.5, 0)) = \begin{pmatrix} 0 \\ -126.8903 \\ 126.8903 \end{pmatrix} \cdot \text{deg}$$

- ABC Voltages at Bus S

$$V_{\text{ABCS.LL}}(M, R_f) := A_{012} \cdot \begin{pmatrix} V_{0LL}(M, R_f)_0 \\ V_{1LL}(M, R_f)_0 \\ V_{2LL}(M, R_f)_0 \end{pmatrix} \quad \left| \overrightarrow{V_{\text{ABCS.LL}}(0.5, 0)} \right| = \begin{pmatrix} 0.9638 \\ 0.9638 \\ 0.8462 \end{pmatrix} \cdot \text{pu} \quad \arg(V_{\text{ABCS.LL}}(0.5, 0)) = \begin{pmatrix} -26.0368 \\ -153.9632 \\ 90 \end{pmatrix} \cdot \text{deg}$$

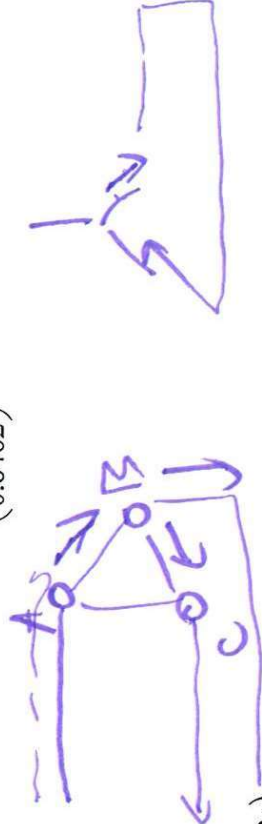

- Branch currents
- Relay 1 currents

$$I_{1_B1.LL}(M, R_f) := \frac{V_{1LL}(M, R_f)_1 - V_{1LL}(M, R_f)_4}{M \cdot Z_{L11}} \quad |I_{1_B1.LL}(0.5, 0)| = 1.5385 \quad \arg(I_{1_B1.LL}(0.5, 0)) = -90 \cdot \text{deg}$$

$$I_{2_B1.LL}(M, R_f) := \frac{V_{2LL}(M, R_f)_1 - V_{2LL}(M, R_f)_4}{M \cdot Z_{L12}} \quad |I_{2_B1.LL}(0.5, 0)| = 1.5385 \quad \arg(I_{2_B1.LL}(0.5, 0)) = 90 \cdot \text{deg}$$

$$I_0_{B1LL}(M, R_f) := \frac{V_{0LL}(M, R_f)_1 - V_{0LL}(M, R_f)_4}{M \cdot Z_{L10}}$$

$$\arg(I_0_{B1LL}(0.5, 0)) = 0 \cdot \text{deg}$$

$$I_{ABC_B1LL}(M, R_f) := A_{012} \cdot \begin{pmatrix} I_0_{B1LL}(M, R_f) \\ I_1_{B1LL}(M, R_f) \\ I_2_{B1LL}(M, R_f) \end{pmatrix}$$

$$\overline{I_{ABC_B1LL}(0.5, 0)} = \begin{pmatrix} 0 \\ 2.6647 \\ 2.6647 \end{pmatrix} \cdot \text{pu} \quad \arg(I_{ABC_B1LL}(0.5, 0)) = \begin{pmatrix} 21.2839 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

- LV side of transformer (Bus S)

$$I_1_{BSLL}(M, R_f) := \frac{V_S \cdot e^{-j \cdot 30 \text{deg}} - V_{1LL}(M, R_f)_0}{jX_{G11}}$$

$$\arg(I_1_{BSLL}(0.5, 0)) = -120 \cdot \text{deg}$$

$$I_2_{BSLL}(M, R_f) := \frac{0 - V_{2LL}(M, R_f)_0}{jX_{G12}}$$


$$\arg(I_2_{BSLL}(0.5, 0)) = 120 \cdot \text{deg}$$

$$I_0_{BSLL} := 0$$

$$I_{ABC_BSLL}(M, R_f) := A_{012} \cdot \begin{pmatrix} I_0_{BSLL} \\ I_1_{BSLL}(M, R_f) \\ I_2_{BSLL}(M, R_f) \end{pmatrix}$$

$$\overline{I_{ABC_BSLL}(0.5, 0)} = \begin{pmatrix} 1.5385 \\ 1.5385 \\ 3.0769 \end{pmatrix} \cdot \text{pu} \quad \arg(I_{ABC_BSLL}(0.5, 0)) = \begin{pmatrix} 180 \\ 180 \\ 0 \end{pmatrix} \cdot \text{deg}$$

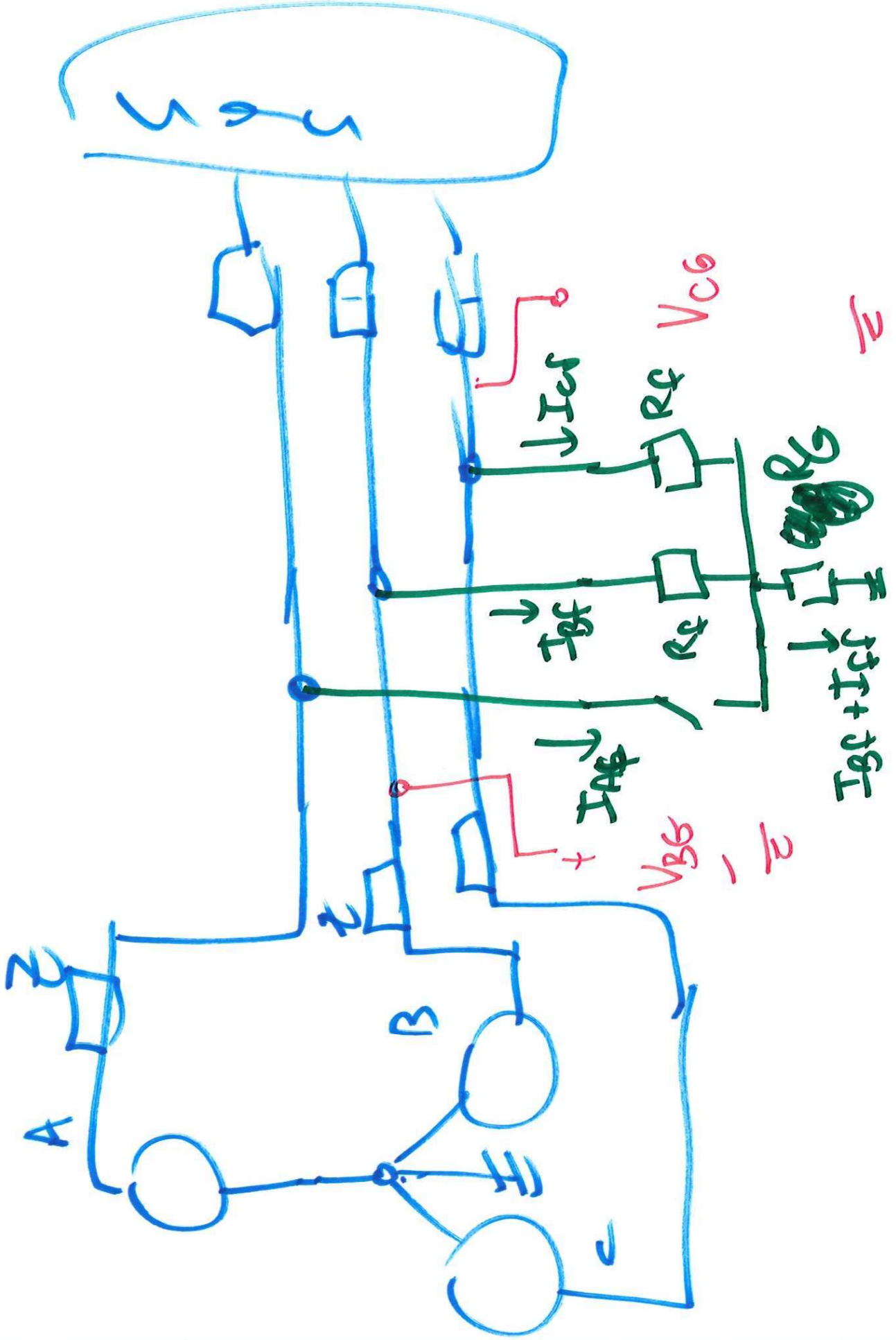△ side the largest phase current is larger than any of fault side for LL fault



constraints

$$I_{Af} = 0$$

we don't know I_B relative to I_C

$$V_{BG} = I_{Bf} \cdot R_f + (I_{Bf} + I_{Cf}) R_G$$

$$V_{CG} = I_{Cf} \cdot R_f + (I_{Bf} + I_{Cf}) R_G$$

Derivation of the DLG Fault Sequence Connections

A. ABC Domain Boundary Conditions

$$I_a = 0$$

$$I_b = I_g \quad I_c = I_f$$

B. Transform Boundary Conditions to Sequence Domain (phase A components)

$$I_a = 0 = I_0 + I_1 + I_2$$

$$I_b = I_0 + a^2 \cdot I_1 + a \cdot I_2$$

$$I_c = I_0 + a \cdot I_1 + a^2 \cdot I_2$$

(1)

$$V_{BG} = I_b \cdot (R_f + R_g) + I_c \cdot R_g$$

(2)

$$V_{CG} = (I_b + I_c) \cdot R_g + I_c \cdot (R_f)$$

$$= I_b \cdot R_g + I_c \cdot (R_f + R_g)$$

C. Now rewrite equations (1) and (2) in the sequence domain

$$V_{BG} = V_0 + a^2 \cdot V_1 + a \cdot V_2 = I_b \cdot (R_f + R_g) + I_c \cdot R_g$$

$$= (I_0 + a^2 \cdot I_1 + a \cdot I_2) \cdot (R_f + R_g) + (I_0 + a \cdot I_1 + a^2 \cdot I_2) \cdot R_g$$

(3)

$$V_{CG} = V_0 + a \cdot V_1 + a^2 \cdot V_2 = I_b \cdot R_g + I_c \cdot (R_f + R_g)$$

$$= (I_0 + a^2 \cdot I_1 + a \cdot I_2) \cdot R_g + (I_0 + a \cdot I_1 + a^2 \cdot I_2) \cdot (R_f + R_g)$$

(4)

D. Now subtract equation (4) from equation (3):

$$V_{BG} - V_{CG} = (V_0 - V_0) + (a^2 - a) \cdot V_1 + (a - a^2) \cdot V_2 = (a^2 - a) \cdot I_1 \cdot R_f + (a - a^2) \cdot I_2 \cdot R_f$$

Simplifies to:

$$(a^2 - a) \cdot V_1 - (a - a^2) \cdot V_2 = (a^2 - a) \cdot I_1 \cdot R_f - (a - a^2) \cdot I_2 \cdot R_f$$

Divide by $(a^2 - a)$:

$$V_1 - V_2 = (I_1 - I_2) \cdot R_f$$

- Collect positive and negative sequence terms

$$V_1 - I_1 \cdot R_f = V_2 - I_2 \cdot R_f \quad (5)$$

E. Now add equation (4) to equation (3):

$$V_{BG} + V_{CG} = 2 \cdot V_0 + (a^2 + a) \cdot V_1 + (a + a^2) \cdot V_2$$

$$= (2 \cdot I_0) \cdot (R_f + 2 \cdot R_g) + (a^2 + a) \cdot I_1 \cdot R_f + (a + a^2) \cdot I_2 \cdot R_f + (2 \cdot (a^2 + a) \cdot (I_1 + I_2)) \cdot R_g$$

- Collect terms:

$$2 \cdot V_0 + (a^2 + a) \cdot (V_1 + V_2) = (R_f + 2 \cdot R_g) \cdot (2 \cdot I_0 + (a^2 + a) \cdot (I_1 + I_2))$$

- Substitute in the following relationship:

$$(a^2 + a) = -1 \text{ which comes from } (1 + a^2 + a) = 0$$

- Resulting equation

$$2 \cdot V_0 - (V_1 + V_2) = (R_f + 2 \cdot R_g) \cdot (2 \cdot I_0 - (I_1 + I_2))$$

- Collect all zero sequence terms on the left-hand side, and positive and negative on right:

$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 4 \cdot I_0 \cdot R_g = (V_1 + V_2) - (I_1 + I_2) \cdot (R_f) - (I_1 + I_2) \cdot (2 \cdot R_g)$$

- Use the boundary condition for the currents:

$$I_1 + I_2 + I_0 = 0 \text{ which implies: } I_1 + I_2 = -I_0$$

- Substitute this only for the R_g term

$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 4 \cdot I_0 \cdot R_g = (V_1 + V_2) - (I_1 + I_2) \cdot (R_f) + (I_0) \cdot (2 \cdot R_g)$$

- Again, collect all zero sequence terms on the left-hand side:

$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 6 \cdot I_0 \cdot R_g = (V_1 + V_2) - (I_1 + I_2) \cdot (R_f)$$

- Substitute in equation (5) on the right hand, resulting in:

$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 6 \cdot I_0 \cdot R_g = 2 \cdot (V_1 - I_1 \cdot R_f)$$

- Divide by 2, leaving:

$$V_0 - I_0 \cdot R_f - 3 \cdot I_0 \cdot R_g = V_1 - I_1 \cdot R_f$$

(6)

F. Final result:

$$V_0 - I_0 \cdot R_f - 3 \cdot I_0 \cdot R_g = V_1 - I_1 \cdot R_f = V_2 - I_2 \cdot R_f$$

