

## Powerflow Example

$$a := 1 \cdot e^{j \cdot 120\text{deg}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$


$$\text{pu} := 1$$

$$\text{MVA} := 1000\text{kW}$$

$$\angle(\text{mag}, \text{ang}) := \text{mag} \cdot \cos(\text{ang} \cdot \text{deg}) + j \cdot \text{mag} \cdot \sin(\text{ang} \cdot \text{deg})$$

The system shown below has two synchronous generators.

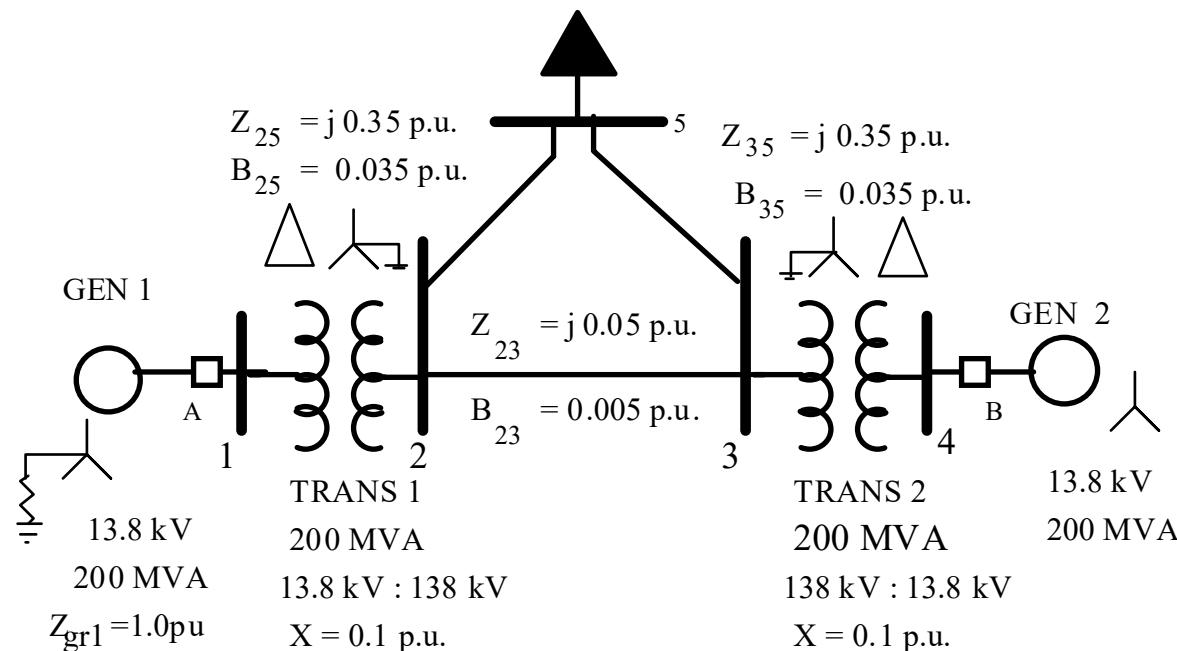- Line impedances are on a 138kV, 100MVA base



$$S_B := 100\text{MVA}$$

- Bus 1 is slack bus
- Set  $|V1| = 1.0\text{pu}$
- Set PG2 to 50MW
- Set  $|V4|$  to 1.0pu (generator 2 terminal voltage)

Set line impedance parameters (set zero sequence line impedances to 3 times the positive sequence values):

$$Z_{L23} := j \cdot 0.05 \text{pu} \quad B_{c23} := 0.005 \cdot \text{pu}$$

$$Z_{L25} := j \cdot 0.35 \text{pu} \quad B_{c25} := 0.035 \cdot \text{pu}$$

$$Z_{L35} := j \cdot 0.35 \text{pu} \quad B_{c35} := 0.035 \cdot \text{pu}$$

Transformer 1 Change of base (zero sequence impedances match positive sequence):

$$X_{t11} := 0.1 \cdot \left( \frac{S_B}{200 \text{MVA}} \right) \quad X_{t11} = 0.05 \cdot \text{pu} \quad X_{t10} := X_{t11}$$

Transformer 2 Change of base (zero sequence impedances match positive sequence):

$$X_{t21} := 0.1 \cdot \left( \frac{S_B}{200 \text{MVA}} \right) \quad X_{t21} = 0.05 \cdot \text{pu} \quad X_{t20} := X_{t11}$$

A. Assuming the load at Bus 5 is 100MW at 0.9 lagging power factor, perform a power flow solution. Use the voltage at Bus 3 as your angle reference

Options,

- (1) Solve the power flow equations for the entire system using Mathcad solve blocks
- (2) Use Powerworld or a similar load flow problem (at least to check results)

- In order to use V3 as the reference angle, use the angle for V3 from the power flow solution and shift the slack bus angle such that the new angle at Bus 3 is 0.

### **(1) Solve Full Powerflow Solution Using MathCAD Solve Block**

- Positive sequence Y bus for power flow calculations (ignore phase shifts for the moment):

$$Y_{11} := \frac{1}{j \cdot X_{t11}} \quad Y_{12} := \frac{-1}{j \cdot X_{t11}} \quad \bullet \quad \text{Symmetry assumed}$$

$$Y_{22} := \frac{1}{j \cdot X_{t11}} + \frac{1}{Z_{L23}} + \frac{1}{Z_{L25}} + \frac{j \cdot B_{c23}}{2} + \frac{j \cdot B_{c25}}{2} \quad Y_{23} := \frac{-1}{Z_{L23}} \quad Y_{25} := \frac{-1}{Z_{L25}}$$

$$Y_{33} := \frac{1}{j \cdot X_{t21}} + \frac{1}{Z_{L23}} + \frac{1}{Z_{L35}} + \frac{j \cdot B_{c23}}{2} + \frac{j \cdot B_{c35}}{2} \quad Y_{34} := \frac{-1}{j \cdot X_{t21}} \quad Y_{35} := \frac{-1}{Z_{L35}}$$

$$Y_{44} := \frac{1}{j \cdot X_{t11}} \quad Y_{55} := \frac{1}{Z_{L25}} + \frac{1}{Z_{L35}} + \left( \frac{j \cdot B_{c25}}{2} + \frac{j \cdot B_{c35}}{2} \right)$$

$$Y_{\text{busPF}} := \begin{pmatrix} Y_{11} & Y_{12} & 0 & 0 & 0 \\ Y_{12} & Y_{22} & Y_{23} & 0 & Y_{25} \\ 0 & Y_{23} & Y_{33} & Y_{34} & Y_{35} \\ 0 & 0 & Y_{34} & Y_{44} & 0 \\ 0 & Y_{25} & Y_{35} & 0 & Y_{55} \end{pmatrix} \quad Y_{\text{busPF}} = \begin{pmatrix} -20i & 20i & 0 & 0 & 0 \\ 20i & -42.8371i & 20i & 0 & 2.8571i \\ 0 & 20i & -42.8371i & 20i & 2.8571i \\ 0 & 0 & 20i & -20i & 0 \\ 0 & 2.8571i & 2.8571i & 0 & -5.6793i \end{pmatrix}$$

$$P2 := 0 \quad P3 := 0 \quad P4 := 0.5 \text{pu} \quad P5 := -1.0 \text{pu}$$

$$Q2 := 0 \quad Q3 := 0 \quad Q5 := P5 \cdot \tan(\arccos(0.9)) \quad Q5 = -0.4843 \cdot \text{pu}$$

$$V1 := 1 \quad V4 := 1 \quad a1 := 0$$

- P5 and Q5 are negative injections since they represent a load

- Initial guesses

$$V2 := 1 \quad a2 := 0 \text{deg}$$

$$V3 := 1 \quad a3 := 0 \text{deg}$$

$$a4 := 0$$

$$V5 := 1 \quad a5 := 0\text{deg}$$

Given

$$P2 = V2 \cdot V1 \cdot \text{Im}(Y_{12}) \cdot \sin(a2 - a1) + V2 \cdot V3 \cdot \text{Im}(Y_{23}) \cdot \sin(a2 - a3) + V2 \cdot V5 \cdot \text{Im}(Y_{25}) \cdot \sin(a2 - a5)$$

$$P3 = V3 \cdot V4 \cdot \text{Im}(Y_{34}) \cdot \sin(a3 - a4) + V3 \cdot V2 \cdot \text{Im}(Y_{23}) \cdot \sin(a3 - a2) + V3 \cdot V5 \cdot \text{Im}(Y_{35}) \cdot \sin(a3 - a5)$$

$$P4 = V4 \cdot V3 \cdot \text{Im}(Y_{34}) \cdot \sin(a4 - a3)$$

- Need to add additional terms to include transformer phase shift

$$P5 = V5 \cdot V2 \cdot \text{Im}(Y_{25}) \cdot \sin(a5 - a2) + V5 \cdot V3 \cdot \text{Im}(Y_{35}) \cdot \sin(a5 - a2)$$

$$Q2 = -V2^2 \text{Im}(Y_{22}) - V2 \cdot V1 \cdot \text{Im}(Y_{12}) \cdot \cos(a2 - a1) - V2 \cdot V3 \cdot \text{Im}(Y_{23}) \cdot \cos(a2 - a3) - V2 \cdot V5 \cdot \text{Im}(Y_{25}) \cdot \cos(a2 - a5)$$

$$Q3 = -V3^2 \text{Im}(Y_{33}) - V3 \cdot V4 \cdot \text{Im}(Y_{34}) \cdot \cos(a3 - a4) - V3 \cdot V2 \cdot \text{Im}(Y_{23}) \cdot \cos(a3 - a2) - V3 \cdot V5 \cdot \text{Im}(Y_{35}) \cdot \cos(a3 - a5)$$

$$Q5 = -V5^2 \text{Im}(Y_{55}) - V5 \cdot V2 \cdot \text{Im}(Y_{25}) \cdot \cos(a5 - a2) - V5 \cdot V3 \cdot \text{Im}(Y_{35}) \cdot \cos(a5 - a2)$$

$$X := \text{Find}(V2, a2, V3, a3, a4, V5, a5)$$

$$mV2 := X_0 \quad mV2 = 0.9819 \cdot \text{pu} \quad \theta_2 := X_1 \quad \theta_2 = -1.459 \cdot \text{deg}$$

$$mV3 := X_2 \quad mV3 = 0.9819 \cdot \text{pu} \quad \theta_3 := X_3 \quad \theta_3 = -1.459 \cdot \text{deg}$$

$$mV5 := X_5 \quad mV5 = 0.8687 \cdot \text{pu} \quad \theta_4 := X_4 \quad \theta_4 = 0 \cdot \text{deg}$$

$$\theta_5 := X_6 \quad \theta_5 = -13.2983 \cdot \text{deg}$$

- Note, that if we include the transformer phase shift, we need to subtract 30 degrees from the voltages at Bus 1 and Bus 4:

$$\theta_{1\_LV} := \alpha_1 - 30\text{deg} \quad \theta_{1\_LV} = -30\cdot\text{deg}$$

$$\theta_{4\_LV} := \alpha_4 - 30\text{deg} \quad \theta_{4\_LV} = -30\cdot\text{deg}$$

- Finally, we need to shift the angle, by subtracting the angle of  $\theta_3$  to each of the bus angles such that angle at Bus 3 = 0.

$$\theta_{1\_p} := \theta_{1\_LV} - \theta_3 \quad \theta_{1\_p} = -28.541\cdot\text{deg}$$

$$\theta_{2\_p} := \theta_2 - \theta_3 \quad \theta_{2\_p} = 0\cdot\text{deg}$$

$$\theta_{3\_p} := \theta_3 - \theta_3 \quad \theta_{3\_p} = 0\cdot\text{deg}$$

$$\theta_{4\_p} := \theta_{4\_LV} - \theta_3 \quad \theta_{4\_p} = -28.541\cdot\text{deg}$$

$$\theta_{5\_p} := \theta_5 - \theta_3 \quad \theta_{5\_p} = -11.8393\cdot\text{deg}$$

- Calculate generator currents (note that you need to account for transformer phase shift)

$$I_{\text{gen1}} := \frac{[V1 \cdot e^{j \cdot \theta_{1\_p}} - mV2 \cdot e^{j \cdot \theta_{2\_p}} \cdot (e^{-j \cdot 30\text{deg}})]}{(j \cdot X_{t11})} \quad |I_{\text{gen1}}| = 0.6216\cdot\text{pu} \quad \arg(I_{\text{gen1}}) = -64.9864\cdot\text{deg}$$


$$S_{\text{gen1}} := V1 \cdot e^{j \cdot \theta_{1\_p}} \cdot \overline{I_{\text{gen1}}} \quad S_{\text{gen1}} = (0.5 + 0.3692i)\cdot\text{pu}$$

$$I_{\text{gen2}} := \frac{[V4 \cdot e^{j \cdot \theta_{4\_p}} - mV3 \cdot e^{j \cdot \theta_{3\_p}} \cdot (e^{-j \cdot 30\text{deg}})]}{(j \cdot X_{t21})} \quad |I_{\text{gen2}}| = 0.6216\cdot\text{pu} \quad \arg(I_{\text{gen2}}) = -64.9864\cdot\text{deg}$$

$$S_{\text{gen2}} := V4 \cdot e^{j \cdot \theta_{4\_p}} \cdot \overline{I_{\text{gen2}}} \quad S_{\text{gen2}} = (0.5 + 0.3692i)\cdot\text{pu}$$
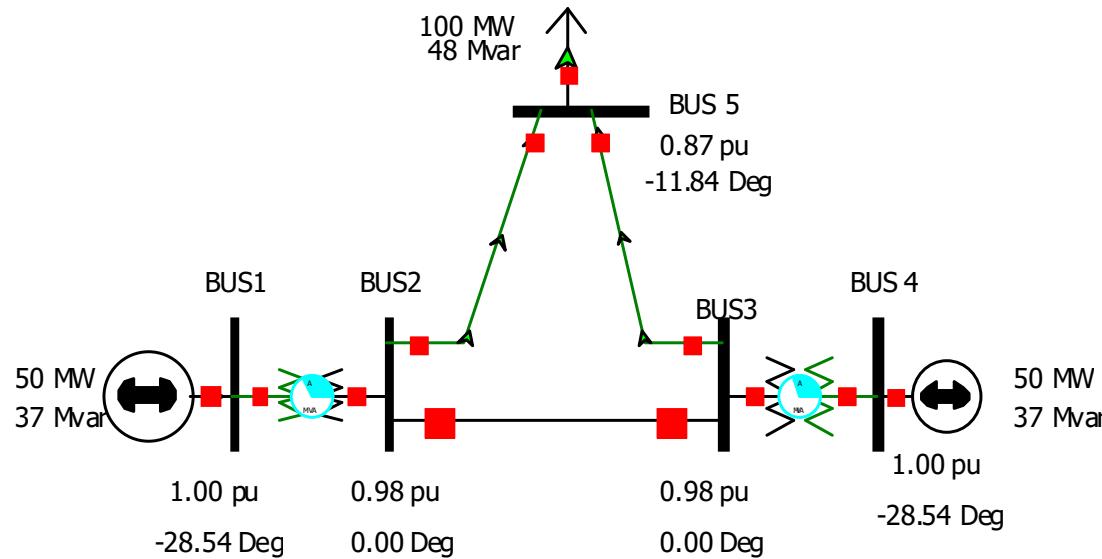
### Powerworld Implementation and Results

- The system was entered into Powerworld, with the system MVA base set to 200MVA
- Slack bus angle (angle of V1) was changed to -28.538 degrees so Bus 3 would be at 0 degrees after first solution.



- Power flow results:

$$V_{Bus1} := 1.0 \angle -28.54$$

$$V_{Bus2} := 0.9819 \angle 0.00$$

$$V_{Bus3} := 0.9819 \angle 0.00$$

$$V_{Bus4} := 1.0 \angle -28.54$$

$$V_{Bus5} := 0.8688 \angle -11.84$$

Earlier we had

$$V_1 = 1 \quad \theta_{1\_p} = -28.541\cdot\text{deg}$$

$$mV_2 = 0.9819 \quad \theta_{2\_p} = 0\cdot\text{deg}$$

$$mV_3 = 0.9819 \quad \theta_{3\_p} = 0\cdot\text{deg}$$

$$V_4 = 1 \quad \theta_{4\_p} = -28.541\cdot\text{deg}$$

$$mV_5 = 0.8687 \quad \theta_{5\_p} = -11.8393\cdot\text{deg}$$

- The results match, so the currents will match

**$Y_{bus}$  with phase shifts included:**

$$Y_{1Bus} := \begin{pmatrix} Y_{11} & \frac{-1 \cdot e^{-j \cdot 30\text{deg}}}{j \cdot X_{t11}} & 0 & 0 & 0 \\ \frac{-1 \cdot e^{j \cdot 30\text{deg}}}{j \cdot X_{t11}} & Y_{22} & \frac{-1}{Z_{L23}} & 0 & \frac{-1}{Z_{L25}} \\ 0 & \frac{-1}{Z_{L23}} & Y_{33} & \frac{-1 \cdot e^{j \cdot 30\text{deg}}}{j X_{t21}} & \frac{-1}{Z_{L35}} \\ 0 & 0 & \frac{-1 \cdot e^{-j \cdot 30\text{deg}}}{j X_{t21}} & Y_{44} & 0 \\ 0 & \frac{-1}{Z_{L25}} & \frac{-1}{Z_{L35}} & 0 & Y_{55} \end{pmatrix}$$

$$Y_{1Bus} = \begin{pmatrix} -20i & 10 + 17.3205i & 0 & 0 & 0 \\ -10 + 17.3205i & -42.8371i & 20i & 0 & 2.8571i \\ 0 & 20i & -42.8371i & -10 + 17.3205i & 2.8571i \\ 0 & 0 & 10 + 17.3205i & -20i & 0 \\ 0 & 2.8571i & 2.8571i & 0 & -5.6793i \end{pmatrix}$$

	Number	Name	Bus 1	Bus 2	Bus 3	Bus 4	Bus 5
1	1	BUS1	0.00 - j20.00	10.00 + j17.32			
2	2	BUS2	-10.00 + j17.32	0.00 - j42.84	-0.00 + j20.00		-0.00 + j2.86
3	3	BUS3		-0.00 + j20.00	0.00 - j42.84	-10.00 + j17.32	-0.00 + j2.86
4	4	BUS 4			10.00 + j17.32	0.00 - j20.00	
5	5	BUS 5		-0.00 + j2.86	-0.00 + j2.86		0.00 - j5.68