

ECE 523  
Symmetrical Components

Session 14

### Derivation of the DLG Fault Sequence Connections

A. ABC Domain Boundary Conditions

$$I_A = 0$$

$$I_B = I_{Bf} \quad I_C = I_{Cf}$$

$$V_{BG} = I_B \cdot (R_f) + (I_B + I_C) \cdot R_g$$

$$= I_B \cdot (R_f + R_g) + I_C \cdot R_g \quad (1)$$

$$V_{CG} = (I_B + I_C) \cdot R_g + I_C \cdot (R_f)$$

$$= I_B \cdot R_g + I_C \cdot (R_f + R_g) \quad (2)$$

B. Transform Boundary Conditions to Sequence Domain (phase A components)

$$I_A = 0 = I_0 + I_1 + I_2$$

$$I_B = I_0 + a^2 \cdot I_1 + a \cdot I_2$$

$$I_C = I_0 + a \cdot I_1 + a^2 \cdot I_2$$

$$V_{BG} = V_0 + a^2 \cdot V_1 + a \cdot V_2$$

$$V_{CG} = V_0 + a \cdot V_1 + a^2 \cdot V_2$$

C. Now rewrite equations (1) and (2) in the sequence domain

$$\begin{aligned} V_{BG} &= V_0 + a^2 \cdot V_1 + a \cdot V_2 = I_B \cdot (R_f + R_g) + I_C \cdot R_g \\ &= (I_0 + a^2 \cdot I_1 + a \cdot I_2) \cdot (R_f + R_g) + (I_0 + a \cdot I_1 + a^2 \cdot I_2) \cdot R_g \end{aligned} \quad (3)$$

$$\begin{aligned} V_{CG} &= V_0 + a \cdot V_1 + a^2 \cdot V_2 = I_B \cdot R_g + I_C \cdot (R_f + R_g) \\ &= (I_0 + a^2 \cdot I_1 + a \cdot I_2) \cdot R_g + (I_0 + a \cdot I_1 + a^2 \cdot I_2) \cdot (R_f + R_g) \end{aligned} \quad (4)$$

D. Now subtract equation (4) from equation (3):

$$\begin{aligned} V_{BG} - V_{CG} &= (V_0 - V_0) + (a^2 - a) \cdot V_1 + (a - a^2) \cdot V_2 \\ &= (I_0 - I_0) \cdot (R_f + 2 \cdot R_g) + (a^2 - a) \cdot I_1 \cdot R_f + (a - a^2) \cdot I_2 \cdot R_f + (a^2 + a - (a^2 + a)) \cdot (I_1 + I_2) \cdot R_g \end{aligned}$$

- Simplifies to:

$$(a^2 - a) \cdot V_1 - (a^2 - a) \cdot V_2 = (a^2 - a) \cdot I_1 \cdot R_f - (a^2 - a) \cdot I_2 \cdot R_f$$

- Divide by  $(a^2 - a)$ :


$$V_1 - V_2 = (I_1 - I_2) \cdot R_f$$

(5)

02/1  
L17

L13 14/16

02/2  
h17

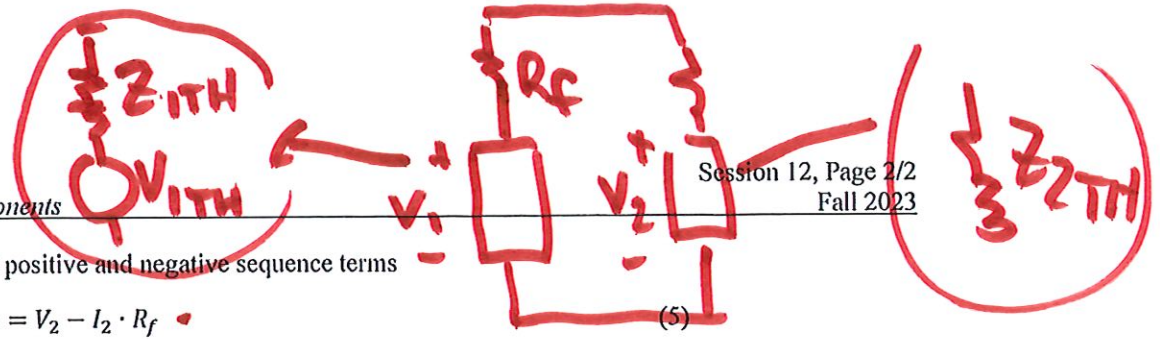

- Collect positive and negative sequence terms

$$V_1 - I_1 \cdot R_f = V_2 - I_2 \cdot R_f \quad (5)$$

E. Now add equation (4) to equation (3):

$$\begin{aligned} V_{BG} + V_{CG} &= 2 \cdot V_0 + (a^2 + a) \cdot V_1 + (a + a^2) \cdot V_2 \\ &= (2 \cdot I_0) \cdot (R_f + 2 \cdot R_g) + (a^2 + a) \cdot I_1 \cdot R_f + (a + a^2) \cdot I_2 \cdot R_f + (2 \cdot (a^2 + a)) \cdot (I_1 + I_2) \cdot R_g \end{aligned}$$

- Collect terms:

$$2 \cdot V_0 + (a^2 + a) \cdot (V_1 + V_2) = (R_f + 2 \cdot R_g) \cdot (2 \cdot I_0 + (a^2 + a) \cdot (I_1 + I_2))$$

- Substitute in the following relationship:

$$(a^2 + a) = -1 \text{ which comes from } (1 + a^2 + a) = 0$$

- Resulting equation

$$2 \cdot V_0 - (V_1 + V_2) = (R_f + 2 \cdot R_g) \cdot (2 \cdot I_0 - (I_1 + I_2))$$

- Collect all zero sequence terms on the left-hand side, and positive and negative on right:

$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 4 \cdot I_0 \cdot R_g = (V_1 + V_2) - (I_1 + I_2) \cdot (R_f) - (I_1 + I_2) \cdot (2 \cdot R_g)$$

- Use the boundary condition for the currents:

$$I_A = I_1 + I_2 + I_0 = 0 \text{ which implies: } I_1 + I_2 = -I_0$$

- Substitute this only for the  $R_g$  term

$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 4 \cdot I_0 \cdot R_g = (V_1 + V_2) - (I_1 + I_2) \cdot (R_f) + (I_0) \cdot (2 \cdot R_g)$$

- Again, collect all zero sequence terms on the left-hand side:


$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 6 \cdot I_0 \cdot R_g = (V_1 + V_2) - (I_1 + I_2) \cdot (R_f)$$

- Substitute in equation (5) on the right hand, resulting in:

$$2 \cdot V_0 - 2 \cdot I_0 \cdot R_f - 6 \cdot I_0 \cdot R_g = 2 \cdot (V_1 - I_1 \cdot R_f)$$

- Divide by 2, leaving:
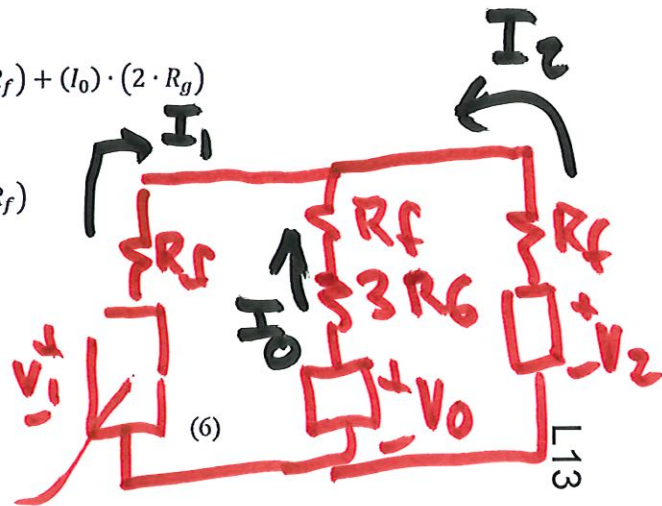
$$V_0 - I_0 \cdot R_f - 3 \cdot I_0 \cdot R_g = V_1 - I_1 \cdot R_f$$




F. Final result:


$$V_0 - I_0 \cdot R_f - 3 \cdot I_0 \cdot R_g = V_1 - I_1 \cdot R_f = V_2 - I_2 \cdot R_f$$

voltages

$$I_A = I_0 + I_1 + I_2 = 0$$

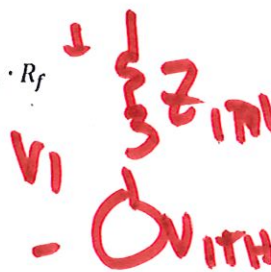

$$I_f R_f + R_G = 0$$

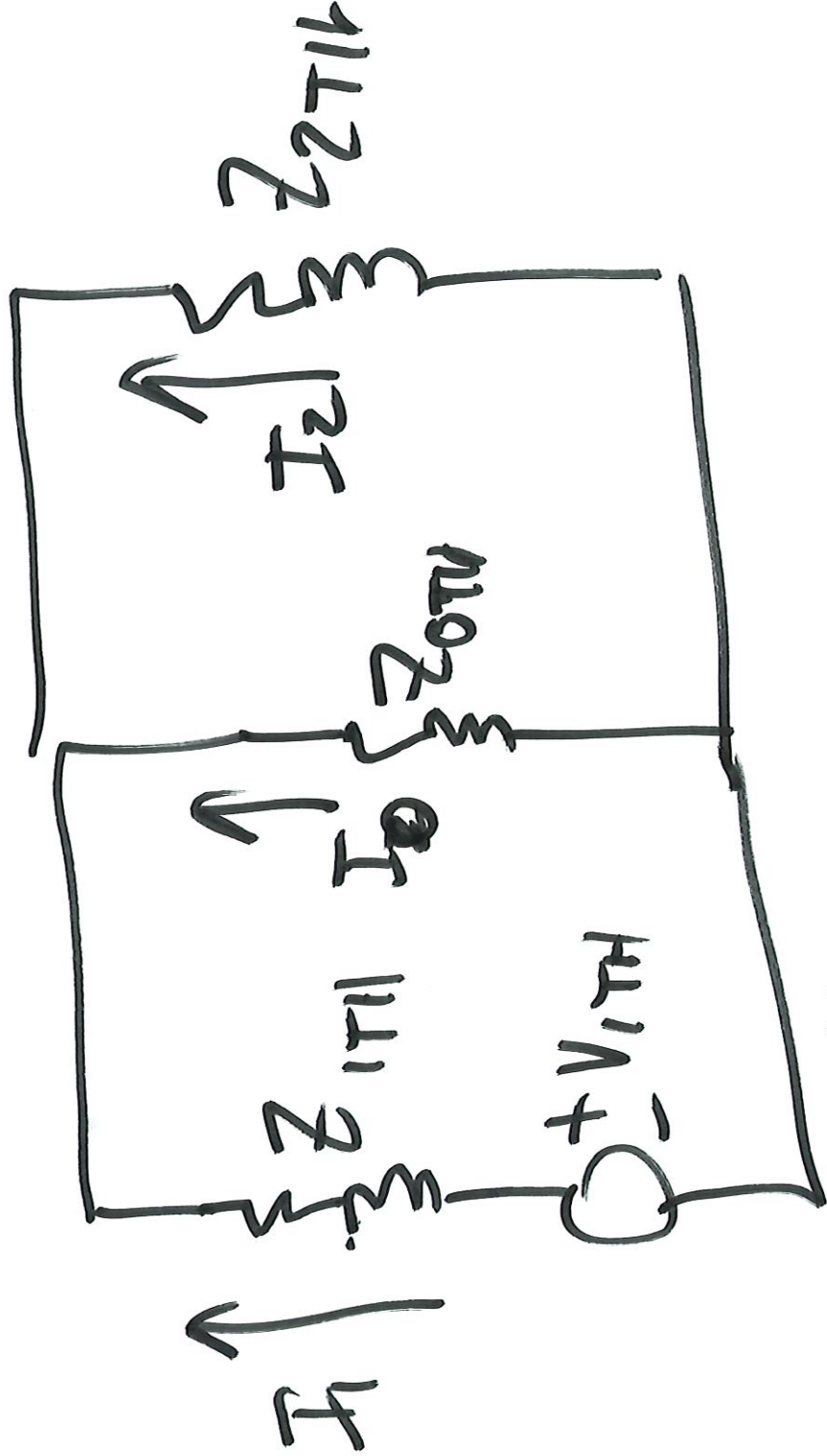

$$I_1 = \frac{V_{IH}}{Z_{IH1} + (Z_{OH2} \parallel Z_{IH2})}$$

Use current dividers for  $I_2 + I_0$

$$\bar{I}_2 = -\bar{I}_1 \left( \frac{\tilde{Z}_{0TH}}{\tilde{Z}_{2TH} + \tilde{Z}_{0TH}} \right)$$

$$\bar{I}_0 = -\bar{I}_1 \left( \frac{\tilde{Z}_{2TH}}{\tilde{Z}_{2TH} + \tilde{Z}_{0TH}} \right)$$

with fault resistances included

$$\bar{I}_1 = \frac{V_{TH}}{(Z_{TH} + R_f) + (Z_{2TH} + R_f) + (Z_{0TH} + R_f + 3R_G)}$$

$$\bar{I}_2 = -\bar{I}_1 \left( \frac{Z_{0TH} + R_f + 3R_f}{Z_{2TH} + R_f + Z_{0TH} + R_f + 3R_G} \right)$$

$$\bar{I}_0 = -\bar{I}_1 \left( \frac{(Z_{2TH} + R_f)}{(Z_{2TH} + R_f + Z_{0TH} + R_f + 3R_G)} \right)$$


Liu 6/20

$$V_{abc\_SLGHV} := A_{012} \cdot \begin{pmatrix} V_{0\_SLGHV} \\ V_{1\_SLGHV} \\ V_{2\_SLGHV} \end{pmatrix}$$

$$\frac{|V_{abc\_SLGHV}|}{0.62} = 1 \cdot pu$$

$$\arg(V_{abc\_SLGHV}) = \begin{pmatrix} 54.06 \\ -90 \\ 125.94 \end{pmatrix} \cdot \text{deg}$$

• Example with two sources:

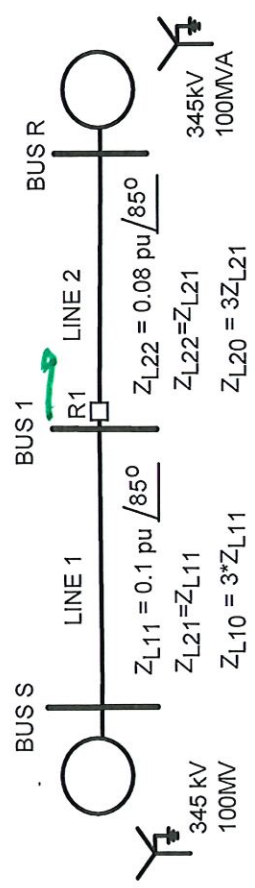

$V_S = 1.0 \text{ pu @ } 0 \text{ deg}$     Per unit line impedances calculated with SB=100MVA and VB=345KV LL  
 $Z_{S1} = j0.03 \text{ pu}$   
 $Z_{S2} = Z_{S1}$   
 $Z_{S0} = 3 \cdot Z_{S1}$

$V_R = 1.0 \text{ pu at } 0 \text{ deg}$   
 $Z_{R1} = j0.06 \text{ pu}$   
 $Z_{R2} = Z_{R1}$   
 $Z_{R0} = 3 \cdot Z_{R1}$

$Z_{L11} := j \cdot 0.03 \text{ pu}$      $Z_{L11} := 0.1 \text{ pu} \cdot e^{j \cdot 85 \text{ deg}}$   
 $Z_{S1}$      $Z_{L11} = 0.01 + 0.1i$

$Z_{L21} := 0.08 \text{ pu} \cdot e^{j \cdot 85 \text{ deg}}$   
 $Z_{L21} = 0.01 + 0.08i$

LM 7/20

$$V_{ABC\_R1}(m) := A_{012} \cdot \begin{pmatrix} V_{R1\_0}(m) \\ V_{R1\_1}(m) \\ V_{R1\_2}(m) \end{pmatrix} \quad \overrightarrow{|V_{ABC\_R1}(0.5)|} = \begin{pmatrix} 0.24 \\ 1.18 \\ 1.18 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(V_{ABC\_R1}(0.5))} = \begin{pmatrix} -0.88 \\ -132.89 \\ 132.99 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC\_R1}(m) := A_{012} \cdot \begin{pmatrix} I_{left\_0}(m) \\ I_{left\_1}(m) \\ I_{left\_2}(m) \end{pmatrix} \quad \overrightarrow{|I_{ABC\_R1}(0.5)|} = \begin{pmatrix} 3.53 \\ 0 \\ 0 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(I_{ABC\_R1}(0.5))} = \begin{pmatrix} -85.88 \\ 49.05 \\ 49.05 \end{pmatrix} \cdot \text{deg}$$

Pre-fault at fault location

DLG faults:

$$I_{f1}(m) := \frac{V_f}{Z_{L2\_1\_thev}(m) + \left( \frac{1}{Z_{L2\_2\_thev}(m)} + \frac{1}{Z_{L2\_0\_thev}(m)} \right)^{-1}}$$

$$I_{f2}(m) := -I_{f1}(m) \cdot \left( \frac{Z_{L2\_0\_thev}(m)}{Z_{L2\_2\_thev}(m) + Z_{L2\_0\_thev}(m)} \right)$$

$$I_{f0}(m) := -I_{f1}(m) \cdot \left( \frac{Z_{L2\_2\_thev}(m)}{Z_{L2\_2\_thev}(m) + Z_{L2\_0\_thev}(m)} \right)$$

Total sequence currents at fault location

(Z2 || Z0)

$$I_{left\_1}(m) := \frac{I_{f1}(m) \cdot [(1-m) \cdot Z_{L21} + Z_{R1}]}{Z_{S1} + Z_{L11} + m \cdot Z_{L21} + [(1-m) \cdot Z_{L21} + Z_{R1}]}$$

pos of pre-fault



L14 8/20

$$I_{\text{left}_2}(m) := \frac{I_{f2}(m) \cdot [(1-m) \cdot Z_{L22} + Z_{R2}]}{Z_{S2} + Z_{L12} + m \cdot Z_{L22} + [(1-m) \cdot Z_{L22} + Z_{R2}]}$$

*202*

$$I_{\text{left}_0}(m) := \frac{I_{f0}(m) \cdot [(1-m) \cdot Z_{L20} + Z_{R0}]}{Z_{S0} + Z_{L10} + m \cdot Z_{L20} + [(1-m) \cdot Z_{L20} + Z_{R0}]}$$

*2050*

$$V_{R1_1}(m) := V_f - I_{\text{left}_1}(m) \cdot (Z_{S1} + Z_{L11})$$

$$V_{R1_2}(m) := 0 - I_{\text{left}_2}(m) \cdot (Z_{S2} + Z_{L12})$$

$$V_{R1_0}(m) := 0 - I_{\text{left}_0}(m) \cdot (Z_{S0} + Z_{L10})$$

*Left side  
for  
V<sub>ABC\_R1</sub>*

$$V_{ABC\_R1}(m) := A_{012} \cdot \begin{pmatrix} V_{R1_0}(m) \\ V_{R1_1}(m) \\ V_{R1_2}(m) \end{pmatrix}$$

$$\begin{matrix} \xrightarrow{|V_{ABC\_R1}(0.5)|} \\ \begin{pmatrix} 1.22 \\ 0.24 \\ 0.24 \end{pmatrix} \cdot \text{pu} \end{matrix}$$


$$\xrightarrow{\arg(V_{ABC\_R1}(0.5))} = \begin{pmatrix} 0.05 \\ -120.88 \\ 119.12 \end{pmatrix} \cdot \text{deg}$$

$$I_{ABC\_R1}(m) := A_{012} \cdot \begin{pmatrix} I_{\text{left}_0}(m) \\ I_{\text{left}_1}(m) \\ I_{\text{left}_2}(m) \end{pmatrix}$$


$$\begin{matrix} \xrightarrow{|I_{ABC\_R1}(0.5)|} \\ \begin{pmatrix} 0 \\ 5.25 \\ 5.25 \end{pmatrix} \cdot \text{pu} \end{matrix}$$

$$\xrightarrow{\arg(I_{ABC\_R1}(0.5 + 10^{-15}))} = \begin{pmatrix} 93.58 \\ 170.22 \\ 18.02 \end{pmatrix} \cdot \text{deg}$$

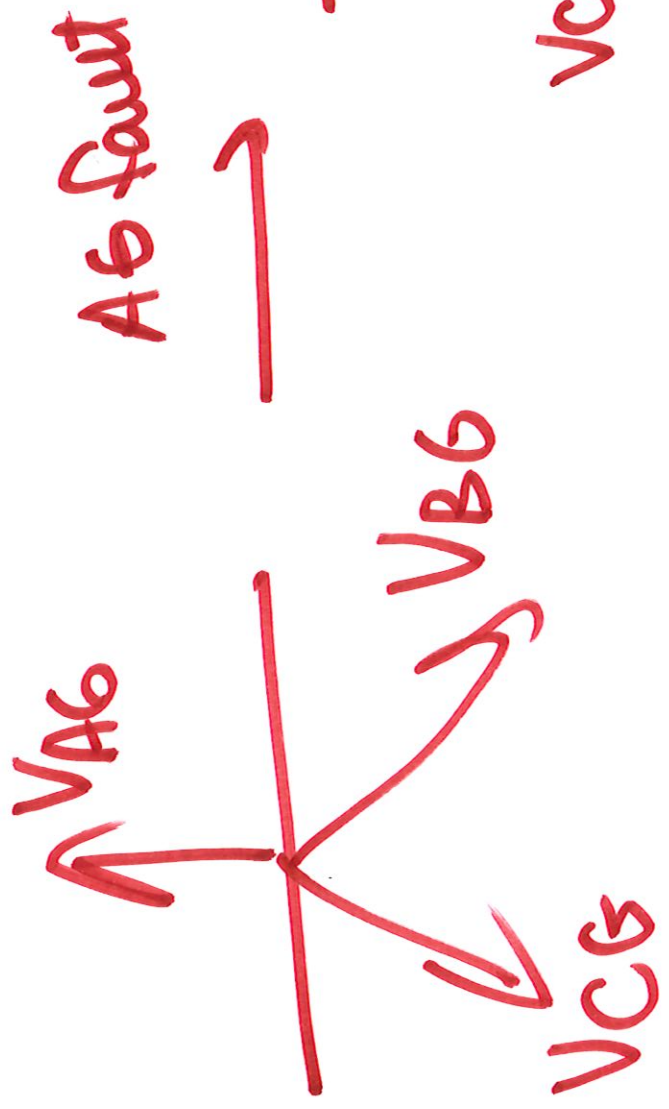- Adding the  $10^{-15}$  avoided a divide by 0 problem in angle calculation



AB fault →

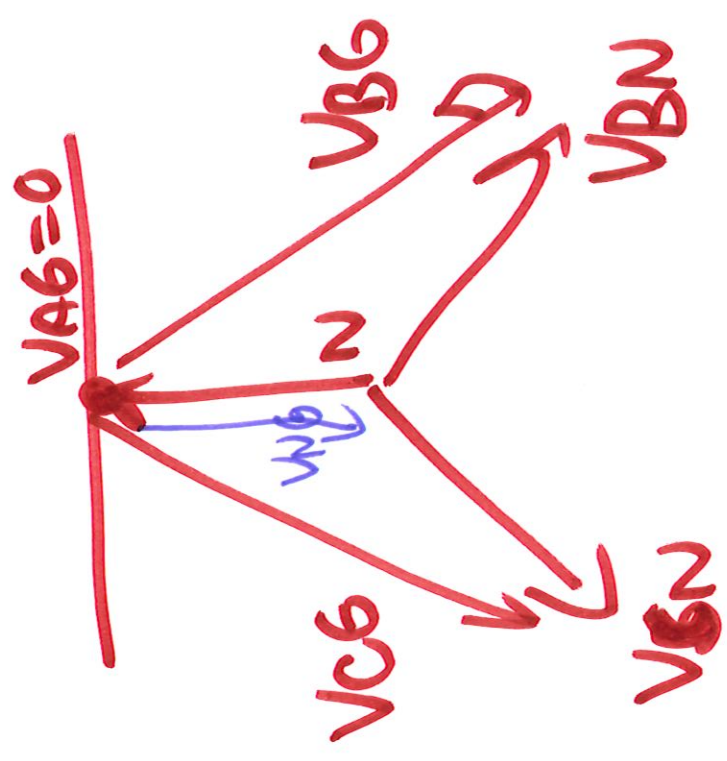

L14 10/20

**DLG Fault:**

*RG increases*  
*RG = ∞*

$$I_{1\_DLG}(M, R_f) := \frac{V_f}{\left( Z_1(M)_{4,4} \right) + \left[ \frac{1}{Z_2(M)_{4,4}} + \frac{1}{Z_0(M)_{4,4} + 3 \cdot R_f} \right]^{-1}}$$

$$|I_{1\_DLG}(0.5, 0)| = 2.7269 \quad \arg(I_{1\_DLG}(0.5, 0)) = -90 \text{ deg}$$

Current dividers for  $I_0$  and  $I_2$



$$I_0\_DLG(M, R_f) := -I_{1\_DLG}(M, R_f) \cdot \left[ \frac{Z_2(M)_{4,4}}{Z_2(M)_{4,4} + (Z_0(M)_{4,4} + 3 \cdot R_f)} \right]$$

$$I_2\_DLG(M, R_f) := -I_{1\_DLG}(M, R_f) \cdot \left[ \frac{Z_0(M)_{4,4} + 3 \cdot R_f}{Z_2(M)_{4,4} + (Z_0(M)_{4,4} + 3 \cdot R_f)} \right]$$

$$I_{ABC\_DLG}(M, R_f) := A_{012} \cdot \begin{pmatrix} I_0\_DLG(M, R_f) \\ I_1\_DLG(M, R_f) \\ I_2\_DLG(M, R_f) \end{pmatrix}$$

$$|I_{ABC\_DLG}(0.5, 0)| = \begin{pmatrix} 0 \\ 4.1902 \cdot \text{pu} \\ 4.1902 \end{pmatrix}$$
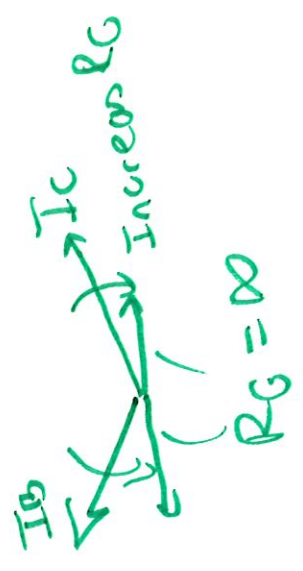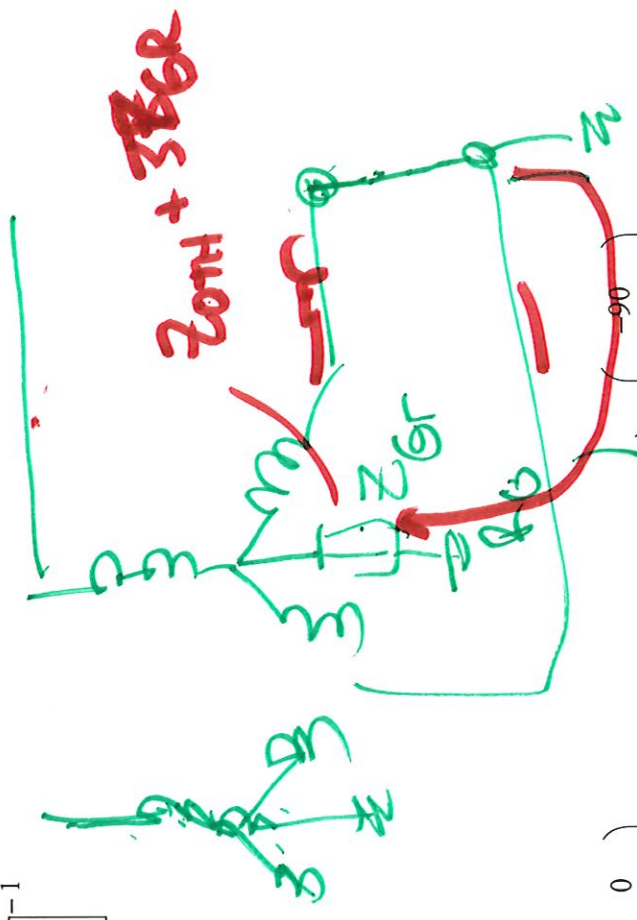
$$\arg(I_{ABC\_DLG}(0.5, 0)) = \begin{pmatrix} 162.5359 \cdot \text{deg} \\ 17.4641 \end{pmatrix}$$



• Angles meaningless when magnitude is 0

• Now find voltages in each sequence component)

L14 11/20


### Unbalanced Fault Analysis Examples

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

Define units: MVA := 1000kW    MVAR := MVA  
 MW := MVA    pu := 1  
 $a := 1 \cdot e^{j \cdot 120 \text{deg}}$


$$\angle(\text{mag}, \text{ang}) := \text{mag} \cdot \cos(\text{ang} \cdot \text{deg}) + j \cdot \text{mag} \cdot \sin(\text{ang} \cdot \text{deg})$$

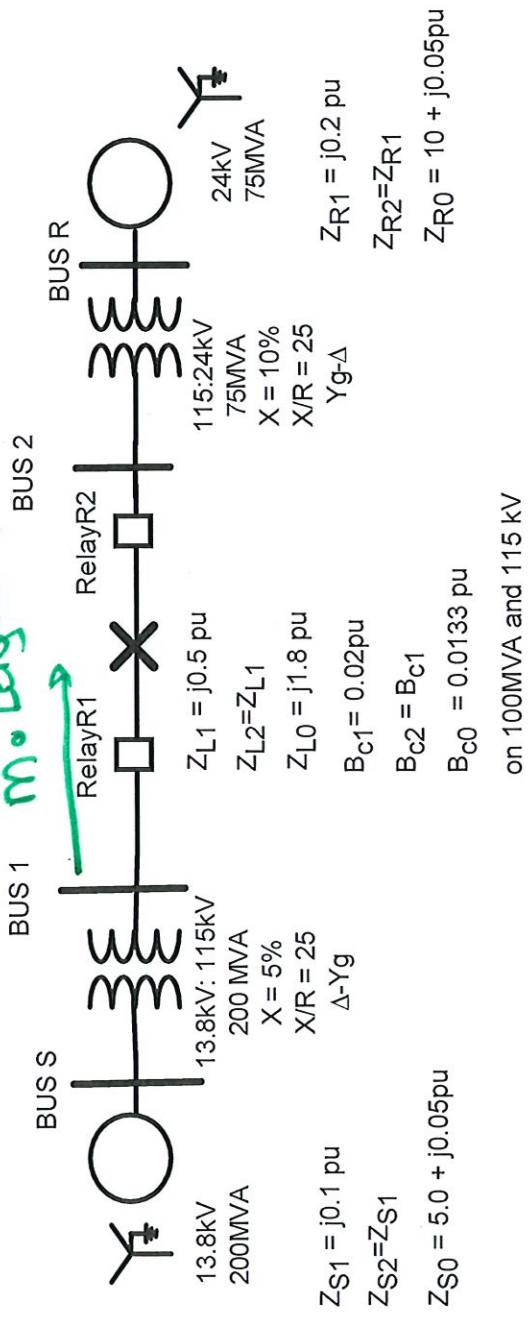*System Description:*  
*m. Length of the line*



Per Unit Change of Base Calculations (hidden, to view double click on the arrow)

LIM 12/20

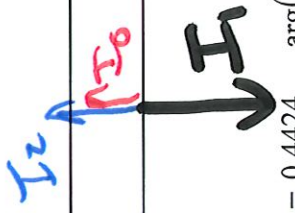

$$I_{0\_B1.DLG}(M, R_f) := \frac{V_{0DLG}(M, R_f)_1 - V_{0DLG}(M, R_f)_4}{M \cdot Z_{L10}}$$

$$|I_{0\_B1.DLG}(0.5, 0)| = 0.4424 \quad \arg(I_{0\_B1.DLG}(0.5, 0)) = 90 \cdot \text{deg}$$

$$I_{ABC\_B1.DLG}(M, R_f) := A_{012} \cdot \begin{pmatrix} I_{0\_B1.DLG}(M, R_f) \\ I_{1\_B1.DLG}(M, R_f) \\ I_{2\_B1.DLG}(M, R_f) \end{pmatrix}$$

$$\begin{pmatrix} 0.1165 \\ 2.7607 \cdot \text{pu} \\ 2.7607 \end{pmatrix} \xrightarrow{|I_{ABC\_B1.DLG}(0.5, 0)|} \begin{pmatrix} -90 \\ 164.8436 \cdot \text{deg} \\ 15.1564 \end{pmatrix}$$

- LV side of transformer (Bus S)

$$V_S \cdot e^{-j \cdot 30 \text{deg}} - V_{1DLG}(M, R_f)_0 = \frac{0 - V_{2DLG}(M, R_f)_0}{jX_{G11}}$$

$$|I_{1\_BS.DLG}(0.5, 0)| = 1.8179 \cdot \text{pu} \quad \arg(I_{1\_BS.DLG}(0.5, 0)) = -120 \cdot \text{deg}$$



$$I_{2\_BS.DLG}(M, R_f) := \frac{0 - V_{2DLG}(M, R_f)_0}{jX_{G12}}$$

$$|I_{2\_BS.DLG}(0.5, 0)| = 1.259 \cdot \text{pu} \quad \arg(I_{2\_BS.DLG}(0.5, 0)) = 120 \cdot \text{deg}$$

$$I_{0\_BS.DLG} := 0$$

$$I_{ABC\_BS.DLG}(M, R_f) := A_{012} \cdot \begin{pmatrix} I_{0\_BS.DLG} \\ I_{1\_BS.DLG}(M, R_f) \\ I_{2\_BS.DLG}(M, R_f) \end{pmatrix}$$


$$\begin{pmatrix} 1.6128 \\ 1.6128 \cdot \text{pu} \\ 3.0769 \end{pmatrix} \xrightarrow{|I_{ABC\_BS.DLG}(0.5, 0)|} \begin{pmatrix} -162.5359 \\ 162.5359 \cdot \text{deg} \\ 0 \end{pmatrix}$$

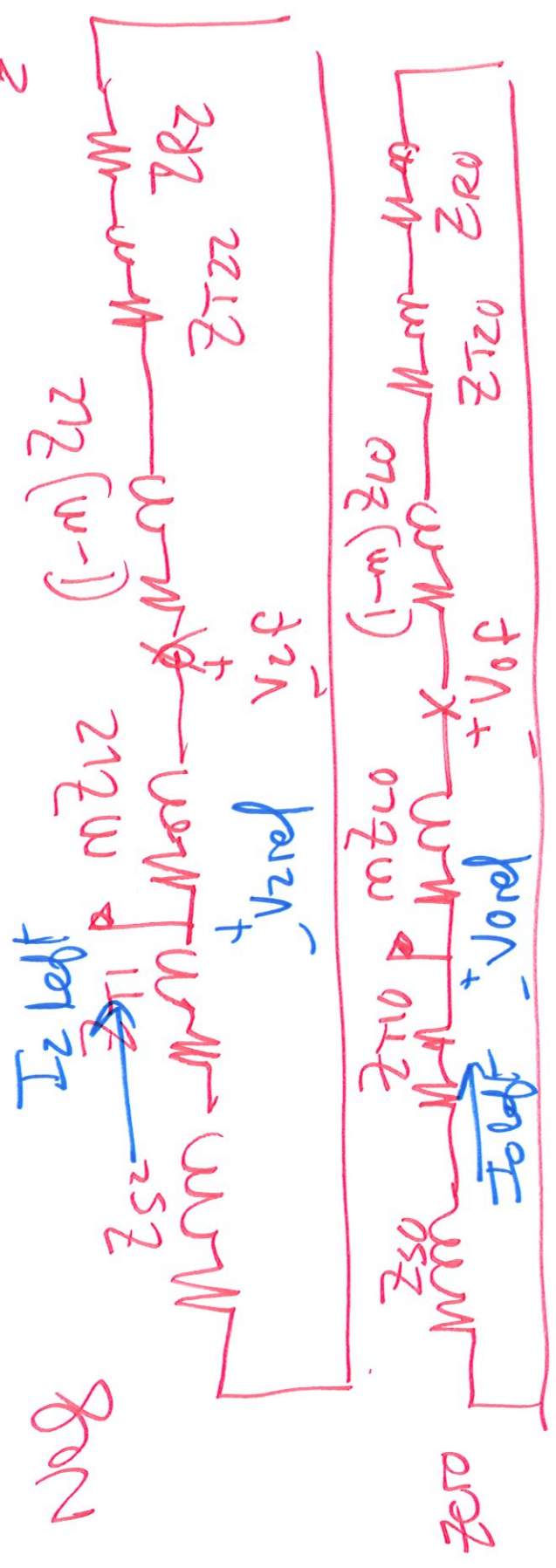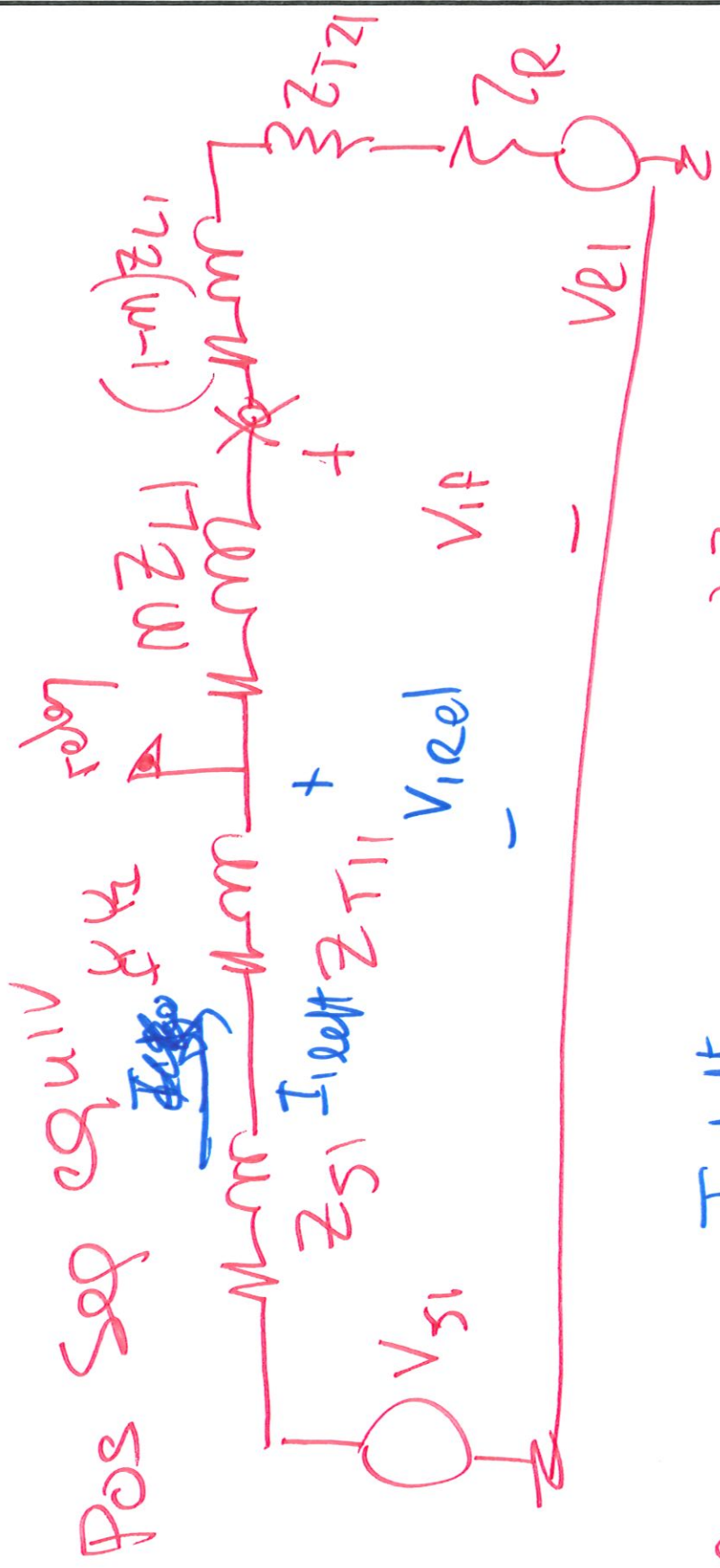


# Symmetrical components


DLG

$\Rightarrow R_f = R_G = 0$

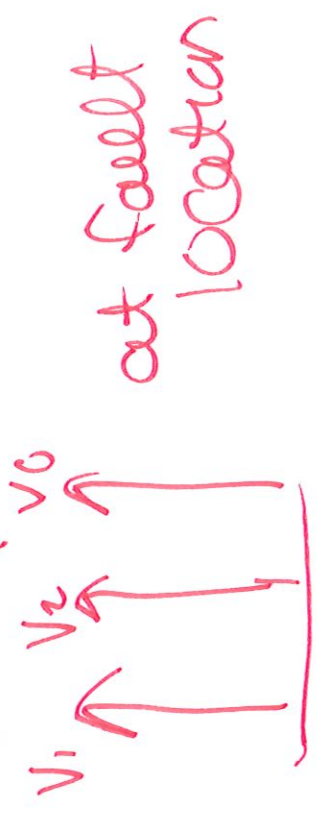


At a relay at end of a line

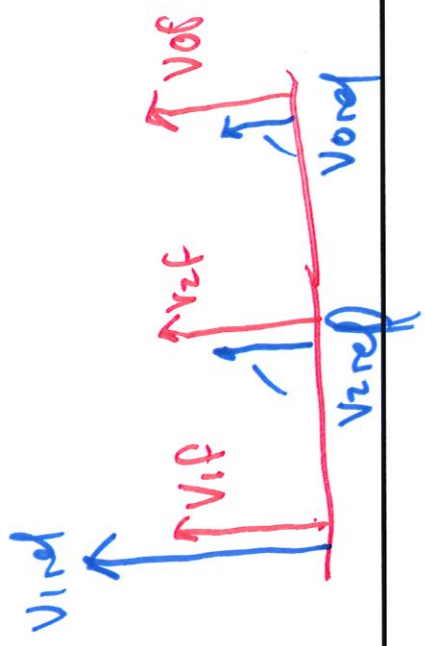

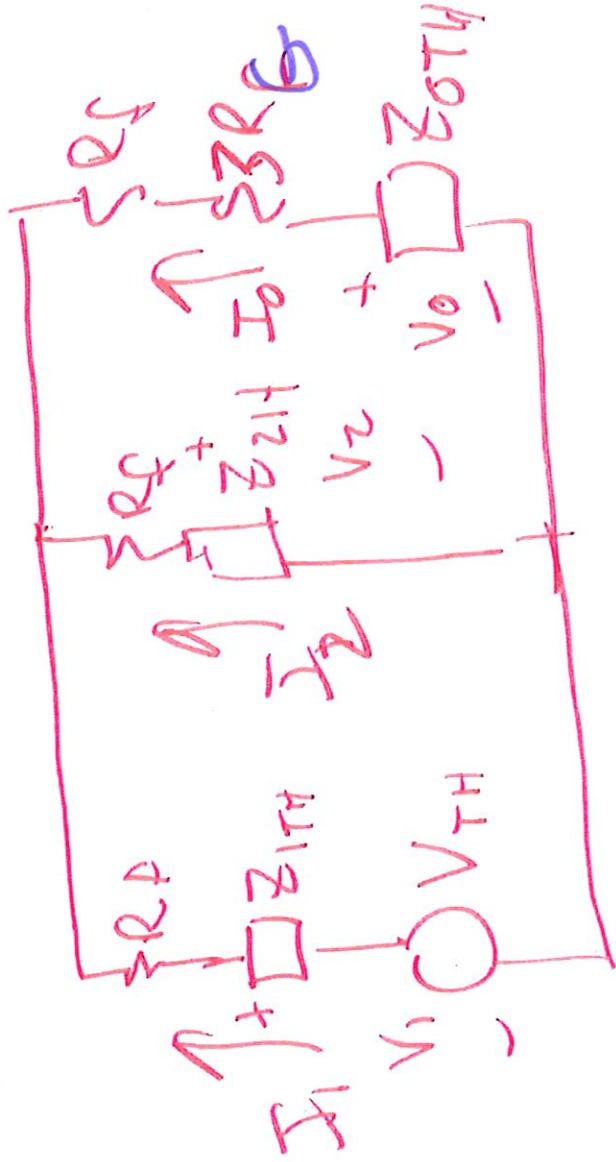





# Voltage Profile

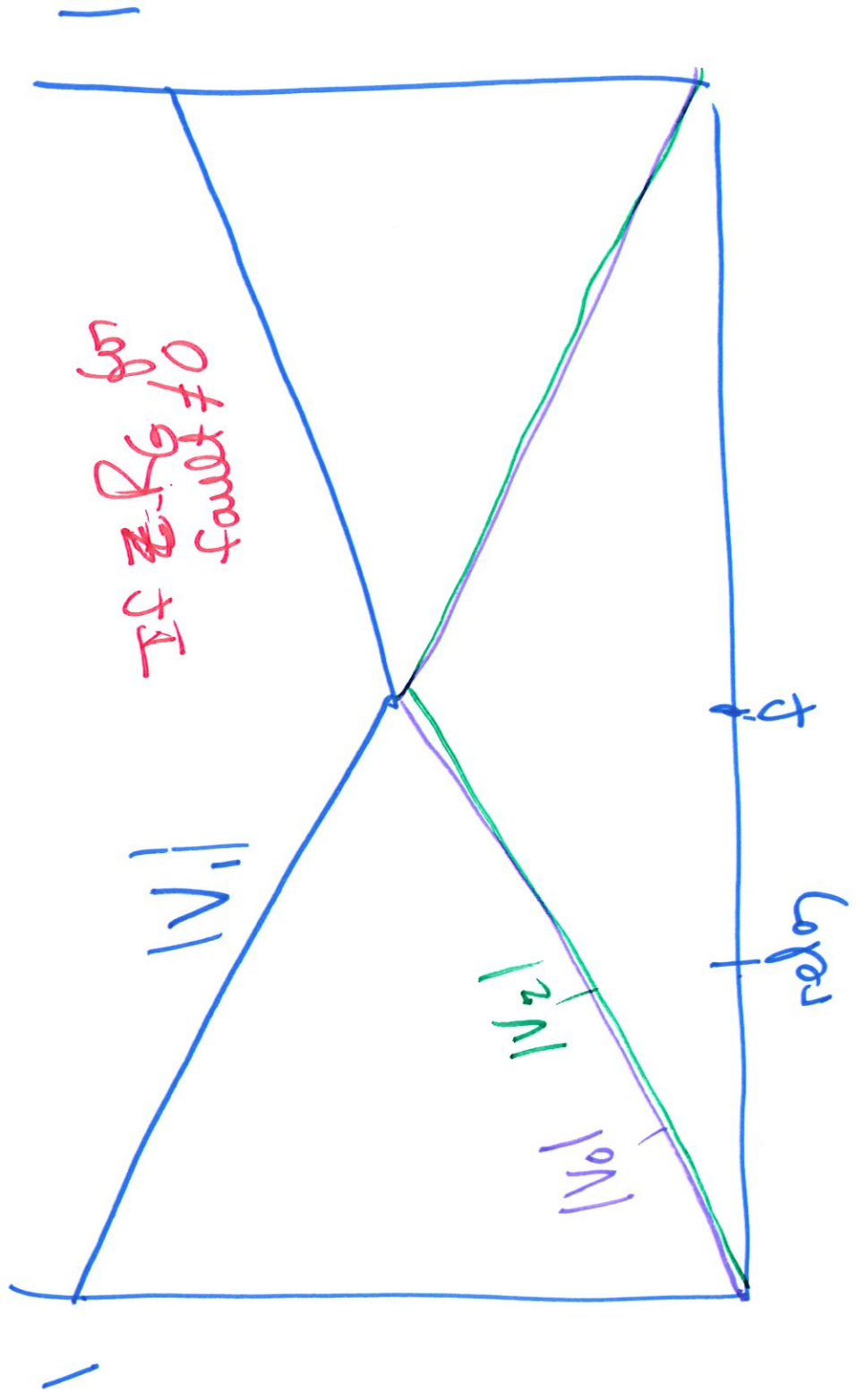


$R_G \neq 0$

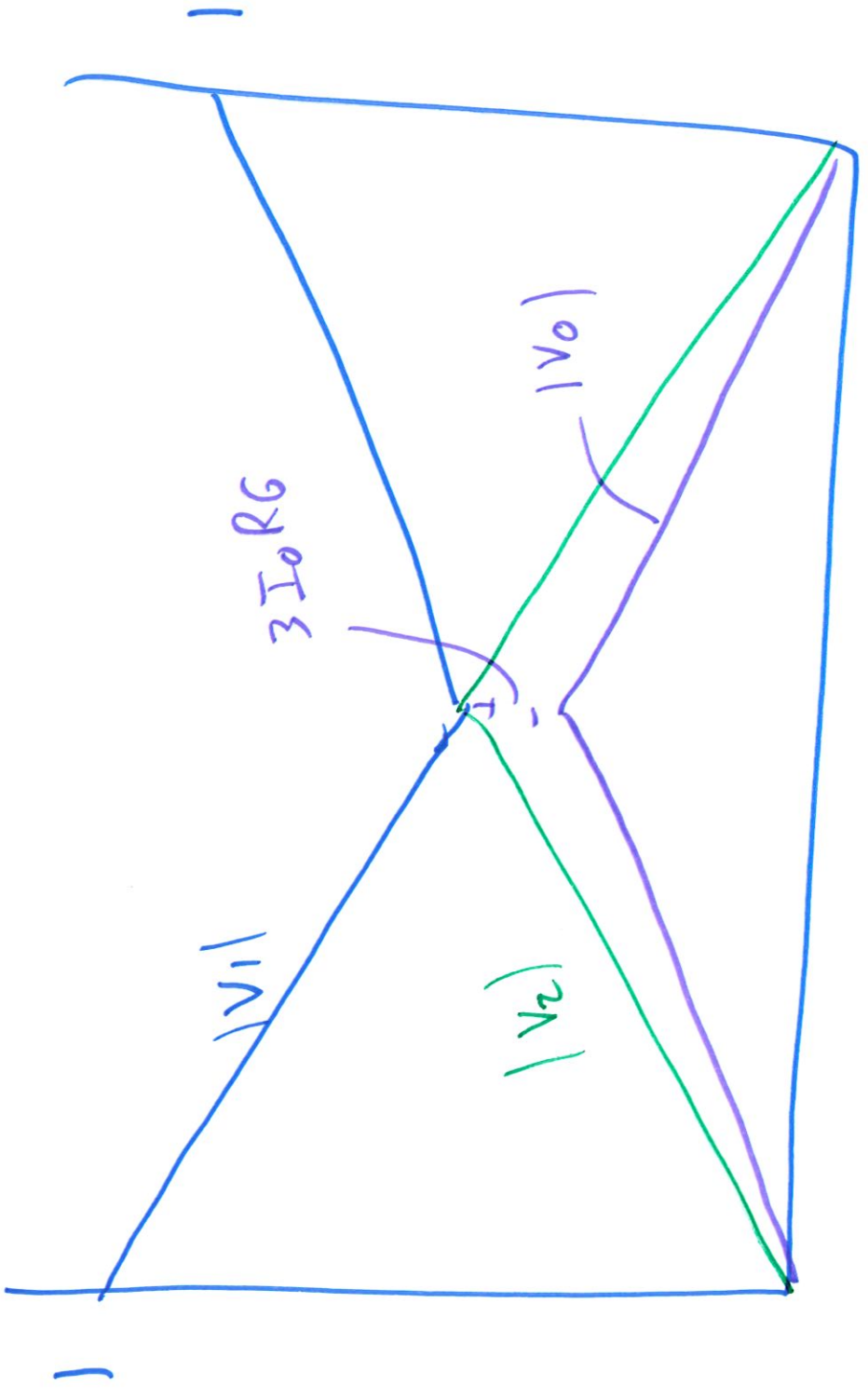

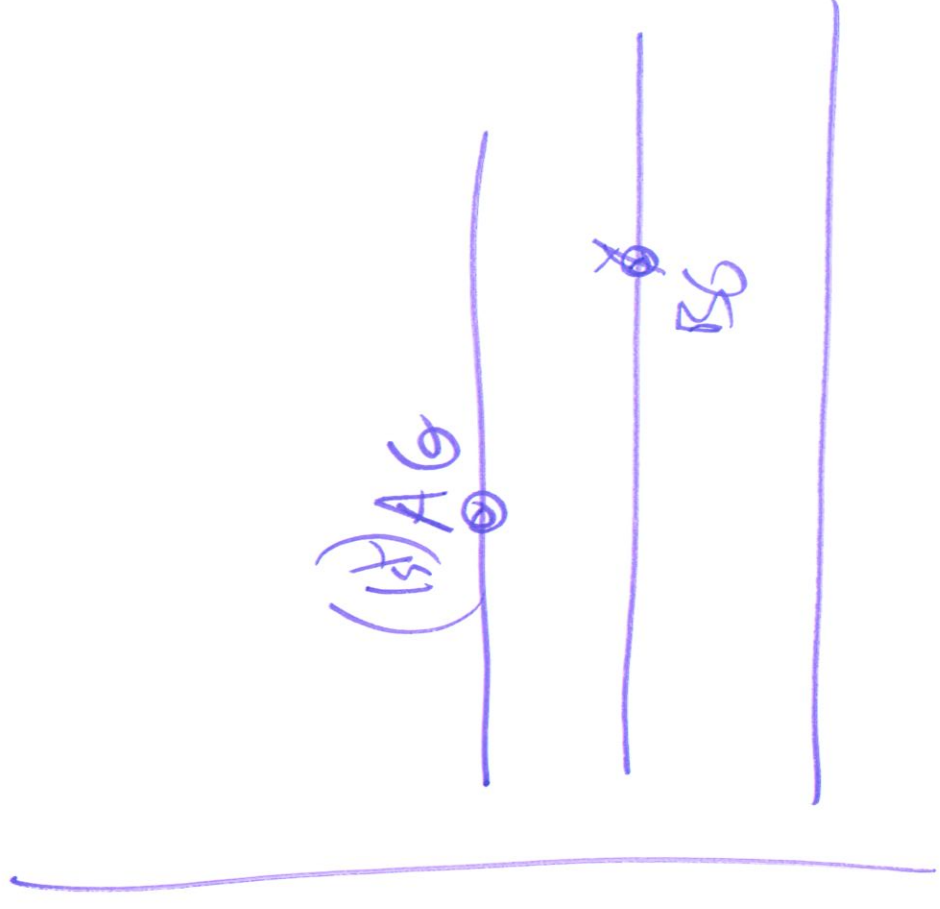

substrate

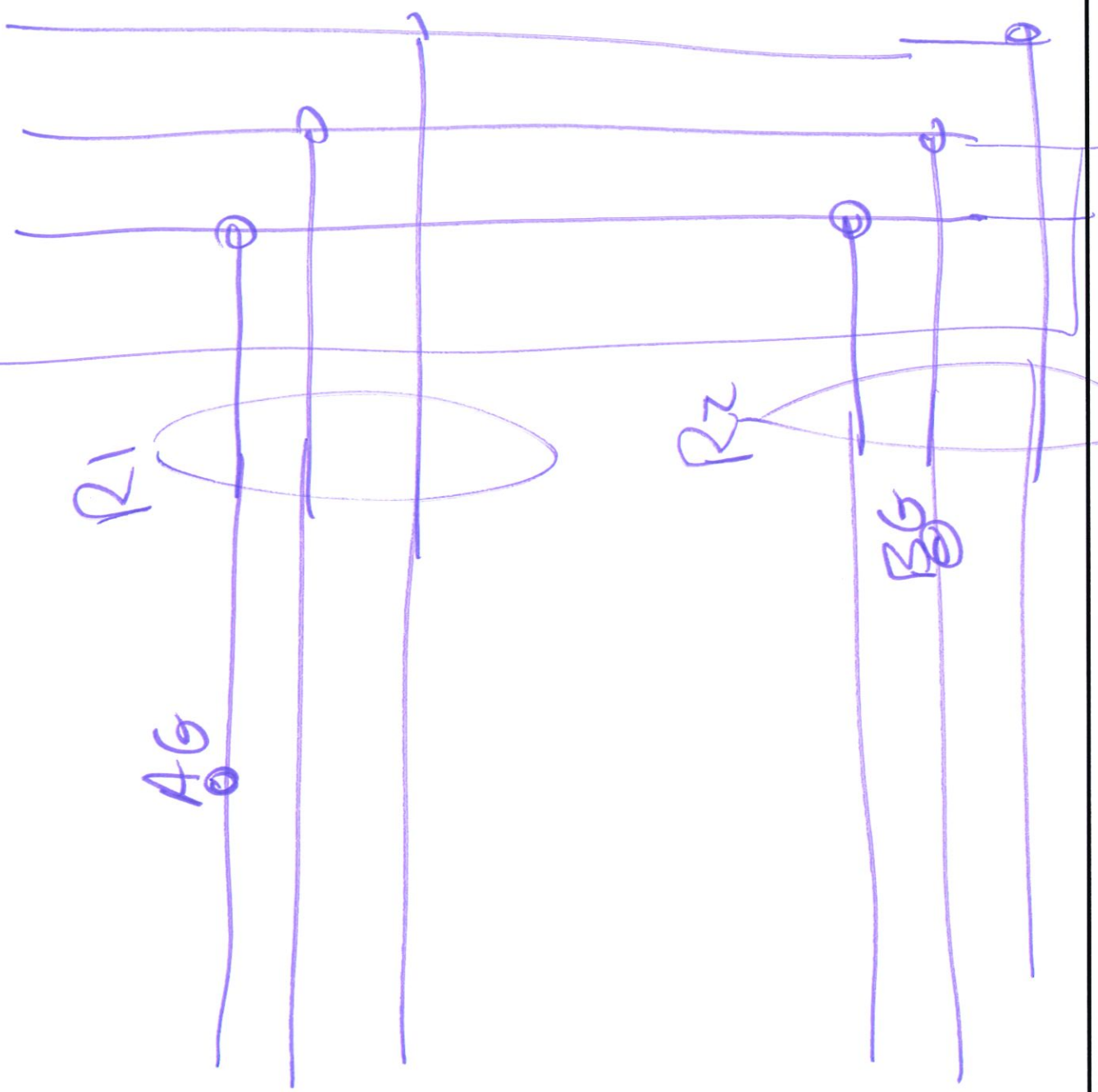

$$R_f \neq 0$$

