

ECE 523  
Symmetrical Components

Session 16




$V_S \angle 0$   $V_R \angle -20$

→ Positive sequence Load Flow

$I_{s1} + I_{s2} + I_{s3} \rightarrow$  won't impact negative or zero sequence networks

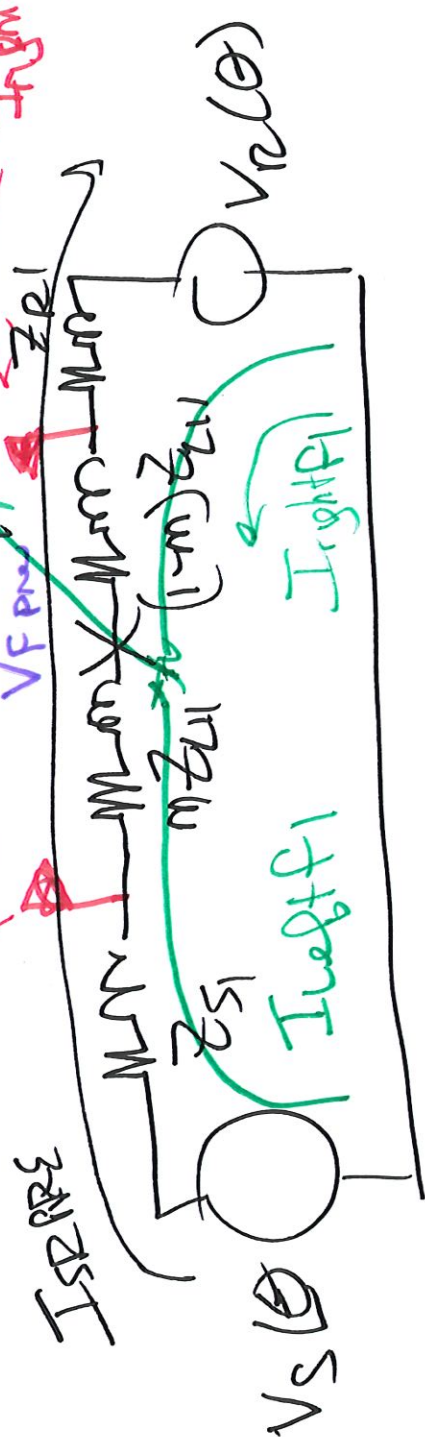Zero sequence  $\rightarrow$   $I_{s1} - I_{s2} - I_{s3}$




# Load connected to a Bus



$P, Q \rightarrow$  convert to  
Impedance and  
put in  $Y_{Bus}$

# Load models?

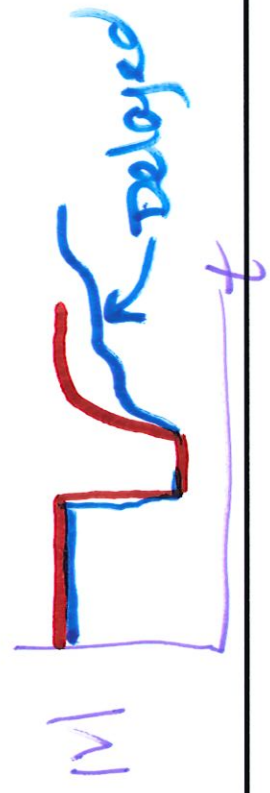
## Fault Induced Delayed Voltage Recovery



ZIP - constant impedance - %  
 constant current -> %  
 constant power -> %

motor load


L -> fault model  
 charge of base

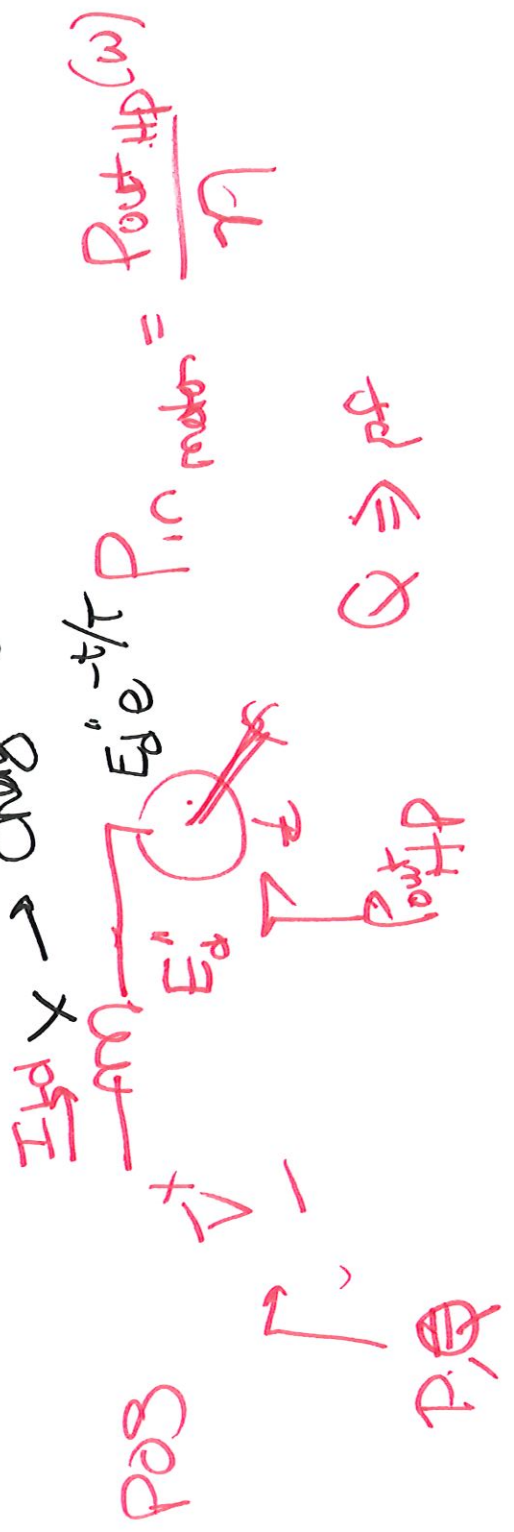

Stalled motor in fault study?

→ no longer rotating

$$E'_d \rightarrow 0$$

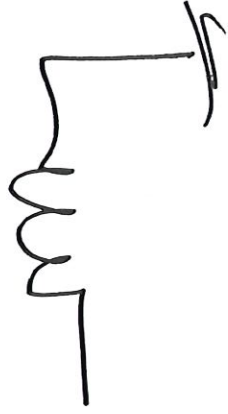

Z I P

40% 20% 40%

calculate impedance based on type

(1) const P, Q (P, pf) 
$$V \left( \frac{V}{Z} \right)^*$$

$$S_{rated pu} = V I^* =$$

$$= \frac{|V|^2}{Z}^*$$

from power flow results

$$Z = \frac{|V|^2}{(S_{rated})^*}$$

from power flow setting

|Z| depends on prefault voltage

② constant current load

→ find  $\bar{I}$  at rated conditions

1.0 pu voltage &  $S_{rated}$

$$\bar{S} = \bar{V} \bar{I}^* \rightarrow \text{solve for } \bar{I}_{rated}$$

$$\bar{Z} = \frac{|V_{prefault}|}{\bar{I}_{rated}} \rightarrow |Z| \text{ varies linearly with } |V_{prefault}|$$

③ constant impedance load


P, Q rated voltage

$$Z_{const Z} = \frac{|V_{rated}|^2}{(S_{rated})^*}$$

→ doesn't change with system voltage

BUS ~~end~~

Pos seq + negative sequence

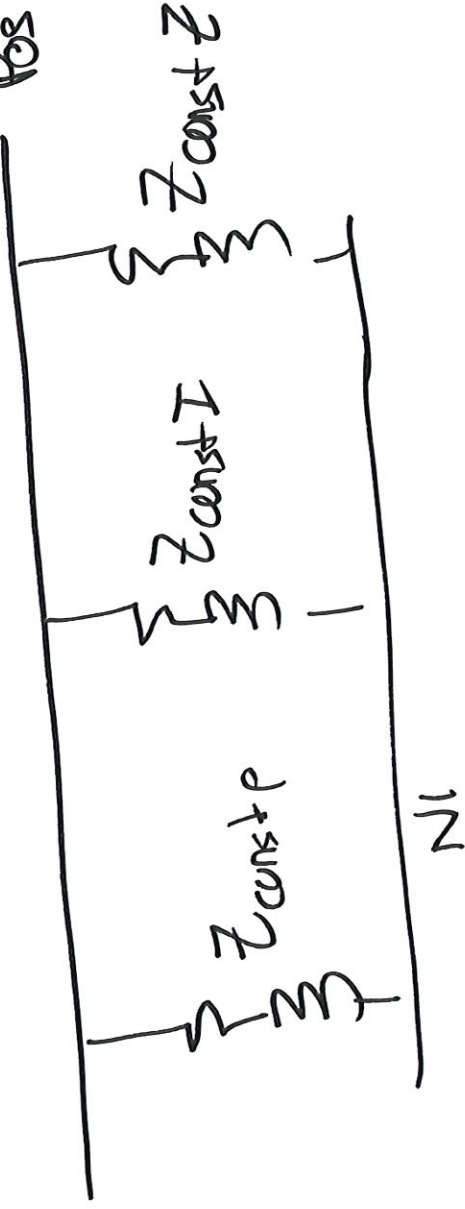



# Zero sequence

- programs model load
- as open in zero sequence
- ungrounded either  
due to  $\Delta$  transformer  
winding or ungrounded  
machine

**Now add shunt Constant Impedance Load load at Bus 1**

Now add a load of 200MVA at unity power factor at Bus 1

$$S_{load} := 200MVA \cdot e^{j \cdot 0 \text{deg}} \quad S_{loadpu} := \frac{S_{load}}{100MVA}$$

$$Z_{load} := \frac{1.0pu}{S_{loadpu}} \quad Z_{load} = 0.5 \cdot pu$$

- Treat same in positive, negative sequence
- Powerworld leaves open in zero sequence
- Not always a realistic assumption
- Add load as an admittance at bus 1


• Need positive negative and zero sequence matrices  $m := 0.5$

$$Y_{bus1} := \begin{bmatrix} \frac{1}{Z_{S1}} + \frac{1}{Z_{L11}} & -\frac{1}{Z_{L11}} & 0 & 0 \\ -\frac{1}{Z_{L11}} & \frac{1}{Z_{L11}} + \frac{1}{m \cdot Z_{L21}} + \frac{1}{Z_{load}} & 0 & 0 \\ 0 & \frac{1}{(1-m) \cdot Z_{L21}} + \frac{1}{Z_{R1}} & \frac{1}{(1-m) \cdot Z_{L21}} & \frac{1}{(1-m) \cdot Z_{L21}} \\ 0 & -\frac{1}{m \cdot Z_{L21}} & -\frac{1}{(1-m) \cdot Z_{L21}} & \frac{1}{(1-m) \cdot Z_{L21}} \end{bmatrix}$$

BUS S    BUS 1

BUS R

BUS F  
IF order?

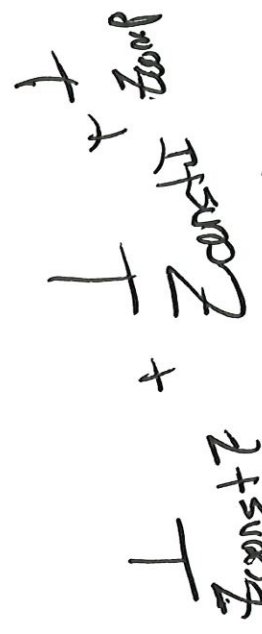

BUS S  
BUS 1  
BUS R  
BUS F

L16 10/16

$$Y_{bus1} = \begin{pmatrix} 0.87 - 43.3i & -0.87 + 9.96i & 0 & 0 \\ -0.87 + 9.96i & 5.05 - 34.87i & 0 & -2.18 + 24.9i \\ 0 & 0 & 2.18 - 41.57i & -2.18 + 24.9i \\ 0 & -2.18 + 24.9i & -2.18 + 24.9i & 4.36 - 49.81i \end{pmatrix}$$

$$Z_{bus1} := Y_{bus1}^{-1}$$

$$Z_{bus1} = \begin{pmatrix} 6.67 \times 10^{-4} + 0.03i & 0 + 0.02i & 4.88 \times 10^{-4} + 0.01i & 0 + 0.01i \\ 0 + 0.02i & 0.01 + 0.07i & 0 + 0.03i & 0.01 + 0.05i \\ 4.88 \times 10^{-4} + 0.01i & 0 + 0.03i & 0 + 0.05i & 0 + 0.04i \\ 0 + 0.01i & 0.01 + 0.05i & 0 + 0.04i & 0.01 + 0.06i \end{pmatrix}$$

- Add the load at Bus 1 in the negative sequence matrix as well.

$$Y_{bus2} := \begin{bmatrix} \frac{1}{Z_{S2}} + \frac{1}{Z_{L12}} & \frac{-1}{Z_{L12}} & 0 & 0 \\ \frac{-1}{Z_{L12}} & \frac{1}{Z_{L12}} + \frac{1}{m \cdot Z_{L22}} + \frac{1}{Z_{load}} & 0 & \frac{-1}{m \cdot Z_{L22}} \\ 0 & 0 & \frac{1}{(1-m) \cdot Z_{L22}} + \frac{1}{Z_{R2}} & \frac{-1}{(1-m) \cdot Z_{L22}} \\ 0 & \frac{-1}{m \cdot Z_{L22}} & \frac{-1}{(1-m) \cdot Z_{L22}} & \frac{1}{m \cdot Z_{L22}} + \frac{1}{(1-m) \cdot Z_{L22}} \end{bmatrix}$$

$$Z_{bus2} := Y_{bus2}^{-1}$$

- But the load is not in the zero sequence matrix

*load open to seq network*

$$Y_{bus0} := \begin{bmatrix} \frac{1}{Z_{S0}} + \frac{1}{Z_{L10}} & \frac{-1}{Z_{L10}} & 0 & 0 \\ \frac{-1}{Z_{L10}} & \frac{1}{Z_{L10}} + \frac{1}{m \cdot Z_{L20}} & 0 & \frac{-1}{m \cdot Z_{L20}} \\ 0 & 0 & \frac{1}{(1-m) \cdot Z_{L20}} + \frac{1}{Z_{R0}} & \frac{-1}{(1-m) \cdot Z_{L20}} \\ 0 & \frac{-1}{m \cdot Z_{L20}} & \frac{-1}{(1-m) \cdot Z_{L20}} & \frac{1}{m \cdot Z_{L20}} + \frac{1}{(1-m) \cdot Z_{L20}} \end{bmatrix}$$


$$Y_{bus0} = \begin{pmatrix} 0.29 - 14.43i & -0.29 + 3.32i & 0 & 0 \\ -0.29 + 3.32i & 1.02 - 11.62i & 0 & -0.73 + 8.3i \\ 0 & 0 & 0.73 - 13.86i & -0.73 + 8.3i \\ 0 & -0.73 + 8.3i & -0.73 + 8.3i & 1.45 - 16.6i \end{pmatrix}$$

$$Z_{bus0} := Y_{bus0}^{-1}$$

46 12/16

$$Z_{bus0} = \begin{pmatrix} 5.82 \times 10^{-4} + 0.08i & -3.88 \times 10^{-4} + 0.05i & -0 + 0.02i & -7.76 \times 10^{-4} + 0.03i \\ -3.88 \times 10^{-4} + 0.05i & 0.01 + 0.2i & 7.76 \times 10^{-4} + 0.09i & 0.01 + 0.14i \\ -0 + 0.02i & 7.76 \times 10^{-4} + 0.09i & 0 + 0.14i & 0 + 0.11i \\ -7.76 \times 10^{-4} + 0.03i & 0.01 + 0.14i & 0 + 0.11i & 0.01 + 0.19i \end{pmatrix}$$

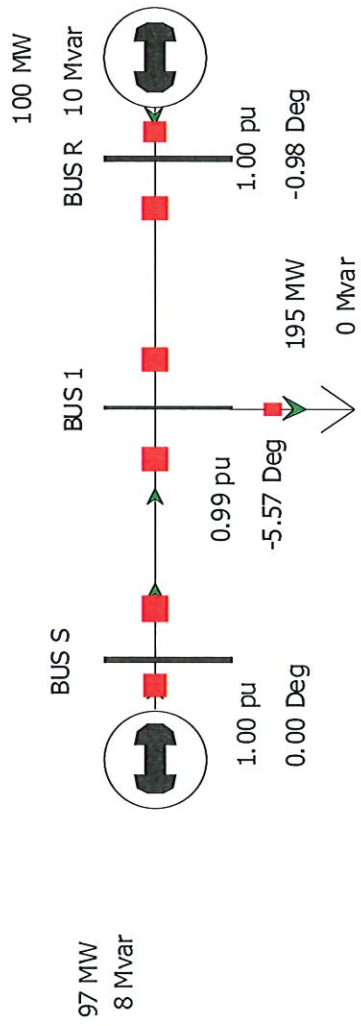- Powerflow simulation needed to find the bus voltages  
- Set generator 2 at 100MW



- Bus Voltages from powerflow results (add the fault point so the powerflow results include it):

$$\angle(\text{mag}, \text{ang}) := \text{mag} \cdot \cos(\text{ang} \cdot \text{deg}) + j \cdot \text{mag} \cdot \sin(\text{ang} \cdot \text{deg})$$

$$\text{BUS S: } V_S := (1.0 \text{ pu}) \angle 0.0$$

$$\text{BUS I: } V_1 := (0.9885) \angle -5.57$$

From Powerflow

L16 13/16

$$\Delta V2 := Z_{bus2} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ -I2\_SLG \end{pmatrix}$$

$$V2 := \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} + \Delta V2$$

$$\Delta V0 := Z_{bus0} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ -I0\_SLG \end{pmatrix}$$

$$V0 := \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \end{pmatrix} + \Delta V0$$

*IF distributed with system fault suggests imbalance should use unbalanced power flow results*

- Relay 1 voltage:

$$V_{ABC\_B1} := A_{012} \cdot \begin{pmatrix} V01 \\ V11 \\ V21 \end{pmatrix}$$

$$\overrightarrow{|V_{ABC\_B1}|} = \begin{pmatrix} 0.2328 \\ 1.2038 \\ 1.1417 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(V_{ABC\_B1})} = \begin{pmatrix} -9.52 \\ -137.28 \\ 128.99 \end{pmatrix} \cdot deg$$

- Relay 1 current:

$$I_{B1\_F\_1} := \frac{V11 - V13}{m \cdot ZL21}$$

$$|I_{B1\_F\_1}| = 1.35$$

$$\arg(I_{B1\_F\_1}) = -126.61 \cdot deg$$

L16 04/16

BUSR:  $V_R := (1.0) \angle -0.98$

BUSF:  $V_{\text{faultpt}} := (0.9934) \angle -3.26$

$$I_{0\_SLG} := \frac{V_{\text{faultpt}}}{Z_{\text{bus}1_{3,3}} + Z_{\text{bus}2_{3,3}} + Z_{\text{bus}0_{3,3}}}$$

$I_{1\_SLG} := I_{0\_SLG}$

$I_{2\_SLG} := I_{0\_SLG}$

$|I_{0\_SLG}| = 3.17$

$\arg(I_{0\_SLG}) = -88.83 \cdot \text{deg}$


$$I_{\text{ABC\_SLG}} := A_{012} \cdot \begin{pmatrix} I_{0\_SLG} \\ I_{1\_SLG} \\ I_{2\_SLG} \end{pmatrix}$$

$$|I_{\text{ABC\_SLG}}| = \begin{pmatrix} 9.516 \\ 0 \\ 0 \end{pmatrix} \cdot \text{pu}$$

$$\arg(I_{\text{ABC\_SLG}}) = \begin{pmatrix} -88.83 \\ 27.81 \\ 27.81 \end{pmatrix} \cdot \text{deg}$$

• Now find the voltages:
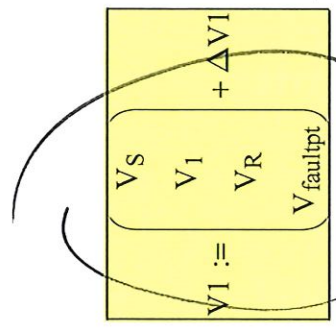
$$\Delta V1 := Z_{\text{bus}1} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ -I_{1\_SLG} \end{pmatrix}$$





Pre-fault from fault flow voltages

Distributed Generation  
→ either on distributor  
system


— on transmission connected

30 connect  
→ TRANS FORMER  
connectors  
var

single phase

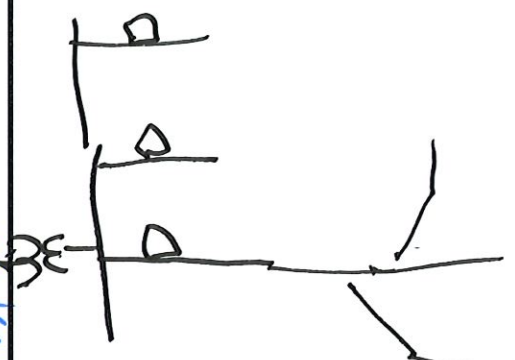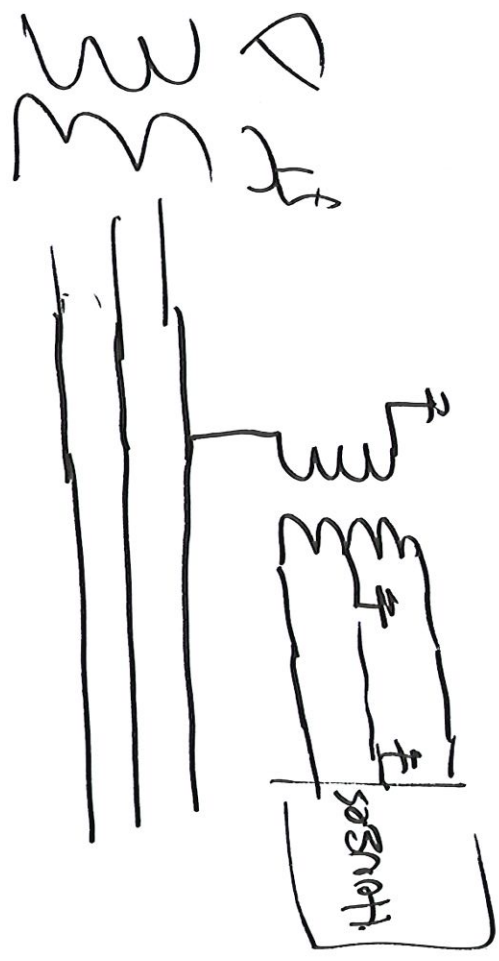



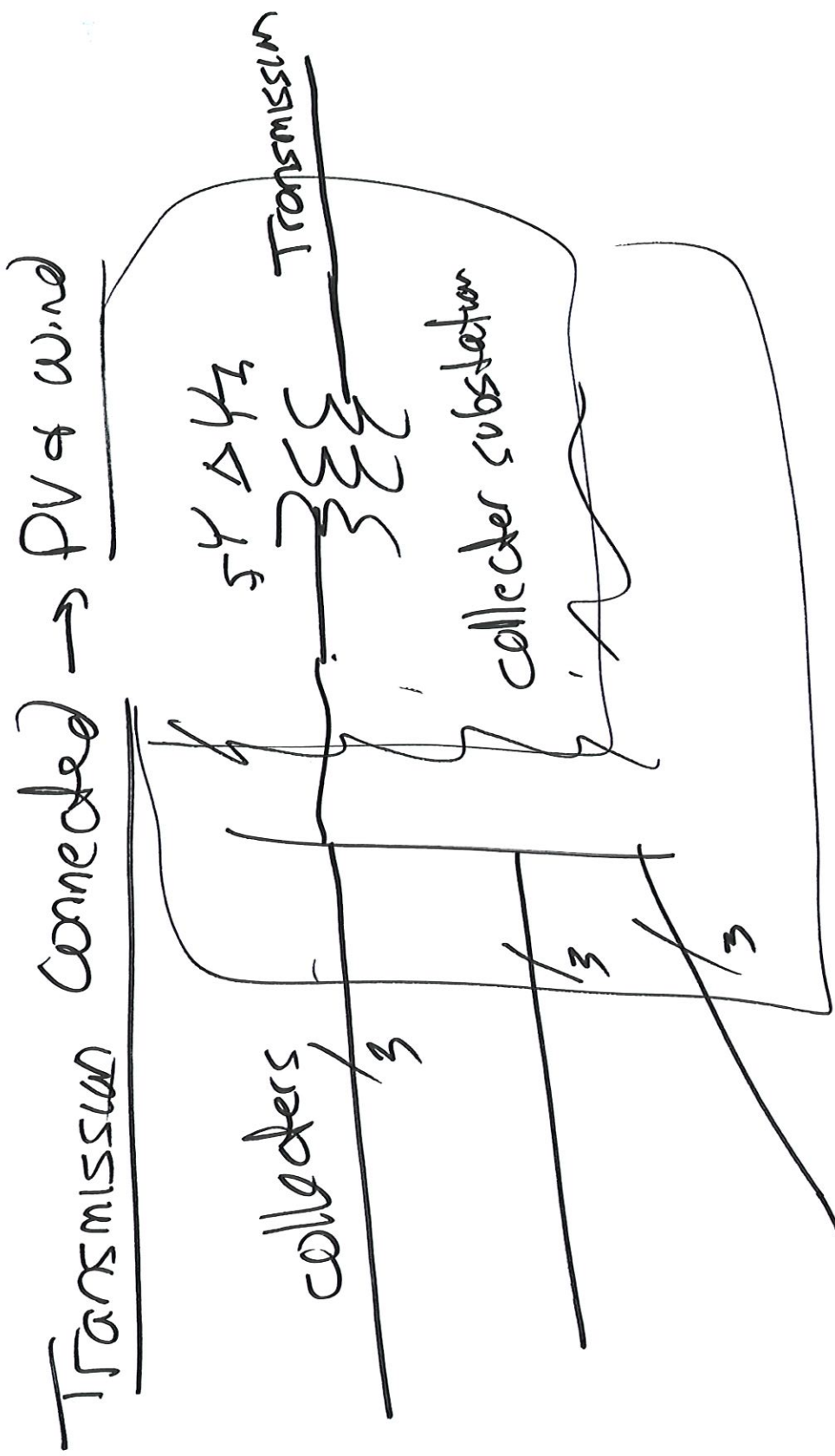

IEEE 2800  
 -> PV & wind & storage  
 -> Rules for  $V_2$  &  $\theta_2$   
 in fault response