

ECE 523
Symmetrical Components

Session 17


Exam 1

- Take home exam
- 72 hours
- Available Oct 27 ~ morning
 - complete by Nov 6 night
- Topics - up through series faults

ECE 523: Homework #4

~~Due Session 19 (October 31)~~ **Session 20, Oct 26**

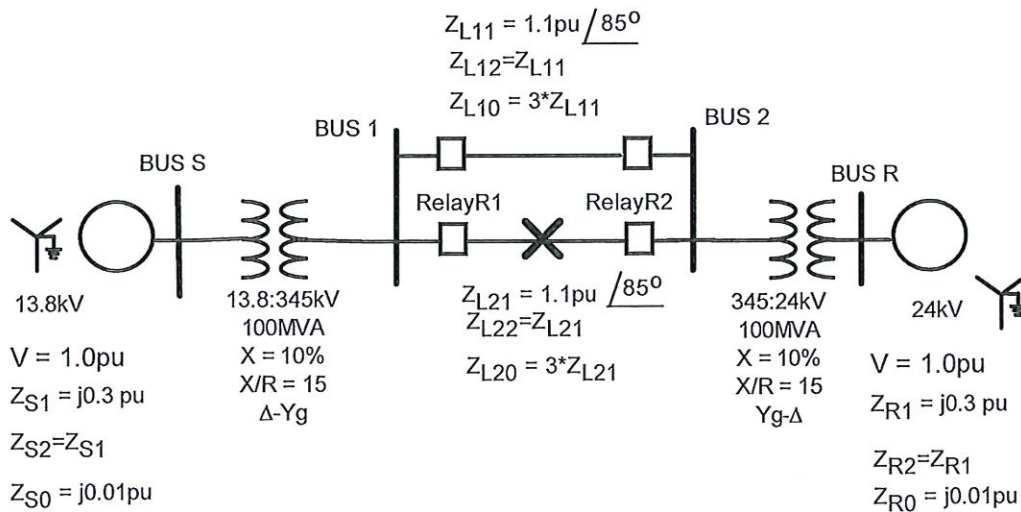1. Do the following for the circuit below using Z_{bus} matrix methods assuming faults 33% of the way down line 2 (the lower of the two lines). No change of base calculations needed.
- Set the voltage source at Bus S is 1.0 at -30 degrees (this is to account for the transformer phase shift), and the voltage at Bus R to be 1.0 is -50 degrees. Calculate the prefault voltage magnitude and angle at each bus, including the fault point based on the prefault power flow. Check your results with a Powerworld or a similar program.
 - Calculate the voltages and currents in the sequence domain and in the abc domain at RelayR1 and RelayR2, for 3 phase, SLG, LL, and DLG faults with $R_f = 0.3$ pu (for the DLG put the resistance in the ground path). Again, check your results with Powerworld or a similar program.



2 series fault case

52/2
L17

Series faults (abnormal conditions)

- in a line, transformer, etc
- large, temporary condition

Common cases

1. ~~one~~ one phase abnormal
other two normal

⇒ single pole open (single phase open)

A. Intentional - trip faulted phase


for SLG at both ends

B. Unintentional - Breaker failure - one end

2. Phased open \rightarrow breaker failure
- one pole fails to open


3. Unbalanced impedance

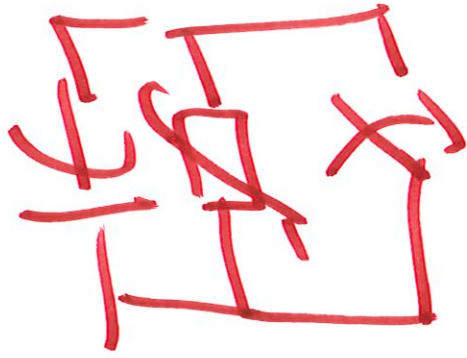A. \rightarrow series capacitor
 \rightarrow MOV



B. mismatched transformers
→ large power transformers
→ single phase

Analysis of series faults

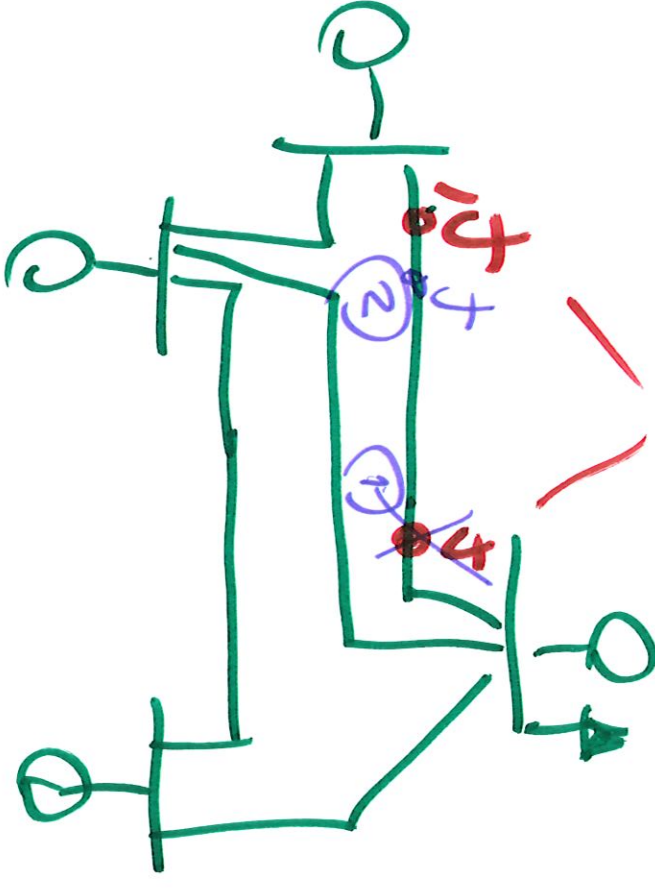


- ① Phasors
- symmetrical components
- Two port Thevenin equivalent from f-f'


- ② Electromagnetic transients simulation

Thevenin Equivalent

1. Single port equivalent circuits

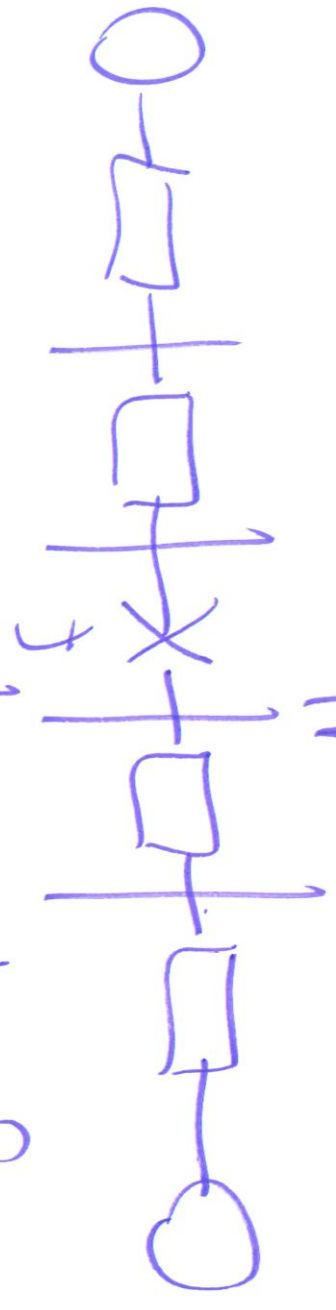

pos

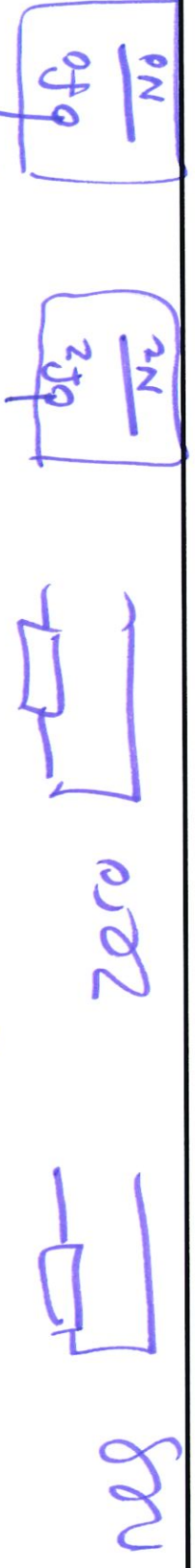


neg

$$\frac{df_2}{N_2}$$


$$\frac{df_0}{N_0}$$

2. Two port Thevenin Equivalent

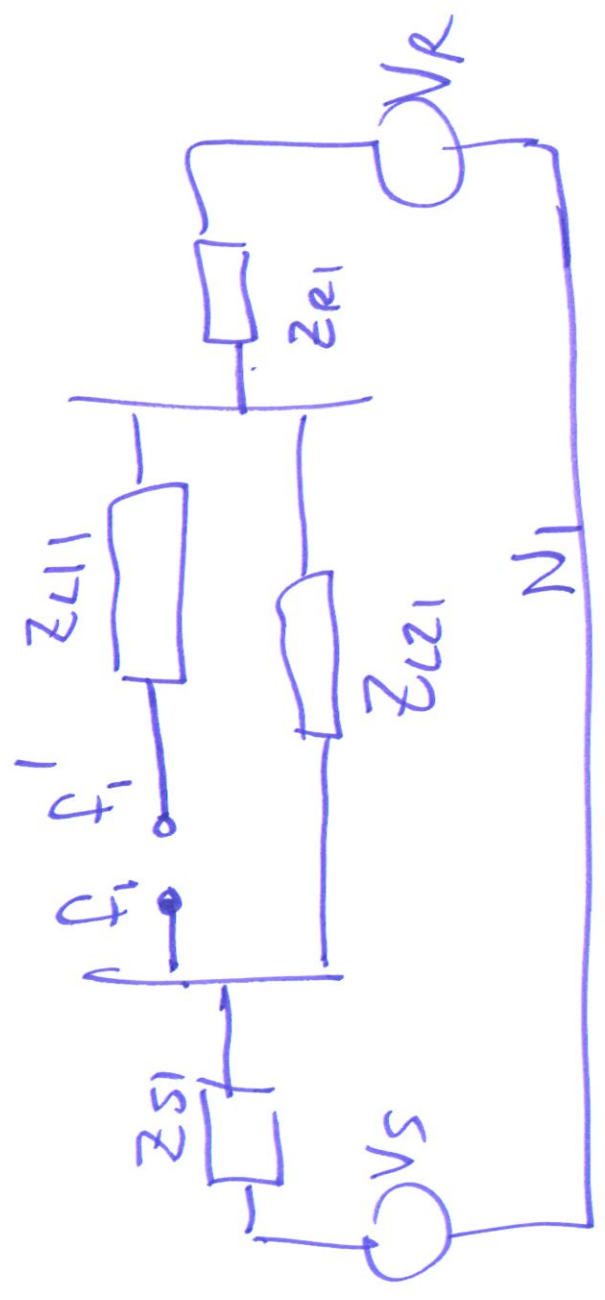


~~$V_S \neq V_R$~~
 $V_S \neq V_R$

Need to have
 load flow
 on system

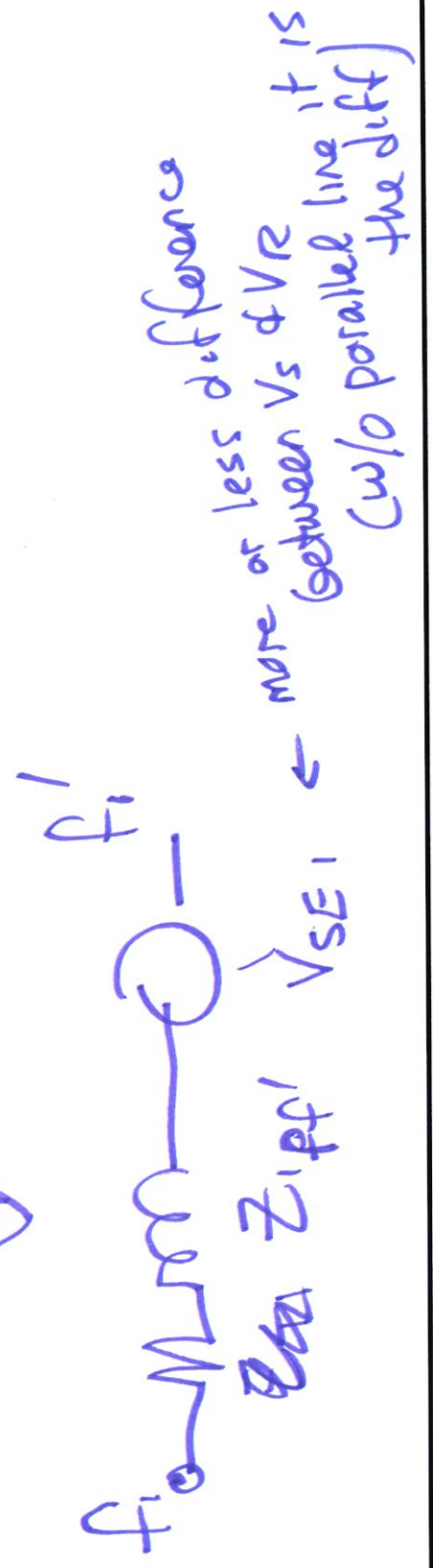

more or less difference
 (between V_S & V_R
 c/w/o parallel line it is
 the diff)

Symbol

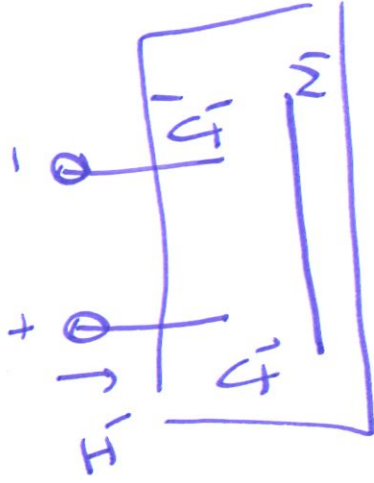

L17 10/25

Series Fault Examples

pu := 1 MVA := 1000kW


$$a := 1e^{j \cdot 120 \text{deg}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

Single Phase Open Examples

Example 1:

- System one-line diagram:

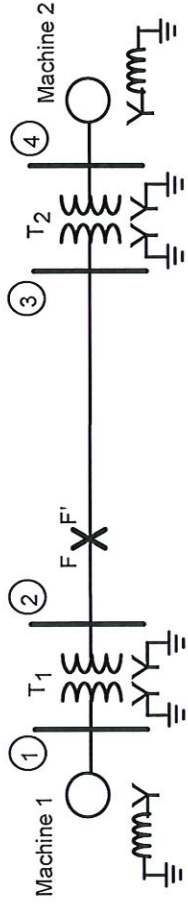

Machines 1 and 2: $S_{Mach} := 100 \text{MVA}$ $V_{machine} := 20 \text{kV}$

$X_{dMach} := 20\%$ $X_{1Mach} := X_{dMach}$ $X_{2Mach} := X_{1Mach}$

$X_{0Mach} := 4\%$ $X_{nMach} := 5\%$

Transformers T1 and T2: $S_{Tran} := 1000 \text{MVA}$ $V_{HV} := 345 \text{kV}$ $V_{LV} := 20 \text{kV}$

Transmission Line $X_{L1} := 15\%$ $X_{L2} := X_{L1}$ $X_{L0} := 50\%$

$S_{Base} := 100 \text{MVA}$

$X_T := 8\%$

$X_1 = X_2 = X_0$
 $R = 0$

L17 11/25

$$V_{BLine} := 345kV \quad V_{Bmach} := V_{BLine} \cdot \left(\frac{V_{LV}}{V_{HV}} \right) \quad V_{Bmach} = 20 \cdot kV$$

No change of base calculations are needed for this system.

Determine internal source voltages: voltage behind reactance for the sources

$$magS_{pre} := 80MVA \quad pf_{pre} := 0.85 \text{ lagging} \quad \theta_{pre} := \text{acos}(pf_{pre}) \quad \theta_{pre} = 31.79 \cdot \text{deg}$$

at Bus 3

$$S_{pre} := \frac{magS_{pre}}{S_{Base}} \cdot e^{j \cdot \theta_{pre}} \quad S_{pre} = (0.68 + 0.42i) \cdot pu \quad |S_{pre}| = 0.8 \cdot pu$$

Assume bus 3 voltage is 1.0 pu at and angle of 0 degrees.

$$V_3 := 1.0$$

$$I_{load} := \left(\frac{S_{pre}}{V_3} \right) \quad I_{load} = 0.68 - 0.42i \quad |I_{load}| = 0.8 \cdot pu \quad \arg(I_{load}) = -31.79 \cdot \text{deg}$$

Internal voltage on the motor (since we don't know steady-state synchronous reactance, use X1):

$$E_2 := V_3 - I_{load} \cdot j(X_T + X_{IMach}) \quad |E_2| = 0.9 \quad \phi_2 := \arg(E_2) \quad \phi_2 = -12.18 \cdot \text{deg}$$

Generator internal voltage:

$$E_1 := V_3 + I_{load} \cdot (j \cdot X_{L1} + j \cdot X_T + j \cdot X_{IMach}) \quad |E_1| = 1.22 \cdot pu \quad \phi_1 := \arg(E_1) \quad \phi_1 = 13.9 \cdot \text{deg}$$


L17 12/25

Check result by calculating power transfer between sources and current:

$$P_{trans} := \frac{|E_1| \cdot |E_2| \cdot \sin(\phi_1 - \phi_2)}{2 \cdot X_{1Mach} + 2 \cdot X_T + X_{L1}} \quad P_{trans} - \text{Re}(S_{pre}) = 0$$

$$I_{trans} := \frac{E_1 - E_2}{j(2 \cdot X_{1Mach} + 2 \cdot X_T + X_{L1})} \quad I_{trans} - I_{load} = 0$$

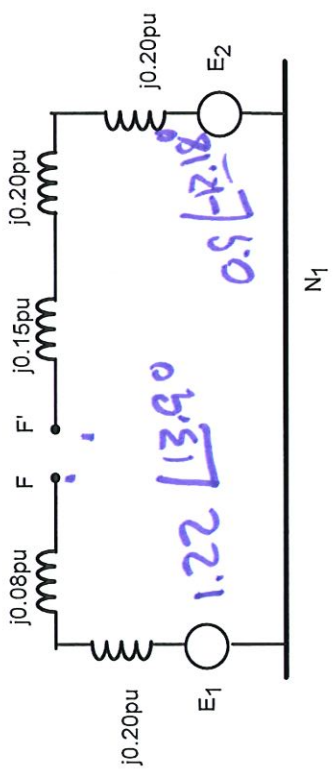- Positive sequence equivalent circuit (with phase open point indicated).



Find total impedance counterclockwise around loop from F to F'


$$Z_{1total} := j \cdot (X_{1Mach} + X_T + X_{L1} + X_T + X_{1Mach})$$

$$Z_{1total} = 0.71i \cdot pu$$

$$Z_{1FF'} := Z_{1total}$$

$$V_{equiv} := E_1 - E_2 = V_{SE}$$

- Negative sequence equivalent circuit:

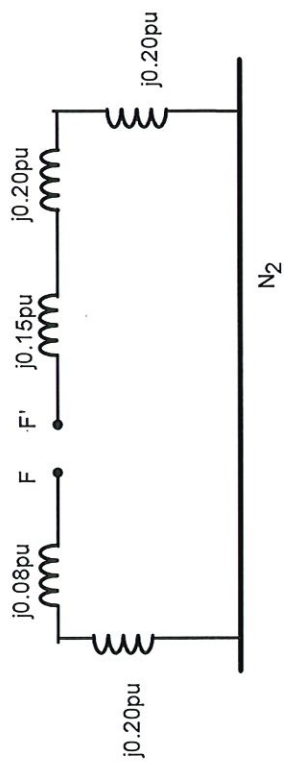

Find total impedance counterclockwise around loop from F to F'


$$Z_{2total} := j \cdot (X_{2Mach} + X_T + X_{L2} + X_T + X_{2Mach})$$

$$Z_{2total} = 0.71i \cdot pu$$

$$Z_{2FF'} := Z_{2total}$$

L17 13/25

- Zero sequence equivalent:

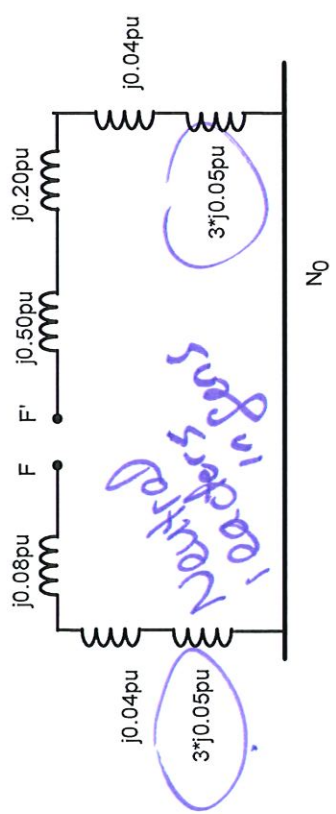


Find total impedance counterclockwise around loop from F to F'

$$Z_{0total} := j \cdot (2 \cdot X_{0Mach} + 2 \cdot X_T + X_{L0} + 2 \cdot 3 \cdot X_{nMach})$$

$$Z_{0total} = 1.04i \cdot pu$$

$$Z_{OFF'} := Z_{0total}$$

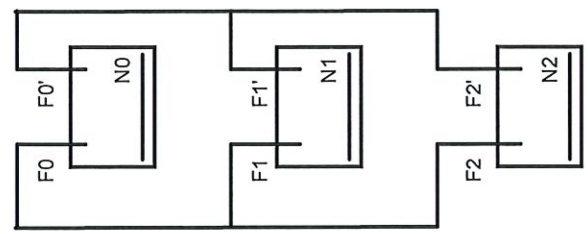Now solve for the single phase open circuit currents and voltages:



$$I_1 := \frac{V_{equiv}}{Z_{1FF'} + \left(\frac{1}{Z_{2FF'}} + \frac{1}{Z_{0FF'}} \right)^{-1}}$$

$$I_2 := -I_1 \cdot \left(\frac{Z_{0FF'}}{Z_{2FF'} + Z_{0FF'}} \right)$$

$$I_0 := -I_1 \cdot \left(\frac{Z_{2FF'}}{Z_{2FF'} + Z_{0FF'}} \right)$$

$$I_1 = (0.43 - 0.26i) \cdot pu$$

$$|I_1| = 0.5 \cdot pu \quad \arg(I_1) = -31.79 \cdot deg$$


$$I_2 = (-0.25 + 0.16i) \cdot pu$$

$$|I_2| = 0.3 \cdot pu \quad \arg(I_2) = 148.21 \cdot deg$$

$$I_0 = (-0.17 + 0.11i) \cdot pu$$



$$|I_0| = 0.2 \cdot pu \quad \arg(I_0) = 148.21 \cdot deg$$

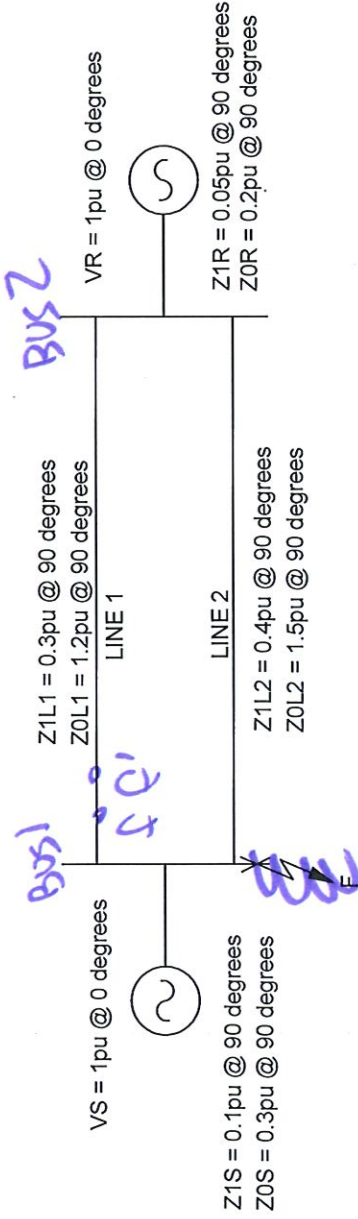Example 2 For the system shown below, develop the sequence connection diagram for a single-phase open on Line 1.




$$Z_{1S} := j \cdot 0.1pu \quad Z_{1R} := j \cdot 0.05pu \quad Z_{0S} := j \cdot 0.3pu \quad Z_{0R} := j \cdot 0.2pu$$
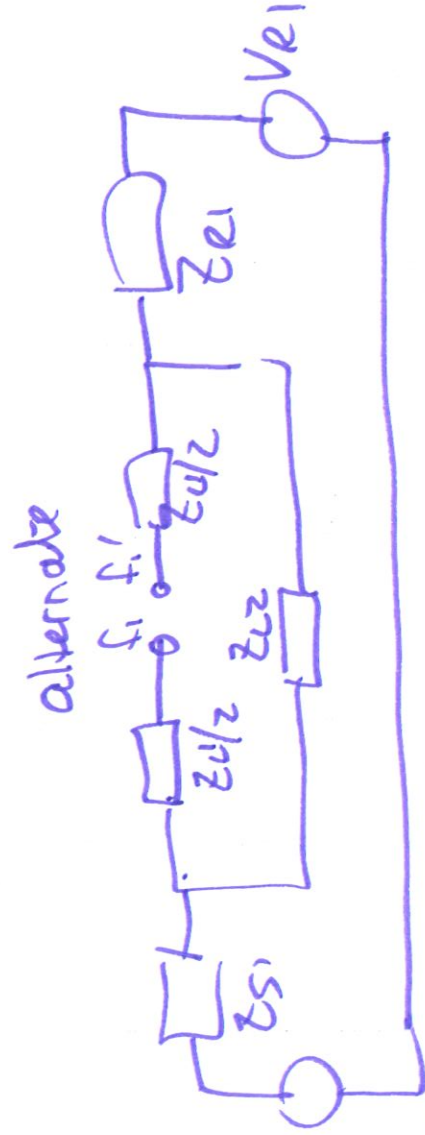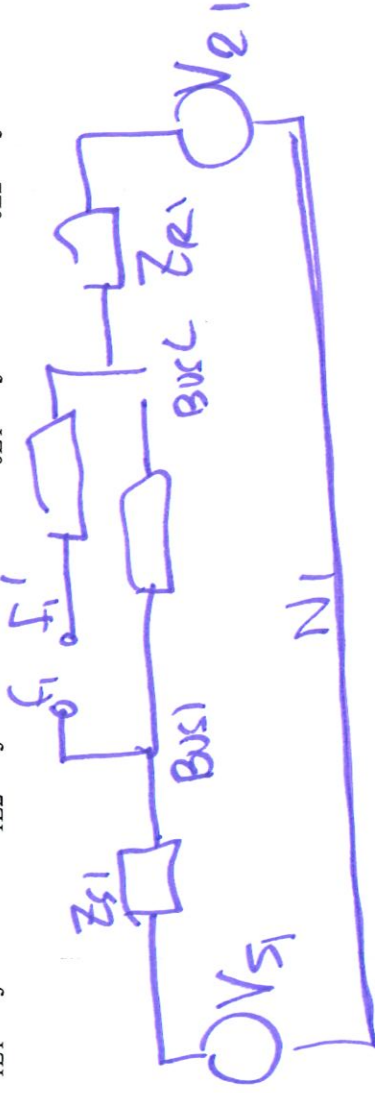
$$Z_{1L1} := j \cdot 0.3 \quad Z_{1L2} := j \cdot 0.4 \quad Z_{0L1} := j \cdot 1.2 \quad Z_{0L2} := j \cdot 1.5$$




finding V_{TH} & Z_{TH} with parallel paths


Redraw diagram:

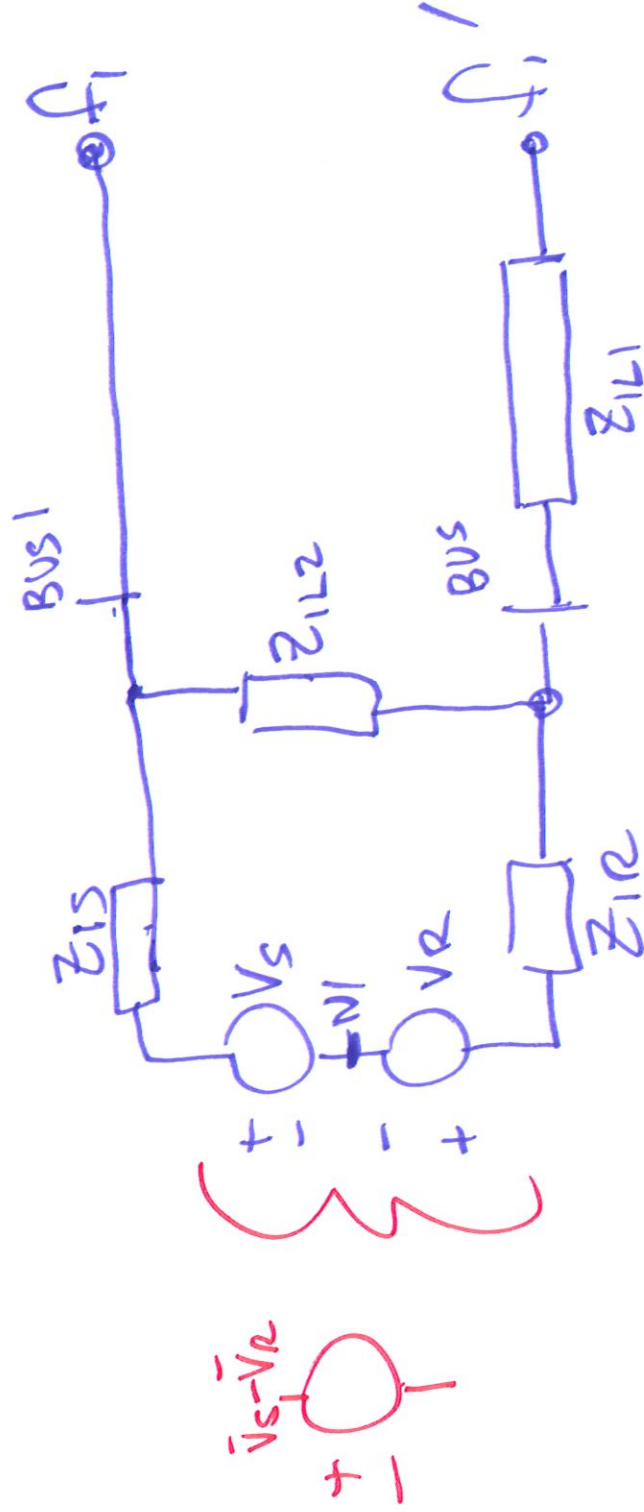


Redraw

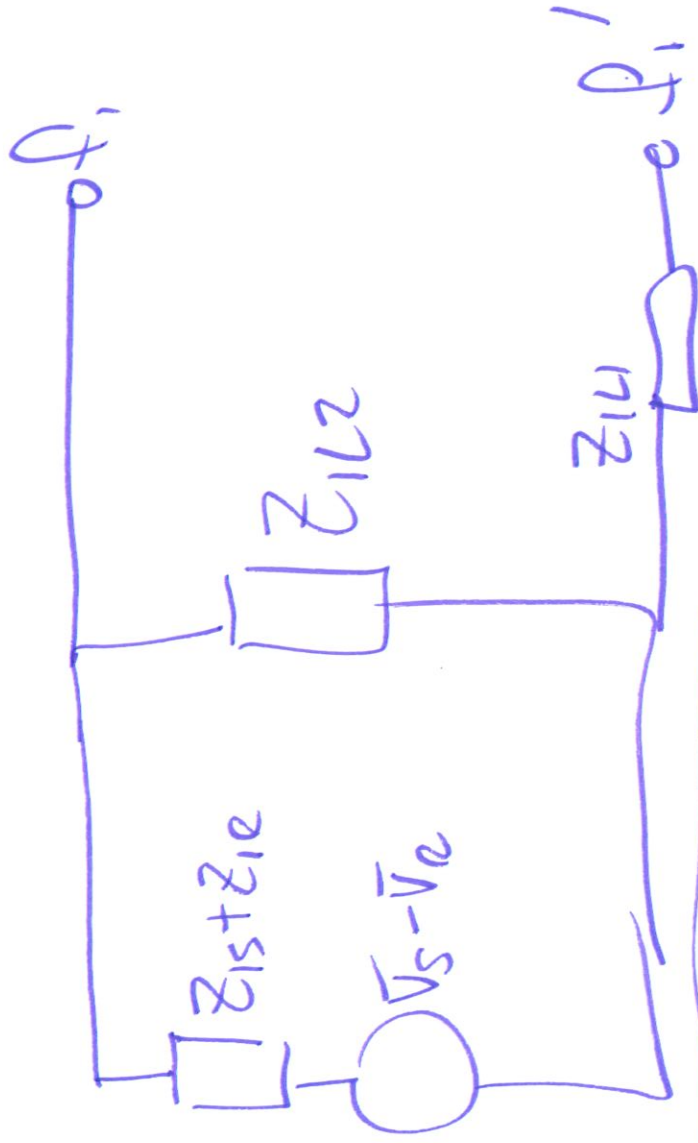

Norton equiv

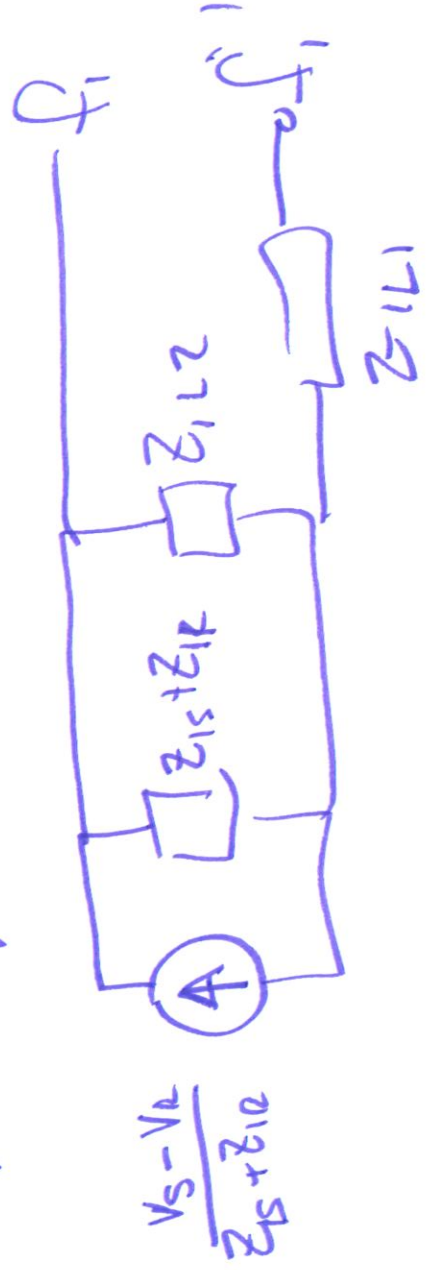


$$\frac{V_s - V_a}{Z_s + Z_e}$$

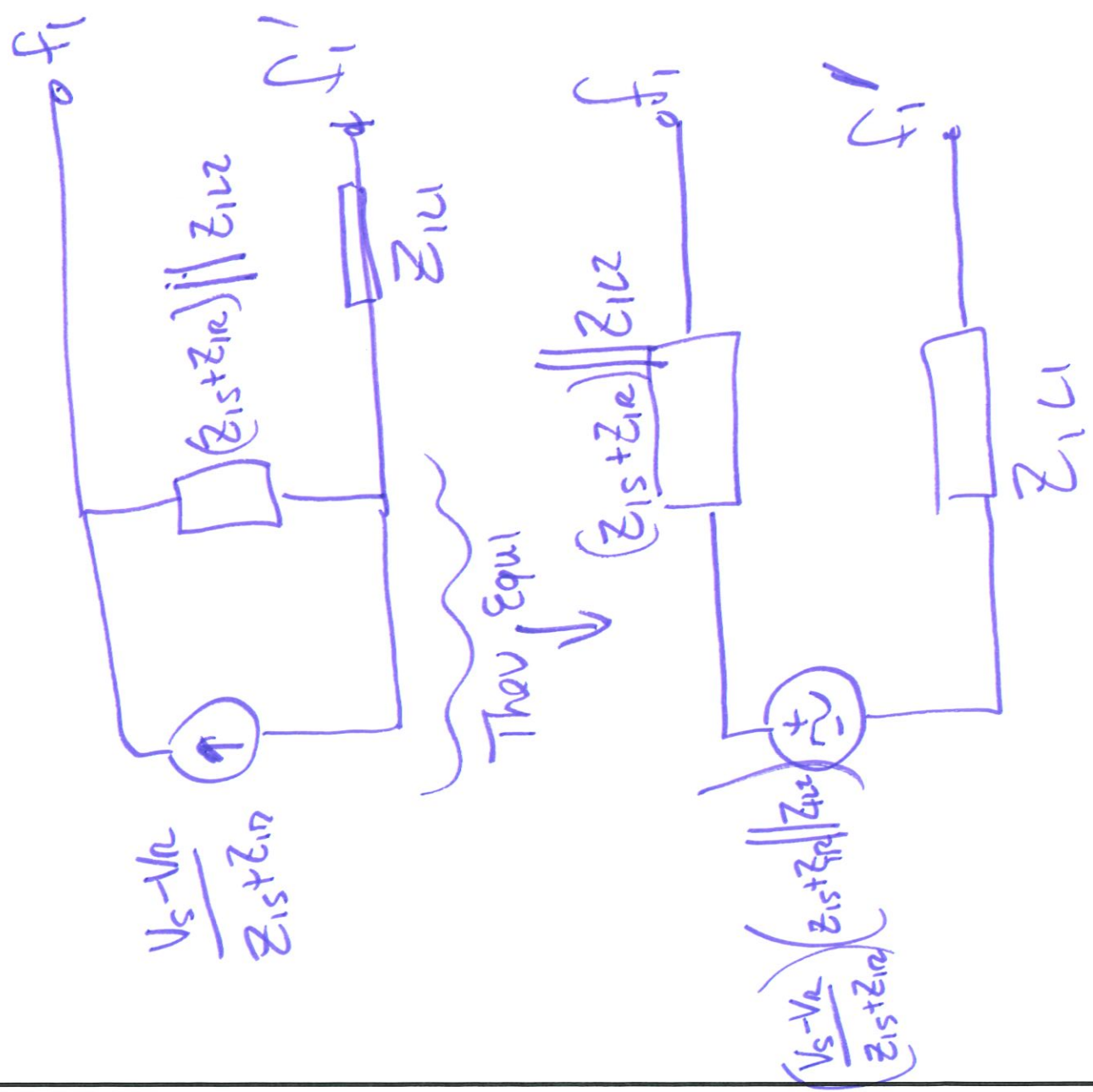

L17 19/25

Phase A open analysis:

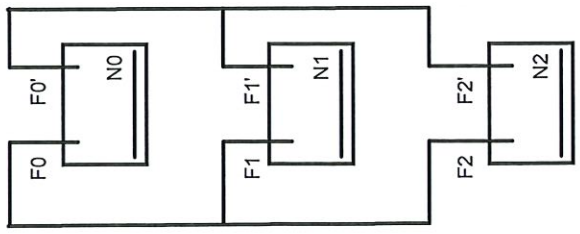

Equivalent voltage source for phase A open analysis:

$$V_{se} := V_S - V_R \quad V_{se} = (0.06 - 0.34i) \cdot pu$$

Norton Equivalent Current:

$$I_{se} := \frac{V_{se}}{Z_{1R} + Z_{1S}} \quad I_{se} = (-2.28 - 0.4i) \cdot pu$$

Equivalent Parallel Impedance:

$$Z_{eq} := \left(\frac{1}{Z_{1L2}} + \frac{1}{Z_{1S} + Z_{1R}} \right)^{-1} \quad Z_{eq} = 0.11i \cdot pu$$

Convert back to Thevenin Equivalent Voltage

$$V_f := Z_{eq} \cdot I_{se} \quad |V_f| = 0.25 \cdot pu \quad \arg(V_f) = -80 \cdot deg$$

two part theorem
two voltage

Positive sequence current in line 1:

$$I_{1L1_open} := \frac{V_f}{Z_{1equiv} + \left(\frac{1}{Z_{2equiv}} + \frac{1}{Z_{0equiv}} \right)^{-1}} \quad |I_{1L1_open}| = 0.34 \cdot pu$$

$$\arg(I_{1L1_open}) = -170 \cdot deg$$

Negative sequence current in line 1 (current divider on the line 1 current)

$$I_{2L1_open} := -I_{1L1_open} \cdot \frac{Z_{0equiv}}{Z_{2equiv} + Z_{0equiv}} \quad |I_{2L1_open}| = 0.27 \cdot pu$$

$$\arg(I_{2L1_open}) = 10 \cdot deg$$

Series unbalance

Assuming one phase different than other two

$$\bar{Z}_A \neq \bar{Z}_B = \bar{Z}_C$$

$$\bar{Z}_B = \bar{Z}_C$$

Phasor Domain

$$\begin{bmatrix} V_{AGf} - V_{AGf'} \\ V_{BGf} - V_{BGf'} \\ V_{CGf} - V_{CGf'} \end{bmatrix} =$$

$$\begin{bmatrix} V_{AA'} \\ V_{BB'} \\ V_{CC'} \end{bmatrix} =$$

$$\begin{bmatrix} Z_A & 0 & 0 \\ 0 & Z_B & 0 \\ 0 & 0 & Z_C \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix}$$

↓
symmetrical components

$$\begin{bmatrix} V_{AA'} \\ V_{BB'} \\ V_{CC'} \end{bmatrix} = \begin{bmatrix} A_{010} \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_{off1} \\ V_{off1} \\ V_{2off1} \end{bmatrix}$$

$$\begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} A_{012} \\ 0 \\ 0 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

$$V_{off'} = V_{of} - V_{of'}$$

$$\begin{bmatrix} A_{012} \end{bmatrix}^{-1} \begin{bmatrix} V_{off1} \\ V_{1off1} \\ V_{2off1} \end{bmatrix} = \begin{bmatrix} A_{012} \end{bmatrix}$$

[I]

$$\begin{bmatrix} Z_A & 0 & 0 \\ 0 & Z_B & 0 \\ 0 & 0 & Z_C \end{bmatrix}^{-1} \begin{bmatrix} A_{012} \\ 0 \\ 0 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

Because $Z_A \neq Z_B = Z_C$



Impedance matrix

$$\begin{bmatrix} V_{AA'0} \\ V_{AA'1} \\ V_{AA'2} \end{bmatrix} = \mathbf{I} \mathbf{Z}$$

$$\Downarrow$$

$$\begin{bmatrix} Z_A + 2Z_B & Z_A - Z_B & Z_A - Z_B \\ Z_A - Z_B & Z_A + 2Z_B & Z_A - Z_B \\ Z_A - Z_B & Z_A - Z_B & Z_A + 2Z_B \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

Now figure out how sequence networks connected ...

L17 23/25

- Now substitute for V_{aa0} with

$$V_{aa0} - I_0 \cdot Z_B = V_{aa1} - I_1 \cdot Z_B$$

from (1)

becomes: $V_{aa0} = V_{aa1} - I_1 \cdot Z_B + I_0 \cdot Z_B$

- Resulting in:

$$V_{aa1} - I_1 \cdot Z_B + I_0 \cdot Z_B + V_{aa1} = \frac{1}{3} \cdot [(I_0 + I_1) \cdot (2 \cdot Z_A + Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B)]$$

- Rearrange terms over several steps::

$$2 \cdot V_{aa1} - I_1 \cdot Z_B = \frac{1}{3} \cdot [(I_0 + I_1) \cdot (2 \cdot Z_A + Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B) - 3 \cdot I_0 \cdot Z_B]$$

$$2 \cdot V_{aa1} - I_1 \cdot Z_B = \frac{1}{3} \cdot [I_0 \cdot (2 \cdot Z_A + Z_B - 3 \cdot Z_B) + I_1 \cdot (2 \cdot Z_A + Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B)]$$

$$2 \cdot V_{aa1} - I_1 \cdot Z_B = \frac{1}{3} \cdot [2I_0 \cdot (Z_A - Z_B) + I_1 \cdot (2 \cdot Z_A + Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B)]$$

$$2 \cdot V_{aa1} - 2I_1 \cdot Z_B = \frac{1}{3} \cdot [2I_0 \cdot (Z_A - Z_B) + I_1 \cdot (2 \cdot Z_A + Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B)] - I_1 \cdot Z_B$$

$$2 \cdot V_{aa1} - 2I_1 \cdot Z_B = \frac{1}{3} \cdot [2I_0 \cdot (Z_A - Z_B) + I_1 \cdot (2 \cdot Z_A + Z_B - 3Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B)]$$

L17 24/25

Series Unbalance Derivation

$$\begin{bmatrix} V_{AA'0} \\ V_{AA'1} \\ V_{AA'2} \end{bmatrix} = \begin{bmatrix} Z_{012} \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

First step:

$$V_{aa'0} - V_{aa'1} = \frac{1}{3} \cdot I_0 \cdot [(Z_A + 2 \cdot Z_B) - (Z_A - Z_B)] + I_1 \cdot [(Z_A - Z_B)] + I_2 \cdot [(Z_A - Z_B) - (Z_A - Z_B)]$$

- Simplifying

$$V_{aa'0} - V_{aa'1} = \frac{1}{3} \cdot [Z_B \cdot (3 \cdot I_0 - 3 \cdot I_1)] = Z_B \cdot (I_0 - I_1)$$

- Rearrange terms so all zero sequence terms on one side and positive sequence on the other:

$$V_{aa'0} - I_0 \cdot Z_B = V_{aa'1} - I_1 \cdot Z_B$$

- Similarly, using $V_0 - V_2$ we get:

(1)

$$V_{aa'0} - I_0 \cdot Z_B = V_{aa'2} - I_2 \cdot Z_B = V_{aa'1} - I_1 \cdot Z_B$$

Second Step:

$$V_{aa'0} + V_{aa'1} = \frac{1}{3} \cdot I_0 \cdot [(Z_A + 2 \cdot Z_B) + (Z_A - Z_B)] + I_1 \cdot [(Z_A - Z_B)] + I_2 \cdot [(Z_A - Z_B) + (Z_A - Z_B)]$$

- Simplifying

$$V_{aa'0} + V_{aa'1} = \frac{1}{3} \cdot [(I_0 + I_1) \cdot (2 \cdot Z_A + Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B)]$$

L17 25/25

$$2 \cdot V_{aa1} - 2I_1 \cdot Z_B = \frac{1}{3} [2I_0 \cdot (Z_A - Z_B) + 2I_1 \cdot (Z_A - Z_B) + 2 \cdot I_2 \cdot (Z_A - Z_B)]$$

- Divide everything by 2:

$$V_{aa1} - I_1 \cdot Z_B = \frac{1}{3} [I_0 \cdot (Z_A - Z_B) + I_1 \cdot (Z_A - Z_B) + I_2 \cdot (Z_A - Z_B)]$$

Finally we get:

$$(V_{aa1} - I_1 \cdot Z_B) = \frac{1}{3} [(Z_A - Z_B) \cdot (I_0 + I_1 + I_2)] \quad (2)$$

$$(V_{AA0} - I_0 Z_B) =$$

$$V_{AA2} - I_2 Z_B =$$

4 circuits "parallel" - - -