

Series Fault Examples

pu := 1 MVA := 1000kW


$$a := 1e^{j \cdot 120\text{deg}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$

Single Phase Open Examples

Example 1:

- System one-line diagram:

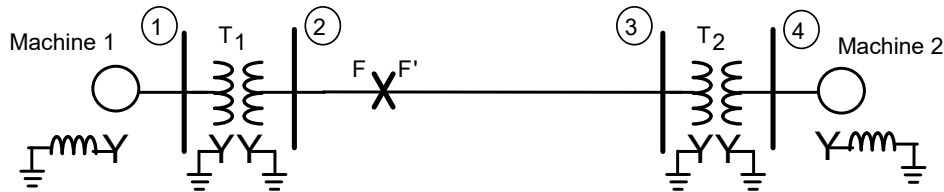

Machines 1 and 2: $S_{\text{Mach}} := 100\text{MVA}$ $V_{\text{machine}} := 20\text{kV}$
 $X_{\text{dMach}''} := 20\%$ $X_{1\text{Mach}} := X_{\text{dMach}''}$ $X_{2\text{Mach}} := X_{1\text{Mach}}$
 $X_{0\text{Mach}} := 4\%$ $X_{\text{nMach}} := 5\%$

Transformers T1 and T2: $S_{\text{Tran}} := 1000\text{MVA}$ $V_{\text{HV}} := 345\text{kV}$ $V_{\text{LV}} := 20\text{kV}$ $X_{\text{T}} := 8\%$

Transmission Line $X_{\text{L1}} := 15\%$ $X_{\text{L2}} := X_{\text{L1}}$ $X_{\text{L0}} := 50\%$

$S_{\text{Base}} := 100\text{MVA}$

$$V_{B_{Line}} := 345 \text{ kV} \quad V_{B_{mach}} := V_{B_{Line}} \cdot \left(\frac{V_{LV}}{V_{HV}} \right) \quad V_{B_{mach}} = 20 \cdot \text{kV}$$

No change of base calculations are needed for this system.

Determine internal source voltages:

$$\text{mag}S_{pre} := 80 \text{ MVA} \quad \text{pf}_{pre} := 0.85 \text{ lagging} \quad \theta_{pre} := \text{acos}(\text{pf}_{pre}) \quad \theta_{pre} = 31.79 \cdot \text{deg}$$

$$S_{pre} := \frac{\text{mag}S_{pre}}{S_{Base}} \cdot e^{j \cdot \theta_{pre}} \quad S_{pre} = (0.68 + 0.42i) \cdot \text{pu} \quad |S_{pre}| = 0.8 \cdot \text{pu}$$

Assume bus 3 voltage is 1.0 pu at and angle of 0 degrees.

$$V_3 := 1.0$$

$$I_{load} := \overline{\left(\frac{S_{pre}}{V_3} \right)} \quad I_{load} = 0.68 - 0.42i \quad |I_{load}| = 0.8 \cdot \text{pu} \quad \arg(I_{load}) = -31.79 \cdot \text{deg}$$

Internal voltage on the motor (since we don't know steady-state synchronous reactance, use X1):

$$E_2 := V_3 - I_{load} \cdot j(X_T + X_{1Mach}) \quad |E_2| = 0.9 \quad \phi_2 := \arg(E_2) \quad \phi_2 = -12.18 \cdot \text{deg}$$

Generator internal voltage:


$$E_1 := V_3 + I_{load} \cdot (j \cdot X_{L1} + j \cdot X_T + j \cdot X_{1Mach}) \quad |E_1| = 1.22 \cdot \text{pu} \quad \phi_1 := \arg(E_1) \quad \phi_1 = 13.9 \cdot \text{deg}$$

Check result by calculating power transfer between sources and current:

$$P_{\text{trans}} := \frac{|E_1| \cdot |E_2| \cdot \sin(\phi_1 - \phi_2)}{2 \cdot X_{1\text{Mach}} + 2 \cdot X_T + X_{L1}} \quad P_{\text{trans}} - \text{Re}(S_{\text{pre}}) = 0$$

$$I_{\text{trans}} := \frac{E_1 - E_2}{j(2 \cdot X_{1\text{Mach}} + 2 \cdot X_T + X_{L1})} \quad I_{\text{trans}} - I_{\text{load}} = 0$$

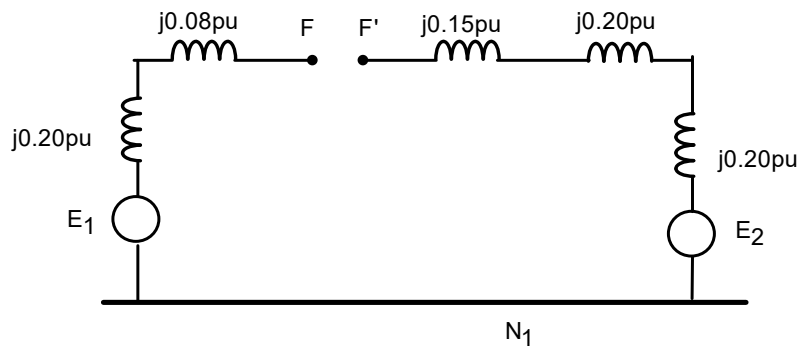- Positive sequence equivalent circuit (with phase open point indicated).



Find total impedance counterclockwise around loop from F to F'


$$Z_{1\text{total}} := j \cdot (X_{1\text{Mach}} + X_T + X_{L1} + X_T + X_{1\text{Mach}})$$

$$Z_{1\text{total}} = 0.71i \cdot \text{pu}$$

$$Z_{1\text{FF}'} := Z_{1\text{total}}$$

$$V_{\text{equiv}} := E_1 - E_2$$

- Negative sequence equivalent circuit:

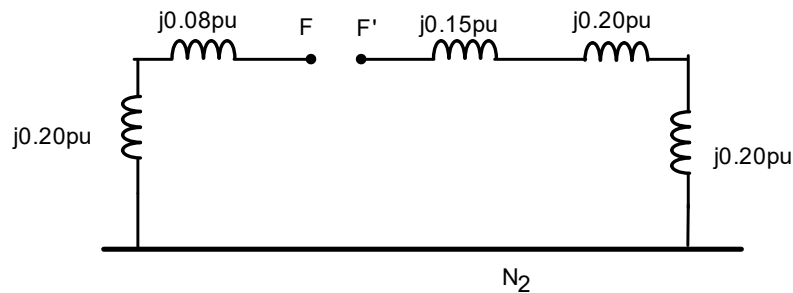


Find total impedance counterclockwise around loop from F to F'

$$Z_{2\text{total}} := j \cdot (X_{2\text{Mach}} + X_T + X_{L2} + X_T + X_{2\text{Mach}})$$

$$Z_{2\text{total}} = 0.71i \cdot \text{pu}$$

$$Z_{2\text{FF}'} := Z_{2\text{total}}$$

- Zero sequence equivalent:

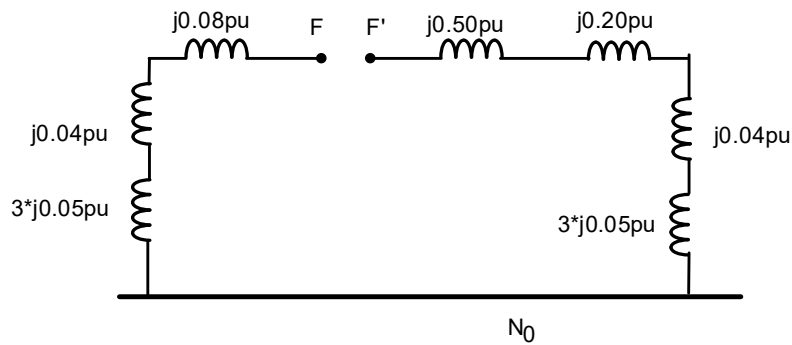


Find total impedance counterclockwise around loop from F to F'

$$Z_{0total} := j \cdot (2 \cdot X_{0Mach} + 2 \cdot X_T + X_{L0} + 2 \cdot 3 \cdot X_{nMach})$$

$$Z_{0total} = 1.04i \cdot pu$$

$$Z_{0FF'} := Z_{0total}$$

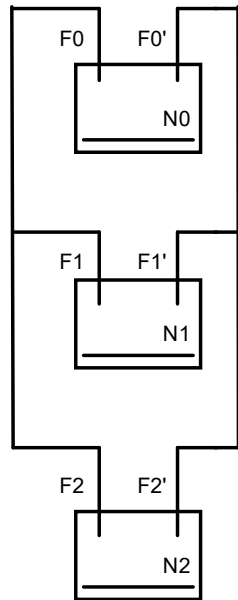Now solve for the single phase open circuit currents and voltages:



$$I_1 := \frac{V_{equiv}}{Z_{1FF'} + \left(\frac{1}{Z_{2FF'}} + \frac{1}{Z_{0FF'}} \right)^{-1}}$$

$$I_1 = (0.43 - 0.26i) \cdot pu$$

$$|I_1| = 0.5 \cdot pu \quad \arg(I_1) = -31.79 \cdot deg$$

$$I_2 := -I_1 \cdot \left(\frac{Z_{0FF'}}{Z_{2FF'} + Z_{0FF'}} \right)$$

$$I_2 = (-0.25 + 0.16i) \cdot pu$$

$$|I_2| = 0.3 \cdot pu \quad \arg(I_2) = 148.21 \cdot deg$$

$$I_0 := -I_1 \cdot \left(\frac{Z_{2FF'}}{Z_{2FF'} + Z_{0FF'}} \right)$$

$$I_0 = (-0.17 + 0.11i) \cdot pu$$

$$|I_0| = 0.2 \cdot pu \quad \arg(I_0) = 148.21 \cdot deg$$

$$I_{abc} := A_{012} \cdot \begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix} \quad \overrightarrow{|I_{abc}|} = \begin{pmatrix} 0 \\ 0.76 \\ 0.76 \end{pmatrix} \cdot \text{pu} \quad \arg(I_{abc_1}) = -145.57 \cdot \text{deg}$$

$$\arg(I_{abc_2}) = 82 \cdot \text{deg}$$

Using the right have the sequence equivalent circuits:

$$V_{3\text{new}1} := E_2 + I_1 \cdot j \cdot (X_{1\text{Mach}} + X_T) \quad |V_{3\text{new}1}| = 0.96 \cdot \text{pu} \quad \arg(V_{3\text{new}1}) = -4.25 \cdot \text{deg}$$

$$V_{3\text{new}2} := 0 + I_2 \cdot j \cdot (X_{2\text{Mach}} + X_T) \quad |V_{3\text{new}2}| = 0.08 \cdot \text{pu} \quad \arg(V_{3\text{new}2}) = -121.79 \cdot \text{deg}$$

$$V_{3\text{new}0} := 0 + I_0 \cdot j \cdot (X_{0\text{Mach}} + X_T + 3 \cdot X_{n\text{Mach}}) \quad |V_{3\text{new}0}| = 0.05 \cdot \text{pu} \quad \arg(V_{3\text{new}0}) = -121.79 \cdot \text{deg}$$


$$V_{3\text{new}ABC} := A_{012} \cdot \begin{pmatrix} V_{3\text{new}0} \\ V_{3\text{new}1} \\ V_{3\text{new}2} \end{pmatrix} \quad \overrightarrow{|V_{3\text{new}ABC}|} = \begin{pmatrix} 0.903 \\ 0.971 \\ 1.014 \end{pmatrix} \cdot \text{pu} \quad \arg(V_{3\text{new}ABC}) = \begin{pmatrix} -12.06 \\ -119.95 \\ 118.58 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{ABC} := 1.0 \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} - V_{3\text{new}ABC}$$


$$\overrightarrow{|\Delta V_{ABC}|} = \begin{pmatrix} 0.22 \\ 0.03 \\ 0.03 \end{pmatrix}$$

$$\arg(\Delta V_{ABC}) = \begin{pmatrix} 58.21 \\ -121.79 \\ -121.79 \end{pmatrix} \cdot \text{deg}$$


ATP simulation results:

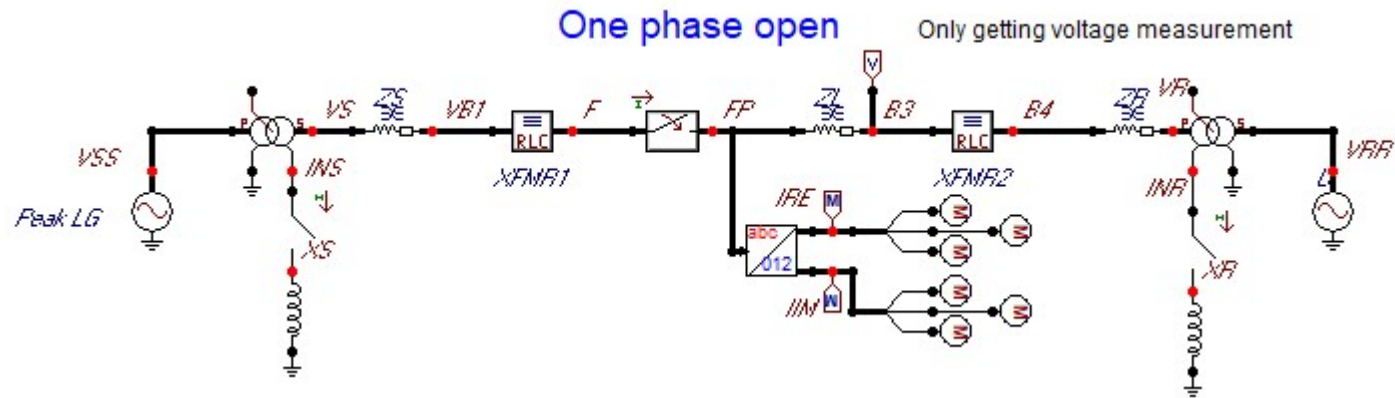


Currents


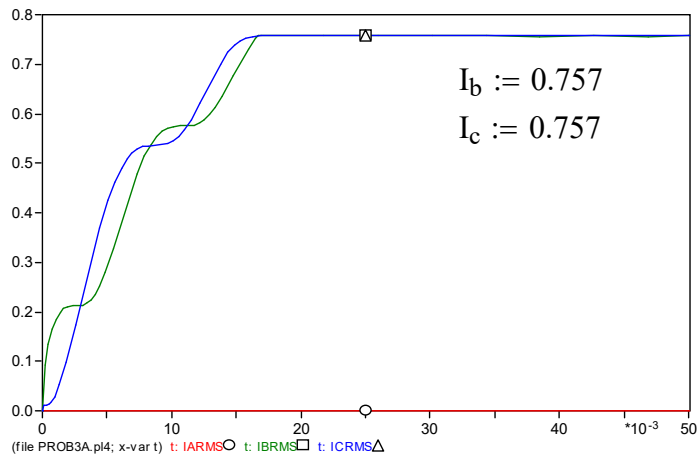


Voltages

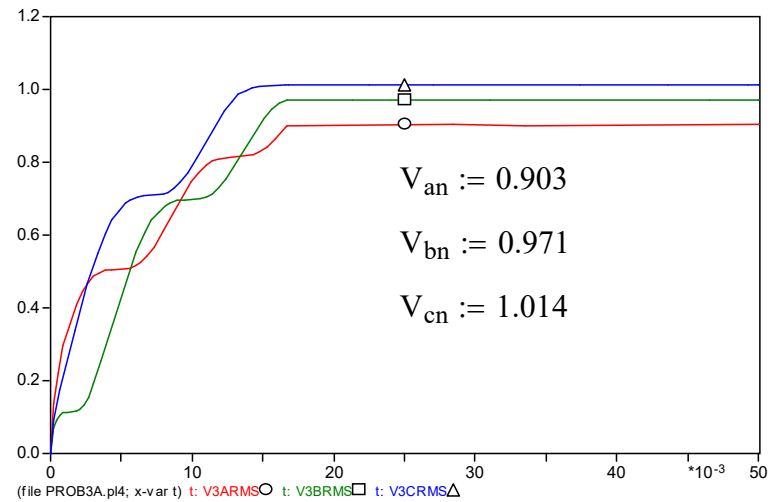


PSCAD/EMTDC implementation

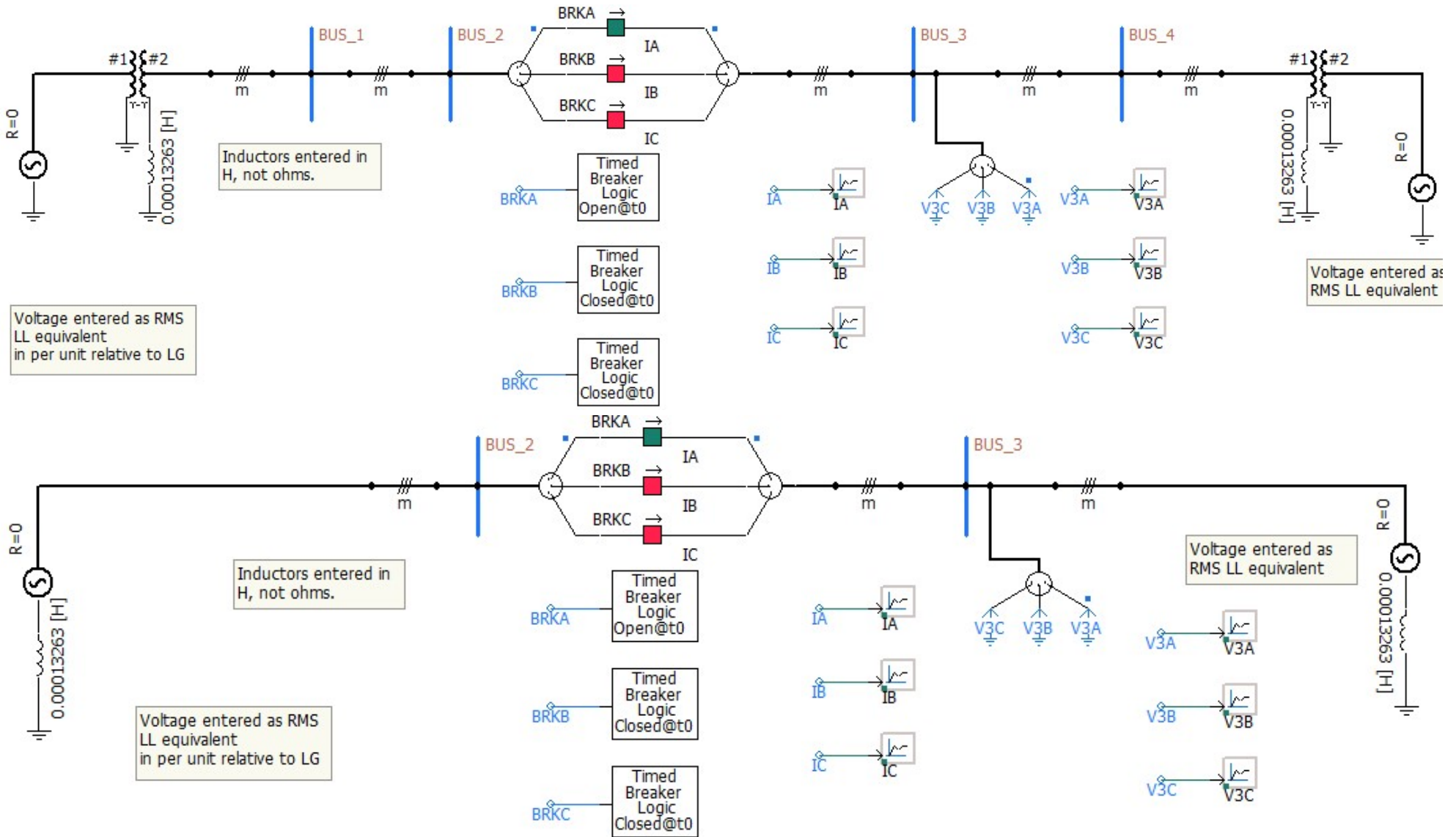


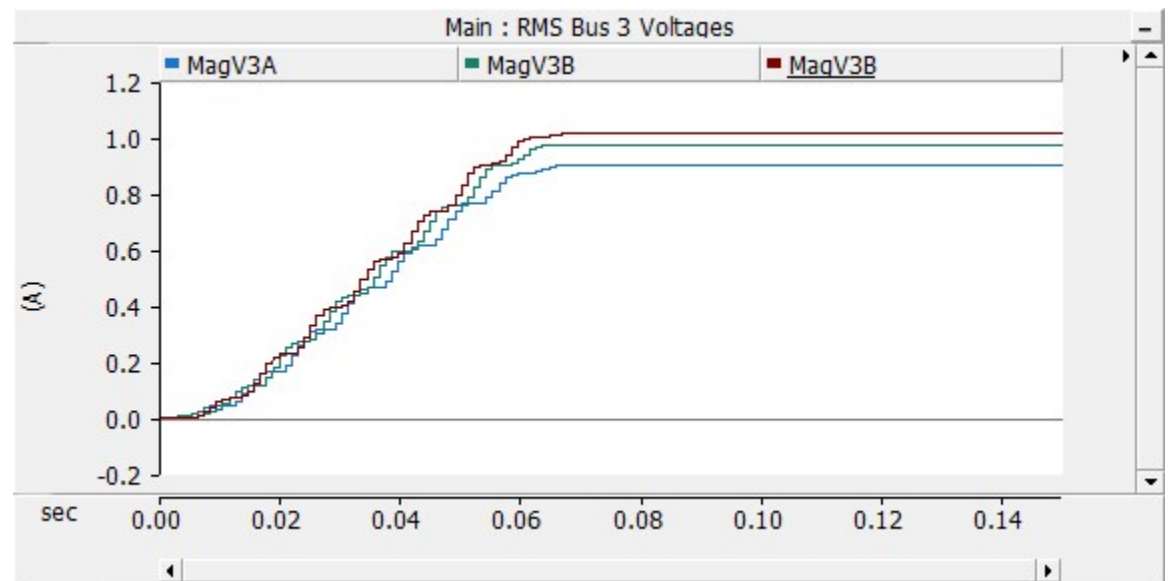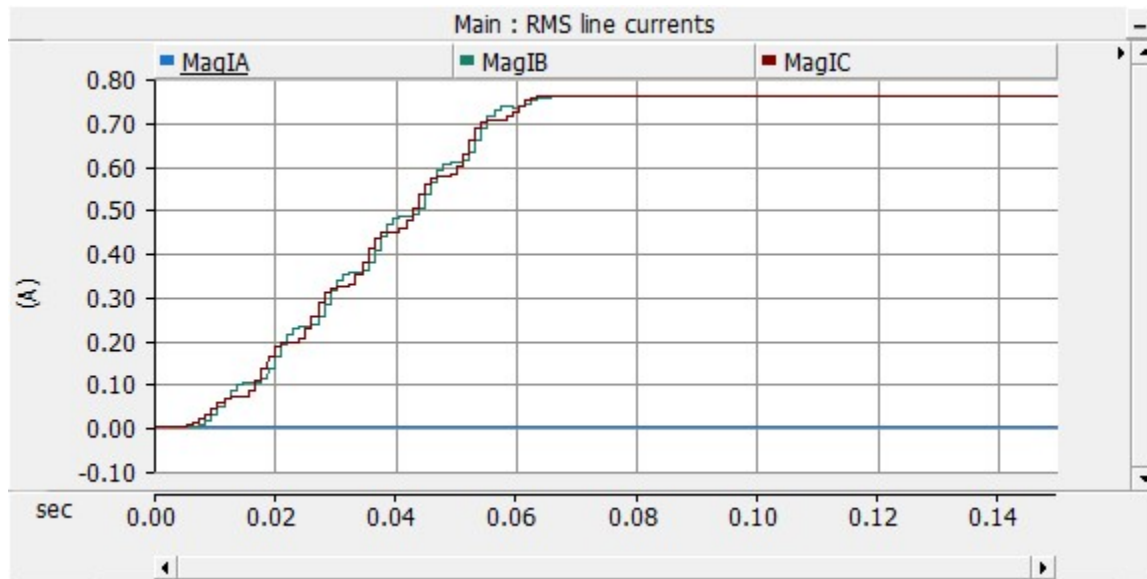

EMTP-RV Implementation

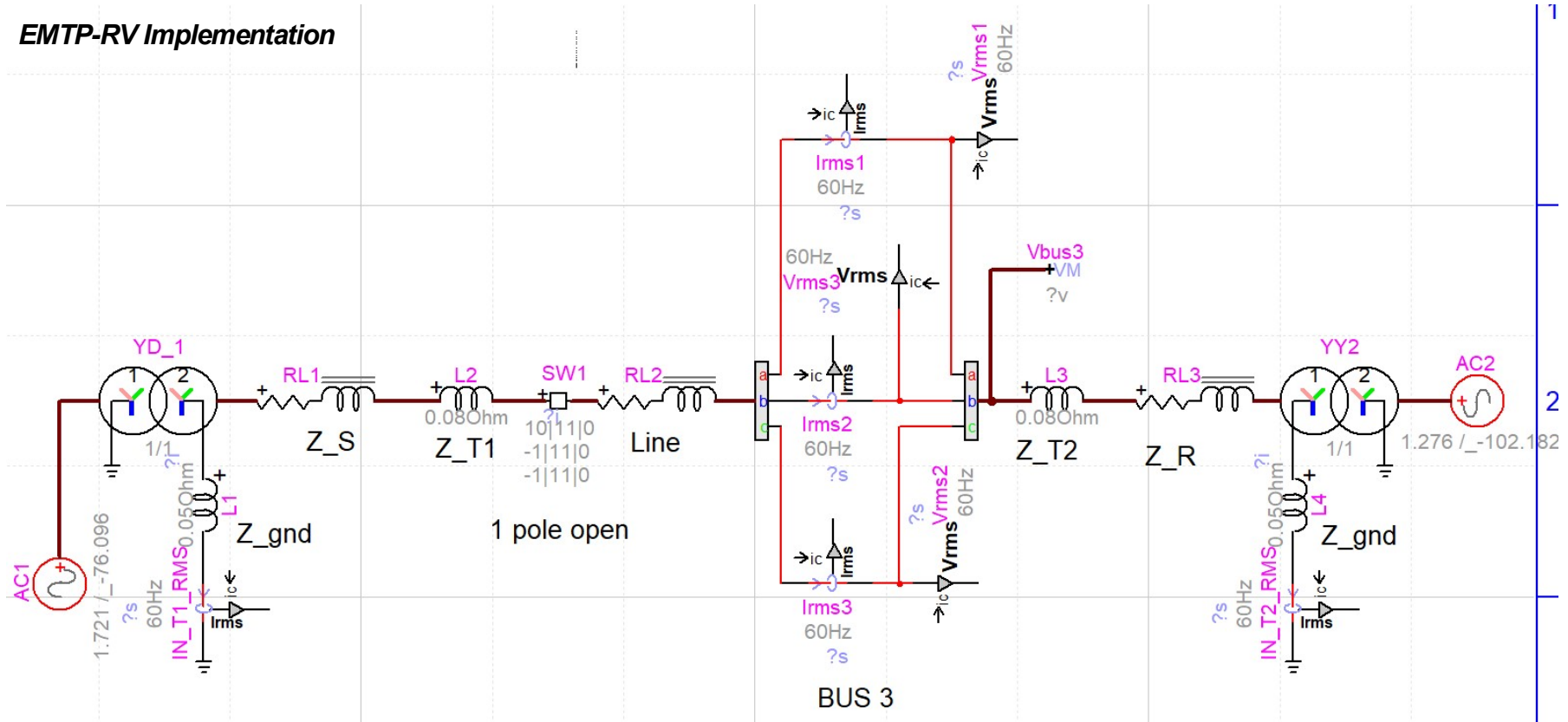


Currents

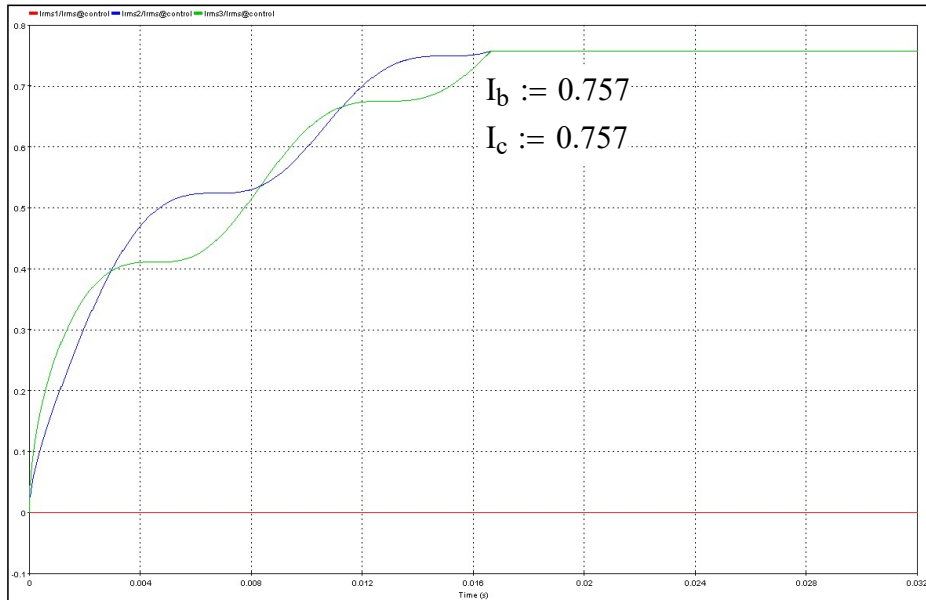


[EMT1] example1_RV.m - Tue Oct 17 09:58:47 PDT 2023 - C:\j\cour\EE\EE523\fall23\Lectures\L17\EMTP-RV\example1_RV_sl

Voltages

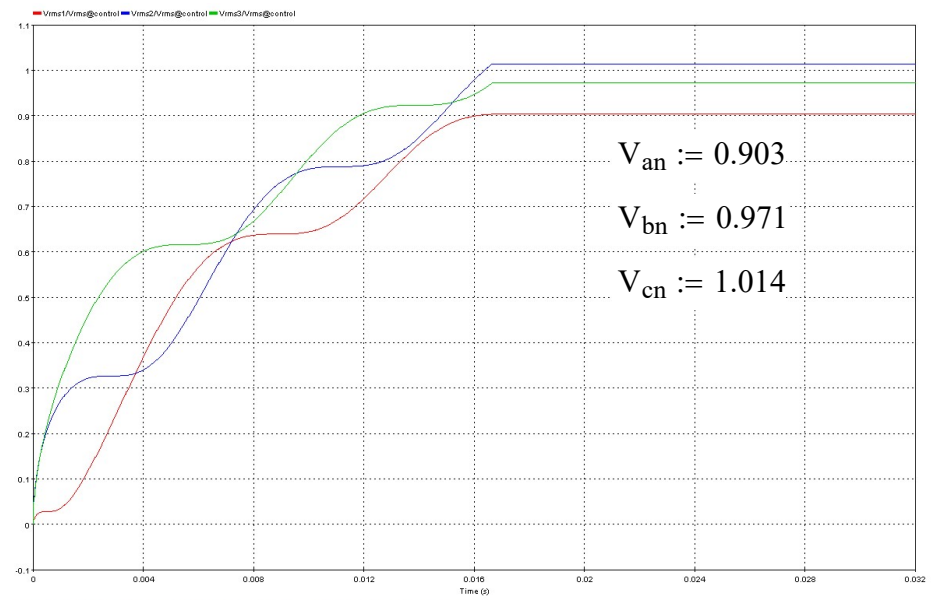

[EMT1] example1_RV.m - Tue Oct 17 09:58:47 PDT 2023 - C:\j\cour\EE\EE523\fall23\Lectures\L17\EMTP-RV\example1_RV_sl

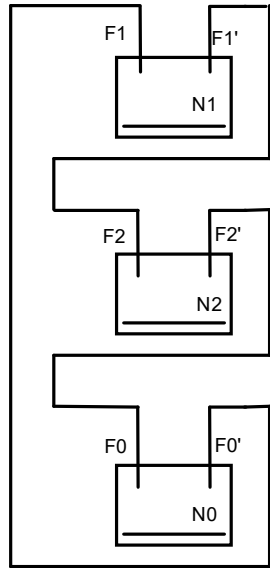Now solve the two phase open circuit below for the sequence currents:



$$I_1 := \frac{V_{\text{equiv}}}{Z_{1FF'} + Z_{2FF'} + Z_{0FF'}}$$

$$I_1 = (0.2 - 0.12i) \cdot \text{pu}$$

$$|I_1| = 0.23 \cdot \text{pu} \quad \arg(I_1) = -31.79 \cdot \text{deg}$$

$$I_2 := I_1 \quad I_0 := I_1$$

$$I_{\text{abc}} := A_{012} \cdot \begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix}$$

$$\overrightarrow{|I_{\text{abc}}|} = \begin{pmatrix} 0.69 \\ 0 \\ 0 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(I_{\text{abc}})} = \begin{pmatrix} -31.79 \\ 81.87 \\ 81.87 \end{pmatrix} \cdot \text{deg}$$

$$V_{3\text{new}1} := E_2 + I_1 \cdot j \cdot (X_{1\text{Mach}} + X_T)$$

$$V_{3\text{new}1} = (0.92 - 0.14i) \cdot \text{pu}$$

$$V_{3\text{new}2} := 0 + I_2 \cdot j \cdot (X_{2\text{Mach}} + X_T)$$

$$V_{3\text{new}2} = (0.03 + 0.05i) \cdot \text{pu}$$

$$V_{3\text{new}0} := 0 + I_0 \cdot j \cdot (X_{0\text{Mach}} + X_T + 3 \cdot X_{\text{nMach}})$$

$$V_{3\text{new}0} = (0.03 + 0.05i) \cdot \text{pu}$$

$$V_{3\text{new}ABC} := A_{012} \cdot \begin{pmatrix} V_{3\text{new}0} \\ V_{3\text{new}1} \\ V_{3\text{new}2} \end{pmatrix}$$

$$\overrightarrow{|V_{3\text{new}ABC}|} = \begin{pmatrix} 0.983 \\ 0.905 \\ 0.901 \end{pmatrix} \cdot \text{pu}$$



$$\overrightarrow{\arg(V_{3\text{new}ABC})} = \begin{pmatrix} -1.6 \\ -132.16 \\ 107.93 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{ABC} := 1.0 \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} - V_{3\text{new}ABC}$$


$$\overrightarrow{|\Delta V_{ABC}|} = \begin{pmatrix} 0.03 \\ 0.22 \\ 0.22 \end{pmatrix} \cdot \text{pu}$$


$$\overrightarrow{\arg(\Delta V_{ABC})} = \begin{pmatrix} 58.21 \\ -61.27 \\ 177.7 \end{pmatrix} \cdot \text{deg}$$

ATP Simulation Results:

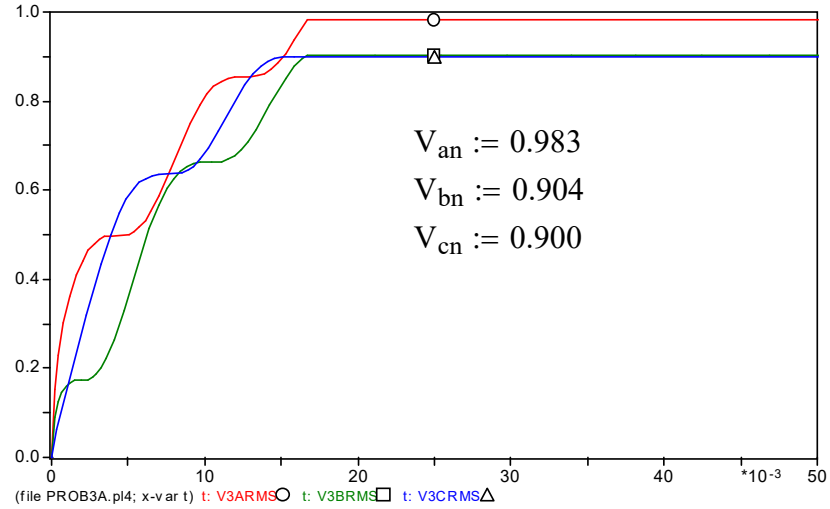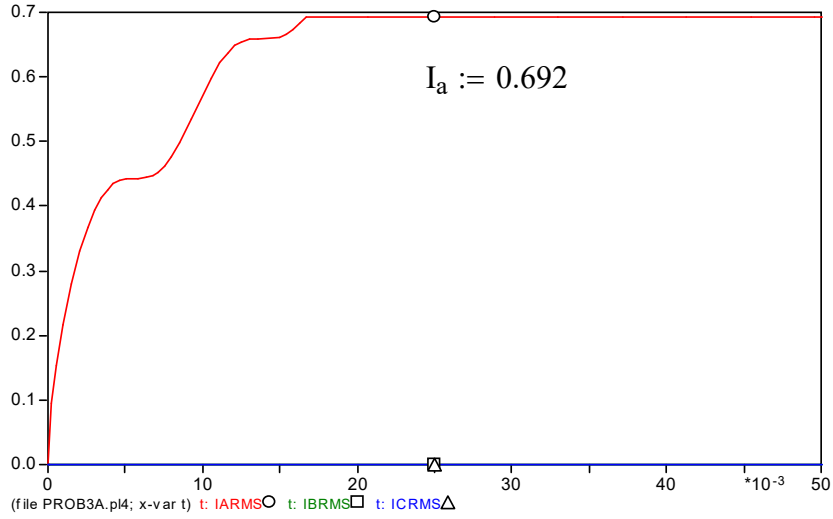


PSCAD/EMTDC Simulation Results:

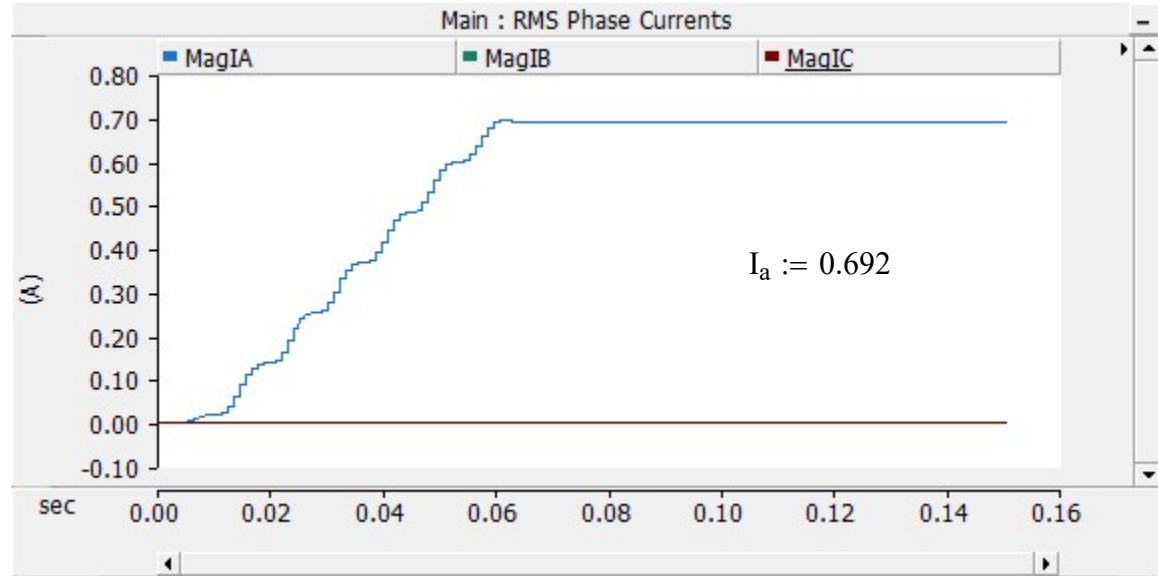


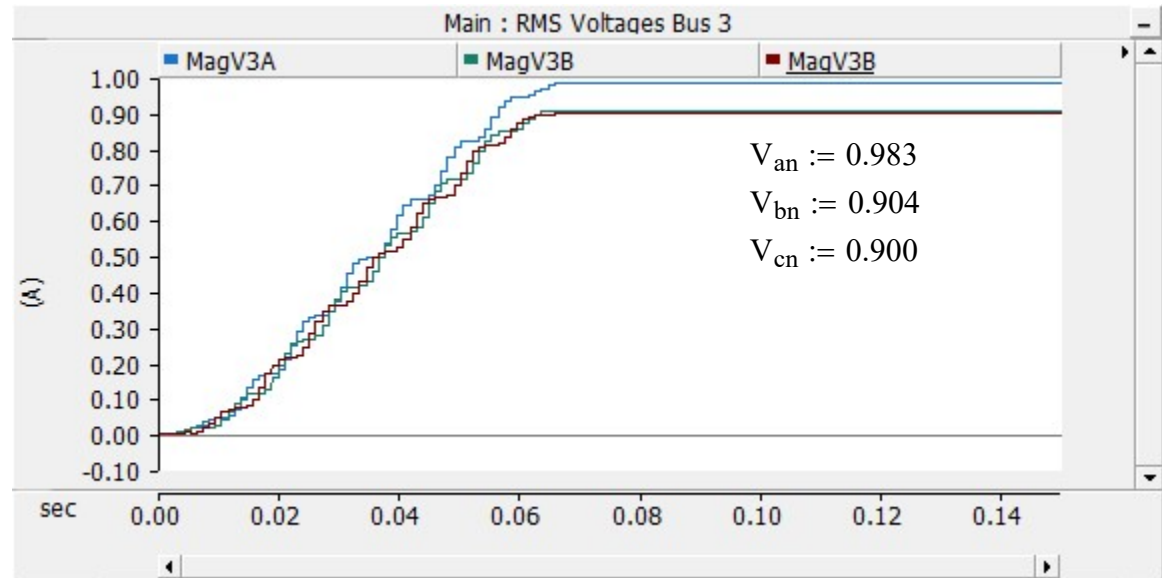

EMTP-RV Simulation Results:

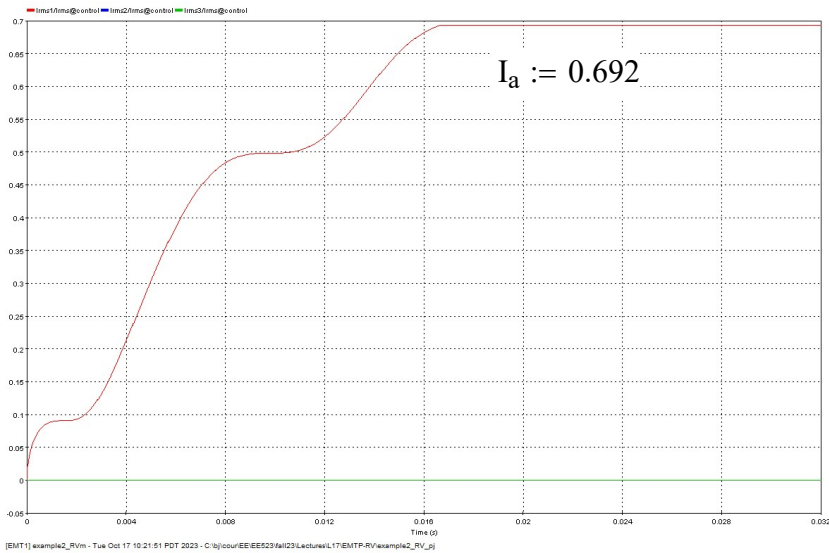


[EMT1] example2_RV.m - Tue Oct 17 10:21:51 PDT 2023 - C:\jocou\EE\EE523\fall23\Lecture\17\EMTP-RV\example2_RV.pl

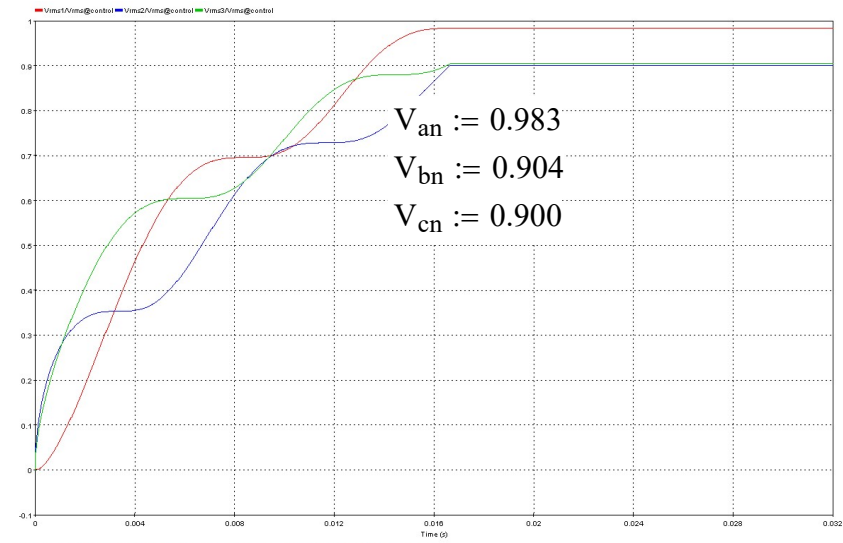


[EMT1] example2_RV.m - Tue Oct 17 10:21:51 PDT 2023 - C:\jocou\EE\EE523\fall23\Lecture\17\EMTP-RV\example2_RV.pl

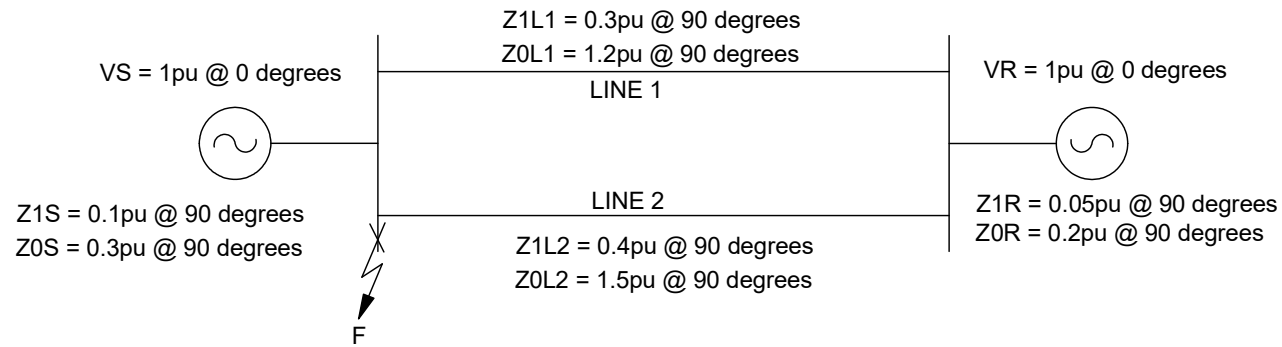Example 2 For the system shown below, develop the sequence connection diagram for a single-phase open on Line 1.



$$Z_{1S} := j \cdot 0.1 \text{ pu} \quad Z_{1R} := j \cdot 0.05 \text{ pu} \quad Z_{0S} := j \cdot 0.3 \text{ pu} \quad Z_{0R} := j \cdot 0.2 \text{ pu}$$
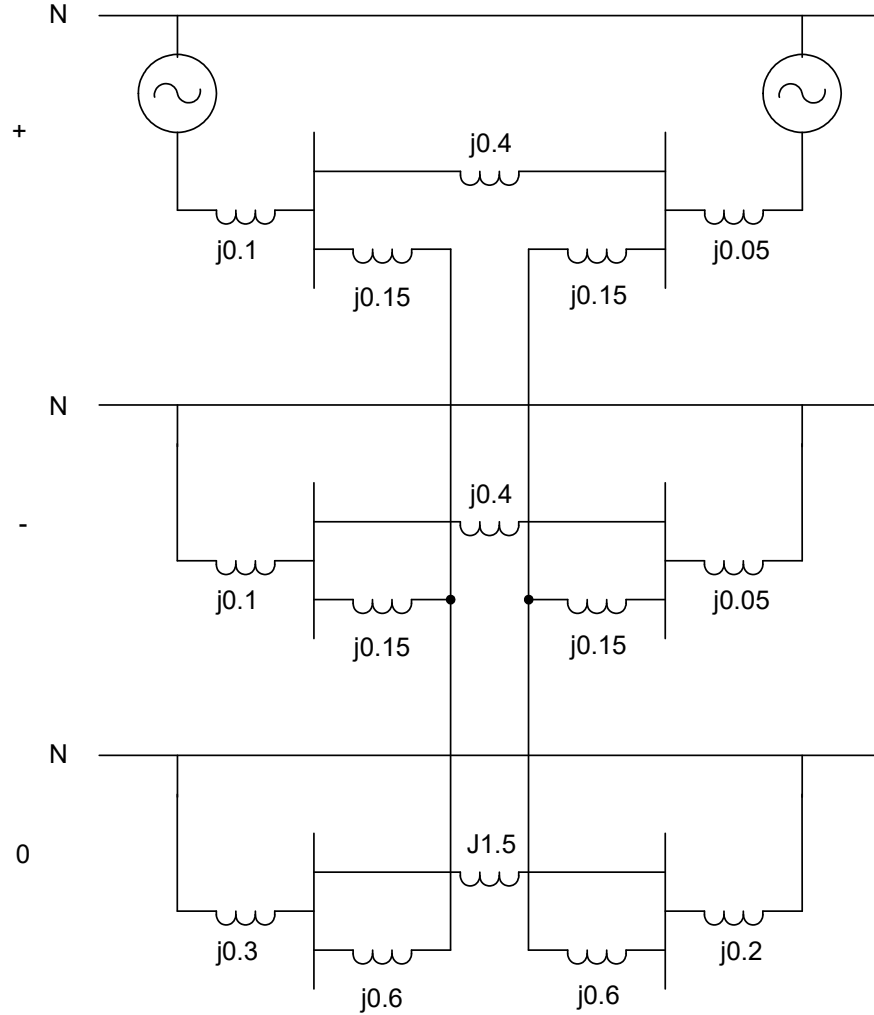
$$Z_{1L1} := j \cdot 0.3 \quad Z_{1L2} := j \cdot 0.4 \quad Z_{0L1} := j \cdot 1.2 \quad Z_{0L2} := j \cdot 1.5$$



$$Z_{1\text{equiv}} := \frac{Z_{1L1}}{2} + \left(\frac{1}{Z_{1S} + Z_{1R}} + \frac{1}{Z_{1L2}} \right)^{-1} + \frac{Z_{1L1}}{2}$$

$$Z_{1\text{equiv}} = 0.41i \cdot \text{pu}$$

$$Z_{2\text{equiv}} := Z_{1\text{equiv}}$$

$$Z_{0\text{equiv}} := Z_{0L1} + \left(\frac{1}{Z_{0S} + Z_{0R}} + \frac{1}{Z_{0L2}} \right)^{-1}$$

$$Z_{0\text{equiv}} = 1.58i \cdot \text{pu}$$

Using the sequence diagrams above calculate the positive-, negative-, and zero-sequence currents on Line 2 with $V_R = 1\text{pu} @ 20 \text{ degrees}$.

$$V_S := 1\text{pu} \cdot e^{j \cdot 0\text{deg}} \quad V_R := 1\text{pu} \cdot e^{j \cdot 20\text{deg}}$$

Total pre-fault current:

$$I_{\text{sourceprefault}} := \frac{V_S - V_R}{Z_{1S} + Z_{1R} + \left(\frac{1}{Z_{1L1}} + \frac{1}{Z_{1L2}} \right)^{-1}} \quad |I_{\text{sourceprefault}}| = 1.08 \cdot \text{pu} \quad \arg(I_{\text{sourceprefault}}) = -170 \cdot \text{deg}$$

Current dividers to find the current in lines 1 and 2:


$$I_{L1_prefault} := I_{\text{sourceprefault}} \cdot \left(\frac{Z_{1L2}}{Z_{1L1} + Z_{1L2}} \right) \quad |I_{L1_prefault}| = 0.62 \cdot \text{pu} \quad \arg(I_{L1_prefault}) = -170 \cdot \text{deg}$$

$$I_{L2_prefault} := I_{\text{sourceprefault}} \cdot \left(\frac{Z_{1L1}}{Z_{1L1} + Z_{1L2}} \right) \quad |I_{L2_prefault}| = 0.46 \cdot \text{pu} \quad \arg(I_{L2_prefault}) = -170 \cdot \text{deg}$$

$$I_{\text{ABCL1_prefault}} := I_{L1_prefault} \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} \quad \overrightarrow{|I_{\text{ABCL1_prefault}}|} = \begin{pmatrix} 0.62 \\ 0.62 \\ 0.62 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(I_{\text{ABCL1_prefault}})} = \begin{pmatrix} -170 \\ 70 \\ -50 \end{pmatrix} \cdot \text{deg}$$

$$I_{\text{ABCL2_prefault}} := I_{L2_prefault} \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} \quad \overrightarrow{|I_{\text{ABCL2_prefault}}|} = \begin{pmatrix} 0.46 \\ 0.46 \\ 0.46 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(I_{\text{ABCL2_prefault}})} = \begin{pmatrix} -170 \\ 70 \\ -50 \end{pmatrix} \cdot \text{deg}$$

Phase A open analysis:

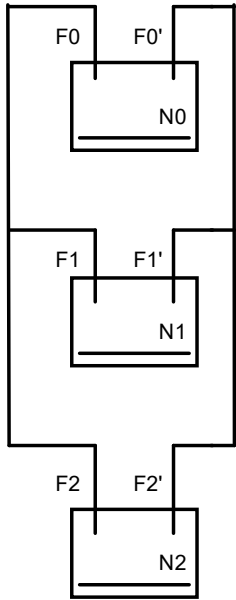

Equivalent voltage source for phase A open analysis:

$$V_{se} := V_S - V_R \quad V_{se} = (0.06 - 0.34i) \cdot \text{pu}$$

Norton Equivalent Current:

$$I_{se} := \frac{V_{se}}{Z_{1R} + Z_{1S}} \quad I_{se} = (-2.28 - 0.4i) \cdot \text{pu}$$

Equivalent Parallel Impedance:

$$Z_{eq} := \left(\frac{1}{Z_{1L2}} + \frac{1}{Z_{1S} + Z_{1R}} \right)^{-1} \quad Z_{eq} = 0.11i \cdot \text{pu}$$

Convert back to Thevenin Equivalent Voltage

$$V_f := Z_{eq} \cdot I_{se} \quad |V_f| = 0.25 \cdot \text{pu} \quad \arg(V_f) = -80 \cdot \text{deg}$$

Positive sequence current in line 1:

$$I_{1L1_open} := \frac{V_f}{Z_{1equiv} + \left(\frac{1}{Z_{2equiv}} + \frac{1}{Z_{0equiv}} \right)^{-1}} \quad |I_{1L1_open}| = 0.34 \cdot \text{pu}$$

$$\arg(I_{1L1_open}) = -170 \cdot \text{deg}$$

Negative sequence current in line 1 (current divider on the line 1 current)

$$I_{2L1_open} := -I_{1L1_open} \cdot \frac{Z_{0equiv}}{Z_{2equiv} + Z_{0equiv}} \quad |I_{2L1_open}| = 0.27 \cdot \text{pu}$$

$$\arg(I_{2L1_open}) = 10 \cdot \text{deg}$$

Zero sequence current in line 1 (current divider on the line 1 current)

$$I_{0L1_open} := -I_{1L1_open} \cdot \frac{Z_{2equiv}}{Z_{2equiv} + Z_{0equiv}} \quad |I_{0L1_open}| = 0.07 \cdot pu \quad \arg(I_{0L1_open}) = 10 \cdot deg$$

$$I_{ABC_Line1} := A_{012} \cdot \begin{pmatrix} I_{0L1_open} \\ I_{1L1_open} \\ I_{2L1_open} \end{pmatrix}$$

$$|I_{ABC_Line1}| = \begin{pmatrix} 0 \\ 0.545 \\ 0.545 \end{pmatrix} \cdot pu$$

$$\arg(I_{ABC_Line1}_1) = 88.74 \cdot deg$$

$$\arg(I_{ABC_Line1}_2) = -68.74 \cdot deg$$

Note that the magnitude on phase A is 0 and a little smaller on the unfaulted phases. There is also a phase shift compared to pre-fault

Now to find the line 2 current, we need to do another current divider on each of the sequence currents from line 1, since the sequence currents could either pass through the sources or line 1 to return to line 1.

Positive sequence load current in line two ignoring open line

$$I_{LineA2} := \frac{V_S - V_R}{Z_{1S} + Z_{1L2} + Z_{1R}}$$

$$|I_{LineA2}| = 0.631$$

$$\arg(I_{LineA2}) = -170 \cdot deg$$

$$I_{1L2} := -I_{1L1_open} \cdot \left(\frac{Z_{1S} + Z_{1R}}{Z_{1S} + Z_{1R} + Z_{1L2}} \right) + I_{LineA2} \quad |I_{1L2}| = 0.54 \cdot \text{pu} \quad \arg(I_{1L2}) = -170 \cdot \text{deg}$$

$$I_{2L2} := -I_{2L1_open} \cdot \left(\frac{Z_{1S} + Z_{1R}}{Z_{1S} + Z_{1R} + Z_{1L2}} \right) \quad |I_{2L2}| = 0.07 \cdot \text{pu} \quad \arg(I_{2L2}) = -170 \cdot \text{deg}$$

$$I_{0L2} := -I_{0L1_open} \cdot \left(\frac{Z_{0S} + Z_{0R}}{Z_{0S} + Z_{0R} + Z_{0L2}} \right) \quad |I_{0L2}| = 0.02 \cdot \text{pu} \quad \arg(I_{0L2}) = -170 \cdot \text{deg}$$

$$I_{ABC_Line2} := A_{012} \cdot \begin{pmatrix} I_{0L2} \\ I_{1L2} \\ I_{2L2} \end{pmatrix} \quad |I_{ABC_Line2}| = \begin{pmatrix} 0.63 \\ 0.494 \\ 0.494 \end{pmatrix} \cdot \text{pu} \quad \arg(I_{ABC_Line2}) = \begin{pmatrix} -170 \\ 64.29 \\ -44.29 \end{pmatrix} \cdot \text{deg}$$

- See course web page for ATP, PSCAD/EMTDC, and EMTP-RV examples