
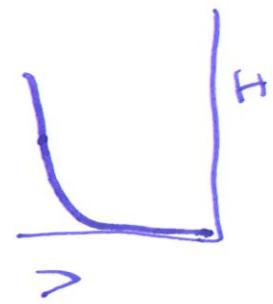


ECE 523
Symmetrical Components
Session 19

Series faults

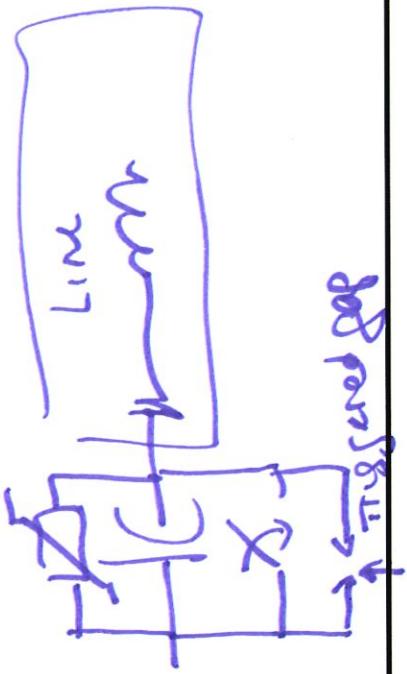- one phase open
 - intentional - Single pole tripping
 - breaker failure to close
- general series imbalance
 - one phase different than other two
 - most common cases one with series capacitors




- two poles open
 - breaker failure

To ~~analyze~~ analyze series faults
you must model power flow

LIA 3/18

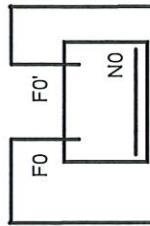
Now solve for the single phase open circuit currents and voltages:



$$I_1 := \frac{V_{\text{equiv}}}{Z_{1FF'} + \left(\frac{1}{Z_{2FF'}} + \frac{1}{Z_{0FF'}} \right)^{-1}}$$

$$I_1 = (0.43 - 0.26i) \cdot \text{pu}$$

$$|I_1| = 0.5 \cdot \text{pu} \quad \arg(I_1) = -31.79 \cdot \text{deg}$$

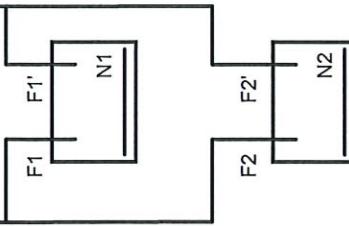

$$I_2 := -I_1 \cdot \left(\frac{Z_{0FF'}}{Z_{2FF'} + Z_{0FF'}} \right)$$

$$I_2 = (-0.25 + 0.16i) \cdot \text{pu}$$

$$|I_2| = 0.3 \cdot \text{pu} \quad \arg(I_2) = 148.21 \cdot \text{deg}$$

$$I_0 := -I_1 \cdot \left(\frac{Z_{2FF'}}{Z_{2FF'} + Z_{0FF'}} \right)$$

$$I_0 = (-0.17 + 0.11i) \cdot \text{pu}$$

$$|I_0| = 0.2 \cdot \text{pu} \quad \arg(I_0) = 148.21 \cdot \text{deg}$$

Relevant was 0.9 at -31.79 deg A

$$\overrightarrow{|I_{abc}|} = \begin{pmatrix} 0 \\ 0.76 \\ 0.76 \end{pmatrix} \cdot \text{pu}$$

$$\arg(I_{abc_1}) = -145.57 \cdot \text{deg}$$

$$\arg(I_{abc_2}) = 82 \cdot \text{deg}$$

Using the right have the sequence equivalent circuits:

$$V_{3\text{new1}} := E_2 + I_1 \cdot j \cdot (X_{1\text{Mach}} + X_T)$$

$$\arg(V_{3\text{new1}}) = -4.25 \cdot \text{deg}$$

$$V_{3\text{new2}} := 0 + I_2 \cdot j \cdot (X_{2\text{Mach}} + X_T)$$

$$\arg(V_{3\text{new2}}) = -121.79 \cdot \text{deg}$$

$$|V_{3\text{new1}}| = 0.96 \cdot \text{pu}$$

$$|V_{3\text{new2}}| = 0.08 \cdot \text{pu}$$

19 4/18

$$V_{3\text{new}0} := 0 + I_0 \cdot j \cdot (X_{0\text{Mach}} + X_T + 3 \cdot X_{n\text{Mach}})$$

$$|V_{3\text{new}0}| = 0.05 \cdot \text{pu}$$

$$V_{3\text{newABC}} := A_{012} \cdot \begin{pmatrix} V_{3\text{new}0} \\ V_{3\text{new}1} \\ V_{3\text{new}2} \end{pmatrix} \quad \overrightarrow{|V_{3\text{newABC}}|} = \begin{pmatrix} 0.9 \\ 0.97 \\ 1.01 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(V_{3\text{newABC}})} = \begin{pmatrix} -12.06 \\ -119.95 \\ 118.58 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{ABC} := 1.0 \cdot \begin{pmatrix} 1 \\ 2 \\ a \end{pmatrix} - V_{3\text{newABC}} \quad \overrightarrow{|\Delta V_{ABC}|} = \begin{pmatrix} 0.22 \\ 0.03 \\ 0.03 \end{pmatrix}$$

$$\overrightarrow{\arg(\Delta V_{ABC})} = \begin{pmatrix} 58.21 \\ -121.79 \\ -121.79 \end{pmatrix} \cdot \text{deg}$$

Solve using Zbus method. First get the Zbus matrices for the positive, negative and zero sequence networks:

$$Y_{\text{bus}1} := \begin{pmatrix} \frac{1}{j \cdot X_{1\text{Mach}}} + \frac{1}{j \cdot X_T} & \frac{-1}{j \cdot X_T} & 0 & 0 \\ \frac{-1}{j \cdot X_T} & \frac{1}{j \cdot X_T} + \frac{1}{j \cdot X_{L1}} & \frac{-1}{j \cdot X_{L1}} & 0 \\ 0 & \frac{-1}{j \cdot X_{L1}} & \frac{1}{j \cdot X_T} + \frac{1}{j \cdot X_{L1}} & \frac{-1}{j \cdot X_T} \\ 0 & 0 & \frac{-1}{j \cdot X_T} & \frac{1}{j \cdot X_{1\text{Mach}}} + \frac{1}{j \cdot X_T} \end{pmatrix}$$

Handwritten notes: Zbus1 is symmetric, Zbus2 is anti-symmetric

$$Z_{\text{bus}2} := Z_{\text{bus}1}$$

$$Y_{bus0} := \begin{pmatrix} \left(\frac{1}{jX_0Mach + 3jX_{nMach}} + \frac{1}{jX_T} \right) & -\frac{1}{jX_T} & 0 \\ -\frac{1}{jX_T} & \frac{1}{jX_T} + \frac{1}{jX_{L0}} & -\frac{1}{jX_{L0}} \\ 0 & \frac{-1}{jX_{L0}} & \frac{1}{jX_T} + \frac{1}{jX_{L0}} \\ 0 & 0 & \frac{-1}{jX_T} + \frac{1}{jX_0Mach + 3jX_{nMach}} + \frac{1}{jX_T} \end{pmatrix}$$

$$Z_{bus0} := Y_{bus0}^{-1}$$

Reset origin for matrices and vectors:
ORIGIN := 1

Equivalent impedances looking into the network from the open segment. See section 12.6 in the book by Grainger and Stevenson or 6.6.4 in the Tlies, 1st edition or 7.6.4 in Tlies 2nd edition.

$$Z_{1pp'} := \frac{-j(X_{L1})^2}{Z_{bus12,2} + Z_{bus13,3} - 2Z_{bus12,3} - jX_{L1}}$$

$$Z_{1pp'} = 0.71 \cdot pu$$

$$Z_{1total} = 0.71 \cdot pu$$

- Notice that: the denominator has the Thevenin impedance at the bus on either side of the open condition, and subtracts the transfer impedance and the line impedance.

$$Z_{2pp'} := Z_{1pp'}$$

$$Z_{0pp'} := \frac{-(jX_{L0})^2}{Z_{bus02,2} + Z_{bus03,3} - 2Z_{bus02,3} - jX_{L0}}$$

$$Z_{0pp'} = 1.04i \cdot pu$$

$$\begin{aligned} \text{Same as calculated above} \\ Z_{0total} = 1.04i \cdot pu \end{aligned}$$

L19 6/18

Find the sequence currents based on the prefault load current:

$$\begin{aligned}
 I_{1aopen} &:= I_{trans} \cdot \frac{Z_{1pp}}{Z_{1pp'} + \left(\frac{1}{Z_{0pp'}} + \frac{1}{Z_{2pp'}} \right)^{-1}} & |I_{1aopen}| &= 0.5 \cdot \text{pu} & \arg(I_{1aopen}) &= -31.79 \cdot \text{deg} \\
 I_{2aopen} &:= -I_{1aopen} \cdot \left(\frac{Z_{0pp'}}{Z_{2pp'} + Z_{0pp'}} \right) & |I_{2aopen}| &= 0.3 \cdot \text{pu} & \arg(I_{2aopen}) &= 148.21 \cdot \text{deg} \\
 I_{0aopen} &:= -I_{1aopen} \cdot \left(\frac{Z_{2pp'}}{Z_{2pp'} + Z_{0pp'}} \right) & |I_{0aopen}| &= 0.2 \cdot \text{pu} & \arg(I_{0aopen}) &= 148.21 \cdot \text{deg} \\
 I_{ABC_Line_Aopen} &:= A_{012} \cdot \begin{pmatrix} I_{0aopen} \\ I_{1aopen} \\ I_{2aopen} \end{pmatrix} & |I_{ABC_Line_Aopen}| &= \begin{pmatrix} 0 \\ 0.7571 \\ 0.7571 \end{pmatrix} \cdot \text{pu} & \arg(I_{ABC_Line_Aopen}) &= \begin{pmatrix} -26.57 \\ -145.57 \\ 82 \end{pmatrix} \cdot \text{deg}
 \end{aligned}$$

Sequence voltages across the open circuit (based on the sequence connection for 1 phase open):

$$V_{1Aopen} := I_{1aopen} \cdot \frac{Z_{2pp'} \cdot Z_{0pp'}}{Z_{2pp'} + Z_{0pp'}} \quad |V_{1Aopen}| = 0.21 \cdot \text{pu} \quad \arg(V_{1Aopen}) = 58.21 \cdot \text{deg}$$

Since the positive, negative and zero sequence voltages are equal for the phase A open case:

$$V_{2Aopen} := V_{1Aopen} \quad V_{0Aopen} := V_{1Aopen}$$

$$V_{1Aopen} = V_{0Aopen} - I_1 \cdot Z_{1pp'}$$

L19 7/18

current injections with series fault

Calculate change in voltage at each bus due to the open

$$\Delta V_{1A_Open} := Z_{bus1} \cdot \begin{pmatrix} 0 \\ \frac{V_{1Aopen}}{j \cdot X_{L1}} \\ -\frac{V_{1Aopen}}{j \cdot X_{L1}} \\ 0 \end{pmatrix}$$

- Positive injection for sending end of line with series fault
- Negative injection for receiving end of line with series fault

$$|V_{1A_Open}| = \begin{pmatrix} 1.15 \\ 1.12 \\ 0.96 \\ 0.94 \end{pmatrix} \text{ pu}$$

$$\overrightarrow{\arg(V_{1A_Open})} = \begin{pmatrix} 10.4 \\ 8.88 \\ -4.25 \\ -6.41 \end{pmatrix} \cdot \text{deg}$$

$$V_{2A_Open} := Z_{bus2} \cdot \begin{pmatrix} 0 \\ \frac{V_{2Aopen}}{j \cdot X_{L2}} \\ -\frac{V_{2Aopen}}{j \cdot X_{L2}} \\ 0 \end{pmatrix}$$

$$|V_{2A_Open}| = \begin{pmatrix} 0.06 \\ 0.08 \\ 0.08 \\ 0.06 \end{pmatrix} \text{ pu}$$

$$\overrightarrow{\arg(V_{2A_Open})} = \begin{pmatrix} 58.21 \\ 58.21 \\ -121.79 \\ -121.79 \end{pmatrix} \cdot \text{deg}$$

$$\begin{aligned} V0_A_{Open} &:= Z_{bus0} \cdot \begin{pmatrix} 0 \\ \frac{V0_{Aopen}}{j \cdot X_{L0}} \\ -\frac{V0_{Aopen}}{j \cdot X_{L0}} \\ 0 \end{pmatrix} = \overrightarrow{\left| V0_{A_Open} \right|} = \begin{pmatrix} 0.04 \\ 0.05 \\ 0.05 \\ 0.04 \end{pmatrix} \cdot pu \\ &\quad \overrightarrow{\arg(V0_{A_Open})} = \begin{pmatrix} 58.21 \\ 58.21 \\ -121.79 \\ -121.79 \end{pmatrix} \cdot deg \end{aligned}$$

Calculate Transformer T1 Current:

$$I_{T1_Aopen} := \frac{V1_{A_Open}_1 - V1_{A_Open}_2}{j \cdot X_T}$$

$$I_{T2_Aopen} := \frac{V2_{A_Open}_1 - V2_{A_Open}_2}{j \cdot X_T}$$

$$I_{T0_Aopen} := \frac{V0_{A_Open}_1 - V0_{A_Open}_2}{j \cdot X_T}$$

$$\begin{aligned} I_{ABC_T1_Aopen} &:= A_{012} \cdot \begin{pmatrix} I_{T0_Aopen} \\ I_{T1_Aopen} \\ I_{T2_Aopen} \end{pmatrix} = \overrightarrow{\left| I_{ABC_T1_Aopen} \right|} = \begin{pmatrix} 0 \\ 0.7571 \\ 0.7571 \end{pmatrix} \cdot pu \\ &\quad \overrightarrow{\arg(I_{ABC_T1_Aopen})} = \begin{pmatrix} 97.99 \\ -145.57 \\ 82 \end{pmatrix} \end{aligned}$$

Same as above

- Approach can be used on any branch except the one with the series fault.

$$V_{3ABC_Aopen} := A_{012} \cdot \begin{pmatrix} V0_{A_Open_3} \\ V1_{A_Open_3} \\ V2_{A_Open_3} \end{pmatrix}$$

$$\overrightarrow{|V_{3ABC_Aopen}|} = \begin{pmatrix} 0.9 \\ 0.97 \\ 1.01 \end{pmatrix} \text{ pu}$$

$$\overrightarrow{\arg(V_{3ABC_Aopen})} = \begin{pmatrix} -12.06 \\ -119.95 \\ 118.58 \end{pmatrix} \cdot \text{deg}$$

Alternate approach to get just the change in voltage at Bus 3:

$$\Delta V_{3_1aopen} := \left(\frac{Z_{bus1_{3,2}} - Z_{bus1_{3,3}}}{j \cdot X_{L1}} \right) \cdot V_{1Aopen} \quad |\Delta V_{3_1aopen}| = 0.0835 \cdot \text{pu} \quad \arg(\Delta V_{3_1aopen}) = -121.79 \cdot \text{deg}$$

$$\Delta V_{3_2aopen} := \left(\frac{Z_{bus2_{3,2}} - Z_{bus2_{3,3}}}{j \cdot X_{L2}} \right) \cdot V_{2Aopen} \quad |\Delta V_{3_2aopen}| = 0.0835 \cdot \text{pu} \quad \arg(\Delta V_{3_2aopen}) = -121.79 \cdot \text{deg}$$

$$\Delta V_{3_0aopen} := \left(\frac{Z_{bus0_{3,2}} - Z_{bus0_{3,3}}}{j \cdot X_{L0}} \right) \cdot V_{0Aopen} \quad |\Delta V_{3_0aopen}| = 0.055 \cdot \text{pu} \quad \arg(\Delta V_{3_0aopen}) = -121.79 \cdot \text{deg}$$

$$\Delta V_{3ABC} := A_{012} \cdot \begin{pmatrix} \Delta V_{3_0aopen} \\ \Delta V_{3_1aopen} \\ \Delta V_{3_2aopen} \end{pmatrix}$$

$$\overrightarrow{|\Delta V_{3ABC}|} = \begin{pmatrix} 0.22 \\ 0.03 \\ 0.03 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(\Delta V_{3ABC})} = \begin{pmatrix} -121.79 \\ 58.21 \\ 58.21 \end{pmatrix} \cdot \text{deg}$$

$$V_{3ABC_aopen} := 1.0 \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} + \Delta V_{3ABC}$$

$$\overrightarrow{|V_{3ABC_aopen}|} = \begin{pmatrix} 0.9 \\ 0.97 \\ 1.01 \end{pmatrix} \cdot \text{pu}$$


$$\overrightarrow{\arg(V_{3ABC_aopen})} = \begin{pmatrix} -12.06 \\ -119.95 \\ 118.58 \end{pmatrix} \cdot \text{deg}$$

From above:

$$\overrightarrow{|V_{3\text{newABC}}|} = \begin{pmatrix} 0.9 \\ 0.97 \\ 1.01 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(V_{3\text{newABC}})} = \begin{pmatrix} -12.06 \\ -119.95 \\ 118.58 \end{pmatrix} \cdot \text{deg}$$

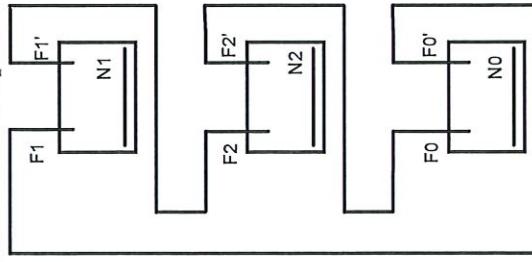Now solve the two phase open circuit below for the sequence currents:



$$I_1 := \frac{\overrightarrow{V}_{\text{equiv}}}{Z_{1FF'} + Z_{2FF'} + Z_{0FF'}}$$

$$|I_1| = 0.23 \cdot \text{pu} \quad \arg(I_1) = -31.79 \cdot \text{deg}$$

$$I_2 := I_1 \quad I_0 := I_1$$

$$I_{abc} := A_{012} \cdot \begin{pmatrix} I_0 \\ I_1 \\ I_2 \end{pmatrix}$$

$$\overrightarrow{|I_{abc}|} = \begin{pmatrix} 0.69 \\ 0 \\ 0 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(I_{abc})} = \begin{pmatrix} -31.79 \\ 81.87 \\ 81.87 \end{pmatrix} \cdot \text{deg}$$

$$V_{3\text{new1}} := E_2 + I_1 \cdot j \cdot (X_{1\text{Mach}} + X_T)$$

$$V_{3\text{new2}} := 0 + I_2 \cdot j \cdot (X_{2\text{Mach}} + X_T)$$

$$V_{3\text{new0}} := 0 + I_0 \cdot j \cdot (X_{0\text{Mach}} + X_T + 3 \cdot X_{n\text{Mach}})$$

$$V_{3\text{new1}} = (0.92 - 0.14j) \cdot \text{pu}$$

$$V_{3\text{new2}} = (0.03 + 0.05j) \cdot \text{pu}$$

$$V_{3\text{new0}} = (0.03 + 0.05j) \cdot \text{pu}$$

some points

$$V_{3\text{newABC}} := A_{012} \cdot \begin{pmatrix} V_{3\text{new0}} \\ V_{3\text{new1}} \\ V_{3\text{new2}} \end{pmatrix} \quad \overrightarrow{|V_{3\text{newABC}}|} = \begin{pmatrix} 0.98 \\ 0.9 \\ 0.9 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(V_{3\text{newABC}})} = \begin{pmatrix} -1.6 \\ -132.16 \\ 107.93 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{ABC} := 1.0 \cdot \begin{pmatrix} 1 \\ a^2 \\ a \end{pmatrix} - V_{3\text{newABC}}$$

$$\overrightarrow{|\Delta V_{ABC}|} = \begin{pmatrix} 0.03 \\ 0.22 \\ 0.22 \end{pmatrix} \cdot \text{pu}$$

$$\overrightarrow{\arg(\Delta V_{ABC})} = \begin{pmatrix} 58.21 \\ -61.27 \\ 177.7 \end{pmatrix} \cdot \text{deg}$$

Using Zbus approach

- Finding the current:

$$I_{1\text{bcopen}} := I_{\text{trans}} \cdot \left(\frac{Z_{1\text{pp}'}}{Z_{1\text{pp}'} + Z_{2\text{pp}'} + Z_{0\text{pp}'}} \right) \quad |I_{1\text{bcopen}}| = 0.23 \cdot \text{pu} \quad \arg(I_{1\text{bcopen}}) = -31.79 \cdot \text{deg}$$

$$I_{2\text{bcopen}} := I_{1\text{bcopen}} \quad I_{0\text{bcopen}} := I_{1\text{bcopen}}$$


$$I_{ABC_bcopen} := A_{012} \cdot \begin{pmatrix} I_{0\text{bcopen}} \\ I_{1\text{bcopen}} \\ I_{2\text{bcopen}} \end{pmatrix} \quad \overrightarrow{|I_{ABC_bcopen}|} = \begin{pmatrix} 0.69 \\ 0 \\ 0 \end{pmatrix} \quad \overrightarrow{\arg(I_{ABC_bcopen})} = \begin{pmatrix} -31.79 \\ 78.69 \\ 78.69 \end{pmatrix} \cdot \text{deg}$$

- Finding the voltage across the open circuit (from the sequence network connections):

$$V_{1\text{bcopen}} := I_{1\text{bcopen}} \cdot (Z_{2\text{pp}'} + Z_{0\text{pp}'}) \quad |V_{1\text{bcopen}}| = 0.4 \cdot \text{pu} \quad \arg(V_{1\text{bcopen}}) = 58.21 \cdot \text{deg}$$

$\text{V}_{1\text{bcopen}} = \text{I}_{1\text{bcopen}} \cdot (Z_{2\text{pp}'} + Z_{0\text{pp}'})$

Sequence networks in
networks

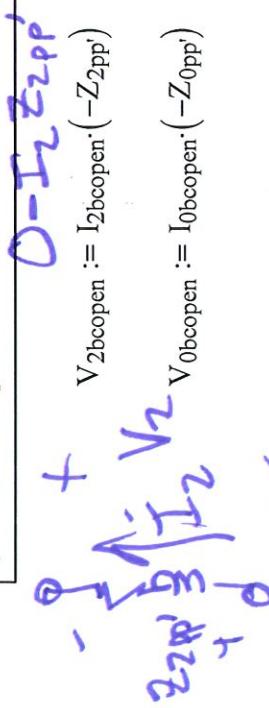

$$V_{2bcopen} := I_{2bcopen} \cdot (-Z_{2pp})$$

$$|V_{2bcopen}| = 0.16 \text{ pu}$$

$$\arg(V_{2bcopen}) = -121.79 \text{ deg}$$

$$V_{0bcopen} := I_{0bcopen} \cdot (-Z_{0pp})$$

$$|V_{0bcopen}| = 0.24 \text{ pu}$$

$$\arg(V_{0bcopen}) = -121.79 \text{ deg}$$

- Alternate way for finding the voltage across the open circuit (from the sequence network connections):

$$V_{1bcopenA} := I_{trans} \cdot \left[\frac{Z_{1pp} \cdot (Z_{2pp'} + Z_{0pp'})}{Z_{1pp'} + Z_{2pp'} + Z_{0pp'}} \right] \quad |V_{1bcopenA}| = 0.4 \text{ pu} \quad \arg(V_{1bcopenA}) = 58.21 \text{ deg}$$

$$V_{2bcopenA} := I_{trans} \cdot \left(\frac{-Z_{1pp} \cdot Z_{2pp'}}{Z_{1pp'} + Z_{2pp'} + Z_{0pp'}} \right) \quad |V_{2bcopenA}| = 0.16 \text{ pu} \quad \arg(V_{2bcopenA}) = -121.79 \text{ deg}$$

$$V_{0bcopenA} := I_{trans} \cdot \left(\frac{-Z_{1pp} \cdot Z_{0pp'}}{Z_{1pp'} + Z_{2pp'} + Z_{0pp'}} \right) \quad |V_{0bcopenA}| = 0.24 \text{ pu} \quad \arg(V_{0bcopenA}) = -121.79 \text{ deg}$$

Calculate change in voltage at each bus due to the two phase open

$$\Delta V_{1BC_Open} := Z_{bus1} \cdot \begin{pmatrix} 0 \\ \frac{V_{1bcopen}}{j \cdot X_{L1}} \\ -\frac{V_{1bcopen}}{j \cdot X_{L1}} \\ 0 \end{pmatrix} \quad V_{1BC_Open} := \begin{pmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{pmatrix} + \Delta V_{1BC_Open}$$

Some
and
use
single
for
pole
open

119 13) 18

$$\overrightarrow{|V_{1BC_Open}|} = \begin{pmatrix} 1.18 \\ 1.17 \\ 0.93 \\ 0.92 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(V_{1BC_Open})} = \begin{pmatrix} 12.34 \\ 11.69 \\ -8.41 \\ -9.47 \end{pmatrix} \cdot deg$$

$$V_{2BC_Open} := Z_{bus2} \cdot \begin{pmatrix} 0 \\ \frac{V_{2bcopen}}{j \cdot X_{L2}} \\ -\frac{V_{2bcopen}}{j \cdot X_{L2}} \\ 0 \end{pmatrix}$$


$$\overrightarrow{|V_{2BC_Open}|} = \begin{pmatrix} 0.05 \\ 0.06 \\ 0.06 \\ 0.05 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(V_{2BC_Open})} = \begin{pmatrix} -121.79 \\ -121.79 \\ 58.21 \\ 58.21 \end{pmatrix} \cdot deg$$

$$V_{0BC_Open} := Z_{bus0} \cdot \begin{pmatrix} 0 \\ \frac{V_{0bcopen}}{j \cdot X_{L0}} \\ -\frac{V_{0bcopen}}{j \cdot X_{L0}} \\ 0 \end{pmatrix}$$

$$\overrightarrow{|V_{0BC_Open}|} = \begin{pmatrix} 0.04 \\ 0.06 \\ 0.06 \\ 0.04 \end{pmatrix} \cdot pu$$
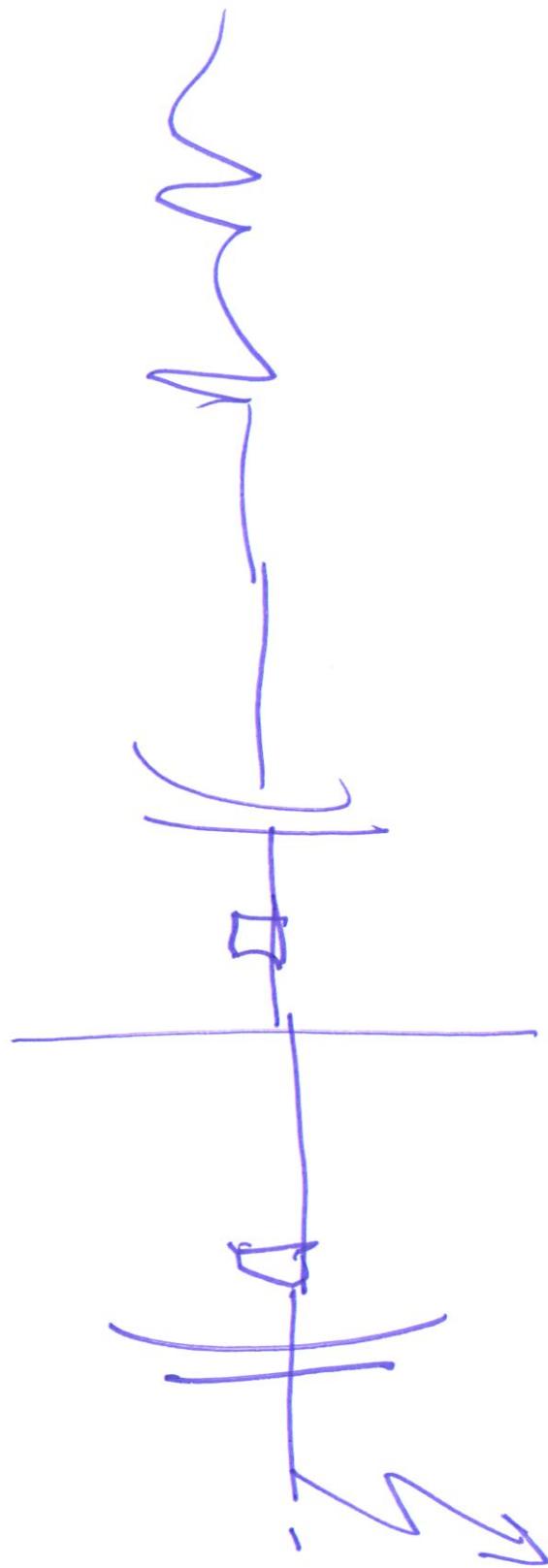
$$\overrightarrow{\arg(V_{0BC_Open})} = \begin{pmatrix} -121.79 \\ -121.79 \\ 58.21 \\ 58.21 \end{pmatrix} \cdot deg$$



Electromagnetic Transient Simulators (EMT)

- Series faults and
Simultaneous faults
may be more easily
studied with EMT
simulator

6/18
L19

U_I What Are Electromagnetic Transients?

ECE 523
Lecture 19

- Power systems normally in steady-state
 - » Or Quasi-steady-state
 - » Allows use of RMS phasors
- Switching, operations, faults, lightning,
 - » Response frequencies from DC to MHz
 - » Generally dies out rapidly (higher freq.)
 - » Large voltage and currents are possible
 - » RLC response to change in voltage or current

Intro to EMTP simulation

1

Fall 2023

U_I Why Analyze Transients?

ECE 523
Lecture 19

- Power systems operate in sinusoidal steady-state majority of time
- Sudden changes cause large voltage and currents
 - » Including faults and response to clearing faults
- Protection decisions before transients die out → or even based on transients

Intro to EMTP simulation

2

Fall 2023

2

1

11/19/18

U_I

Circuit Simulation

ECE 523
Lecture 19

- Output often as time domain waveforms
- Often want instantaneous peak values of $v(t)$ and $i(t)$
 - » Or in some cases energy
 - » Peaks missed with RMS or harmonic solutions

Intro to EMTP simulation

3

Fall 2023

U_I

Transient Network Analyzer (TNA)

ECE 523
Lecture 19

- Predates use of digital computers
 - » Analog computer model
 - » Hybrid: digital controls
- Real-time digital simulators
- Cost limits to small class of problems
 - » Closed loop testing of control hardware

Intro to EMTP simulation

4

Fall 2023

4

2

U_I Off-Line Time Domain
SimulationECE 523
Lecture 19

- Digital computer simulation of transients
- General purpose equation solvers:
MATLAB, MathCAD
- Analog electronic and integrated circuits:
SPICE, Saber
- Not really designed for power system
transients

Intro to EMTP simulation

5

Fall 2023

 U_I The Electromagnetic
Transients Program-EMTPECE 523
Lecture 19

- Hermann Dommel, Germany, then BPA
- Numerically solves difference equations
- Fixed versus variable time-step
- EMTP has become an industry standard
(verified models)
- Modules in other power systems programs
- Matlab toolbox

Intro to EMTP simulation

6

Fall 2023