

Mutual Coupling in Fault Analysis

$$\text{MVA} := 1000\text{kW}$$

$$\text{pu} := 1$$

$$a := 1 \cdot e^{j \frac{2\pi}{3}}$$

$$A_{012} := \begin{pmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{pmatrix}$$


$$S_{\text{base}} := 100\text{MVA}$$

$$V_{\text{base}} := 138\text{kV}$$

$$Z_{\text{base}} := \frac{V_{\text{base}}^2}{S_{\text{base}}}$$

$$Z_{\text{base}} = 190.44\Omega$$
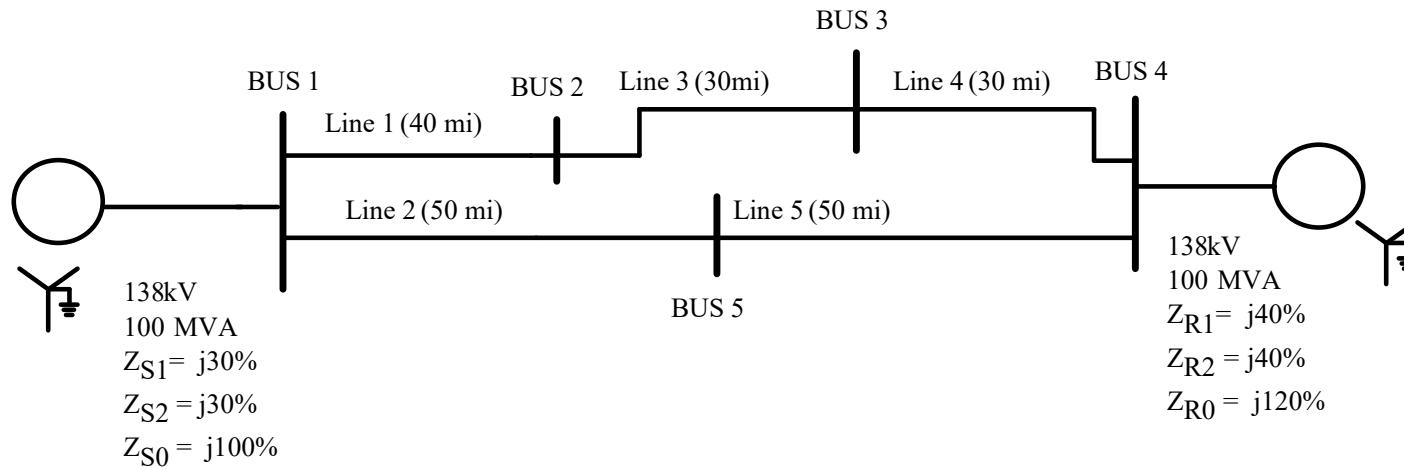
$$I_{\text{base}} := \frac{S_{\text{base}}}{\sqrt{3} \cdot V_{\text{base}}} \quad I_{\text{base}} = 418.37\text{A}$$



- Source impedances:

$$Z_{S1} := j \cdot 0.3\text{pu} \quad Z_{R1} := j \cdot 0.4\text{pu}$$

$$Z_{S0} := j \cdot 1.0\text{pu} \quad Z_{R0} := j \cdot 1.2\text{pu}$$

- Line impedances from lecture 32 handout:

- Line 1, 40 mile length

$$Z_{0\text{Line}1} := (22.55548 + j \cdot 110.79032)\text{ohm}$$

$$Z_{1\text{Line}1} := (11.12 + j \cdot 32.16612)\text{ohm}$$

$$Z_{1L1} := \frac{Z_{1\text{Line}1}}{Z_{\text{base}}} \quad Z_{1L1} = (0.058 + 0.169i) \cdot \text{pu}$$

$$Z_{0L1} := \frac{Z_{0\text{Line}1}}{Z_{\text{base}}} \quad Z_{0L1} = (0.118 + 0.582i) \cdot \text{pu}$$

- Line 2, 50 mile length

$$Z_{0\text{Line}2} := 1.2 \cdot (22.55548 + j \cdot 110.79032)\text{ohm}$$

$$Z_{1\text{Line}2} := 1.2 \cdot (11.12 + j \cdot 32.16612)\text{ohm}$$

$$Z_{1L2} := \frac{Z_{1\text{Line}2}}{Z_{\text{base}}} \quad Z_{1L2} = (0.07 + 0.203i) \cdot \text{pu}$$

$$Z_{0L2} := \frac{Z_{0\text{Line}2}}{Z_{\text{base}}} \quad Z_{0L2} = (0.142 + 0.698i) \cdot \text{pu}$$

- Line 1 and line 2 have 40 miles that are mutually coupled (just use zero sequence coupling)

$$Z_{0M_12} := (11.43548 + j \cdot 48.71333)\text{ohm}$$

$$Z_{0M12} := \frac{Z_{0M_12}}{Z_{\text{base}}} \quad Z_{0M12} = (0.06 + 0.256i) \cdot \text{pu}$$

- Line 3 is 30 miles with the same tower configuration as above, 20 miles of which is not close enough for mutual coupling.

$$Z_{1L3} := 0.75 \cdot Z_{1L1} \quad \text{Note that 30 miles is } 3/4 \text{ of the length of line 1}$$

$$Z_{0L3} := 0.75 \cdot Z_{0L1}$$

- Line 2 and line 3 have 10 miles that are mutually coupled (just use zero sequence coupling)

$$Z_{0M23} := 0.25 \cdot (Z_{0M12})$$

- Line 4 is 30 miles with same tower configuration that is not close enough for mutual coupling

$$Z_{1L4} := 0.75 \cdot Z_{1L1}$$

$$Z_{0L4} := 0.75 \cdot Z_{0L1}$$

- Line 5 is 50 miles with same tower configuration that is not close enough for mutual coupling

$$Z_{1L5} := 1.2 \cdot Z_{1L1}$$

$$Z_{0L5} := 1.2 \cdot Z_{0L1}$$

- First, create the positive sequence Y_{bus} for fault study using the common formulation approach. Note that there is no mutual coupling for the positive sequence.

$$Y_{bus1} := \begin{pmatrix} \frac{1}{Z_{S1}} + \frac{1}{Z_{1L1}} + \frac{1}{Z_{1L2}} & \frac{-1}{Z_{1L1}} & 0 & 0 & \frac{-1}{Z_{1L2}} \\ \frac{-1}{Z_{1L1}} & \frac{1}{Z_{1L1}} + \frac{1}{Z_{1L3}} & \frac{-1}{Z_{1L3}} & 0 & 0 \\ 0 & \frac{-1}{Z_{1L3}} & \frac{1}{Z_{1L3}} + \frac{1}{Z_{1L4}} & \frac{-1}{Z_{1L4}} & 0 \\ 0 & 0 & \frac{-1}{Z_{1L4}} & \frac{1}{Z_{R1}} + \frac{1}{Z_{1L4}} + \frac{1}{Z_{1L5}} & \frac{-1}{Z_{1L5}} \\ \frac{-1}{Z_{1L2}} & 0 & 0 & \frac{-1}{Z_{1L5}} & \frac{1}{Z_{1L2}} + \frac{1}{Z_{1L5}} \end{pmatrix}$$

$$Y_{bus1} = \begin{pmatrix} 3.352 - 13.029i & -1.828 + 5.288i & 0 & 0 & -1.524 + 4.407i \\ -1.828 + 5.288i & 4.266 - 12.34i & -2.438 + 7.051i & 0 & 0 \\ 0 & -2.438 + 7.051i & 4.875 - 14.103i & -2.438 + 7.051i & 0 \\ 0 & 0 & -2.438 + 7.051i & 3.961 - 13.958i & -1.524 + 4.407i \\ -1.524 + 4.407i & 0 & 0 & -1.524 + 4.407i & 3.047 - 8.814i \end{pmatrix} \cdot pu$$

- Now build the Y_{bus} , using the incidence matrix approach (again, no mutual coupling for positive sequence)


Mapping to digraph

$$Y_{pr1} := \begin{pmatrix} \frac{1}{Z_{S1}} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \frac{1}{Z_{R1}} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{Z_{1L1}} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & \frac{1}{Z_{1L2}} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \frac{1}{Z_{1L3}} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \frac{1}{Z_{1L4}} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & \frac{1}{Z_{1L5}} \end{pmatrix} \quad \begin{matrix} \mathbf{a} \\ \mathbf{b} \\ \mathbf{c} \\ \mathbf{d} \\ \mathbf{e} \\ \mathbf{f} \\ \mathbf{g} \end{matrix}$$

- Note that the matrix Y_{pr} , actually comes from the primitive impedance matrix. We will modify this matrix later to add zero sequence mutual coupling.

$$Z_{pr1} := \begin{pmatrix} Z_{S1} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Z_{R1} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{1L1} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & Z_{1L2} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & Z_{1L3} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & Z_{1L4} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Z_{1L5} \end{pmatrix} \quad Y_{pr1}^{-1} - Z_{pr1} = \begin{pmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{pmatrix}$$

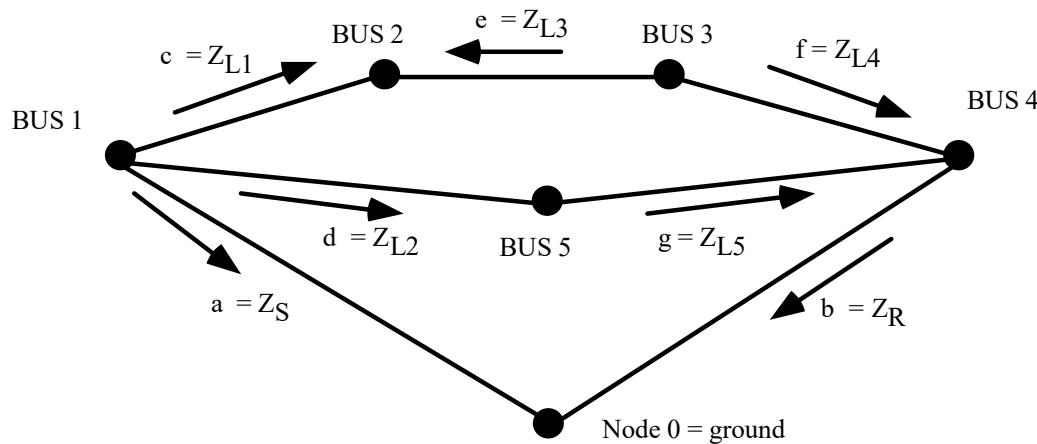- Directed graph representing the system (we will use the polarities of the arrows for the incidence matrix)



Incidence matrix

- Each row corresponds to a branch
- Each column corresponds to a node (note that matrix is not generally square)
 - a. Enter a 0 if no connection between the node and branch for that cell
 - b. Enter a (+1) if the current is leaving a node
 - c. Enter a (-1) if the current is entering a node
 - d. No row and column associated with ground node

Node number: 1 2 3 4 5 Branch

$$A_{\text{incid}} := \begin{pmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & -1 \\ 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & 0 & -1 & 1 \end{pmatrix}$$

$$Y_{\text{bus1_alt}} := A_{\text{incid}}^T \cdot Y_{\text{pr1}} \cdot A_{\text{incid}}$$

$$Y_{\text{bus1_alt}} = \begin{pmatrix} 3.352 - 13.029i & -1.828 + 5.288i & 0 & 0 & -1.524 + 4.407i \\ -1.828 + 5.288i & 4.266 - 12.34i & -2.438 + 7.051i & 0 & 0 \\ 0 & -2.438 + 7.051i & 4.875 - 14.103i & -2.438 + 7.051i & 0 \\ 0 & 0 & -2.438 + 7.051i & 3.961 - 13.958i & -1.524 + 4.407i \\ -1.524 + 4.407i & 0 & 0 & -1.524 + 4.407i & 3.047 - 8.814i \end{pmatrix}$$

$$Y_{bus1_alt} - Y_{bus1} = \begin{pmatrix} 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{pmatrix}$$

$$Y_{bus2} := Y_{bus1}$$

- Now for zero sequence matrix. Now we need to include the zero sequence mutual coupling
 - It will be put into the Z_{pr0} matrix as off-diagonal terms
 - The sign of the offdiagonal terms depends on the sign of the associated links in the digraph (positive signs if the arrows point the same way and negative otherwise.

Mapping to digraph

$$Z_{pr0M} := \begin{pmatrix} Z_{S0} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Z_{R0} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{0L1} & Z_{0M12} & 0 & 0 & 0 \\ 0 & 0 & Z_{0M12} & Z_{0L2} & -Z_{0M23} & 0 & 0 \\ 0 & 0 & 0 & -Z_{0M23} & Z_{0L3} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & Z_{0L4} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Z_{0L5} \end{pmatrix} \begin{matrix} \mathbf{a} \\ \mathbf{b} \\ \mathbf{c} \\ \mathbf{d} \\ \mathbf{e} \\ \mathbf{f} \\ \mathbf{g} \end{matrix}$$

and for later comparisons, the same matrix, with no mutual terms.

$$Z_{\text{pr0_noM}} := \begin{pmatrix} Z_{S0} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Z_{R0} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{0L1} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & Z_{0L2} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & Z_{0L3} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & Z_{0L4} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Z_{0L5} \end{pmatrix}$$

$$Y_{\text{bus0_M}} := A_{\text{incid}}^T \cdot Z_{\text{pr0M}}^{-1} \cdot A_{\text{incid}}$$

$$Y_{\text{bus0_NoM}} := A_{\text{incid}}^T \cdot Z_{\text{pr0_noM}}^{-1} \cdot A_{\text{incid}}$$

$$Y_{\text{bus0_M}} = \begin{pmatrix} 0.46 - 3.17i & -0.29 + 1.37i & 0.03 - 0.14i & 0 & -0.2 + 0.93i \\ -0.29 + 1.37i & 0.8 - 4i & -0.44 + 2.13i & 0 & -0.08 + 0.5i \\ 0.03 - 0.14i & -0.44 + 2.13i & 0.9 - 4.44i & -0.45 + 2.2i & -0.04 + 0.25i \\ 0 & 0 & -0.45 + 2.2i & 0.73 - 4.41i & -0.28 + 1.38i \\ -0.2 + 0.93i & -0.08 + 0.5i & -0.04 + 0.25i & -0.28 + 1.38i & 0.6 - 3.05i \end{pmatrix}$$

Matches Powerworld Matrix:

Name	Bus 1	Bus 2	Bus 3	Bus 4	Bus 5
BUS1	0.46 - j3.17	-0.29 + j1.37	0.03 - j0.14		-0.20 + j0.93
BUS2	-0.29 + j1.37	0.80 - j4.00	-0.44 + j2.13		-0.08 + j0.50
BUS3	0.03 - j0.14	-0.44 + j2.13	0.90 - j4.44	-0.45 + j2.20	-0.04 + j0.25
BUS4			-0.45 + j2.20	0.73 - j4.41	-0.28 + j1.38
BUS5	-0.20 + j0.93	-0.08 + j0.50	-0.04 + j0.25	-0.28 + j1.38	0.60 - j3.05

$$Y_{bus0_NoM} = \begin{pmatrix} 0.616 - 4.026i & -0.336 + 1.651i & 0 & 0 & -0.28 + 1.375i \\ -0.336 + 1.651i & 0.784 - 3.851i & -0.448 + 2.201i & 0 & 0 \\ 0 & -0.448 + 2.201i & 0.896 - 4.401i & -0.448 + 2.201i & 0 \\ 0 & 0 & -0.448 + 2.201i & 0.728 - 4.409i & -0.28 + 1.375i \\ -0.28 + 1.375i & 0 & 0 & -0.28 + 1.375i & 0.56 - 2.751i \end{pmatrix}$$

$$Z_{0_M} := Y_{bus0_M}^{-1}$$

$$Z_{0_NoM} := Y_{bus0_NoM}^{-1}$$

$$Z_{0_M} = \begin{pmatrix} 0.019 + 0.676i & -1.425 \times 10^{-3} + 0.539i & -0.013 + 0.459i & -0.023 + 0.389i & -6.347 \times 10^{-3} + 0.507i \\ -1.425 \times 10^{-3} + 0.539i & 0.068 + 0.882i & 0.034 + 0.715i & 1.71 \times 10^{-3} + 0.553i & 0.016 + 0.615i \\ -0.013 + 0.459i & 0.034 + 0.715i & 0.069 + 0.901i & 0.016 + 0.649i & 0.016 + 0.622i \\ -0.023 + 0.389i & 1.71 \times 10^{-3} + 0.553i & 0.016 + 0.649i & 0.028 + 0.733i & 7.617 \times 10^{-3} + 0.592i \\ -6.347 \times 10^{-3} + 0.507i & 0.016 + 0.615i & 0.016 + 0.622i & 7.617 \times 10^{-3} + 0.592i & 0.068 + 0.887i \end{pmatrix}$$

$$Z_{0_NoM} = \begin{pmatrix} 0.017 + 0.657i & 2.047 \times 10^{-3} + 0.559i & -9.21 \times 10^{-3} + 0.485i & -0.02 + 0.411i & -1.706 \times 10^{-3} + 0.534i \\ 2.047 \times 10^{-3} + 0.559i & 0.071 + 0.896i & 0.034 + 0.713i & -2.456 \times 10^{-3} + 0.529i & -2.047 \times 10^{-4} + 0.544i \\ -9.21 \times 10^{-3} + 0.485i & 0.034 + 0.713i & 0.067 + 0.884i & 0.011 + 0.618i & 9.21 \times 10^{-4} + 0.552i \\ -0.02 + 0.411i & -2.456 \times 10^{-3} + 0.529i & 0.011 + 0.618i & 0.025 + 0.707i & 2.047 \times 10^{-3} + 0.559i \\ -1.706 \times 10^{-3} + 0.534i & -2.047 \times 10^{-4} + 0.544i & 9.21 \times 10^{-4} + 0.552i & 2.047 \times 10^{-3} + 0.559i & 0.071 + 0.896i \end{pmatrix}$$

$$Z_{\text{Bus1}} := Y_{\text{bus1}}^{-1} \quad Z_{\text{Bus2}} := Z_{\text{Bus1}}$$

Now lets look at a SLG fault at Bus 5:

Assume no prefault powerflow, and 1.0pu voltage everywhere prefault.... $V_f := 1.0\text{pu}$

Case 1: No mutual coupling:



$$I_{0_NoM} := \frac{V_f}{Z_{\text{Bus1}}_{4,4} + Z_{\text{Bus2}}_{4,4} + Z_{0_NoM}_{4,4}} \quad |I_{0_NoM}| = 0.69\text{pu} \quad \arg(I_{0_NoM}) = -84.39\text{deg}$$

$$I_{1_NoM} := I_{0_NoM} \quad I_{2_NoM} := I_{1_NoM}$$

$$I_{ABC_SLG_NoM} := A_{012} \cdot \begin{pmatrix} I_{0_NoM} \\ I_{1_NoM} \\ I_{2_NoM} \end{pmatrix} \quad \xrightarrow{|I_{ABC_SLG_NoM}|} \begin{pmatrix} 2.069 \\ 0 \\ 0 \end{pmatrix} \quad \xrightarrow{\arg(I_{ABC_SLG_NoM})} \begin{pmatrix} -84.39 \\ 19.537 \\ 19.537 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{1_NoM} := Z_{\text{Bus1}} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{1_NoM} \end{pmatrix} \quad V_{1_NoM} := \begin{pmatrix} 1.0 \\ 1.0 \\ 1.0 \\ 1.0 \\ 1.0 \end{pmatrix} + \Delta V_{1_NoM}$$

$$\overrightarrow{|V_{1\text{NoM}}|} = \begin{pmatrix} 0.886 \\ 0.883 \\ 0.88 \\ 0.878 \\ 0.81 \end{pmatrix} \quad \overrightarrow{\arg(V_{1\text{NoM}})} = \begin{pmatrix} -0.783 \\ -0.753 \\ -0.73 \\ -0.706 \\ 0.407 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V_{2\text{NoM}} := Z_{\text{Bus2}} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{2\text{-NoM}} \end{pmatrix} \quad V_{2\text{NoM}} := \Delta V_{2\text{NoM}}$$

$$\Delta V_{0\text{NoM}} := Z_{0\text{-NoM}} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{0\text{-NoM}} \end{pmatrix} \quad V_{0\text{NoM}} := \Delta V_{0\text{NoM}}$$

$$V_{ABC_B1_NoM} := A_{012} \cdot \begin{pmatrix} V_{0\text{NoM}_0} \\ V_{1\text{NoM}_0} \\ V_{2\text{NoM}_0} \end{pmatrix} \quad \overrightarrow{|V_{ABC_B1_NoM}|} = \begin{pmatrix} 0.4097 \\ 1.1663 \\ 1.1284 \end{pmatrix} \cdot \text{pu} \quad \overrightarrow{\arg(V_{ABC_B1_NoM})} = \begin{pmatrix} -8.623 \\ -130.178 \\ 131.822 \end{pmatrix} \cdot \text{deg}$$

$$V_{ABC_B2_NoM} := A_{012} \cdot \begin{pmatrix} V0_{NoM_1} \\ V1_{NoM_1} \\ V2_{NoM_1} \end{pmatrix}$$

$$\overrightarrow{|V_{ABC_B2_NoM}|} = \begin{pmatrix} 0.3962 \\ 1.1687 \\ 1.1307 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(V_{ABC_B2_NoM})} = \begin{pmatrix} -8.714 \\ -130.308 \\ 131.962 \end{pmatrix} \cdot deg$$

$$I_{1_L1_NoM} := \frac{V1_{NoM_0} - V1_{NoM_1}}{Z_{1L1}}$$

$$I_{2_L1_NoM} := \frac{V2_{NoM_0} - V2_{NoM_1}}{Z_{1L1}}$$

$$I_{0_L1_NoM} := \frac{V0_{NoM_0} - V0_{NoM_1}}{Z_{0L1}}$$

$$I_{ABC_L1_NoM} := A_{012} \cdot \begin{pmatrix} I0_{L1_NoM} \\ I1_{L1_NoM} \\ I2_{L1_NoM} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L1_NoM}|} = \begin{pmatrix} 0.0487 \\ 0.007 \\ 0.007 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC_L1_NoM})} = \begin{pmatrix} -80.275 \\ 102.864 \\ 102.864 \end{pmatrix} \cdot deg$$

$$I_{1_L2_NoM} := \frac{V1_{NoM_0} - V1_{NoM_4}}{Z_{1L2}}$$

$$I_{2_L2_NoM} := \frac{V2_{NoM_0} - V2_{NoM_4}}{Z_{1L2}}$$

$$I_{0_L2_NoM} := \frac{V_{0NoM_0} - V_{0NoM_4}}{Z_{0L2}}$$

$$I_{ABC_L2_NoM} := A_{012} \cdot \begin{pmatrix} I_{0_L2_NoM} \\ I_{1_L2_NoM} \\ I_{2_L2_NoM} \end{pmatrix}$$

$$I_{1_L3_NoM} := \frac{V_{1NoM_1} - V_{1NoM_2}}{Z_{1L3}}$$

$$I_{2_L3_NoM} := \frac{V_{2NoM_1} - V_{2NoM_2}}{Z_{1L3}}$$

$$I_{0_L3_NoM} := \frac{V_{0NoM_1} - V_{0NoM_2}}{Z_{0L3}}$$

$$I_{ABC_L3_NoM} := A_{012} \cdot \begin{pmatrix} I_{0_L3_NoM} \\ I_{1_L3_NoM} \\ I_{2_L3_NoM} \end{pmatrix}$$

$$I_{ABC_L3_NoM} + I_{ABC_L1_NoM} = \begin{pmatrix} 0.016 - 0.096i \\ -3.116 \times 10^{-3} + 0.014i \\ -3.116 \times 10^{-3} + 0.014i \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L2_NoM}|} = \begin{pmatrix} 1.0853 \\ 0.0073 \\ 0.0073 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC_L2_NoM})} = \begin{pmatrix} -84.197 \\ 102.864 \\ 102.864 \end{pmatrix} \cdot deg$$

$$\overrightarrow{\arg(I_{ABC_L3_NoM})} = \begin{pmatrix} -80.275 \\ 102.864 \\ 102.864 \end{pmatrix} \cdot deg$$



Case 2: With mutual coupling:

$$I_{0_M} := \frac{V_f}{Z_{\text{Bus1}}_{4,4} + Z_{\text{Bus2}}_{4,4} + Z_{0_M}_{4,4}} \quad |I_{0_M}| = 0.694 \cdot \text{pu} \quad \arg(I_{0_M}) = -84.48 \cdot \text{deg}$$

$$I_{1_M} := I_{0_M} \quad I_{2_M} := I_{1_M}$$

$$I_{\text{ABC_SLG_M}} := A_{012} \cdot \begin{pmatrix} I_{0_M} \\ I_{1_M} \\ I_{2_M} \end{pmatrix} \quad \overrightarrow{|I_{\text{ABC_SLG_M}}|} = \begin{pmatrix} 2.081 \\ 0 \\ 0 \end{pmatrix} \quad \overrightarrow{\arg(I_{\text{ABC_SLG_M}})} = \begin{pmatrix} -84.48 \\ 13.173 \\ 13.173 \end{pmatrix} \cdot \text{deg}$$

- Very close match to Powerworld results

$$\Delta V_{1M} := Z_{\text{Bus1}} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{1_M} \end{pmatrix} \quad V_{1M} := \begin{pmatrix} 1.0 \\ 1.0 \\ 1.0 \\ 1.0 \\ 1.0 \end{pmatrix} + \Delta V_{1M}$$

$$\overrightarrow{|V_{1M}|} = \begin{pmatrix} 0.885 \\ 0.882 \\ 0.879 \\ 0.877 \\ 0.809 \end{pmatrix} \quad \overrightarrow{\arg(V_{1M})} = \begin{pmatrix} -0.777 \\ -0.746 \\ -0.722 \\ -0.699 \\ 0.431 \end{pmatrix} \cdot \text{deg}$$

$$\Delta V2_M := Z_{Bus2} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{2_M} \end{pmatrix}$$

$$V2_M := \Delta V2_M$$

$$\Delta V0_M := Z_{0_M} \cdot \begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -I_{0_M} \end{pmatrix}$$

$$V0_M := \Delta V0_M$$

$$V_{ABC_B1_M} := A_{012} \cdot \begin{pmatrix} V0_{M_0} \\ V1_{M_0} \\ V2_{M_0} \end{pmatrix}$$

$$\overrightarrow{|V_{ABC_B1_M}|} = \begin{pmatrix} 0.4253 \\ 1.1558 \\ 1.1159 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(V_{ABC_B1_M})} = \begin{pmatrix} -8.412 \\ -129.471 \\ 131.182 \end{pmatrix} \cdot deg$$

$$V_{ABC_B2_M} := A_{012} \cdot \begin{pmatrix} V0_{M_1} \\ V1_{M_1} \\ V2_{M_1} \end{pmatrix}$$

$$\overrightarrow{|V_{ABC_B2_M}|} = \begin{pmatrix} 0.3423 \\ 1.1973 \\ 1.1708 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(V_{ABC_B2_M})} = \begin{pmatrix} -8.838 \\ -132.399 \\ 133.597 \end{pmatrix} \cdot deg$$

Compare to Powerworld

Name	Phase Volt A	Phase Volt B	Phase Volt C	Phase Ang A	Phase Ang B	Phase Ang C
BUS1	0.4253	1.15581	1.11585	-8.41	-129.47	131.18
BUS2	0.34229	1.19733	1.17075	-8.84	-132.4	133.6
BUS3	0.33257	1.19963	1.17171	-9.06	-132.45	133.71
BUS4	0.3491	1.18713	1.15225	-9.17	-131.47	133.02
BUS5	0	1.28049	1.25553	0	-136.32	137.53

- First get the positive and negative sequence currents in each of the three branches involved in the mutual coupled lines

$$I_{1_L1_M} := \frac{V1_{M0} - V1_{M1}}{Z_{1L1}} \quad |I_{1_L1_M}| = 0.019 \quad \arg(I_{1_L1_M}) = -79.972 \cdot \text{deg}$$

$$I_{2_L1_M} := \frac{V2_{M0} - V2_{M1}}{Z_{1L1}} \quad |I_{2_L1_M}| = 0.019 \quad \arg(I_{2_L1_M}) = -79.972 \cdot \text{deg}$$

$$I_{1_L2_M} := \frac{V1_{M0} - V1_{M4}}{Z_{1L2}} \quad |I_{1_L2_M}| = 0.366 \quad \arg(I_{1_L2_M}) = -84.241 \cdot \text{deg}$$

$$I_{2_L2_M} := \frac{V2_{M0} - V2_{M4}}{Z_{1L2}} \quad |I_{2_L2_M}| = 0.366 \quad \arg(I_{2_L2_M}) = -84.241 \cdot \text{deg}$$

$$I_{1_L3_M} := \frac{V_{1M_1} - V_{1M_2}}{Z_{1L3}} \quad |I_{1_L3_M}| = 0.019 \cdot \text{pu} \quad \arg(I_{1_L3_M}) = -79.972 \cdot \text{deg}$$

$$I_{2_L3_M} := \frac{V_{2M_1} - V_{2M_2}}{Z_{1L3}} \quad |I_{2_L3_M}| = 0.019 \cdot \text{pu} \quad \arg(I_{2_L3_M}) = -79.972 \cdot \text{deg}$$

- The zero sequence calculation is little more tricky. This is based on equation 12.19 in the text book
- We need terms from the matrix of impedance primitives, recall:

$$Z_{pr0M} := \begin{pmatrix} Z_{S0} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & Z_{R0} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & Z_{0L1} & Z_{0M12} & 0 & 0 & 0 \\ 0 & 0 & Z_{0M12} & Z_{0L2} & -Z_{0M23} & 0 & 0 \\ 0 & 0 & 0 & -Z_{0M23} & Z_{0L3} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & Z_{0L4} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & Z_{0L5} \end{pmatrix} \quad \text{We need the } 3 \times 3 \text{ block in the middle of the matrix.}$$

$$Z_{\text{mutual0}} := \text{submatrix}(Z_{pr0M}, 2, 4, 2, 4) \quad Z_{\text{mutual0}} = \begin{pmatrix} 0.118 + 0.582i & 0.06 + 0.256i & 0 \\ 0.06 + 0.256i & 0.142 + 0.698i & -0.015 - 0.064i \\ 0 & -0.015 - 0.064i & 0.089 + 0.436i \end{pmatrix}$$

$$\begin{pmatrix} I_{0_L1_M} \\ I_{0_L2_M} \\ I_{0_L3_M} \end{pmatrix} := Z_{\text{mutual}0}^{-1} \cdot \begin{pmatrix} V_{0M_0} - V_{0M_1} \\ V_{0M_0} - V_{0M_4} \\ V_{0M_2} - V_{0M_1} \end{pmatrix}$$

$|I_{0_L1_M}| = 0.048 \quad \arg(I_{0_L1_M}) = 90.677 \cdot \text{deg}$
 $|I_{0_L2_M}| = 0.4 \quad \arg(I_{0_L2_M}) = -84.435 \cdot \text{deg}$
 • Note sign on I_{0_L3} , dot polarity $|I_{0_L3_M}| = 0.048 \quad \arg(-I_{0_L3_M}) = 90.677 \cdot \text{deg}$

$$I_{ABC_L1_M} := A_{012} \cdot \begin{pmatrix} I_{0_L1_M} \\ I_{1_L1_M} \\ I_{2_L1_M} \end{pmatrix}$$

$\overrightarrow{|I_{ABC_L1_M}|} = \begin{pmatrix} 0.013 \\ 0.0669 \\ 0.0669 \end{pmatrix} \cdot \text{pu}$ $\overrightarrow{\arg(I_{ABC_L1_M})} = \begin{pmatrix} 62.941 \\ 93.277 \\ 93.277 \end{pmatrix} \cdot \text{deg}$

$\overrightarrow{|I_{ABC_L1_NoM}|} = \begin{pmatrix} 0.0487 \\ 0.007 \\ 0.007 \end{pmatrix} \cdot \text{pu}$ $\overrightarrow{\arg(I_{ABC_L1_NoM})} = \begin{pmatrix} -80.275 \\ 102.864 \\ 102.864 \end{pmatrix} \cdot \text{deg}$

$$I_{ABC_L2_M} := A_{012} \cdot \begin{pmatrix} I_{0_L2_M} \\ I_{1_L2_M} \\ I_{2_L2_M} \end{pmatrix}$$

$\overrightarrow{|I_{ABC_L2_M}|} = \begin{pmatrix} 1.1325 \\ 0.0336 \\ 0.0336 \end{pmatrix} \cdot \text{pu}$ $\overrightarrow{\arg(I_{ABC_L2_M})} = \begin{pmatrix} -84.309 \\ -86.547 \\ -86.547 \end{pmatrix} \cdot \text{deg}$

$\overrightarrow{|I_{ABC_L2_NoM}|} = \begin{pmatrix} 1.0853 \\ 0.0073 \\ 0.0073 \end{pmatrix} \cdot \text{pu}$ $\overrightarrow{\arg(I_{ABC_L2_NoM})} = \begin{pmatrix} -80.275 \\ 102.864 \\ 102.864 \end{pmatrix} \cdot \text{deg}$

$$I_{ABC_L3_M} := A_{012} \cdot \begin{pmatrix} -I_{0_L3_M} \\ I_{1_L3_M} \\ I_{2_L3_M} \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L3_M}|} = \begin{pmatrix} 0.013 \\ 0.0669 \\ 0.0669 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC_L3_M})} = \begin{pmatrix} 62.941 \\ 93.277 \\ 93.277 \end{pmatrix} \cdot deg$$

$$\overrightarrow{|I_{ABC_L3_NoM}|} = \begin{pmatrix} 0.0487 \\ 0.007 \\ 0.007 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC_L3_NoM})} = \begin{pmatrix} -80.275 \\ 102.864 \\ 102.864 \end{pmatrix} \cdot deg$$

$$I_{ABC_L3_M} - I_{ABC_L1_M} = \begin{pmatrix} 0 \\ 0 \\ 0 \end{pmatrix}$$

$$\overrightarrow{|I_{ABC_L1_M}|} = \begin{pmatrix} 0.013 \\ 0.0669 \\ 0.0669 \end{pmatrix} \cdot pu$$

$$\overrightarrow{\arg(I_{ABC_L1_M})} = \begin{pmatrix} 62.941 \\ 93.277 \\ 93.277 \end{pmatrix} \cdot deg$$

Powerworld Results

Phase Cur A From	Phase Ang A From	Phase Cur B From	Phase Ang B From	Phase Cur C From	Phase Ang C From
0.01303	62.95	0.06689	93.28	0.06689	93.28
1.13243	-84.31	0.03359	-86.54	0.03359	-86.54
0.01303	62.95	0.06689	93.28	0.06689	93.28
0.01303	62.95	0.06689	93.28	0.06689	93.28
0.94891	95.32	0.03359	-86.54	0.03359	-86.54